

# HindPhotostat



## Hind Photostat & Book Store

Best Quality Classroom Topper Hand Written Notes to Crack GATE, IES, PSU's & Other Government Competitive/ Entrance Exams

**MADE EASY**  
**ELECTRICAL ENGINEERING**  
**POWER ELECTRONICS**  
**BY-JAGDEESH SIR**

- Theory
- Explanation
- Derivation
- Example
- Shortcuts
- Previous Years Question With Solution

Visit us:-[www.hindphotostat.com](http://www.hindphotostat.com)

Courier Facility All Over India  
(DTDC & INDIA POST)  
Mob-9311989030

## Topics:

- (i) Power semiconductor devices
- (ii) Phase controlled rectifier (AC-DC) and Appl's: Charging battery  
DC Drive  
Solar cell

### Power semiconductor devices:-

- |                      |             |
|----------------------|-------------|
| (i) Power diode      | (vi) GTO    |
| (ii) SCR (thyristor) | (vii) TRIAC |
| (iii) LASCR          | (viii) DIAC |
| (iv) ASCR            |             |
| (v) RCT              |             |

### Power transistor ( $f \uparrow$ )

- ③ → Power BJT
  - ① → Power MOSFET
  - ② → IGBT
- ↳ switching frequency order

Cycloconv.  $\leftarrow AC \rightarrow DC \rightarrow DC \rightarrow AC$

### Power electronics:-

Static V-I characteristics and firing/gating circuits for thyristor, MOSFET, IGBT; DC to DC conversion: Buck and Buck-Boost converters; single and three phase configuration of uncontrolled rectifiers; voltage and current commutated thyristor based converters; Bidirectional ac to dc voltage source converters; Magnitude and phase of line current harmonics for uncontrolled and thyristor based converters; Power factor and distortion factor of ac to dc converters; VSI, CSI, PWM.

# Topics :

- (i) Power semiconductor devices
- \* (ii) phase controlled Rectifiers (AC  $\rightleftharpoons$  DC)
  - and application : charging Battery : DC drive
  - : solar cell : HVDC

Solar energy can be stored in the form of DC system but our utility system are in AC system. so conversion is needed and this is possible by using phase controlled Rectifier. (converter).  
 Suppose we want to control the DC machine then phase controlled Rectifier is used.

- \* (iii) switched mode DC  $\rightarrow$  DC converters (choppers)
- \* (iv) switched mode DC  $\rightarrow$  AC converters (inverters)


(v) AC drive  
only for ESE

(vi) Resonant converters

(vii) high frequency T/F and Inductors for PE Application.


(viii) SMPS

## Power electronics :- ?

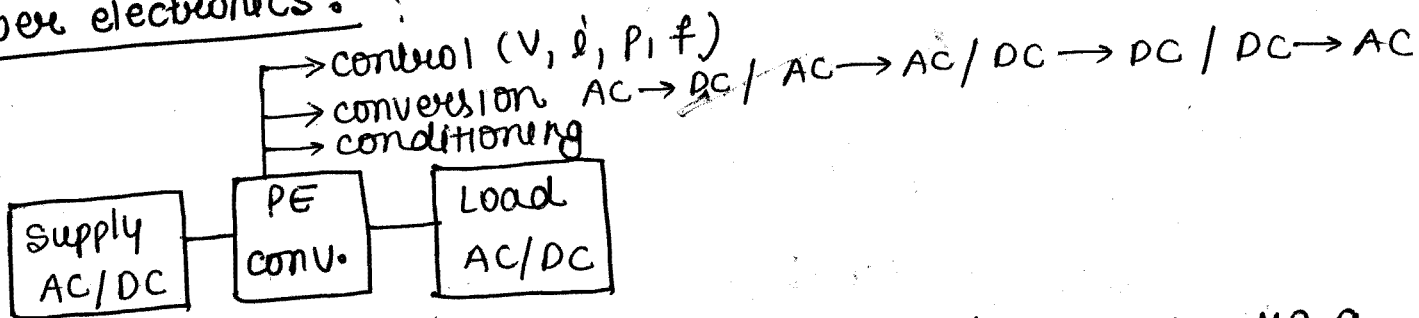


Due to the mismatching of power in both side we require a device which is known as power converters.

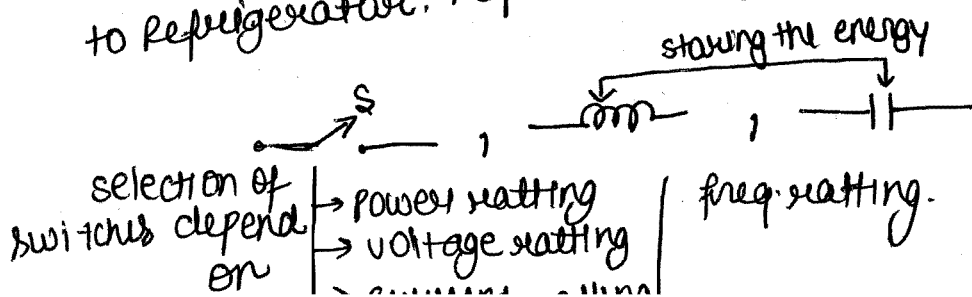Between the sensitive load & power supply we use power electronic converter so to minimize the voltage fluctuation. EX-: stabilizer to Refrigerator. i.e; conditioning of electrical power



~~Not used~~  
 because power dissipation element.

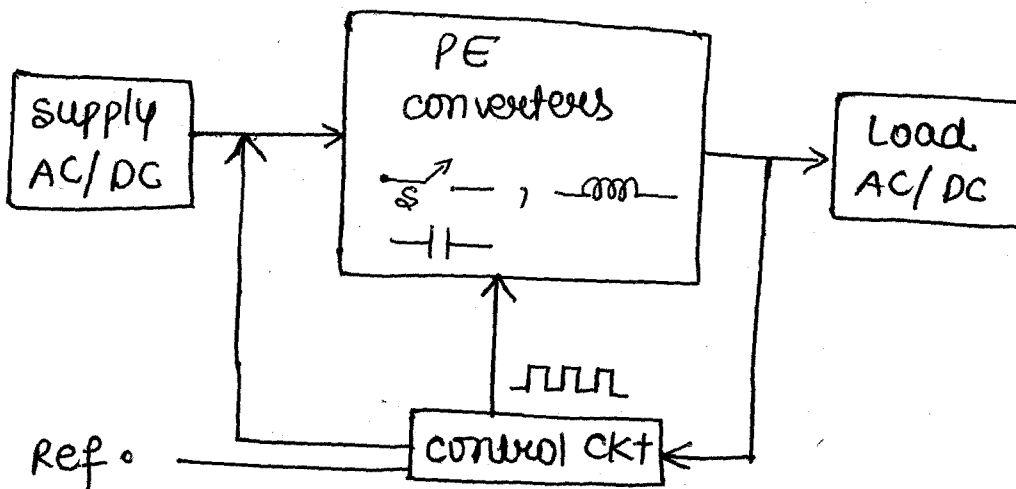(ON/OFF) control the switches we need control ckt and it is low power circuit or signal level ckt. here we can use resistive element.



power electronic deals with control, conversion and conditioning of electric power using semiconductor devices & these sc devices should operate with high efficiency. In power electronic, semiconductor devices are mainly used as switches.

In this devices there will be two terminal Anode (A) & cathode (K). But some of the devices are also having Gate terminal also.

suppose diode is only having two terminal Anode & cathode not having Gate (G) terminal that's why diode is uncontrolled device.

cycloconverter :  $\phi_0, \phi_1$   
AC  $\rightarrow$  AC

High power & low speed  
in drive

Semiconductor switches :-


(i) uncontrolled switch : (eg)  $A \rightarrow \text{Diode} \rightarrow K$ , DIAC

In the diode device there is no gate terminal so the ON/OFF state of diode will not decide then who decide the ON/OFF state of device? Nature of the ckt will decide it.

(ii) semi controlled switch : (eg)  $A \rightarrow \text{SCR} \rightarrow K$ , TRIAC


In SCR, the anode & cathode terminal is connected to the supply & load respectively & Gate terminal is only decide the ON state but we can not decide the turn OFF time by using Gate terminal.

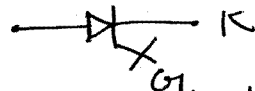(iii) Fully controlled switches: (eg) GTO



Gate is controlled terminal which decide both ON & OFF state.  
 when we give  $+I_g$  to gate terminal then GTO  $\equiv$  ON  
 $-I_g$  to gate terminal then GTO  $\equiv$  OFF

(eg) BJT, MOSFET, IGBT


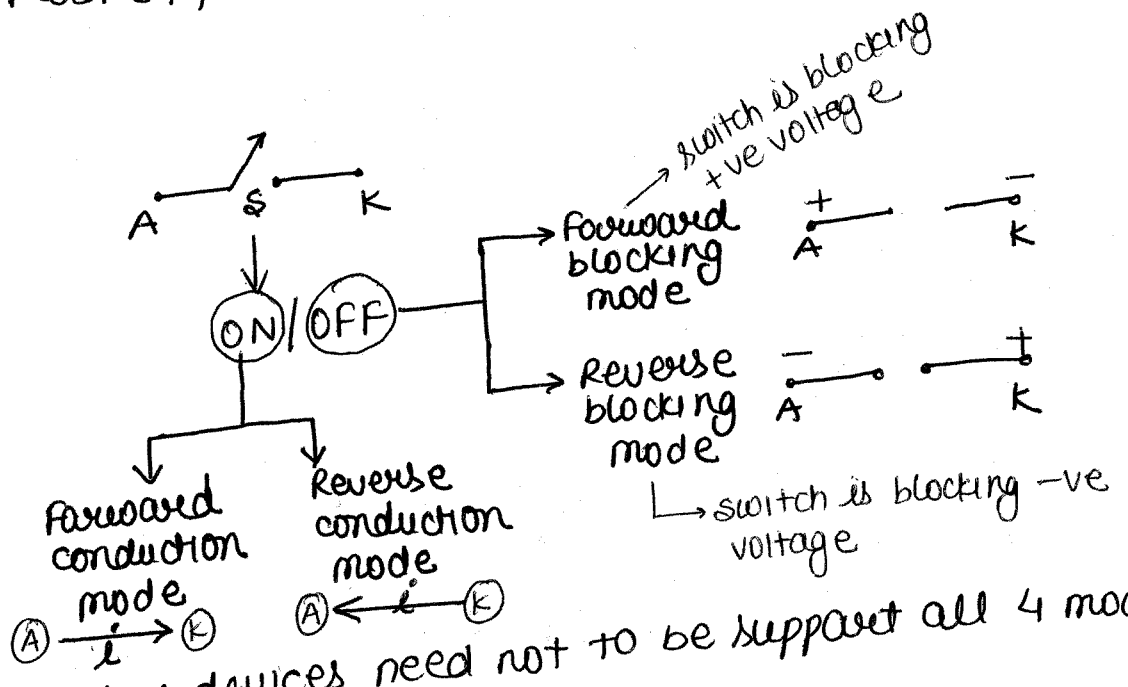


NOTE:-


All the semiconductor devices need not to be support all 4 mode.

Eg:-

(Diode)

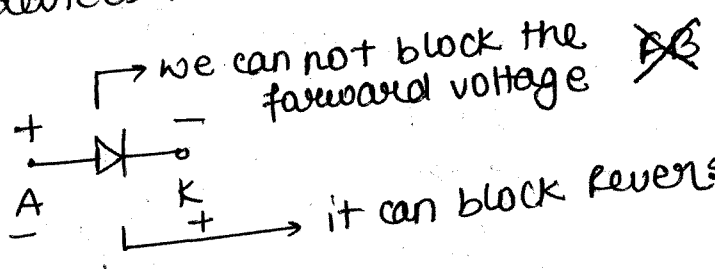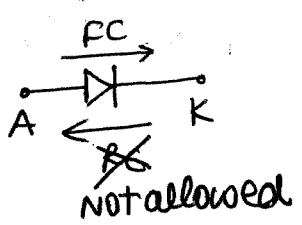

SCR

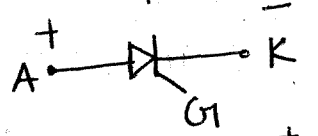


it can block the reverse voltage also when Gate=0 & current direction is only one way.

FB RB  
 ↓  
 bipolar blocking capability

Diode	SCR
FC, RB	FB, RB, FC bipolar capability blocking with unidirectional current

Four-mode of an ideal switch :-

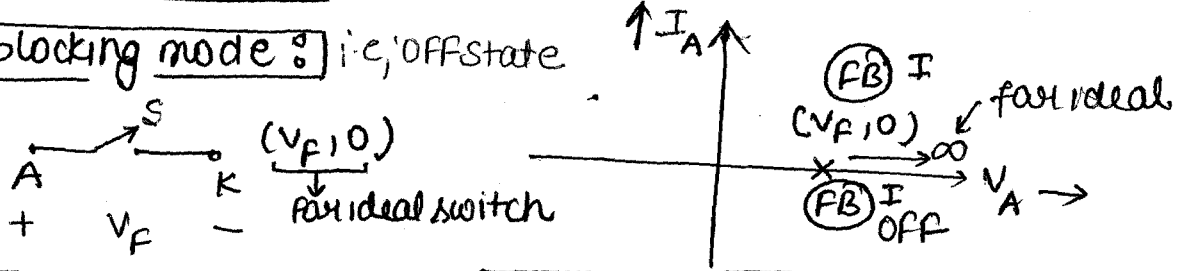
(i) Forward blocking mode :- i.e., OFF state





An ideal device when blocking the forward voltage ( $V_F$ ) then current passing through the device is zero Amp but in practical some leakage current flow through it due to minority current now, we are having some losses in semiconductor device even in the OFF state i.e., **blocking power loss** =  $[V_F \times I_{leakage}]$ . If it is ideal switch then it can block  $\infty$  voltage through it. But practically it is not possible to apply  $\infty$  voltage across it.

**voltage rating** : that much maximum voltage semiconductor device can block. [withstand in blocking state]

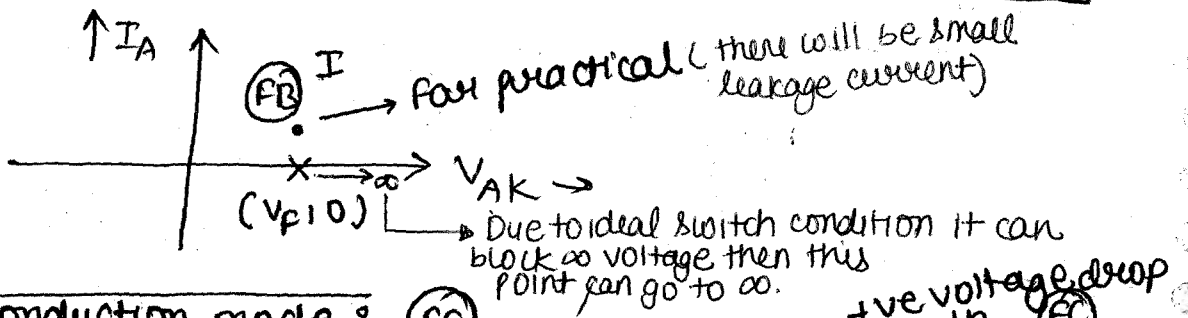X  $\rightarrow$  ideal  
o  $\rightarrow$  practical




(ii) Forward conduction mode :- (FC)

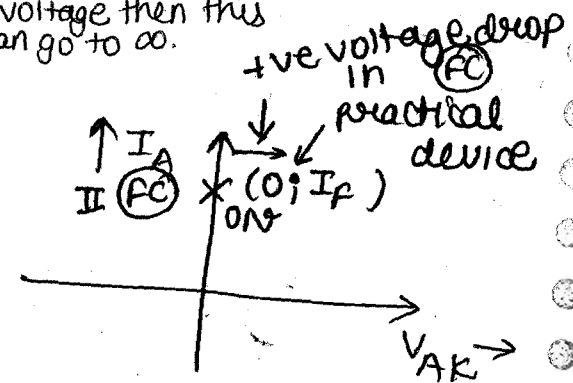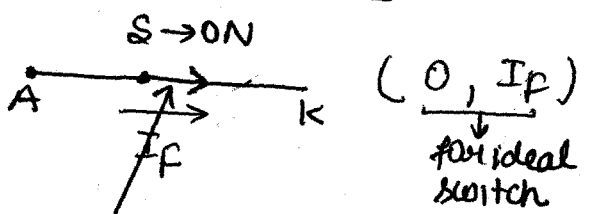

voltage drop in practical case there will be **conduction loss** in the device  $= (V_{drop}) \times I_F$ . **major loss among all three losses**.

**Switching power loss** : The variation of current & voltage from (FB) mode to (FC) mode there will be loss in it which is known as switching power loss.

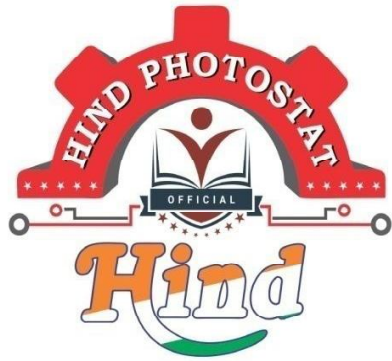It is depend on the switching frequency of switch ( $f$ ) if  $f \uparrow$  then **switching power loss**  $\uparrow$



# HindPhotostat



## Hind Photostat & Book Store

Best Quality Classroom Topper Hand Written Notes to Crack GATE, IES, PSU's & Other Government Competitive/ Entrance Exams

**MADE EASY**  
**ELECTRICAL ENGINEERING**  
**Power System-1**  
By. Balaji Sir

- Theory
- Explanation
- Derivation
- Example
- Shortcuts
- Previous Years Question With Solution

Visit us:- [www.hindphotostat.com](http://www.hindphotostat.com)

Courier Facility All Over India  
(DTDC & INDIA POST)  
Mob-9311989030



# HindPhotostat



**MADE EASY , IES MASTER , ACE ACADEMY , KREATRYX**

**ESE , GATE, PSU BEST QUALITY TOPPER HAND WRITTEN NOTES  
MINIMUM PRICE AVAILABLE @ OUR WEBSITE**

- |                                |                           |
|--------------------------------|---------------------------|
| 1. ELECTRONICS ENGINEERING     | 2. ELECTRICAL ENGINEERING |
| 3. MECHANICAL ENGINEERING      | 4. CIVIL ENGINEERING      |
| 5. INSTRUMENTATION ENGINEERING | 6. COMPUTER SCIENCE       |

**IES , GATE , PSU TEST SERIES AVAILABLE @ OUR WEBSITE**

❖ IES –PRELIMS & MAINS

❖ GATE

➤ **NOTE;- ALL ENGINEERING BRANCHS**

➤ **ALL PSUs PREVIOUS YEAR QUESTION PAPER @ OUR WEBSITE**

## **PUBLICATIONS BOOKS -**

**MADE EASY , IES MASTER , ACE ACADEMY , KREATRYX , GATE ACADEMY , ARIHANT , GK**

**RAKESH YADAV , KD CAMPUS , FOUNDATION , MC –GRAW HILL (TMH) , PEARSON...OTHERS**

**HEAVY DISCOUNTS BOOKS AVAILABLE @ OUR WEBSITE**

<b>F230, Lado Sarai New Delhi-110030 Phone: 9311 989 030</b>	<b>Shop No: 46 100 Futa M.G. Rd Near Made Easy Ghitorni, New Delhi-30 Phone:9711475393</b>	<b>F518 Near Kali Maa Mandir Lado Sarai New Delhi-110030 Phone: 9560 163 471</b>	<b>Shop No.7/8 Saidulajab Market Neb Sarai More, Saket, New Delhi-30</b>
--	--	--	--

**Website: [www.hindPhotostat.com](http://www.hindPhotostat.com)**

**Contact Us: 9311 989 030**

**Courier Facility All Over India**

**(DTDC & INDIA POST)**



Standard voltages used in India :-

HVAC RMS line to line voltage / line voltage (kV) :

Transmission Network voltage (kV) -

- 1200 kV (maximum in India) Maharashtra
- 765, 400
- 220, 132
- 66

Distribution Network voltages (kV) -

- 33 kV, 11 kV

Industrials uses - 6.6 kV, 3.3 kV, 1.1 kV, 400V

Houses uses - 230V (phase voltage)

Frequency  $f = 50 \text{ Hz}$

HVDC  $\pm 500 \text{ kV}, \pm 800 \text{ kV}, f = 0 \text{ Hz}$

Q.N:- The rated voltage of a 3-phase power system is -  
- RMS line to line voltage

All India Installed capacity sector : 382.730 GW

Coal : 209294.5 MW

Gas : 24924 MW

Nuclear : 6780 MW

Hydro : 46209.22 MW

Diesel : 509.71 MW


Renewable Energy : 95012.59 MW  
source

WR : 74320 MW by coal largest power utilisation  
NER : 770 MW by coal smallest

Thermal : Coal + Lignite + Gas + Diesel

30<sup>th</sup> June 2021 → maximum power consumed by 193 GW at 12:46 pm

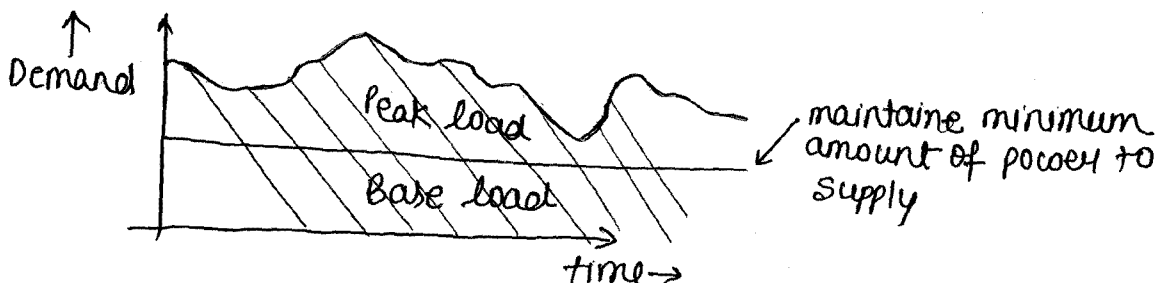
variable load curve : All India Demand (GW) v/s time



Base load :- Thermal plant

Next to peak load : Gas, wind, solar

Peak load :- Hydro plant

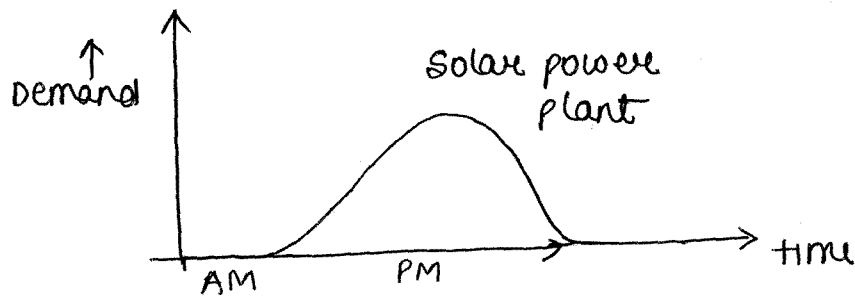

1 kWh = 1 unit

2019-20 1208 kWh per capita consumption

Objectives of power system :-


(i) Cost of electric energy must be low.

- Economic factors
- Economic load dispatch

(ii) Reliable power supply i.e; no interruption of power supply

- power generation methods
- Transmission
- Distribution
- Load flow studies

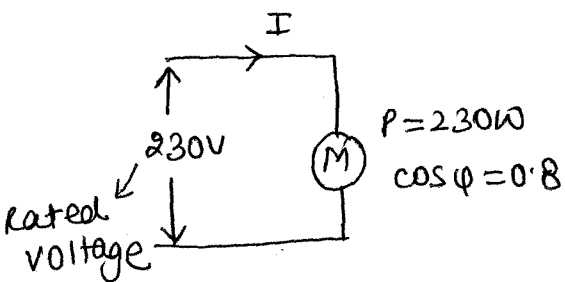(iii) Maintain constant voltage i.e; supply rated voltage to consumer



$$P = VI \cos \phi$$

$$I = \frac{P}{V \cos \phi} = \frac{230}{230 \times 0.8} = 1.25 \text{ A}$$

suppose supply voltage get reduce to  $V = 200$  volts then current drawn

by motor will be  $I = \frac{230}{200 \times 0.8} = 1.4375 \text{ A}$ .

$$\% \text{ increase in current} = \frac{1.4375 - 1.25}{1.25} \times 100 = 15\%$$


current drawn by motor is high value, this will causes overheating

To get constant voltage — voltage / reactive power control

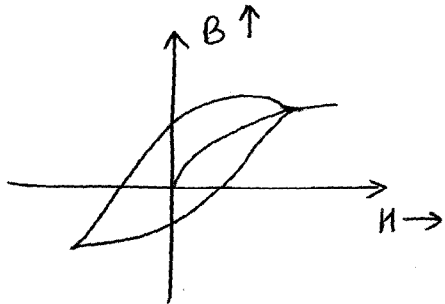(iv) Maintain Rated frequency

$$f = 50 \text{ Hz} \pm 1\% \quad (49.5 \text{ to } 50.5) \text{ Hz (ideal case)}$$

$$= 50 \text{ Hz} \pm 3\% \quad (48.5 \text{ to } 51.3) \text{ Hz (practical case)}$$



power T/F :  $V = 4.44 f \Phi_m N$

$$\downarrow f \propto \Phi \uparrow \rightarrow \text{causes core saturation}$$

For this → load frequency control

(v) Fastest fault identification and clearance of fault in minimum time

- fault analysis
- protection

(vi) Stable generator has to be maintained

- stability

(viii) Flexible power transfer

- power cable

Panther	— 132 KV
Zebra	— 220 KV
Moose	— 400 KV

## - Transmission line Parameters & Performance :-

By using transmission line, electric power is transferred from the remote generating station to the load centre (electric power utilised).

### Material of Transmission line :-

**ACSR - Aluminium conductor steel Reinforced**

Steel is used at the centre because it has higher mechanical strength to withstand and carry large weight of ACSR conductor.

4 layer ACSR (37-30|7)  
 strands ←      ↓      ↓  
                          Al   steel

5 layer ACSR (61-54|7)  
 strands ←      ↓      ↓  
                          Al   steel

No. of strands :  $N = (3x^2 - 3x + 1)$

Total Dia  $D = (2x - 1)d$

$x =$  layer number

$d =$  Dia of each strands

Technical name of ACSR :- Animal like, Zebra, Panther, Moose, Dog etc is used for Aluminium for European standard and bird name like Swan, Sparrow, Raven, Pigeon etc is used as for US standard.

Power carrying capacities at 65°C :-

- At 132 KV with 'Panther' ACSR = 75 MVA
- At 220 KV with 'Zebra' ACSR = 200 MVA
- At 400 KV with 'Moose' ACSR = 500 MVA


$$3\phi T/L \Rightarrow \sqrt{3} V \cdot I \cdot \cos \phi = P_{\phi}$$

$$\sqrt{3} \times 400 \times 10^3 \times I \times 0.95 = 500 \times 10^6$$

$I = 759.67 \text{ A}$  carrying current by Moose
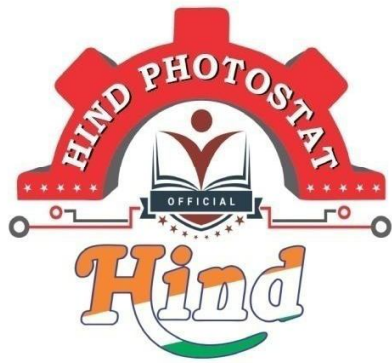
### Tower configuration :-

3 bundle conductor not practically used due to mechanical strength.



# HindPhotostat



## Hind Photostat & Book Store

Best Quality Classroom Topper Hand Written Notes to Crack GATE, IES, PSU's & Other Government Competitive/ Entrance Exams

**MADE EASY**  
**ELECTRICAL ENGINEERING**  
**Power System-2**  
By. Bhoopender Sir

- Theory
- Explanation
- Derivation
- Example
- Shortcuts
- Previous Years Question With Solution

Visit us:- [www.hindphotostat.com](http://www.hindphotostat.com)

Courier Facility All Over India  
(DTDC & INDIA POST)  
Mob-9311989030



# HindPhotostat



**MADE EASY , IES MASTER , ACE ACADEMY , KREATRYX**

**ESE , GATE, PSU BEST QUALITY TOPPER HAND WRITTEN NOTES  
MINIMUM PRICE AVAILABLE @ OUR WEBSITE**

- |                                |                           |
|--------------------------------|---------------------------|
| 1. ELECTRONICS ENGINEERING     | 2. ELECTRICAL ENGINEERING |
| 3. MECHANICAL ENGINEERING      | 4. CIVIL ENGINEERING      |
| 5. INSTRUMENTATION ENGINEERING | 6. COMPUTER SCIENCE       |

**IES , GATE , PSU TEST SERIES AVAILABLE @ OUR WEBSITE**

- ❖ IES –PRELIMS & MAINS
- ❖ GATE

➤ **NOTE;- ALL ENGINEERING BRANCHS**

➤ **ALL PSUs PREVIOUS YEAR QUESTION PAPER @ OUR WEBSITE**

## **PUBLICATIONS BOOKS -**

**MADE EASY , IES MASTER , ACE ACADEMY , KREATRYX , GATE ACADEMY , ARIHANT , GK**

**RAKESH YADAV , KD CAMPUS , FOUNDATION , MC –GRAW HILL (TMH) , PEARSON...OTHERS**

**HEAVY DISCOUNTS BOOKS AVAILABLE @ OUR WEBSITE**

<b>F230, Lado Sarai New Delhi-110030 Phone: 9311 989 030</b>	<b>Shop No: 46 100 Futa M.G. Rd Near Made Easy Ghitorni, New Delhi-30 Phone:9711475393</b>	<b>F518 Near Kali Maa Mandir Lado Sarai New Delhi-110030 Phone: 9560 163 471</b>	<b>Shop No.7/8 Saidulajab Market Neb Sarai More, Saket, New Delhi-30</b>
--	--	--	--

**Website: [www.hindPhotostat.com](http://www.hindPhotostat.com)**

**Contact Us: 9311 989 030**

**Courier Facility All Over India**

**(DTDC & INDIA POST)**

# Power System - 2

Book:- Steven Son  
- Nagrath Kothari

- Standard book solved examples.
- IES mains solved problem.
- W.B. | IES previous year
- Gate previous year

--- Bhupendra Singh sir

## # Topics:

For Gate  
5 to 8

For ESE  
Mains (MIMP)

- ① Fault
- ② E.D.
- ③ Load flow
- ④ Stability

"No Selection, Without Revision"






# # Power Analysis of AC Circuit:

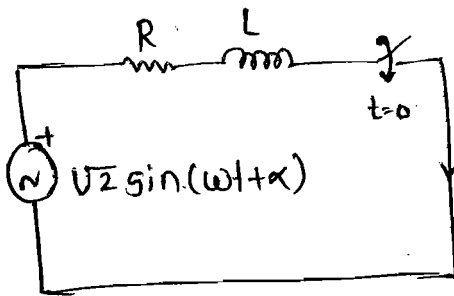
## o AC Circuit:

⇒ A circuit which is in steady state corresponding to a given sinusoidal excitation is called AC circuit.



Sinusoidal exponential  
 $i(t) = i_{SS} + i_{TR}$

--- Not an AC circuit.

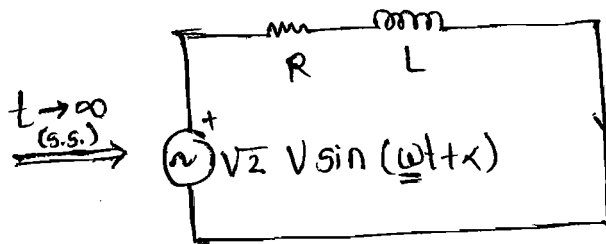

Response freq. is same as the source freq.

$$i(t) = \sqrt{2} \cdot I \sin(\omega t + \beta)$$

--- An AC circuit

- Steady state response nature depends upon the source.
- Transient response nature depends upon circuit itself.

•  $i(t) = i_{SS} + i_{TR}$  --- for Non-AC circuit

$$i(t) = \sqrt{2} \cdot I \sin(\omega t + \beta) + A e^{-t/\tau}$$


∴ Responses are Non-sinusoidal

•  $i(t) = \sqrt{2} \cdot I \sin(\omega t + \beta)$  --- for AC circuit.

∴ Response are sinusoidal.

⇒ All the responses of an AC ckt. are sinusoids with freq. equal to the source freq.

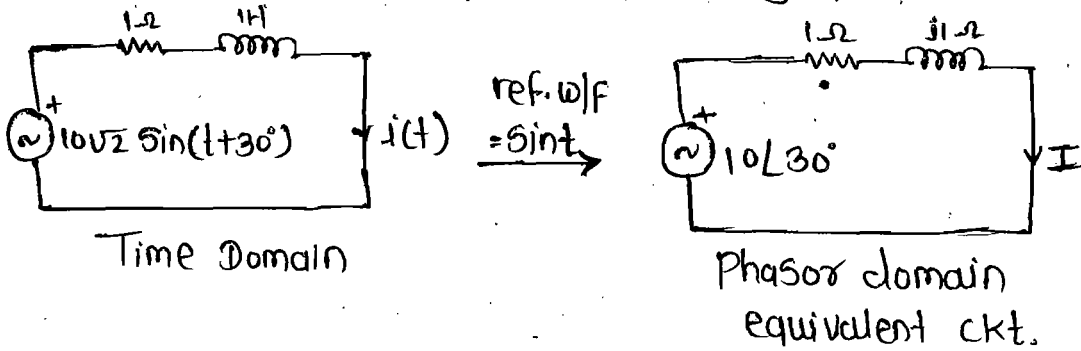⇒ The magnitude (RMS Value) and phase of a response in an AC circuit is computed using phasor technique.



•  $I = \frac{10\angle 30^\circ}{1+j1}$  --- phasor form

$I = \frac{10}{\sqrt{2}} \angle -15^\circ$

Time domain	→	R	L	C
Phasor	→	R	$j\omega L$	$\frac{1}{j\omega C}$
Freq.	→	R	$sL$	$\frac{1}{sC}$

•  $i(t) = 10 \sin(t - 15^\circ)$  --- time domain.

$v_L(t) = 10 \sin(t + 75^\circ)$  ←  $V_L = \frac{10}{\sqrt{2}} \angle 75^\circ$   
 $= \left[ \frac{j1}{1+j1} 10\angle 30^\circ \right]$

⊙ Power Calculation:

⇒ Complex power absorbed by AC ckt. / AC ckt. element:- (Fig ⊙)

$S = VI^* = P + jQ$

Where,

P = Active Power / Avg. power / Useful power  
 Absorbed by AC ckt. / AC ckt. element (Watt)

$\phi$  = Reactive power / lagging VAR absorbed by AC circuit / AC ckt. element (VAR).

$P > 0$  : ckt / ckt element absorbed Active power

$P < 0$  : ckt / ckt. element delivers Active power.

$Q > 0$  : ckt. / ckt. element absorbed Reactive power. (S)

ckt / ckt. element absorbed Lagging VAR (S)

ckt. / ckt. element delivers Leading VAR

$\phi < 0$  : ckt. / ckt. element delivers reactive power (S)

ckt. / ckt. element delivers lagging VAR (S)

ckt. / ckt. element leading VAR (absorbed)

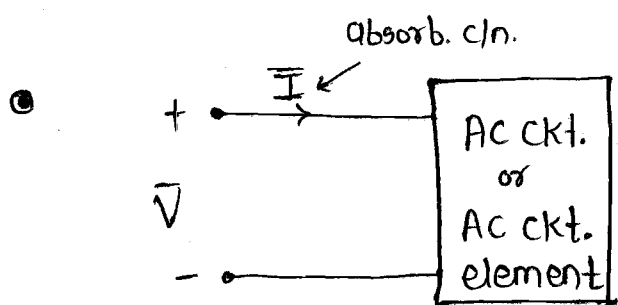


Fig (a)

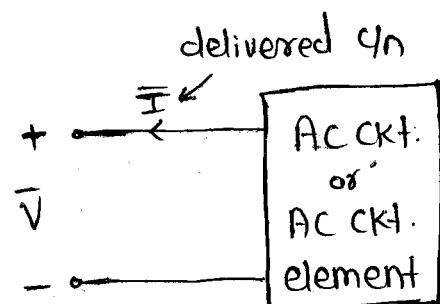


Fig (b)

$\Rightarrow$  Complex power delivered by AC ckt. / AC ckt. element :- (Fig (b))

$$S = \bar{V} \bar{I}^* = P + jQ$$

where,

$P$  = Active power delivered by AC ckt. / AC ckt. element

$Q$  = Reactive power / lagging VAR delivered by AC ckt. / AC ckt. element.

$P > 0$  : ckt. delivers active power


$P < 0$  : ckt. absorbs Active power.

$\phi > 0$  : ckt. delivers reactive power.

ckt. delivers lagging VAR / absorbed lead VAR.

$\phi < 0$  : ckt. absorbed reactive power.

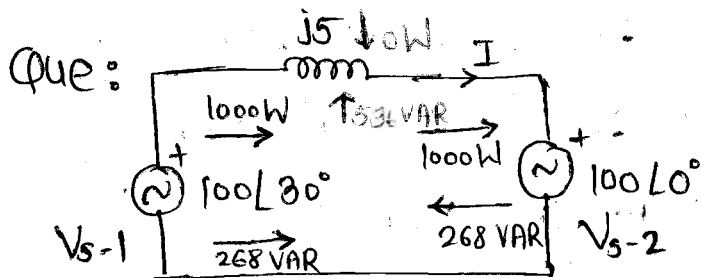ckt. deliver absorbed lagging VAR / delivered lead VAR.



• Pure L & C absorbs 0W  
in AC condition.

• L absorbs Reactive power

• C delivers Reactive power

Sol<sup>n</sup>:

$$I = \frac{100\angle 30^\circ - 100\angle 0^\circ}{j5}$$

$$I = 10.35\angle 15^\circ$$

• Complex power absorbed by  $V_{s-2}$

$$S = VI^*$$

$$= (100\angle 0^\circ) \cdot (10.35\angle 15^\circ)^*$$

$$= (100\angle 0^\circ) \cdot (10.35\angle -15^\circ)$$

$$S = 1000 - j268$$

$\therefore$  Vtg. source absorbs  $1000W$  & delivers  $268 VAR$ .

- Complex Power delivered by  $V_s - 1$

$$S = VI^*$$


$$= (100 \angle 30^\circ) (10.35 \angle 75^\circ)^*$$

$$S = 1000 + j268$$



∴ Vtg. source - 1 delivers 1000W & delivers 268 VAR.

⊛ Note :

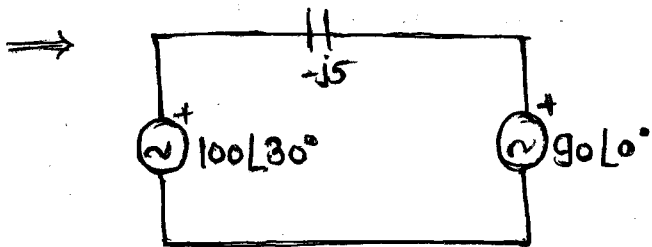
In power system, Active Power always flows from leading vtg. source towards lagging vtg. source, whereas, reactive power generally flows from high vtg. magnitude towards low vtg. magnitude.



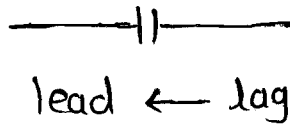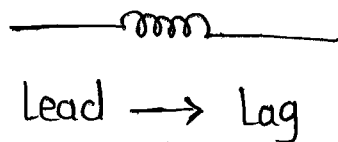In power s/m. ckt. in series branch always inductor & in parallel branch always capacitor.



⊙

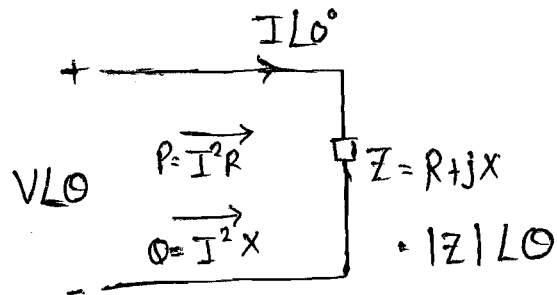

$$|Z| = \sqrt{R^2 + X^2}$$

$$\theta = \tan^{-1}(X/R)$$

$$Z = R + jX = \begin{matrix} X +ve = L \\ X -ve = C \end{matrix}$$

$$Y = G + jB = \begin{matrix} B +ve = C \\ B -ve = L \end{matrix}$$

$$Y = G + jB = \begin{matrix} B +ve = C \\ B -ve = L \end{matrix}$$

$$B -ve = L$$

⊙ Complex power abs. by  $Z = R + jX$


$$S = (V \angle \theta) (I \angle \theta)^* = P + jQ = VI \angle \theta$$

(Active)  $P = VI \cos \theta = VI \frac{R}{|Z|} = I^2 R$  --- (Real part of complex power)

(Reactive)  $Q = VI \sin \theta = VI \frac{X}{|Z|} = I^2 X$  --- (Imag. part of complex power)

⊙ Apparent power:

$$S = I^2 |Z| = VI \text{ --- (magnitude of complex power)}$$

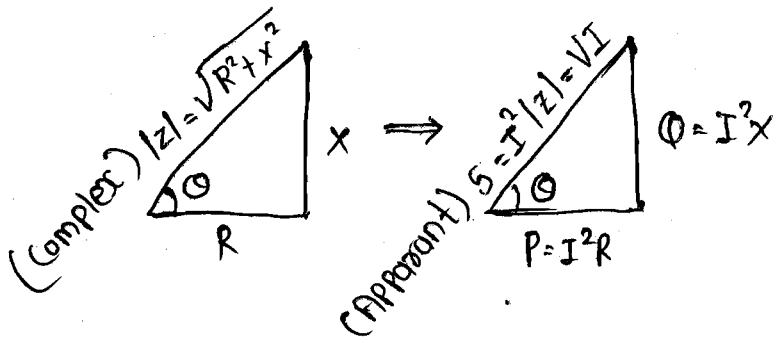

--- power triangle

⊙ Power factor:  $\cos \theta = \frac{P}{S} = \frac{\text{Active Power}}{\text{Apparent Power}}$  --- P.F.

$$\cos \theta = \cos \tan^{-1}\left(\frac{Q}{P}\right) \text{ --- m/c}$$

$\theta$  = angle bet<sup>n</sup> vtg. phasor & c/n phasor

- Resistance: It is the real part of impedance.

- Reactance: It is the imaginary part of impedance.

$R \geq 0 \rightarrow P \geq 0 \Rightarrow Z = R + jX$  : cant delivered  
Active power

⊙  $X > 0$  (Inductive Impedance)

- Inductive impedance absorbed Rea. power
- Inductive impedance absorbed Lag. VAR
- Inductive impedance del. lead. VAR.


$X = 0$  (Resistive Impedance)

-  $\phi = 0$

$X < 0$  (Capacitive Impedance)

- capacitive impedance del. Reactive power
- capacitive impedance del. Lag. VAR
- capacitive impedance absorbed lead. VAR.




e.g.

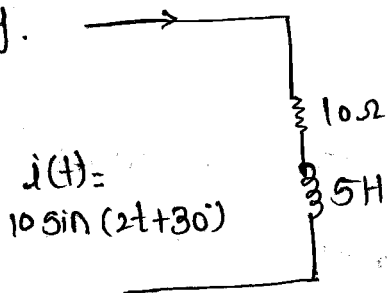




sol<sup>n</sup>:

$P = I^2 R = \left(\frac{10}{\sqrt{2}}\right)^2 \cdot 10 \text{ Watt}$

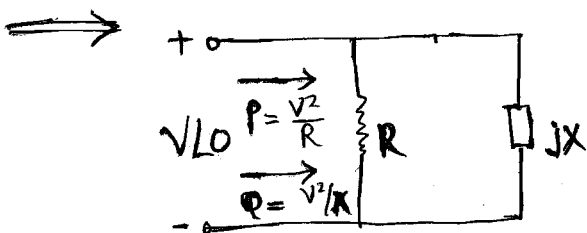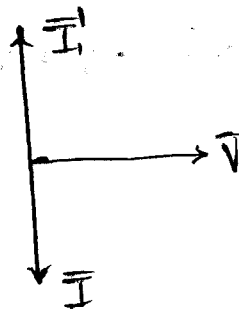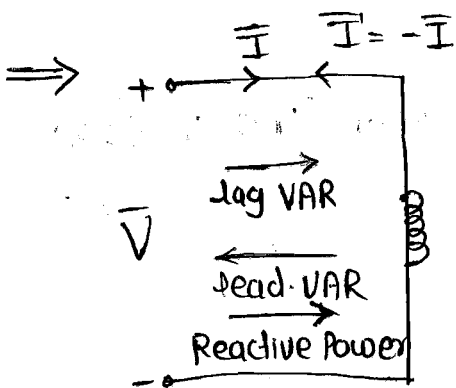$Q = I^2 X = \left(\frac{10}{\sqrt{2}}\right)^2 \cdot (2 \times 5) \text{ VAR}$



• Significance of Reactive Power:

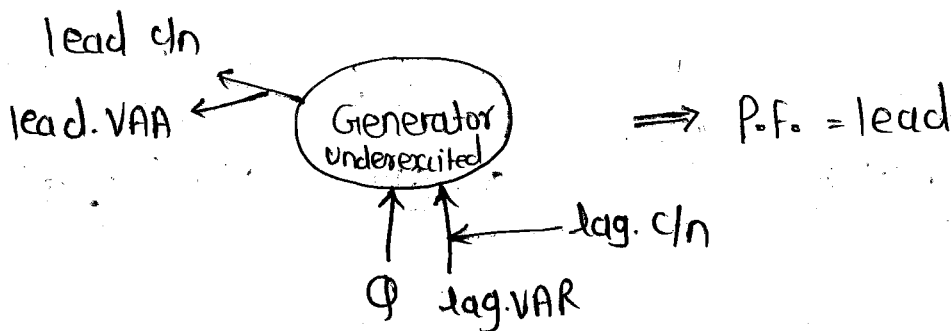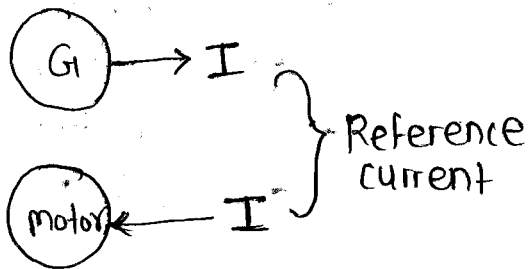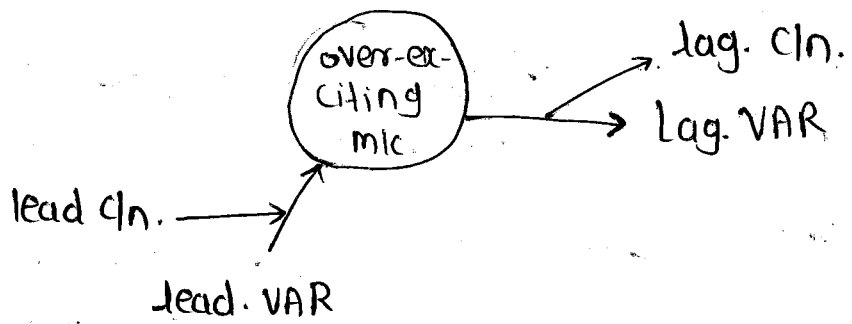

• Flux requirement depends upon operating voltage.



# # Balance 3- $\phi$ System |

9/06/2021  
lec-2

## Concept of phase Sequence

$\Rightarrow$  A polyphase system is said to be balance if

① The magn. of corresponding quantities are equal in each phase.

② The phase difference bet<sup>n</sup> the corresponding quantities is given by,

$$\theta = \frac{360^\circ}{n} ; n \neq 2$$

$$= 90 ; n = 2$$

$$= \frac{360}{3} ; n = 3 \quad \dots \text{for } 3\text{-}\phi \text{ s/m}$$

Que. Current in two phases of two phase s/m is given below.

$$i_a = \sqrt{2} I \cos(\omega t - \phi_1)$$

$$i_b = \sqrt{2} I \sin(\omega t - \phi_2)$$


Find the relationship bet<sup>n</sup>  $\phi_1$  &  $\phi_2$ , so that the s/m is balance.

Sol<sup>n</sup>: leading  $\rightarrow$  +ve  $\Rightarrow$  Anticlockwise

$\cos \omega t$  leads  
 $\sin \omega t$  by  $90^\circ$ .




Lagging  $\rightarrow$  -ve  $\Rightarrow$  clockwise

$$\boxed{\therefore \phi_1 = \phi_2}$$


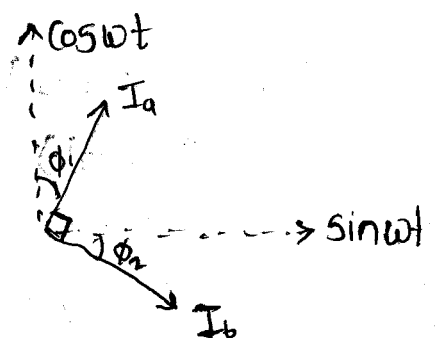


⊙ For 3- $\phi$  System:

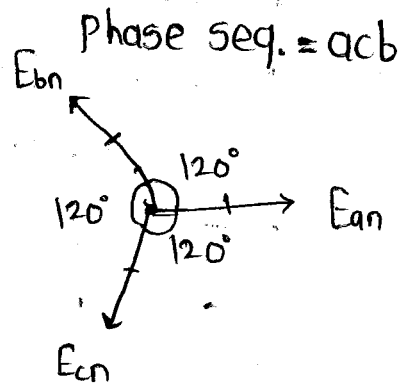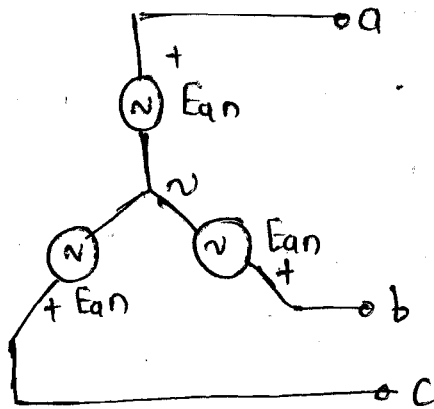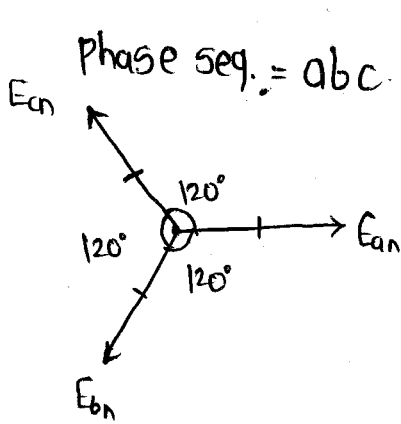Consider, a balance 3- $\phi$  (Ideal) Voltage Source. :  
 ↓  
 No impedance



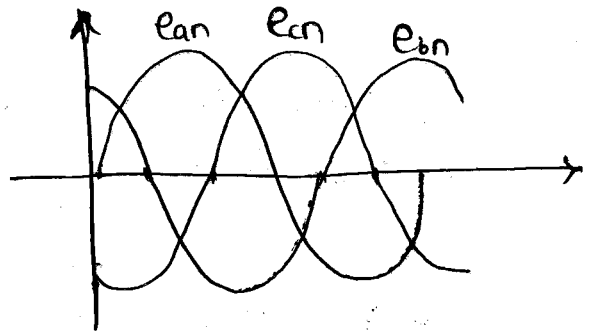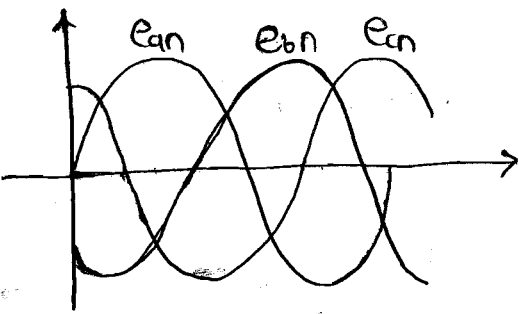⇒ Both phasor dia. is represent balance condition but they do differ phase sequence.





⊙ Phase sequence :

Phase sequence is defined as the order in which the phases attained their maximum value.

⇒ 3- $\phi$  (Ideal) voltage source is ckt. equivalent of a (Ideal) synchronous machine.

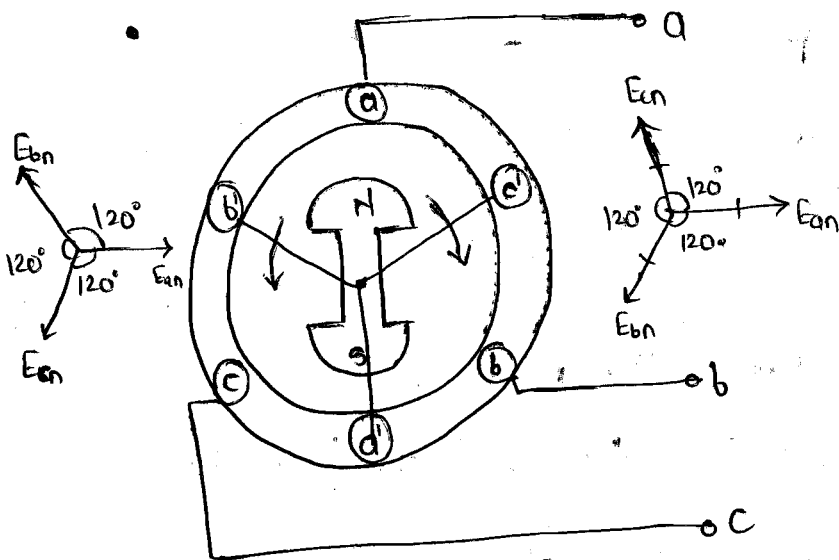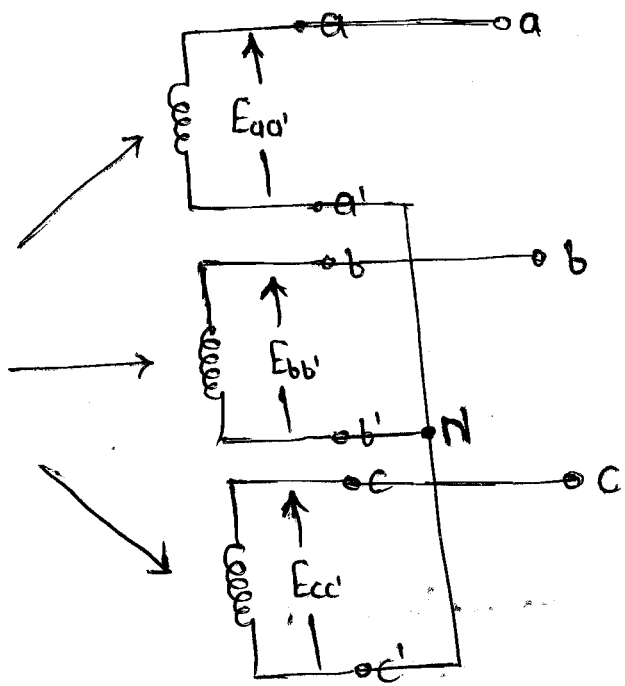
Identical winding  
in all three phases  
to produce equivalent  
magnitude of a  
voltage in all 3- $\phi$ 's.



$$\phi_e = \frac{P}{2} \phi_m$$

① Note:

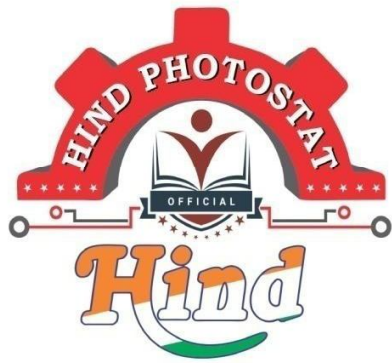- ① Only two type of phase sequence (abc & acb) is possible in a 3- $\phi$  system.
- ② The phase sequence can be reverse by reversing the rotation of rotor, but practically doing it is not possible.
- ③ phase sequence cannot be reverse by reversing the field excitation.



# HindPhotostat



## Hind Photostat & Book Store

Best Quality Classroom Topper Hand Written Notes to Crack GATE, IES, PSU's & Other Government Competitive/ Entrance Exams

### MADE EASY ELECTRICAL ENGINEERING Transformer Machine By.Murli Sir

- Theory
- Explanation
- Derivation
- Example
- Shortcuts
- Previous Years Question With Solution

Visit us:-[www.hindphotostat.com](http://www.hindphotostat.com)

Courier Facility All Over India  
(DTDC & INDIA POST)  
Mob-9311989030



# HindPhotostat



**MADE EASY , IES MASTER , ACE ACADEMY , KREATRYX**

**ESE , GATE, PSU BEST QUALITY TOPPER HANDWRITTEN NOTES  
MINIMUM PRICE AVAILABLE @ OUR WEBSITE**

- |                                |                           |
|--------------------------------|---------------------------|
| 1. ELECTRONICS ENGINEERING     | 2. ELECTRICAL ENGINEERING |
| 3. MECHANICAL ENGINEERING      | 4. CIVIL ENGINEERING      |
| 5. INSTRUMENTATION ENGINEERING | 6. COMPUTER SCIENCE       |

**IES , GATE , PSU TEST SERIES AVAILABLE @ OUR WEBSITE**

❖ IES -PRELIMS & MAINS

❖ GATE

➤ **NOTE;- ALL ENGINEERING BRANCHS**

➤ **ALL PSUs PREVIOUS YEAR QUESTION PAPER @ OUR WEBSITE**

## **PUBLICATIONS BOOKS -**

**MADE EASY , IES MASTER , ACE ACADEMY , KREATRYX , GATE ACADEMY , ARIHANT , GK**

**RAKESH YADAV , KD CAMPUS , FOUNDATION , MC -GRAW HILL (TMH) , PEARSON...OTHERS**

**HEAVY DISCOUNTS BOOKS AVAILABLE @ OUR WEBSITE**

<b>F230, Lado Sarai New Delhi-110030 Phone: 9311 989 030</b>	<b>Shop No: 46 100 Futa M.G. Rd Near Made Easy Ghitorni, New Delhi-30 Phone:8595382884</b>	<b>F518 Near Kali Maa Mandir Lado Sarai New Delhi-110030 Phone: 9560 163 471</b>	<b>Shop No.7/8 Saidulajab Market Neb Sarai More, Saket, New Delhi-30</b>
--	--	--	--

**Website: [www.hindPhotostat.com](http://www.hindPhotostat.com)**

**Contact Us: 9311 989 030**

**Courier Facility All Over India**

**(DTDC & INDIA POST)**

## - TRANSFORMERS :-

### Definition :

(i) Transformer is a static device which transfer AC electrical energy from one circuit to the another through the action of magnetic field.

### key word :

Transfers AC electric energy - through magnetic field

circuit is generalised word for coil and winding.

A magnet is surrounded by magnetic field called flux. Flux is a life of a machine whether you take DC M/C, Induction M/C, synchronous M/C, transformer, these all are working on the flux only. So a machine work because of flux only.

All the electricity we get is through flux only.

A generator works because of flux & a motor rotates because of flux, a transformer transfer the power because of flux only.

(ii) Transformer<sup>mut</sup> operate on the principle of mutual induction. b/w two or more magnetically coupled coils.


key word :- Mutual induction principle b/w two or more magnetically coupled circuits (coil/winding)

(iii) It transform AC electrical energy or power at one voltage level to another voltage level without the change in frequency & power

key word :- Transfer Electrical energy at one voltage level to another (at same F & P)

constant power means that the transformer have highest possible  $\eta$  in all electrical machinery/devices. Efficiency is almost 100% or in a well design transformer efficiency is close to 100%. i.e; if p power is equal to o/p power, the losses are very small & they can be neglected.

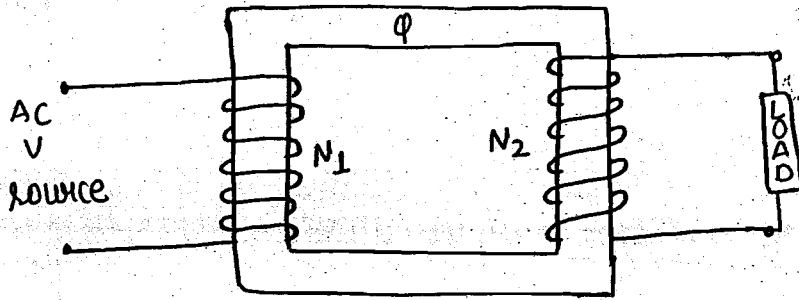(iv) magnetically coupled coils wound on common ferromagnetic core.



the connection b/w these two coils is due to the common flux in the common core. i.e; these two coils are magnetically coupled when we connect the AC power source then there will be flux in transformer. then it produce voltage in another side.

- The coil which is connected to the source is called input winding or primary winding.
- the other winding where is load connected is called secondary or o/p winding.
- If transformer having third winding then it is called as tertiary winding.
- one winding receive the power another one is delivering the power.

### 10 Aspects of transformer :

(i) static device i.e; no moving or rotating part, everything is stationary

Flux : stationary  
conductor : stationary

(ii) Electromagnetic energy conversion device (Internally)  
i.e; externally no energy conversion is occurs

i/p is electrical → o/p is electrical

Internally operation ⇒ Electrical → Magnetic field → Electrical

NOTE :- Transformer is not a electrical machine. It is a device. But we take like as a machine only.

Machine is a electromechanical energy conversion device.

i.e; Electrical ⇌ Mechanical

- (iii) It is singly excited device i.e; we applied voltage to only one winding of a transformer.
- (iv) constant flux device neglecting the transient change in flux.
- (v) constant power
- (vi) constant frequency
- (vii) Magnetically coupled circuits [-ve magnetic coupling in accordance to lenz's law]
- (viii) It is automatic control system [with negative feedback]
- (ix) It is phase shifting device [w.r.t. voltage]
- (x) It works only on AC

### Classification of transformer :-

#### 1. Based on No. of windings :-

If there is 1 winding  $\rightarrow$  Auto T/F

2 windings (primary & secondary)

3 windings (primary & secondary, tertiary)

#### 2. Based on core construction :-

(a) core type transformer

(b) shell type transformer

#### 3. Based on NO. of phases :-

(a) 1- $\phi$  T/F

Three 1- $\phi$  T/F are internally connected to 3- $\phi$  T/F bank.

(b) 3- $\phi$  T/F

#### 4. Based on the operating frequency


(a) Power frequency T/F (25-500 Hz)

(b) Audio frequency T/F (20 Hz to 20 kHz)




5. Based on Application : Many Numerous kind of T/F

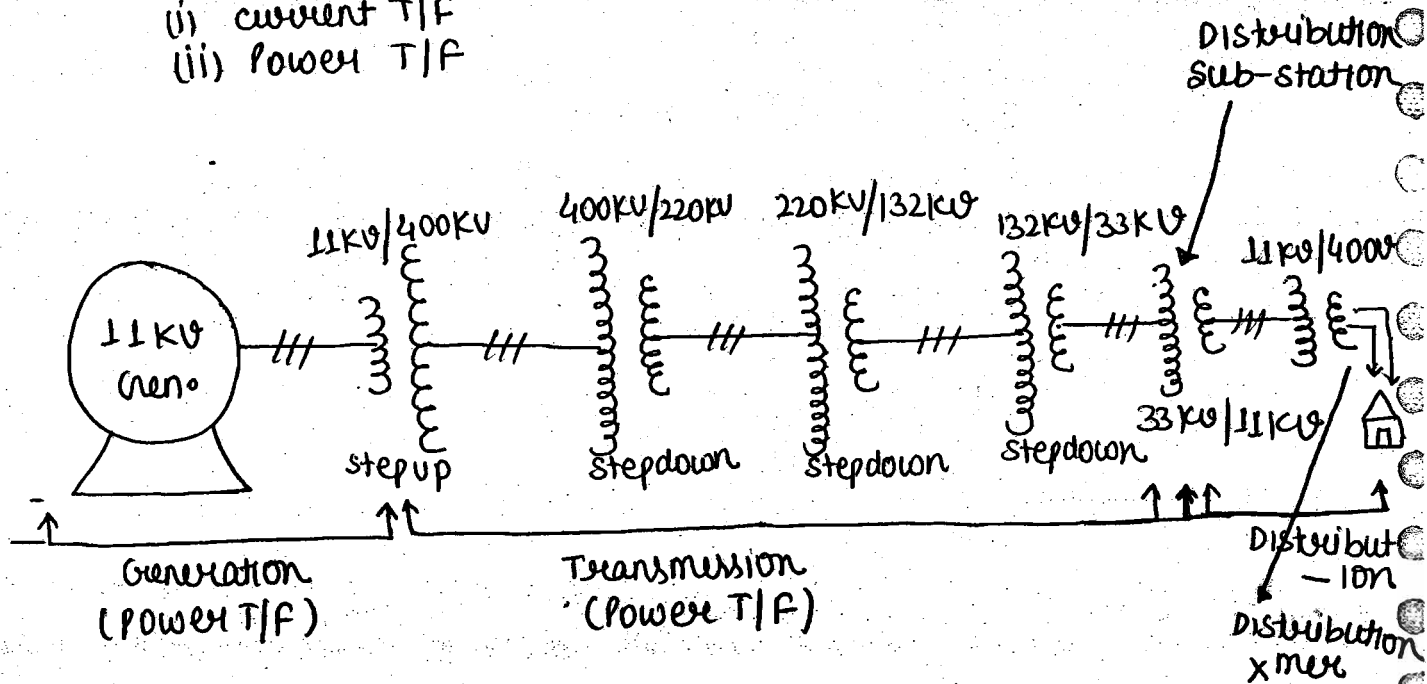- (a) Power system
  - (i) Power T/F
  - (ii) Distribution T/F
- (b) Power electronic
  - (i) Pulse T/F
  - (ii) Gate pulse triggering
- (c) Instrumentation
  - (i) current T/F
  - (ii) power T/F
- (d) Electronic & control system




NOTE:-

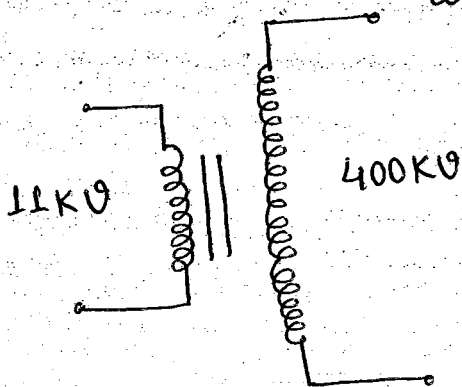Step up  $\longleftrightarrow$  Step down T/F  
 can be used as



Step up mode : 11KV called primary winding.  
 400KV called secondary winding.

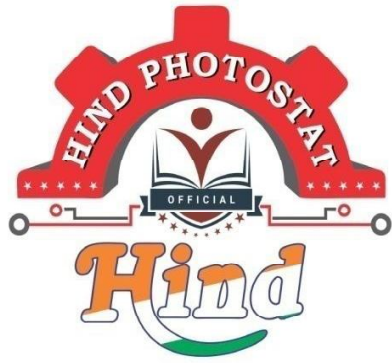Step down mode : 11KV called secondary winding  
 400KV called primary winding.



# HindPhotostat



## Hind Photostat & Book Store

Best Quality Classroom Topper Hand Written Notes to Crack GATE, IES, PSU's & Other Government Competitive/ Entrance Exams

**MADE EASY**  
**ELECTRICAL ENGINEERING**  
**INDUCTION Machine**  
**By.Murli Sir**

- Theory
- Explanation
- Derivation
- Example
- Shortcuts
- Previous Years Question With Solution

Visit us:-[www.hindphotostat.com](http://www.hindphotostat.com)

Courier Facility All Over India  
(DTDC & INDIA POST)  
Mob-9311989030



# HindPhotostat



**MADE EASY , IES MASTER , ACE ACADEMY , KREATRYX**

**ESE , GATE, PSU BEST QUALITY TOPPER HAND WRITTEN NOTES  
MINIMUM PRICE AVAILABLE @ OUR WEBSITE**

- |                                |                           |
|--------------------------------|---------------------------|
| 1. ELECTRONICS ENGINEERING     | 2. ELECTRICAL ENGINEERING |
| 3. MECHANICAL ENGINEERING      | 4. CIVIL ENGINEERING      |
| 5. INSTRUMENTATION ENGINEERING | 6. COMPUTER SCIENCE       |

**IES , GATE , PSU TEST SERIES AVAILABLE @ OUR WEBSITE**

- ❖ IES –PRELIMS & MAINS
- ❖ GATE

➤ **NOTE;- ALL ENGINEERING BRANCHS**

➤ **ALL PSUs PREVIOUS YEAR QUESTION PAPER @ OUR WEBSITE**

## **PUBLICATIONS BOOKS -**

**MADE EASY , IES MASTER , ACE ACADEMY , KREATRYX , GATE ACADEMY , ARIHANT , GK  
RAKESH YADAV , KD CAMPUS , FOUNDATION , MC –GRAW HILL (TMH) , PEARSON...OTHERS**

**HEAVY DISCOUNTS BOOKS AVAILABLE @ OUR WEBSITE**

<b>F230, Lado Sarai New Delhi-110030 Phone: 9311 989 030</b>	<b>Shop No: 46 100 Futa M.G. Rd Near Made Easy Ghitorni, New Delhi-30 Phone: 9711475393</b>	<b>F518 Near Kali Maa Mandir Lado Sarai New Delhi-110030 Phone: 9560 163 471</b>	<b>Shop No.7/8 Saidulajab Market Neb Sarai More, Saket, New Delhi-30</b>
--	---	--	--

**Website: [www.hindPhotostat.com](http://www.hindPhotostat.com)**

**Contact Us: 9311 989 030**

**Courier Facility All Over India**

**(DTDC & INDIA POST)**

## - Induction machine :-

Due to complex construction, commutation problems, maintenance DC m/c find lesser practical applications.

while AC motors has simple construction, less maintenance hence these are most popular (85% motors)

- (i) Induction generator
- (ii) Induction motor


### Rotating Magnetic field (RMF) :-

In IM, the flux is not stationary, it is rotating.

The basic requirement to produce the rotating magnetic field is

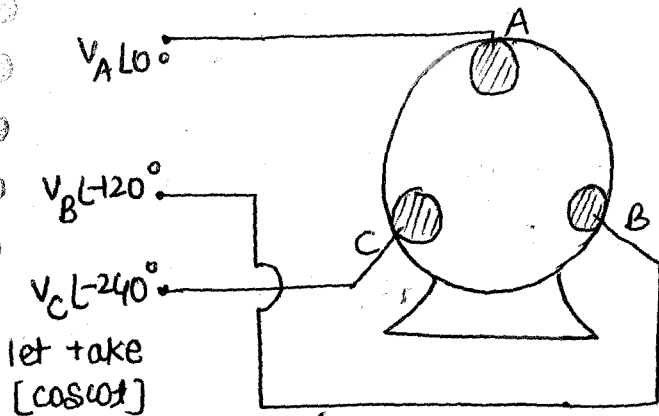- (i) 3  $\phi$  supply ( $120^\circ E$  phase displacement  $\omega \cdot t \cdot \text{time}$ )
  - (ii) 3  $\phi$  winding ( $120^\circ E$  phase displacement  $\omega \cdot t \cdot \text{space}$ )
- } Balance

If we want to generate 3-ph voltages which has  $120^\circ E$  phase displacement we have to design a winding which has exactly  $120^\circ E$  space displacement, the space displacement which we provide in the winding will create time displacement in the voltages which are induced.



Balance winding i.e; Number of turns are equal in all the winding.

Balance supply i.e;  $|V_A| = |V_B| = |V_C|$  &  $120^\circ E$  displacement

$$\text{mmf} = NI$$

$V_A L-0^\circ$	$\longrightarrow I_A N_A$	$\longrightarrow F_A$	$\longrightarrow \vec{\phi}_A$
$V_B L-120^\circ$	$\longrightarrow I_B N_B$	$\longrightarrow F_B$	$\longrightarrow \vec{\phi}_B$
$V_C L-240^\circ$	$\longrightarrow I_C N_C$	$\longrightarrow F_C$	$\longrightarrow \vec{\phi}_C$

$$\text{Net mmf produce} = \vec{F}_A + \vec{F}_B + \vec{F}_C$$

$$\text{Net flux produce} = \vec{\phi}_A + \vec{\phi}_B + \vec{\phi}_C$$

Now,  $I_A = I_m \cos \omega t$

$$N_A = N \cos \theta$$

$$I_B = I_m \cos (\omega t - 120^\circ)$$

$$N_B = N \cos (\theta - 120^\circ)$$

$$I_C = I_m \cos (\omega t - 240^\circ)$$

$$N_C = N \cos (\theta - 240^\circ)$$

where  $\omega t =$  time displacement angle (ele.)

$\theta =$  space displacement angle (ele.)

$$F_A = I_A N_A = I_m \cos \omega t \cdot N \cos \theta$$

$$F_B = I_B N_B = I_m \cos(\omega t - 120^\circ) \cdot N \cos(\theta - 120^\circ)$$

$$F_C = I_C N_C = I_m \cos(\omega t - 240^\circ) \cdot N \cos(\theta - 240^\circ)$$

$$\cos A \cdot \cos B = \frac{1}{2} [\cos(A+B) + \cos(A-B)]$$

Net / Resultant mmf  $F_{net} = F_A + F_B + F_C$

$$F_{net} = I_m N [\cos \omega t \cdot \cos \theta + \cos(\omega t - 120^\circ) \cdot \cos(\theta - 120^\circ) + \cos(\omega t - 240^\circ) \cdot \cos(\theta - 240^\circ)]$$

$$= I_m N \left[ \frac{1}{2} \{ \cos(\omega t + \theta) + \cos(\omega t - \theta) \} + \frac{1}{2} \{ \cos(\omega t - 240^\circ + \theta - 120^\circ) + \cos(\omega t - 120^\circ - \theta + 120^\circ) \} + \frac{1}{2} \{ \cos(\omega t - 240^\circ + \theta - 240^\circ) + \cos(\omega t - 240^\circ - \theta + 240^\circ) \} \right]$$

$$= \frac{I_m N}{2} \left[ \overset{*}{\cos(\omega t + \theta)} + \overset{*}{\cos(\omega t - \theta)} + \overset{*}{\cos(\omega t + \theta - 240^\circ)} + \overset{*}{\cos(\omega t - \theta)} + \overset{*}{\cos(\omega t + \theta - 480^\circ)} + \overset{*}{\cos(\omega t - \theta)} \right] \quad [* + * + * = 0]$$

$$F_{net} = \frac{I_m N}{2} [3 \cos(\omega t - \theta)]$$

$$F_{net} = \frac{3}{2} I_m N \cos(\theta - \omega t)$$

(or)

$$F_{net} = \frac{3}{2} F_m \cos(\theta - \omega t)$$

i.e.; The net mmf wave is cosine or sine, it is travelling w.r.t. space & time both. So; it is function of space angle and time angle. If we don't have the two combination which are 3- $\phi$  supply ( $120^\circ$  E phase displacement) and 3-ph windg ( $120^\circ$  E phase displacement w.r.t. space) then mmf wave don't come like this.

$$\text{speed} = \frac{\text{Distance}}{\text{Time}}$$

Imagine mmf wave has some velocity or speed and displacement  $\omega t$ .

$$\text{speed} = \frac{\omega t}{t} = \omega \text{ Elect-rad/sec}$$

$$N = \text{rpm}$$

$$N/60 = \text{rps}$$

$$\omega = 2\pi f \text{ elet-rad/sec}$$

$$\omega_m = \frac{2\pi N}{60} \text{ mech-rad/sec}$$

$$\theta_e = \frac{P}{2} \theta_m$$

similarly,  $\omega_e = \frac{P}{2} \omega_m \Rightarrow 2\pi f = \frac{P}{2} \cdot \frac{2\pi N}{60}$


$$f = \frac{PN}{120}$$

so,  $N = \frac{120f}{P}$

we know that  $F_{net} = \frac{3}{2} F_m \cos(\theta - \omega t)$

let  $\omega t = 0$  then  $F_{net} = \frac{3}{2} F_m \cos \theta$

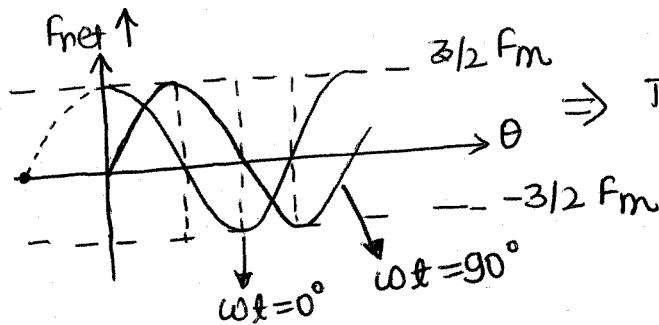let  $\omega t = 90^\circ$  then  $F_{net} = \frac{3}{2} F_m \sin \theta$



Travelling or moving with constant ampli. w.r.t. space

If

$$I_A = I_m \cos \omega t$$
$$I_B = I_m \cos (\omega t)$$
$$I_C = I_m \cos (\omega t)$$

$$N_A = N \cos \theta$$
$$N_B = N \cos (\theta - 120^\circ)$$
$$N_C = N \cos (\theta - 240^\circ)$$

Then  $F_{net} = 0$  if voltage and current are co-phased.


NOTE: By reversing the phase sequence the direction of movement of mmf is also reverse.

Another approach:-

$$\phi_A = \phi_m \sin \omega t$$

$$\phi_B = \phi_m \sin (\omega t - 120^\circ)$$
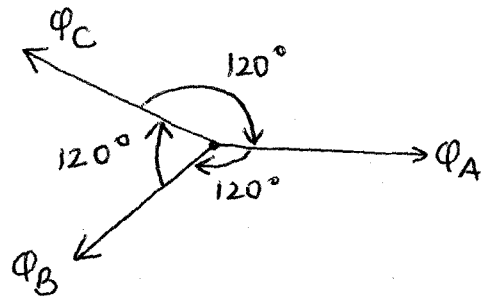
$$\phi_C = \phi_m \sin (\omega t - 240^\circ)$$




At  $\omega t = 0^\circ$

$$\phi_A = 0$$

$$\phi_B = -\sqrt{3}/2 \phi_m$$

$$\phi_C = \sqrt{3}/2 \phi_m$$

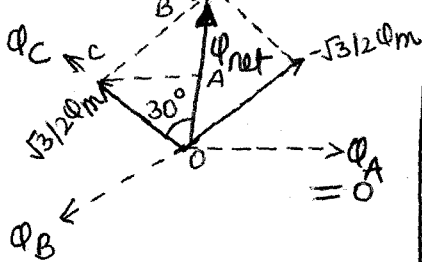

$OB = 2OA$ ,  $\angle AOC = 30^\circ$

From  $\Delta OAC$

$$\cos 30^\circ = \frac{OA}{OC}$$

$$OA = OC \cos 30^\circ$$

$$= \frac{\sqrt{3}}{2} \phi_m \cdot \frac{\sqrt{3}}{2}$$

$$OA = \frac{3}{4} \phi_m$$

$$OB = \phi_{net} = 2OA$$


$$\phi_{net} = \frac{3}{2} \phi_m$$

At  $\omega t = 60^\circ$

$$\phi_A = \sqrt{3}/2 \phi_m$$

$$\phi_B = -\sqrt{3}/2 \phi_m$$

$$\phi_C = 0$$

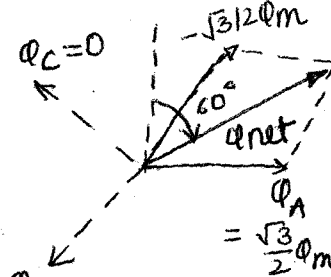


$$\phi_{net} = \frac{3}{2} \phi_m$$

At  $\omega t = 120^\circ$

$$\phi_A = \sqrt{3}/2 \phi_m$$

$$\phi_B = 0$$

$$\phi_C = -\sqrt{3}/2 \phi_m$$

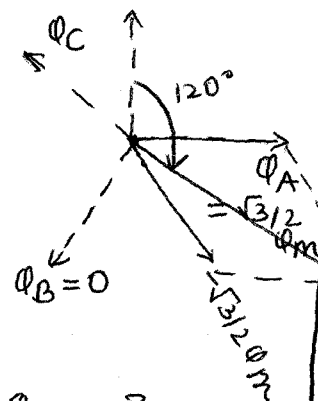


$$\phi_{net} = \frac{3}{2} \phi_m$$

At  $\omega t = 180^\circ$

$$\phi_A = 0$$

$$\phi_B = \sqrt{3}/2 \phi_m$$

$$\phi_C = -\sqrt{3}/2 \phi_m$$

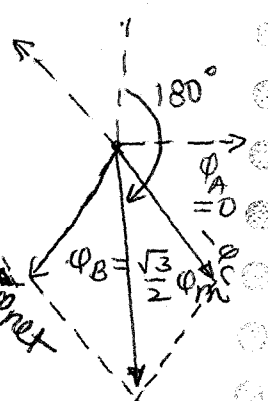

$$\phi_{net} = \frac{3}{2} \phi_m$$

synchronous




i.e; time (moving together with time)

when flux rotate in the m/c then that flux speed will be synchronous speed. It depends on two factors which are frequency and number of pole.

$$\phi_{net} = \frac{3}{2} \phi_m$$

$$N_s = \frac{120f}{P}$$

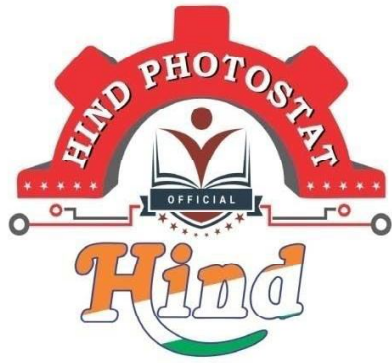

# HindPhotostat



## Hind Photostat & Book Store

Best Quality Classroom Topper Hand Written Notes to Crack GATE, IES, PSU's & Other Government Competitive/ Entrance Exams

### MADE EASY SYNCHRONOUS MACHINE By-MURLI Sir

- Theory
- Explanation
- Derivation
- Example
- Shortcuts
- Previous Years Question With Solution

Visit us:-[www.hindphotostat.com](http://www.hindphotostat.com)

Courier Facility All Over India  
(DTDC & INDIA POST)  
Mob-9311989030





# HindPhotostat



**MADE EASY , IES MASTER , ACE ACADEMY , KREATRYX**

**ESE , GATE, PSU BEST QUALITY TOPPER HAND WRITTEN NOTES  
MINIMUM PRICE AVAILABLE @ OUR WEBSITE**

- |                                |                           |
|--------------------------------|---------------------------|
| 1. ELECTRONICS ENGINEERING     | 2. ELECTRICAL ENGINEERING |
| 3. MECHANICAL ENGINEERING      | 4. CIVIL ENGINEERING      |
| 5. INSTRUMENTATION ENGINEERING | 6. COMPUTER SCIENCE       |

**IES , GATE , PSU TEST SERIES AVAILABLE @ OUR WEBSITE**

❖ IES –PRELIMS & MAINS

❖ GATE

➤ **NOTE;- ALL ENGINEERING BRANCHS**

➤ **ALL PSUs PREVIOUS YEAR QUESTION PAPER @ OUR WEBSITE**

## **PUBLICATIONS BOOKS -**

**MADE EASY , IES MASTER , ACE ACADEMY , KREATRYX , GATE ACADEMY , ARIHANT , GK**

**RAKESH YADAV , KD CAMPUS , FOUNDATION , MC –GRAW HILL (TMH) , PEARSON...OTHERS**

**HEAVY DISCOUNTS BOOKS AVAILABLE @ OUR WEBSITE**

<b>F230, Lado Sarai New Delhi-110030 Phone: 9311 989 030</b>	<b>Shop No: 46 100 Futa M.G. Rd Near Made Easy Ghitorni, New Delhi-30 Phone:9711475393</b>	<b>F518 Near Kali Maa Mandir Lado Sarai New Delhi-110030 Phone: 9560 163 471</b>	<b>Shop No.7/8 Saidulajab Market Neb Sarai More, Saket, New Delhi-30</b>
--	--	--	--


**Website: [www.hindPhotostat.com](http://www.hindPhotostat.com)**

**Contact Us: 9311 989 030**

**Courier Facility All Over India**

**(DTDC & INDIA POST)**

# SYNCHRONOUS MACHINES

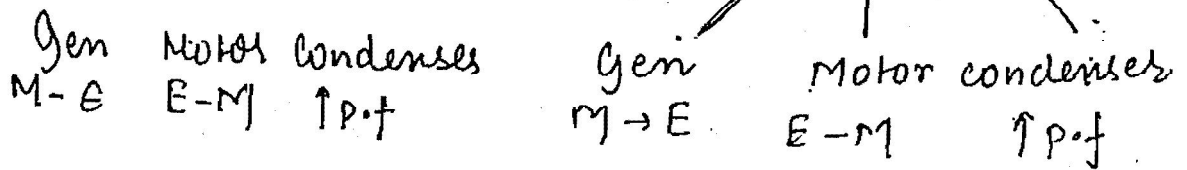

- Commonly used generator in Power Plants universally, also called as alternator as it generates ac voltage which is stepped up to much higher value and transmitted through X-lines.
- They run at a standard speed called as synchronous speed for given freq and No of poles
- These are doubly excited type because rotor is excited by dc supply as well as additional mechanical i/p is given across the rotor
- Principle of operation is according to Faraday Law.
- If a commutator is dropped from a dc generator and if two slip rings are used to collect it is a generator if it is rotated at synchronous speed it can be called as synchronous generator but with rotating armature and stationary field structures.
- In dc generator winding (armature should rotate) for commutator action. In alternators there is no such commutator therefore it is not necessary that the armature should be a rotating member; it can be either rotating or stationary.
- Small rating alternators < 5kVA only may have rotating armature but practically synchronous generators of large rating commonly contain

stationary armature rotating field structure.

## # Advantages of Stationary Armature:-

eg 500 MVA  
11 kV

$$I = \frac{500 \times 10^6}{\sqrt{3} \times 11 \times 10^3} \approx 26243 \text{ A}$$

\* Excit. Voltage is DC

125 - 500 V DC

1 MW power  $I = \frac{1000000}{500} \approx 2000 \text{ A}$

1) Simple Design:- To collect large current from rotating part, becomes very complicated practically and expensive because (3+1) slip ring with HV insulation and high current carrying capacity.

2) Insulation is effective if armature is on stationary part. Stationary slots will offer better insulation as well as they offer more space.

3) Efficient Cooling: It is easy to provide air passage, cooling tubes, water/hydrogen cooling on a stationary part.

4) More O/P: As the rotor is lighter in weight supports high speeds so for a given size it gives more O/P with more speed.

5) Right Construction: - As the winding is on stationary part it has more dynamic balance against electromagnetic stresses during S.C.

Due to more width of slot and teeth they are stronger.


- b) Leakage Reactance:- will be less because stator offers more width in the slots and contains more cu per slot. If it is on rotor depth will be high due to less space which produces more leakage reactance


## CONSTRUCTION DETAILS:-

- Like all other rotating electric machines it contain stationary part Stator, Rotating part Rotor with an air gap.
- The stator basically contain core and windings, rotor contains poles and field winding.
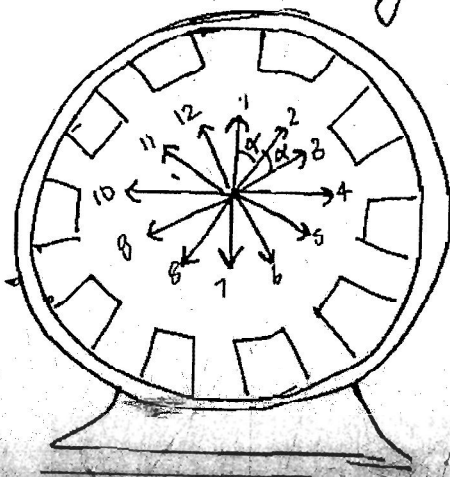
### # STATOR:-

- It contains an outer frame made up of cast iron or steel only for mechanical protection of the entire m/c there is a stator core made up of sheet steel (Si steel lam 0.5mm thickness) to produce least core losses.
- The stator core is punched into slots which are generally open type in practical synchronous m/c they contain 3- $\phi$  winding.



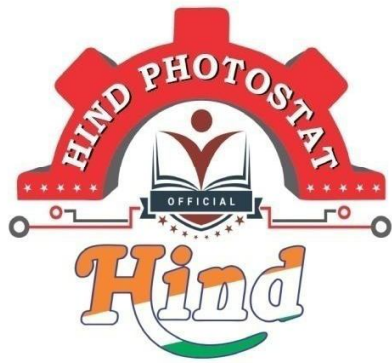

# HindPhotostat



## Hind Photostat & Book Store

Best Quality Classroom Topper Hand Written Notes to Crack GATE, IES, PSU's & Other Government Competitive/ Entrance Exams

### MADE EASY ELECTRICAL ENGINEERING

D.C. Machine  
By.Roshan Sir

- Theory
- Explanation
- Derivation
- Example
- Shortcuts
- Previous Years Question With Solution

Visit us:-[www.hindphotostat.com](http://www.hindphotostat.com)

Courier Facility All Over India  
(DTDC & INDIA POST)  
Mob-9311989030



# HindPhotostat



**MADE EASY , IES MASTER , ACE ACADEMY , KREATRYX**

**ESE , GATE, PSU BEST QUALITY TOPPER HAND WRITTEN NOTES  
MINIMUM PRICE AVAILABLE @ OUR WEBSITE**

- |                                |                           |
|--------------------------------|---------------------------|
| 1. ELECTRONICS ENGINEERING     | 2. ELECTRICAL ENGINEERING |
| 3. MECHANICAL ENGINEERING      | 4. CIVIL ENGINEERING      |
| 5. INSTRUMENTATION ENGINEERING | 6. COMPUTER SCIENCE       |

**IES , GATE , PSU TEST SERIES AVAILABLE @ OUR WEBSITE**

- ❖ IES –PRELIMS & MAINS
- ❖ GATE

➤ **NOTE;- ALL ENGINEERING BRANCHS**

➤ **ALL PSUs PREVIOUS YEAR QUESTION PAPER @ OUR WEBSITE**

## **PUBLICATIONS BOOKS -**

**MADE EASY , IES MASTER , ACE ACADEMY , KREATRYX , GATE ACADEMY , ARIHANT , GK**

**RAKESH YADAV , KD CAMPUS , FOUNDATION , MC –GRAW HILL (TMH) , PEARSON...OTHERS**

**HEAVY DISCOUNTS BOOKS AVAILABLE @ OUR WEBSITE**

<b>F230, Lado Sarai New Delhi-110030 Phone: 9311 989 030</b>	<b>Shop No: 46 100 Futa M.G. Rd Near Made Easy Ghitorni, New Delhi-30 Phone:9711475393</b>	<b>F518 Near Kali Maa Mandir Lado Sarai New Delhi-110030 Phone: 9560 163 471</b>	<b>Shop No.7/8 Saidulajab Market Neb Sarai More, Saket, New Delhi-30</b>
--	--	--	--

**Website: [www.hindPhotostat.com](http://www.hindPhotostat.com)**

**Contact Us: 9311 989 030**

**Courier Facility All Over India**

**(DTDC & INDIA POST)**

# ELECTRICAL

## MACHINE

Lecture 01

- Transformer ] static m/c
  - DC Machine
  - Induction machine
  - Synchronous machine ] Rotating m/c
- \*\* special machine

Basic Concepts of Rotating machine



Rotating m/c are of two types

- (1) Generator [mech energy → Electrical Energy] in presence of mag. field
- (2) Motor [Electrical energy → Mechanical Energy]

Magnetic field acts as a coupler b/w mechanical energy and electrical energy means it provides a medium from one form to another.

Basic Generator

Assumption:  
Lossless system

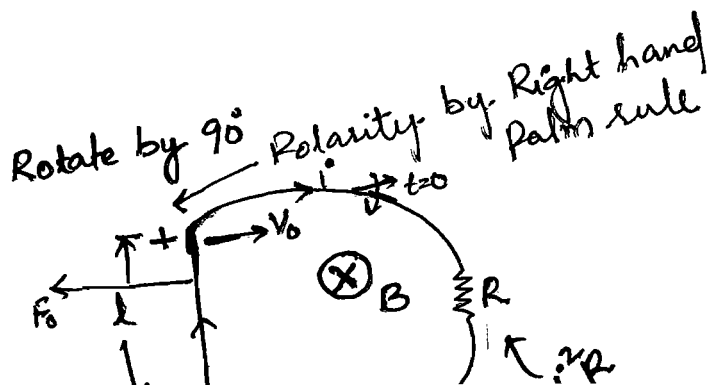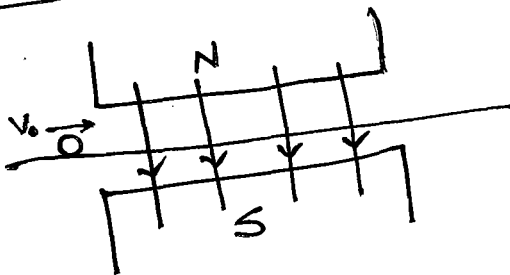

$$e = (\vec{v} \times \vec{B})l$$

$$|e| = vBl \sin\theta$$

$$E_0 = v_0 Bl \quad \because \theta = 90^\circ$$

At  $t = 0$

$$I_0 = \frac{E_0}{R} = \frac{v_0 Bl}{R}$$

As this current carrying conductor is placed in a magnetic field a force is developed in a conductor and is given by

$$F = \vec{l} \times \vec{B}$$


$$F_0 = \vec{I}_0 l \times \vec{B}$$

$$|F_0| = I_0 l B \sin\theta'$$

$$F_0 = I_0 l B \quad \because \theta = 90^\circ$$

(using Right hand Palm rule)

Free body Diagram (FBD) of Conductor

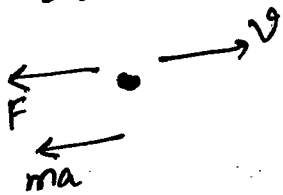

$$ma + f = 0$$

$$m \frac{dv}{dt} + ilB = 0$$

$$\frac{dv}{dt} = -\frac{ilB}{m} \rightarrow (1)$$

$$i = \frac{e}{R} = \frac{vBl}{R} \rightarrow (2)$$

From (1) & (2)

$$v B^2 l^2$$



$$\frac{dv}{v} = \frac{-B^2 l^2}{mR} dt$$

On integrating

$$\ln v = -\frac{B^2 l^2}{mR} t + K_1$$

$$v = e^{-\frac{B^2 l^2}{mR} t} + K_1$$

$$v = K_2 e^{-\frac{B^2 l^2}{mR} t}$$

At  $t=0$   $v=v_0$

$$v = v_0 e^{-\frac{B^2 l^2}{mR} t} \rightarrow (A)$$

$$e = vBl = v_0 B l e^{-\frac{B^2 l^2}{mR} t} \rightarrow (B)$$

$$i = \frac{e}{R} = \frac{v_0 B l}{R} e^{-\frac{B^2 l^2}{mR} t} \rightarrow (C)$$



$$F = i l B = \frac{v_0 B^2 l^2}{R} e^{-\frac{B^2 l^2}{mR} t} \rightarrow (D)$$


### Generator Principle:

An electric generator is based on the principle that whenever a flux is cut by a conductor an emf is induced which will cause a current to flow if the conductor circuit is closed. The direction of induced emf (hence current) is given

by Fleming's Right hand rule. Therefore the essential components of a generator are

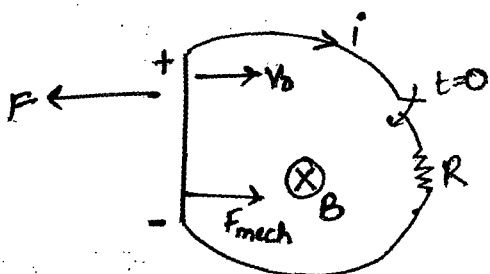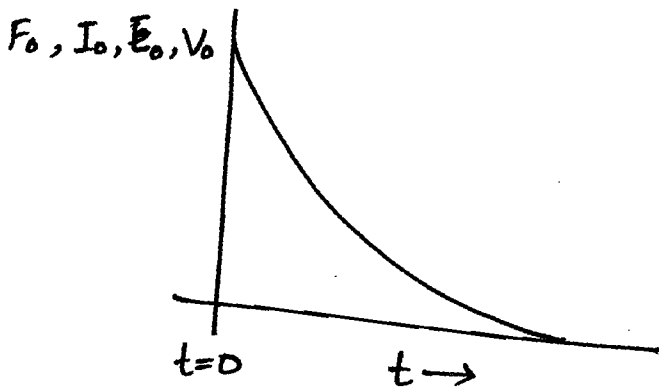- (i) mag. field
- (ii) conductor or group of conductors
- (iii) motion of conductor w.r.t mag. field



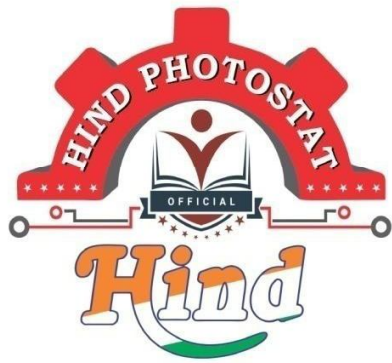

# HindPhotostat



## Hind Photostat & Book Store

Best Quality Classroom Topper Hand Written Notes to Crack GATE, IES, PSU's & Other Government Competitive/ Entrance Exams

### MADE EASY ELECTRICAL ENGINEERING Network Theory By.Aditya Sir

- Theory
- Explanation
- Derivation
- Example
- Shortcuts
- Previous Years Question With Solution

Visit us:-[www.hindphotostat.com](http://www.hindphotostat.com)

Courier Facility All Over India  
(DTDC & INDIA POST)  
Mob-9311989030



# HindPhotostat



**MADE EASY , IES MASTER , ACE ACADEMY , KREATRYX**

**ESE , GATE, PSU BEST QUALITY TOPPER HAND WRITTEN NOTES  
MINIMUM PRICE AVAILABLE @ OUR WEBSITE**

- |                                |                           |
|--------------------------------|---------------------------|
| 1. ELECTRONICS ENGINEERING     | 2. ELECTRICAL ENGINEERING |
| 3. MECHANICAL ENGINEERING      | 4. CIVIL ENGINEERING      |
| 5. INSTRUMENTATION ENGINEERING | 6. COMPUTER SCIENCE       |

**IES , GATE , PSU TEST SERIES AVAILABLE @ OUR WEBSITE**

- ❖ IES –PRELIMS & MAINS
- ❖ GATE

➤ **NOTE;- ALL ENGINEERING BRANCHS**

➤ **ALL PSUs PREVIOUS YEAR QUESTION PAPER @ OUR WEBSITE**

## **PUBLICATIONS BOOKS -**

**MADE EASY , IES MASTER , ACE ACADEMY , KREATRYX , GATE ACADEMY , ARIHANT , GK**

**RAKESH YADAV , KD CAMPUS , FOUNDATION , MC –GRAW HILL (TMH) , PEARSON...OTHERS**

**HEAVY DISCOUNTS BOOKS AVAILABLE @ OUR WEBSITE**

<b>F230, Lado Sarai New Delhi-110030 Phone: 9311 989 030</b>	<b>Shop No: 46 100 Futa M.G. Rd Near Made Easy Ghitorni, New Delhi-30 Phone:9711475393</b>	<b>F518 Near Kali Maa Mandir Lado Sarai New Delhi-110030 Phone: 9560 163 471</b>	<b>Shop No.7/8 Saidulajab Market Neb Sarai More, Saket, New Delhi-30</b>
--	--	--	--

**Website: [www.hindPhotostat.com](http://www.hindPhotostat.com)**

**Contact Us: 9311 989 030**

**Courier Facility All Over India**

**(DTDC & INDIA POST)**

# NETWORK THEORY

-Aditya sir

ESE: 22-24 M

≈ 14 que.

Gate: 10M


## ① Topics:

- ① Basics:
- $\phi, I, V, P, N$
  - R, L, C
  - KVL, KCL, ohm's Law
  - Mesh Nodal
  - Equivalent R, L, C, Z

- ② Two-port Network:
- Parameters (Z, Y, h, g, T, t)
  - Interconnection
  - Gyration


- ③ Theorems:
- Superposition
  - Thevenin
  - Norton's
  - Maximum power Transfer
  - Reciprocity
  - Millman's
  - Compensation
  - Substitution
  - Tellegen's theorem
- Gate
- ESE

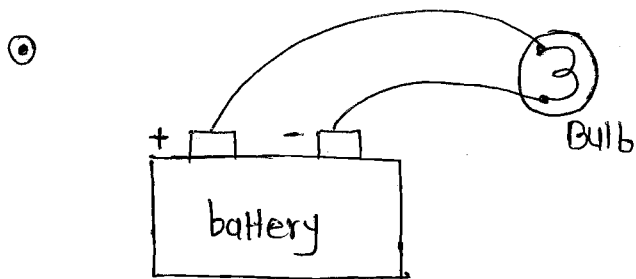- ④ Transient:
- 1<sup>st</sup> order circuit (RC, RL)
  - 2<sup>nd</sup> order circuits
  - Initial condition
  - Laplace transform



Electrical circuit : our main Aim is to transferred the energy from one Point to another Point. Hence for this we require An interconnection bet<sup>n</sup> electrical Compo.

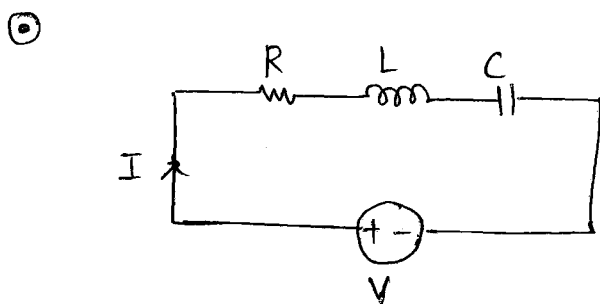Interview  
Highest basic quantity in electrical Network : Charge



① Charge : • charge is the electrical property of the atomic partical of which the Matter consist of. (C)

• [Electrical Property → Atomic Particles → Matter]

charge on  $1e^- : -1.6 \times 10^{-19} C$

Coulomb is the large Unit of charge.

Que: How many electron contributes towards 1C of charge?

Sol<sup>n</sup> :  $1e^- = 1.6 \times 10^{-19} C$

$$1C = \frac{1}{1.6 \times 10^{-19}} e^- S$$

$$1C = 6.24 \times 10^{18} e^- S$$

② Law of conservation of charge :

It states that, charge can be neither be created nor be destroyed. It can be only transferred from one body to another body.

Any eq<sup>n</sup> with the help of show Law of conse. of Charge.

Continuity Eq<sup>n</sup> :  $\nabla \cdot \vec{J} = -\frac{d\rho_v}{dt}$

Lec-2

② Current: The flow of the electrons or the time rate of change of charge through any cross-section is called as a current. (C/s or Amp)


$$I_{av} = \frac{\Delta q}{\Delta t} \text{ C/s or AMP.}$$

• Instantaneous current  $i(t)$ :

$$i(t) = \lim_{\Delta t \rightarrow 0} \frac{\Delta q}{\Delta t} = \frac{dq}{dt}$$

$$i(t) = \frac{dq}{dt}$$

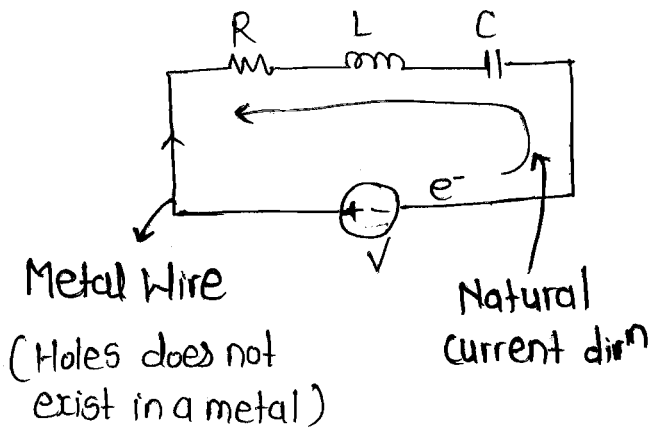• Direction of current in electrical circuit:




Conventionally,  $\text{---} \rightarrow$  the current direction is taken in the direction of the positive charge moment.

Naturally,  $\text{---} \rightarrow$  the current direction is in the direction of the flow of electrons.


③ Voltage: ① To move the electron from one point to another point in a particular direction & external force is required & in an electrical circuit this force is provided by the electromotive force (EMF) & it is given by

$$E = V = \frac{dW}{dq} \text{ J/C or V}$$

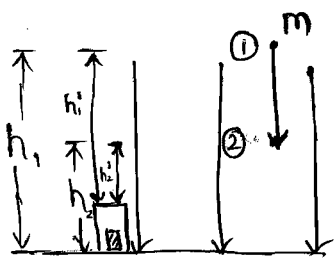② Voltage or potential difference is the energy required to move a unit charge through an element.




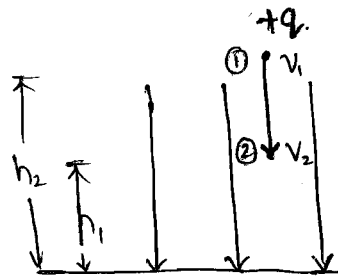Energy gained by the mass in moving from pt. ① to ② :  
 $= mg(h_1 - h_2)$   
 gravitational potential diff.




Energy gained by the charge in moving from pt ① to ② :  
 $= q(V_1 - V_2)$

Electrical potential difference.

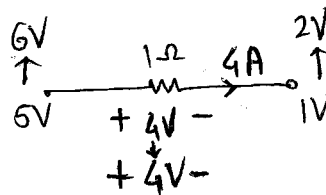


Que:

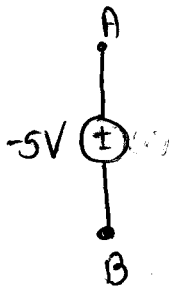

- ①  $V_A > V_B$
- ②  $V_A = V_B$
- ③  $V_A < V_B$
- ④ Cant comment

Sol<sup>n</sup>:

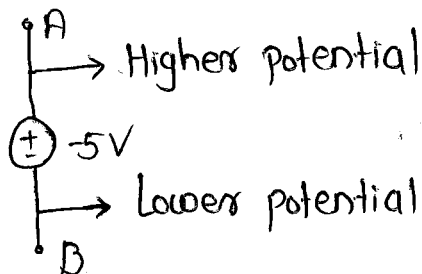

$$\text{Higher Pot.} - \text{Lower Pot.} = -5V$$

$$V_A - V_B = -5V$$


$$V_A = V_B - 5$$

④ Power: It is the time rate of change of Energy [expending or absorbing] and (Watts)

$$P = \frac{dW}{dt} \quad \text{J/s or W}$$


$$P = \frac{dW}{dq} \cdot \frac{dq}{dt}$$

$$P(t) = V(t) \cdot I(t)$$

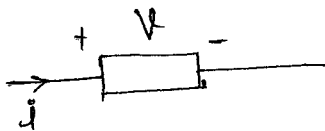

$$P = +VI$$

(a)

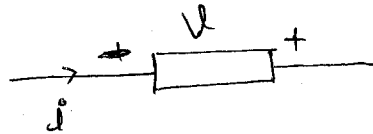

$$P = -VI$$


(b)

- Whenever we calculate the power by using the formula  $V \times I$ , we always get the power absorbed.


Fig. (a) Power absorbed or  
Power received or  
power dissipated

Fig. (b) Power absorbed  
is -ve. or  
power is getting  
delivered  
( $P_{del} = +VI$ )

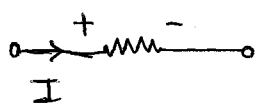Note: ① Whenever current enters into the +ve terminal of the voltage polarity, the element absorbs a power  
② And when the current leaves from the +ve terminal or current enters into the -ve terminal, then the element delivers the power.




Power absorbed

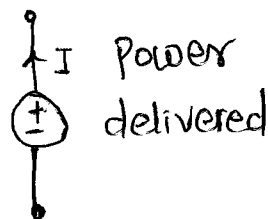


Power delivered

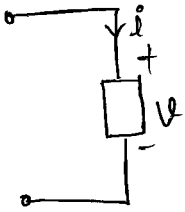- Hence, for determine sign of the power, The voltage polarity & the  $\curvearrowright$  direction are important.







Power abs.  
∴ Load

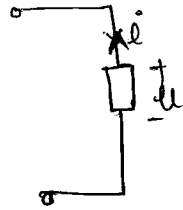


Power deli.  
∴ Source

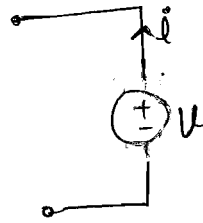


Power deli.  
∴ Source

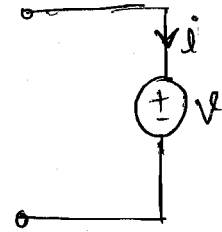

Power abs.  
∴ Sink/Load

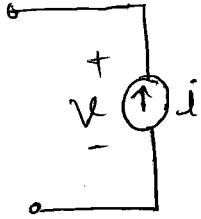

Power del.  
∴ Source

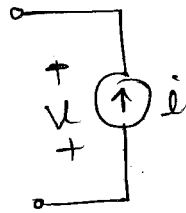

Power abs.  
∴ Load

### ⊙ Law of Conservation of Energy :

It states that, Energy can neither be created nor be destroyed, It only be transform from one form to another form.


∴ In Any Electrical Circuit :

$$\sum P = 0$$

$$\sum P_{del.} = \sum P_{abs.}$$

- The algebraic sum of the power at any instant of time in a circuit must be equal to zero.

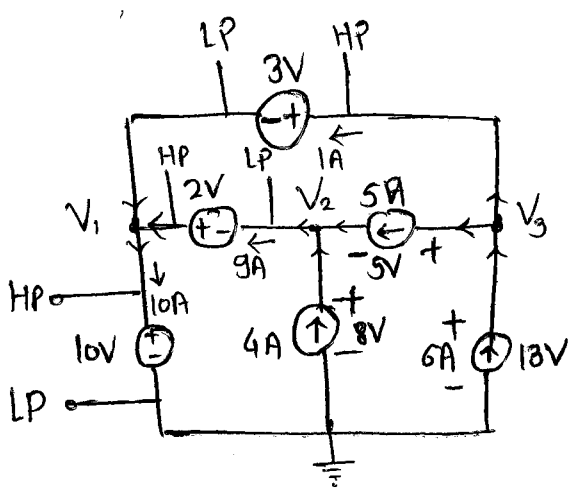Lec-3 Que. Find the power of each element In the below given electrical Network.



Sol<sup>n</sup>:

$$P_{10V} = +10 \times 10 = +100 \text{ W}$$

$$P_{2V} = -9 \times 2 = -18 \text{ W}$$

$$P_{3V} = +3 \times 1 = 3 \text{ W}$$

• By Nodal Analysis:

$$V_1 - 0 = 10V$$

$$V_1 = 10V$$

$$V_1 - V_2 = 2V$$

$$-V_2 = 2 - 10$$

$$V_2 = 8V$$


$$V_3 - V_1 = 3V$$

$$V_3 = 13V$$

$$P_{4A} = -4 \times 8 = -32 \text{ W}$$

$$P_{5A} = +5 \times 5V = 25 \text{ W}$$
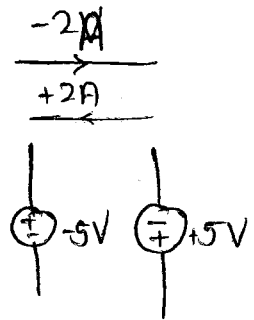
$$P_{6A} = -13 \times 6 = -78 \text{ W}$$



• Not part of Sol<sup>n</sup>:

$$\sum P_{abs.} = +100 + 3 + 25 \quad \text{--- (+Ve Power)}$$

$$= 128 \text{ W}$$

$$\sum P_{del.} = +8 + 32 + 78 \quad \text{--- (-Ve power with +ve sign)}$$

$$= 128 \text{ W}$$

$$\therefore \sum P_{del.} = \sum P_{abs.}$$

Que: How many electrons flow per second through the filament of a 220V & 110W electric bulb.

Sol<sup>n</sup>:  $P = V \times I$        $I = \frac{P}{V} = \frac{110}{220} = \frac{1}{2} \text{ Amp}$

$$I = \frac{Q}{t} = \frac{n \cdot e^-}{t}$$

where,  $n$  = Total no. of  $e^-$

$$\frac{n}{t} = 3.125 \times 10^{18}$$

$$\therefore \frac{n}{t} = \frac{I}{e^-} = \frac{\frac{1}{2}}{1.6 \times 10^{19}}$$

⑤ Energy: It is the capacity or ability to do the work. (J or Watt-sec)

$$W(t) = \int_0^t P(t) \cdot dt$$

$$W(t) = \int_0^t V(t) \cdot i(t) \cdot dt$$

Que. A fully charged mobile phone with a 12V battery

is good for 10 min talktime;

Assume that during the talktime, battery delivers a constant C/n of 2A and its voltage linearly drop from 12V to 10V as shown in the fig.

How much energy does the battery delivered during talktime.

Sol<sup>n</sup>:  $W = \int_0^t P(t) \cdot dt$

$$= \int_0^t V(t) \cdot i(t) \cdot dt$$


$$= 2 \left[ \int_0^{10 \text{ min}} V(t) \cdot dt \right]$$

$$= 2 \left[ \left( \frac{1}{2} \times 10 \text{ min} \times (12 - 10) \right) + (10 \times 10) \right] \cdot 60$$


$$= 2 [10 + 100] 60$$

$$= 2 \times 6600$$

$$W = 13.2 \text{ KJ}$$

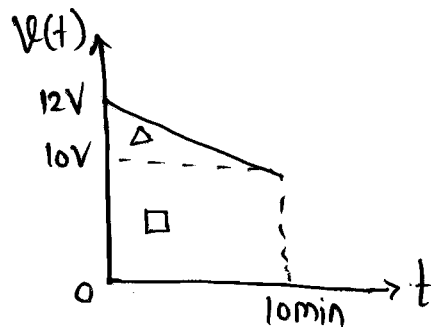

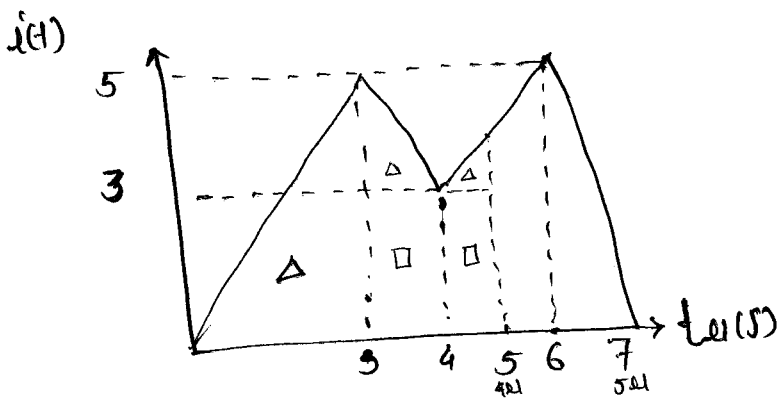que. A c/n  $i(t)$  as shown in the fig. is passed thr a capacitor. A charge in  $\mu\text{C}$  acquire by the cap<sup>r</sup> in 5  $\mu\text{s}$ . will be ---




$$\text{Sol}^n: i(t) = \frac{dq}{dt}$$

$$q = \int_{-\infty}^t i(t) \cdot dt$$

$$q(t) = \int_{-\infty}^0 i(t) \cdot dt + \int_0^t i(t) \cdot dt$$

$$q(t) = q(0) + \int_0^t i(t) \cdot dt$$

$$q(t) = 0 + \int_0^{5u} i(t) \cdot dt$$

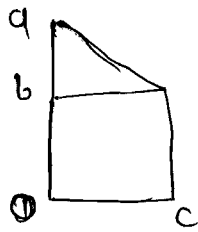

$$\begin{aligned} \text{Area} &= \frac{1}{2}(a-b)c + bc \\ &= \frac{1}{2}ac - \frac{1}{2}bc + bc \\ &= \frac{1}{2}ac + \frac{1}{2}bc \end{aligned}$$

$$\text{Area} = \frac{1}{2}(a+b)c$$

$$\therefore \text{Area} = \int_0^{3u} i(t) \cdot dt + \int_{3u}^{4u} i(t) \cdot dt + \int_{4u}^{5u} i(t) \cdot dt$$

$$= \left[ \frac{1}{2} \times 5 \times 3 \right] + \left[ \frac{1}{2} (5+3) \cdot 1 \right] + \left[ \frac{1}{2} (4+3) \cdot 1 \right]$$

$$= \left[ \frac{15}{2} + \frac{8}{2} + \frac{7}{2} \right] u$$

$$q(t) = \frac{30}{2} u$$

$$q = 15uC$$

que:  $q$  flowing through the ckt<sup>element</sup> is given by.

$i(t) = (8t + 5) A$ . Find amount of charge passing thr the element in an interval of 0 to 3 sec.

Sol<sup>n</sup>: Given;

$$i(t) = (8t + 5) \text{ A}$$

$$q(t) = 0 + \int_0^t i(t) dt$$

$$q(t) = 0 + \int_0^3 (8t + 5) dt$$
$$= 8 \cdot \left[ \frac{t^2}{2} \right]_0^3 + 5 \cdot [t]_0^3$$

$$= 4(3)^2 + 5(3)$$


$$= 36 + 15$$

$$q(t) = 51 \text{ C}$$

Que: The power supplied by a certain battery is constant, 6 W for the 1<sup>st</sup> 5 min. then 0 for the following 2 min. the value that increases from 0 to 10 W for the next 10 min. and a power that decreases linearly from 10 W to 0 in the following 7 min.

① What is the total energy in J. expended during this 24 min. interval. second.

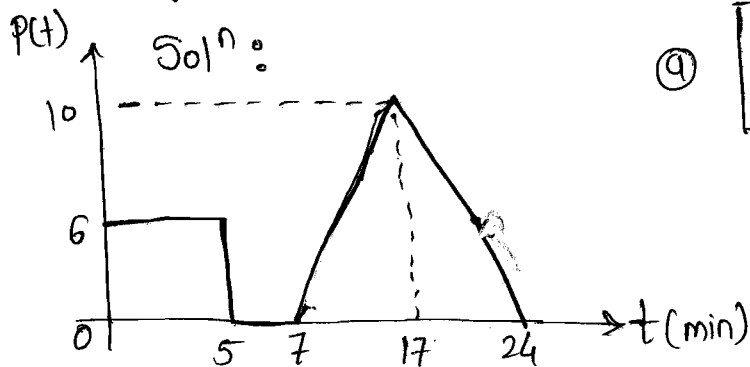② What is the avg. power in Watt during this time.



$$\textcircled{1} \quad W = \int_0^t P(t) \cdot dt$$

$$= [6 \times 5] + \left[ \frac{1}{2} \times 10 \times 10 \right] +$$

$$\left[ \frac{1}{2} \times 10 \times 7 \right]$$

$$= [30 + 50 + 35] \times 60$$

$$= (115 \times 60)$$


$$W = 6900 \text{ J}$$

$$\textcircled{b} \quad P_{\text{av}} = \frac{1}{T} \int_0^T P(t) \cdot dt$$

$$\frac{W}{T} = \frac{115 \times 60}{24 \times 60}$$

$$P_{\text{av}} = \frac{115}{24} = 4.79 \text{ W}$$

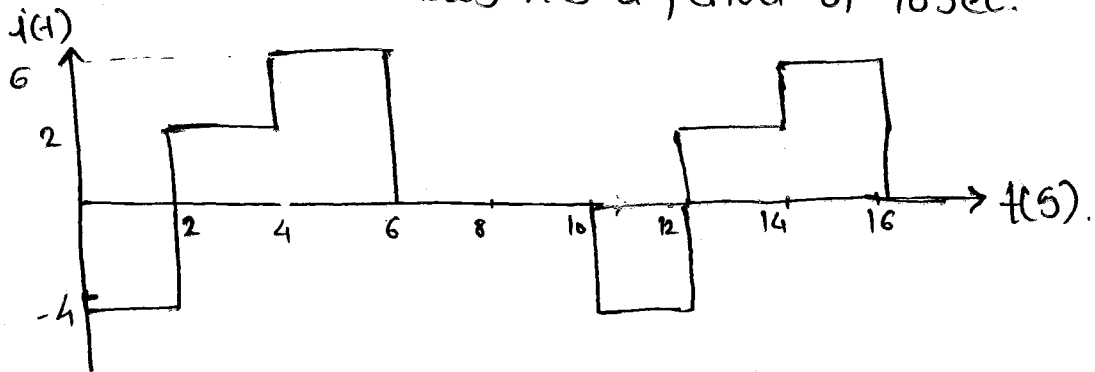Que: The waveform shows has a period of 10 sec.



Ⓐ What is the avg value of  $i(t)$  over one period.

Ⓑ How much charge is transferred in time interval 0 to 12 sec.

Ⓒ If the initial charge is '0' then sketch  $q(t)$  for time interval 0 to 16 sec.

$$\text{Sol}^n: \quad I_{\text{avg}} = \frac{1}{T} \int_0^T i(t) \cdot dt$$

$$= \frac{1}{10} [(-4 \times 2) + [2 \times 2] + [2 \times 6]]$$

$$= \frac{1}{10} \times [-8 + 4 + 12]$$

$$= \frac{16-8}{10}$$

$$= \frac{8}{10}$$

$$I_{\text{avg}} = 0.8 \text{ A}$$

$$\textcircled{b} \quad q(t) = q(0) + \int_0^t i(t) \cdot dt.$$


$$= 0 + [-8 + 4 + 12 - 8]$$

$$q(t) = 0C$$


\textcircled{c} Step  $\int$   $\rightarrow$  ramp

$$\int a \cdot dt = \overset{\text{slope}}{\rightarrow} at$$


$$q(t) = 0 + \int_0^t i(t) dt$$

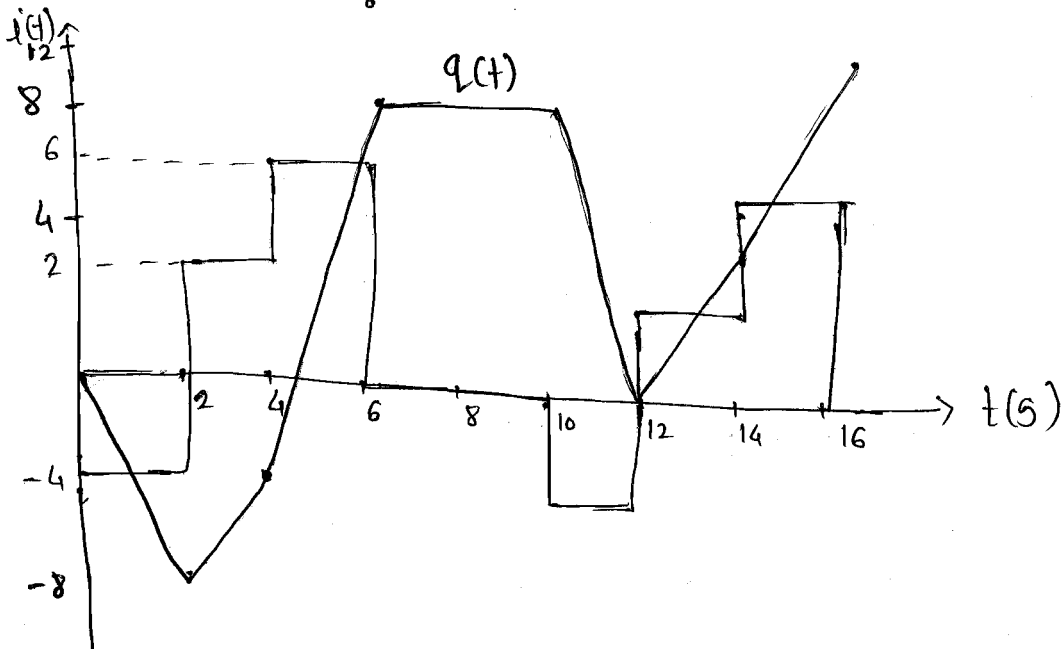

Lec-4

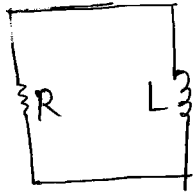

$$Z = \frac{L}{R}$$

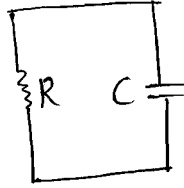

$$Z = RC$$

Interview:

In given ckts.

RL, Why T.C. ( $Z$ )  $\propto \frac{1}{R}$

RC, Why T.C. ( $Z$ )  $\propto R$


## # Circuit Elements:

ckt elements can be completely characterised based on its V-I characteristics:

① Resistor: - If voltage across an element is linearly proportional to the current flowing through it, then that element is called as Resistor.

- Resistor is an element having a property of resistance.

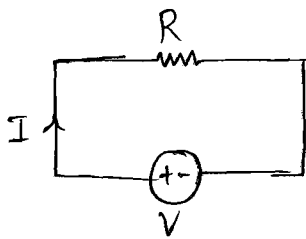Resistance can be described as that property of circuit element which offers, the opposition to flow of the current & in doing so it converts the electrical energy into heat energy.



$$P = V \cdot I$$

$$P = (IR) \cdot I = V \cdot \frac{V}{R}$$

$$P = I^2 R = \frac{V^2}{R}$$

$$W = \int_0^t P \cdot dt$$


$$= \int_0^t I^2 R \cdot dt = \int_0^t \frac{V^2}{R} \cdot dt$$

$$W = I^2 R \cdot t = \frac{V^2}{R} \cdot t$$

$$R = \frac{W}{I^2 t}$$

$$W = \int_0^t (I^2) R \cdot dt$$



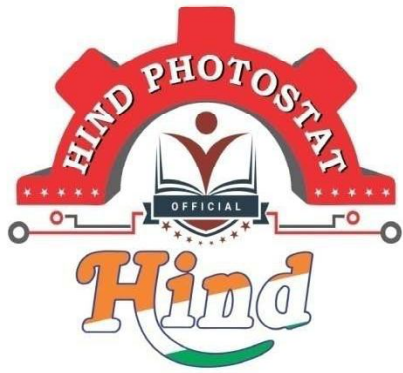

# HindPhotostat



## Hind Photostat & Book Store

Best Quality Classroom Topper Hand Written Notes to Crack GATE, IES, PSU's & Other Government Competitive/ Entrance Exams

### MADE EASY

ELECTRICAL ENGINEERING

E.M.T

By-Himadri Shekhar Sir

- Theory
- Explanation
- Derivation
- Example
- Shortcuts
- Previous Years Question With Solution

Visit us:-[www.hindphotostat.com](http://www.hindphotostat.com)

Courier Facility All Over India  
(DTDC & INDIA POST)  
Mob-9311989030



# HindPhotostat



**MADE EASY , IES MASTER , ACE ACADEMY , KREATRYX**

**ESE , GATE, PSU BEST QUALITY TOPPER HAND WRITTEN NOTES  
MINIMUM PRICE AVAILABLE @ OUR WEBSITE**

- |                                |                           |
|--------------------------------|---------------------------|
| 1. ELECTRONICS ENGINEERING     | 2. ELECTRICAL ENGINEERING |
| 3. MECHANICAL ENGINEERING      | 4. CIVIL ENGINEERING      |
| 5. INSTRUMENTATION ENGINEERING | 6. COMPUTER SCIENCE       |

**IES , GATE , PSU TEST SERIES AVAILABLE @ OUR WEBSITE**

❖ IES –PRELIMS & MAINS

❖ GATE

➤ **NOTE;- ALL ENGINEERING BRANCHS**

➤ **ALL PSUs PREVIOUS YEAR QUESTION PAPER @ OUR WEBSITE**

## **PUBLICATIONS BOOKS -**

**MADE EASY , IES MASTER , ACE ACADEMY , KREATRYX , GATE ACADEMY , ARIHANT , GK  
RAKESH YADAV , KD CAMPUS , FOUNDATION , MC –GRAW HILL (TMH) , PEARSON...OTHERS**

**HEAVY DISCOUNTS BOOKS AVAILABLE @ OUR WEBSITE**

<b>F230, Lado Sarai New Delhi-110030 Phone: 9311 989 030</b>	<b>Shop No: 46 100 Futa M.G. Rd Near Made Easy Ghitorni, New Delhi-30 Phone:9711475393</b>	<b>F518 Near Kali Maa Mandir Lado Sarai New Delhi-110030 Phone: 9560 163 471</b>	<b>Shop No.7/8 Saidulajab Market Neb Sarai More, Saket, New Delhi-30</b>
--	--	--	--

**Website: [www.hindPhotostat.com](http://www.hindPhotostat.com)**

**Contact Us: 9311 989 030**

**Courier Facility All Over India**

**(DTDC & INDIA POST)**

# EMT

- Syllabus (GATE/ESE)

- i) Vector Analysis

- Co-ordinate system
- vector calculus

- ii) Electrostatics

- iii) Magneto statics

- iv) Time Varying field [Maxwell Eqns]

- Average Weightage

Gate : ~ 4 Marks

ESE : 30 Marks

- Reference Book (Optional)  
Sadiku

- Question Practice

Gate PYQ [10-15 Y]

ESE PYQ [10-15 Y]

- Test Series

1  
2  
3  
99  
100

## CHAPTER-01 : VECTOR ANALYSIS

### 01. Co-ordinate Systems:

These are 3 types of coordinate systems

i) Cartesian Co-ordinate System  $\{x, y, z\}$

ii) Cylindrical Co-ordinate System  $\{\rho, \phi, z\}$

iii) Spherical Co-ordinate System  $\{r, \theta, \phi\}$

These 3-co-ordinate system obeys following rules

#### i) Orthogonality:

a) The dot product of two similar unit vectors of same Co-ordinate system results to 1.

$$\hat{a}_x \cdot \hat{a}_x = 1 \quad ; \quad \text{Ca. Co. Sys}$$

$$\hat{a}_y \cdot \hat{a}_y = 1 \quad ; \quad \text{Cy. Co. Sys}$$

$$\hat{a}_z \cdot \hat{a}_z = 1 \quad ; \quad \text{Sp. Co. Sys}$$

b) The dot product of two different unit vectors of Same Co-ordinate system results to 0.

$$\hat{a}_x \cdot \hat{a}_y = 0 \quad \left\{ |\hat{a}_x| |\hat{a}_y| \cos \begin{matrix} \hat{a}_x \\ \hat{a}_y \end{matrix} \right. = 1 * 1 * \cos 90 = 0$$

$$\hat{a}_y \cdot \hat{a}_z = 0$$

$$\hat{a}_z \cdot \hat{a}_x = 0$$

## 02. Orthogonality:

a) The cross product of two similar unit vectors of same co-ordinate system results to 0.


$$\cdot \hat{a}_x \times \hat{a}_x = 0$$

$$\cdot \hat{a}_y \times \hat{a}_y = 0$$

$$\cdot \hat{a}_z \times \hat{a}_z = 0$$

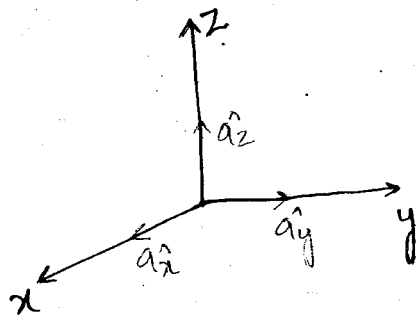b) The cross product of two different unit vectors of the same co-ordinate system results to third unit vector which is mutually perpendicular to the initial vectors.


$$\cdot \hat{a}_x \times \hat{a}_y = \hat{a}_z$$



$$\cdot \hat{a}_y \times \hat{a}_z = \hat{a}_x$$

$$\cdot \hat{a}_z \times \hat{a}_x = \hat{a}_y$$

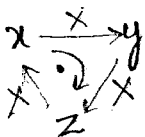
c) The direction of third unit vectors can be found using Right hand curl Rule



Ca Co Sys




Cy Co Sys

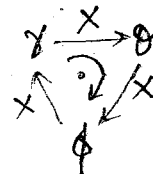

Sp Co Sys


## Right Hand Curl Rule:

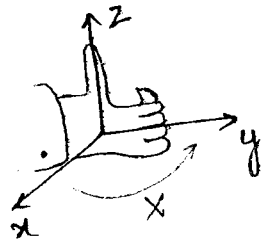


RH curl thumb

$$X \rightarrow Y \equiv Z$$

EX 1:

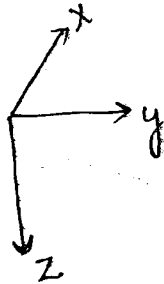



EX 2:

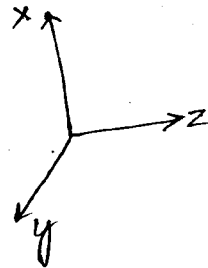

## I) Cartesian Coordinate System $\{x, y, z\}$

$$A_p = A_x \hat{a}_x + A_y \hat{a}_y + A_z \hat{a}_z$$

X:-

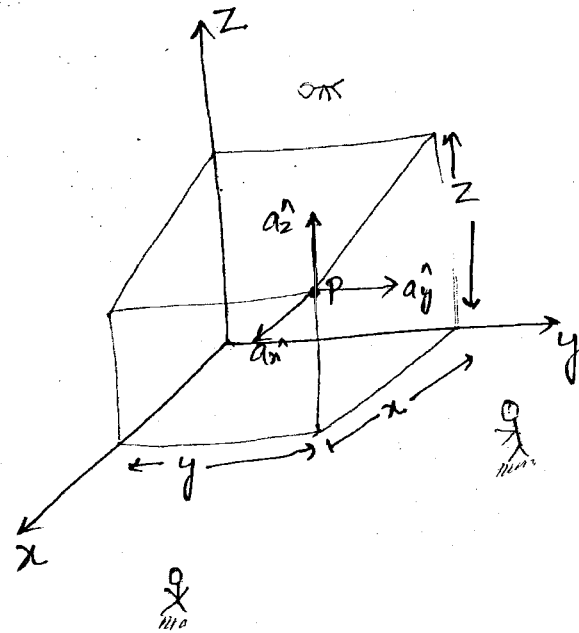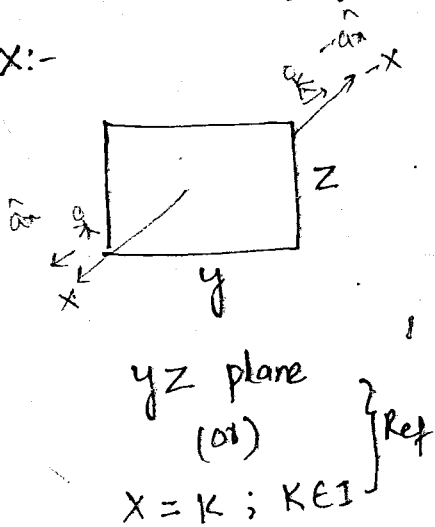


• Perpendicular distance from yz plane is x

• Range of x,  $(-\infty, \infty)$

• Unit normal vector from yz plane i.e.  $X = K, K \in \mathbb{R}$  is  $\pm \hat{a}_x$


Y:-

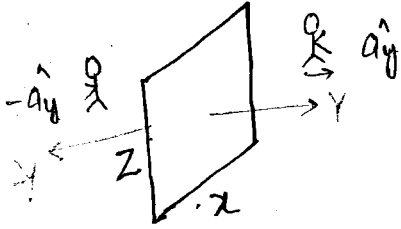

$xz$  plane  $Y = K$   $K \in \mathbb{R}$  (ref)

- Perpendicular distance from  $xz$  plane is  $Y$
- Range of  $Y$ :  $(-\infty, \infty)$
- Unit Normal vector from  $xz$  plane  
ie  $Y = K$   $K \in \mathbb{R}$  is  $\pm \hat{a}_y$


Z:-

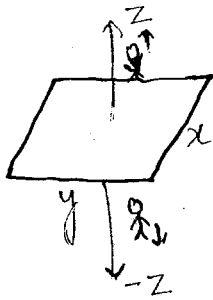

$xy$  plane (or)  $Z = K$ ,  $K \in \mathbb{R}$  (Ref)

- Perpendicular distance from  $xy$  plane is  $Z$
- Range of  $Z$ :  $(-\infty, \infty)$
- Unit normal vector from  $xy$  plane ie  
 $Z = K$   $K \in \mathbb{R}$  is  $\pm \hat{a}_z$

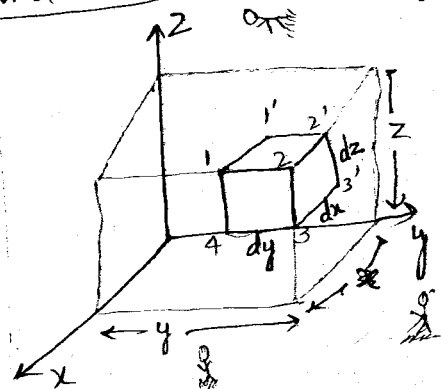Concept of differential length, Area and Volume  
(Graphical Approach)






i) Differential length:  $dl = dx \hat{a}_x + dy \hat{a}_y + dz \hat{a}_z$

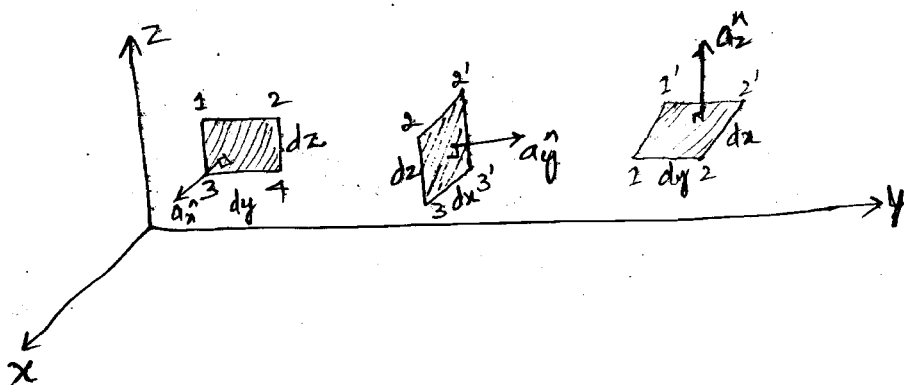ii) Differential Surface area

$$\begin{aligned} ds &= dy dz \hat{a}_x \\ &= dx dz \hat{a}_y \\ &= dx dy \hat{a}_z \end{aligned}$$



iii) Differential volume

$$dv = dx dy dz$$

Analytical Approach

$$\begin{aligned} dl &= dx \hat{a}_x + dy \hat{a}_y + dz \hat{a}_z \\ &= 1 \cdot dx \hat{a}_x + 1 \cdot dy \hat{a}_y + 1 \cdot dz \hat{a}_z \\ &= h_1 \cdot dx \hat{a}_x + h_2 \cdot dy \hat{a}_y + h_3 \cdot dz \hat{a}_z \\ &= h_1 du \hat{a}_u + h_2 dv \hat{a}_v + h_3 dw \hat{a}_w \end{aligned}$$

$h_1, h_2, h_3 =$  Scaling factor

$u, v, w$  parameters

Parameters			Scaling factor		
u	v	w	$h_1$	$h_2$	$h_3$
x	y	z	1	1	1

Ca Co Sep


Area کے 'z' کی direction میں  
 لگائے گا تو 'x' کو freeze  
 کرے گا باقی دونوں کو multiply  
 کرے گا  $dy dz \hat{a}_x$

## II Cylindrical coordinate system

$$\vec{A}_p = A_\rho \hat{a}_\rho + A_\phi \hat{a}_\phi + A_z \hat{a}_z$$

$\rho$ :-

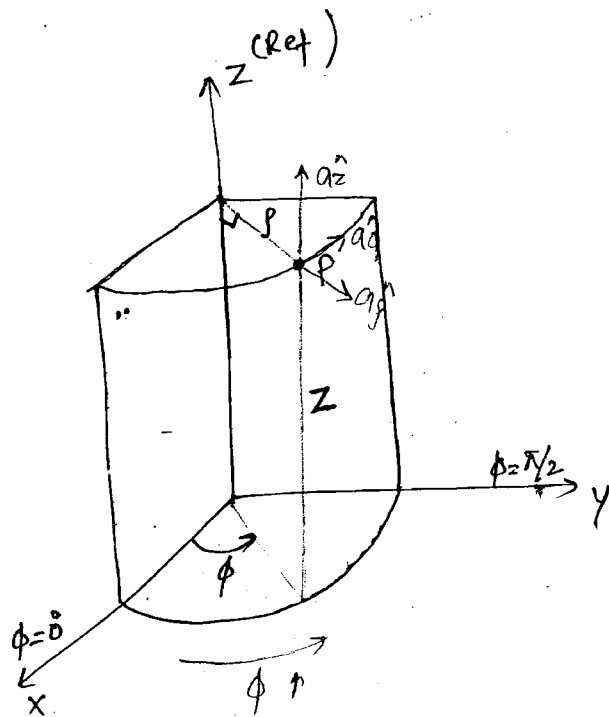- Radial or perpendicular distance of point from a reference axis (z-axis)
- Range of  $\rho$ :  $[0 \rightarrow \infty]$



Physical significance of perpendicular distance in  $\rho$ :


Ex 1:


Axis is along x axis

$f(1,1,1)$

$i(?)$

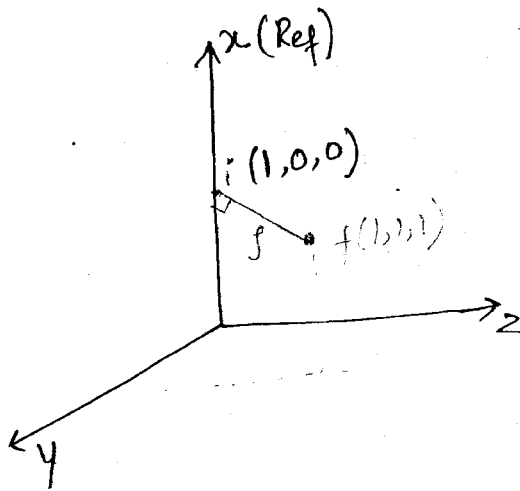provided the final point from initial point is perpendicular to x axis.



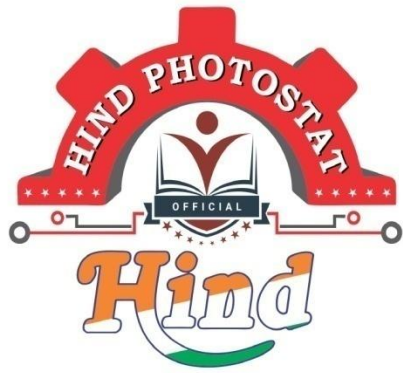

# HindPhotostat



## Hind Photostat & Book Store

**Best Quality Classroom Topper Hand Written Notes to Crack GATE, IES, PSU's & Other Government Competitive/ Entrance Exams**

**MADE EASY**  
**ELECTRICAL ENGINEERING**  
**E.M.I**  
**By. Bala JI Sir**

- Theory
- Explanation
- Derivation
- Example
- Shortcuts
- Previous Years Question With Solution

**Visit us:- [www.hindphotostat.com](http://www.hindphotostat.com)**

**Courier Facility All Over India**  
**(DTDC & INDIA POST)**  
**Mob-9311989030**

# Electrical & Electronic Measurement & Instrumentation

## Electrical (WATE + IES)

- ) Measurement of  $V$
- ) Measurement of  $I$
- ) Measurement of  $P$
- ) measurement of P.F
- ) measurement of Energy
- ) (R, L, C) Resistance, inductance and capacitance
- ) Potentiometer
- ) Instrument transformer

## Electronics (WATE + IES)

- )  $\Phi$ -Meter
- ) Digital meter
- ) CRO
- ) Error Analysis


## Instrumentation (IES)

- ) measurement of non electrical quantities like temp, pressure, flows
- ) data acquisition system

## Books


- (1) A.K. Sawney (Shawney)
- (2) Holding
- (3) Cooper

# Thermal power plant

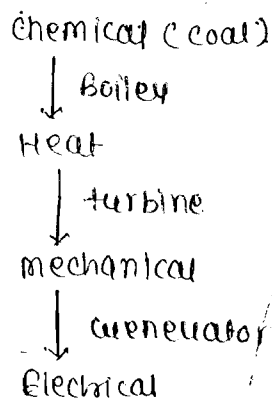

Principle - Rankine cycle.  
(Reheating of steam)

- \* DM - Demineralize water (Base)
- \* CEP = Condensate extraction pump
- \* BFP = highest temp raising pump
- \* HPH = High pressure heater (step by step temp ↑ing)
- \* When coal fire temp around  $1200^{\circ}\text{C}$
- \* ECO = Economiser which takes water in  $120^{\circ}\text{C}$  and give it in  $300^{\circ}\text{C}$
- \* BFP = Boiler feed pump
- \* Inside drum there is a mechanism called turboseparator which separate water and steam.
- \* HPSH = High temperature super heater (steam will pass & its temperature to  $540^{\circ}\text{C}$ )
- \* HPGV = High pressure governing valve, IPGV = Intermediate pressure governing valve
- \* ITHS = Intermediate temperature super heater
- \* ESP = electrostatic precipitation
- \* ESP = collection of air particle
- \* ID Fan (Induced fan) - taking flue gases from boiler
- \* for sending coal into boiler moisture has to be removed for this we use air pre heater (APH) (moisture absorbed by hot air)
- \* Transportation cost is very high for thermal plant.
- \* BFP - highest pressure pump
- \* Separator = remove dissolved gases
- for improving thermal efficiency economiser is used
- \* FD fans = sending oxygen to boiler for proper combustion  
(it will take atmospheric air used for proper combustion)
- \* HW = Hot water

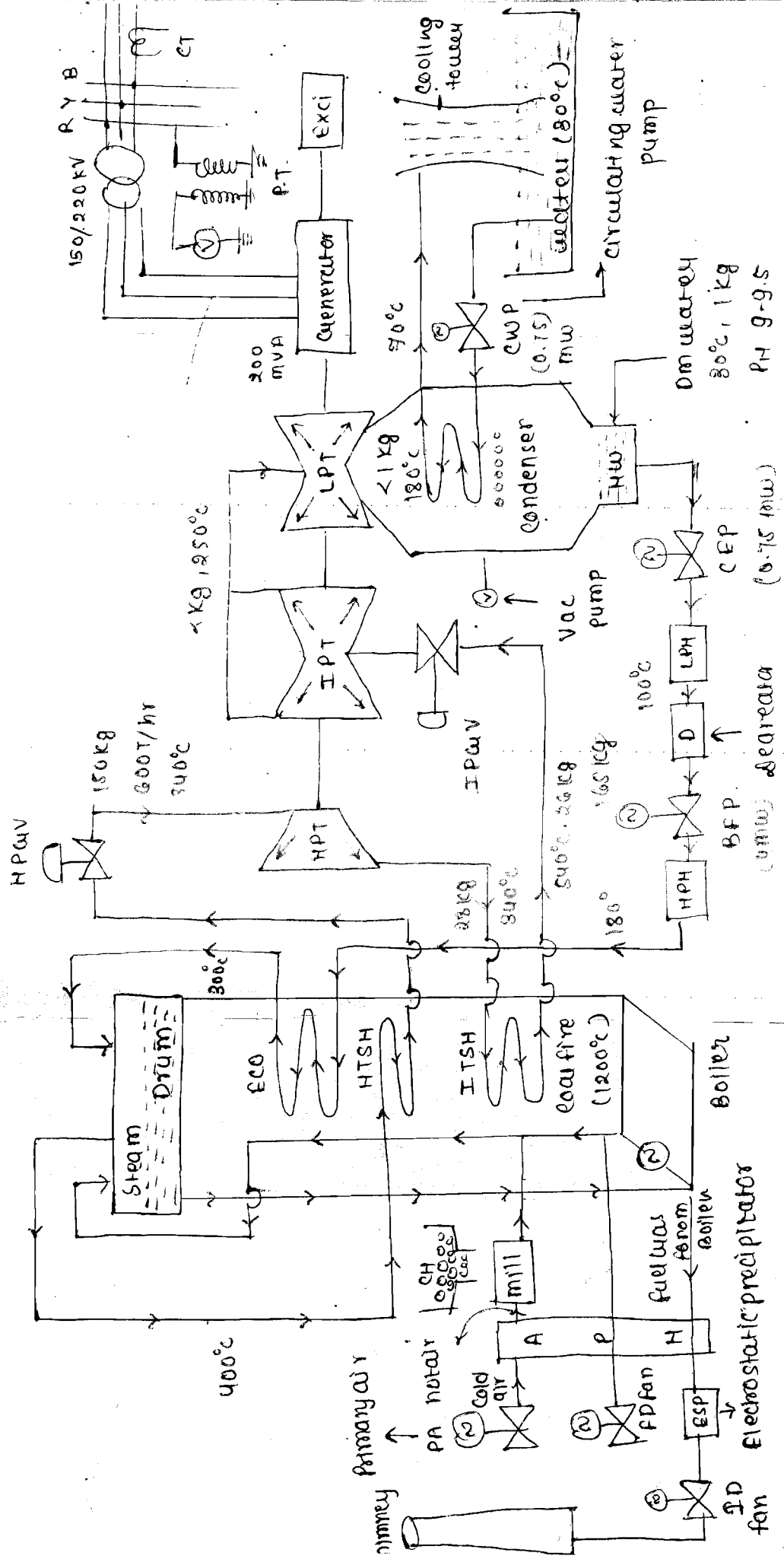

$$\eta_{\text{thermal}} = 40-45\%$$

$$= \eta_B \times \eta_i \times \eta_{ch}$$

$\downarrow \quad \downarrow \quad \downarrow$   
 90% 30-40% 90%

now  $\eta$  due to condence heat loss

Bituminous coal used

Coal chemical / heat Energy

$$= \text{calorific value} \Rightarrow C_p \Rightarrow \text{kcal}$$

$$860 \text{ kcal Heat energy} \\ = 1 \text{ kWhr elec energy}$$

Peafield

$$\eta_{\text{thermal}} = 40\%$$

Bituminous coal :  $C_p = 1720 \text{ kcal / kg}$

$$1 \text{ kg} = \frac{1720}{860} \times 0.4 = 0.8 \text{ kw-hr}$$

$$1 \text{ kw-hr} = \frac{1}{0.8} = 1.25 \text{ kg cal}$$

Generator - 200 mw , 1 day - 24 hrs

$$\text{coal/day} = 200 \times 10^3 \text{ kw} \times 24 \text{ hrs} \times 1.25 \text{ kg}$$


$$= 6000 \times 10^3 \text{ kg} = 6000 \text{ T/day}$$

(1)  $C_p$  in kcal/kg

$$Q = \frac{P_{avg} \times T \times 860}{n_o \times C_p}$$

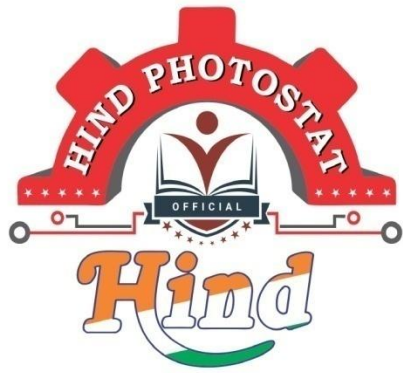2)  $C_p$  is kw-hr/kg

$$Q = \frac{P_{avg} \times T}{n_o \times C_p}$$



# HindPhotostat



## Hind Photostat & Book Store

**Best Quality Classroom Topper Hand Written Notes to Crack GATE, IES, PSU's & Other Government Competitive/ Entrance Exams**

**MADE EASY  
ELECTRICAL ENGINEERING  
Signal & System  
By.Rohit Tripathi Sir**

- Theory
- Explanation
- Derivation
- Example
- Shortcuts
- Previous Years Question With Solution

**Visit us:-[www.hindphotostat.com](http://www.hindphotostat.com)**

**Courier Facility All Over India  
(DTDC & INDIA POST)  
Mob-9311989030**



## Chapters :-

### 1. signals definition and its classification

- Even/Odd
- Periodic / Non-periodic
- conjugate symmetric & conjugate anti symmetric
- Half wave symmetry
- Energy and power signal

### 2. Different operations in signal

- shifting
- scaling
- Reversal
- Differentiation
- Integration
- convolution

### 3. Basic system properties

- static / dynamic system
- Linear / non-linear
- causal / Non-causal
- Stable / unstable
- Time invariant / Time-variant
- Invertible / Non-invertible

### 4. Fourier Series (continuous time)

### 5. Fourier Transform (continuous time)

### 6. Laplace Transform

### 7. Sampling Theorem

### 8. Discrete time signal & system

- Types of signals
- Basic signals
- Different operations on signal
- Types of systems


9. Z-Transform  $\longrightarrow$  GATE + IES
10. Discrete Fourier transform (DFT)  
and  
Fast Fourier transform (FFT)
11. Digital filters
- $\rightarrow$  Infinite impulse response (IIR) filter
  - $\rightarrow$  finite impulse response (FIR) filter
  - $\rightarrow$  Impulse invariance method
  - $\rightarrow$  Bilinear transformation method
12. Discrete cosine transform (DCT)  
 $\longrightarrow$  IES only.

www.hindphotostate.com  
9371989030

## ii Different operations on signal :-

(1) Time shifting :-  $\left\{ \begin{array}{l} \rightarrow \text{Left shifting} \\ \rightarrow \text{Right shifting} \end{array} \right.$



$$x(t) \longrightarrow x(t+k)$$

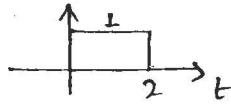

Case (i) :- when  $k > 0$  (Left shifting) :-

Example  $k=1$

$$x(t) \longrightarrow y(t) = x(t+1)$$

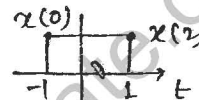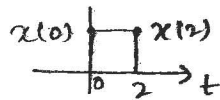



$t=-1 \rightarrow x(0)$   
 $t=1 \rightarrow x(2)$

(Left shifting)

Case (ii) :- when  $k < 0$  (Right shifting) :-

Example  $k=-1$

$$x(t) \longrightarrow y(t) = x(t-1)$$

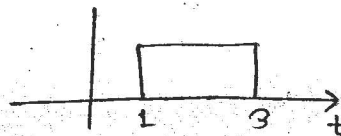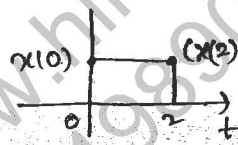


$t=1 \rightarrow x(0)$   
 $t=3 \rightarrow x(2)$

(Right shifting)

(2) Amplitude shifting :-

$\left\{ \begin{array}{l} \rightarrow \text{upward} \\ \rightarrow \text{downward} \end{array} \right.$

$$x(t) \longrightarrow y(t) = k + x(t)$$

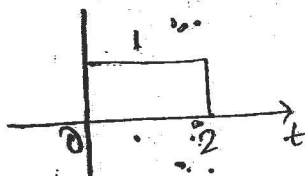

Case (i) when  $k > 0$  (upward shifting)

Example  $k = 1$



$$x(t) \rightarrow 1 + x(t)$$

$$x(t) = \begin{cases} 0 & ; t < 0 \\ 1 & ; 0 \leq t \leq 2 \\ 0 & ; t > 2 \end{cases}$$

$$y(t) = 1 + x(t) = \begin{cases} 1 + 0 & ; t < 0 \\ 1 + 1 & ; 1 \leq t \leq 2 \\ 1 + 0 & ; t > 2 \end{cases}$$

$$y(t) = \begin{cases} 1 & ; t < 0 \\ 2 & ; 1 \leq t \leq 2 \\ 1 & ; t > 2 \end{cases}$$

$$x(t) \rightarrow y(t) = -1 + x(t)$$

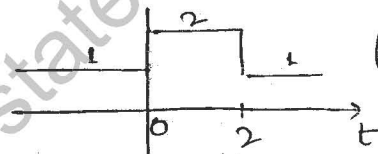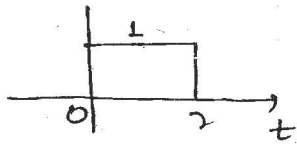

(upward shifting)

Case (ii) when  $k < 0$  (downward shifting)

Example  $k = -1$

$$x(t) \rightarrow y(t) = -1 + x(t)$$



$$x(t) = \begin{cases} 0 & ; t < 0 \\ 1 & ; 0 \leq t \leq 2 \\ 0 & ; t > 2 \end{cases}$$

$$y(t) = -1 + x(t)$$


$$y(t) = \begin{cases} -1 + 0 & ; t < 0 \\ -1 + 1 & ; 0 \leq t \leq 2 \\ -1 + 0 & ; t > 2 \end{cases}$$

$$y(t) = \begin{cases} -1 & ; t < 0 \\ 0 & ; 1 \leq t \leq 2 \\ -1 & ; t > 2 \end{cases}$$

$$x(t) \rightarrow y(t) = -1 + x(t)$$

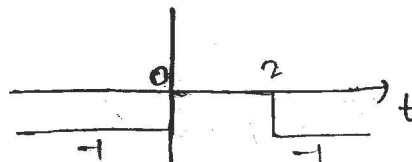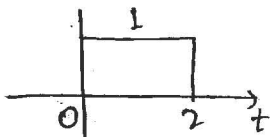

(downward shifting)

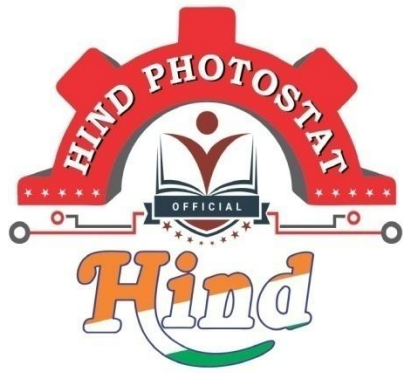

# HindPhotostat



## Hind Photostat & Book Store

**Best Quality Classroom Topper Hand Written Notes to Crack GATE, IES, PSU's & Other Government Competitive/ Entrance Exams**

**MADE EASY**  
**ELECTRICAL ENGINEERING**  
**Digital Electronics**  
**By. Ramesh Sir**

- Theory
- Explanation
- Derivation
- Example
- Shortcuts
- Previous Years Question With Solution

**Visit us:- [www.hindphotostat.com](http://www.hindphotostat.com)**

**Courier Facility All Over India  
(DTDC & INDIA POST)  
Mob-9311989030**



# Introduction

## # Boolean Logical Ideas -

These are categorized into 3 ways -

- 1) Producing the constants  $\rightarrow (0, 1)$  (Null, Identity)
- 2) Unary operations (transfer, complimentary)
  - $\downarrow$  Buffer
  - $\downarrow$  NOT
- 3) Binary operations (AND, OR, NAND, NOR, XOR, EXNOR, Inhibition, Implication)

Note.

For  $n$  input variables we get  $2^n$  combinations and  $2^{2^n}$  ( $2^{2^n}$ ) possible functions.

## # Truth table -

x	y	f <sub>0</sub>	f <sub>1</sub>	f <sub>2</sub>	f <sub>3</sub>	f <sub>4</sub>	f <sub>5</sub>	f <sub>6</sub>	f <sub>7</sub>	f <sub>8</sub>	f <sub>9</sub>	f <sub>10</sub>	f <sub>11</sub>	f <sub>12</sub>	f <sub>13</sub>	f <sub>14</sub>
0	0	0	0	0	0	0	0	0	0	1	1	1	1	1	1	1
0	1	0	0	0	0	1	1	1	1	0	0	0	0	1	1	1
1	0	0	0	1	1	0	0	1	1	0	0	1	1	0	0	1
1	1	0	1	0	1	0	1	0	1	0	1	0	1	0	1	0

$\rightarrow f_0 = 0$  Null

$\rightarrow f_1 = x \cdot y$  AND  
 $x \cdot y$


$\rightarrow f_2 = x \cdot \bar{y}$  Inhibition  
 $x/y$  [x but not y]

$\rightarrow f_3 = x$  transfer [Buffer]

$\rightarrow f_4 = \bar{x} \cdot y$  Inhibition  
 $y/x$  [y but not x]

$\rightarrow f_5 = y$  Buffer

$\rightarrow f_6 = x \oplus y$  EX-OR  
 $= \bar{x}y + x\bar{y}$

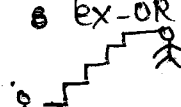Note. For the staircase an escalator  & Ex-OR Logic is used.

$\rightarrow f_7 = x + y$  OR  
 $x \vee y$

$\rightarrow f_8 = \overline{x + y}$  NOR  
 $\bar{x} \wedge \bar{y}$

$$\rightarrow f_9 = x \oplus y \quad \boxed{\text{Ex-NOR}}$$

$$= \bar{x}y + x\bar{y}$$

$$\rightarrow f_{14} = \overline{x \cdot y} \quad \boxed{\text{NAND}}$$

$$= \bar{x} + \bar{y}$$

Note - Ex-NOR is also known as coincidence logic gates or equivalence logic gate.

$$\rightarrow f_{15} = 1 \quad \boxed{\text{Identity}}$$







$$\rightarrow f_{10} = \bar{y} \quad \boxed{\text{NOT}}$$

$$\rightarrow f_{11} = x + \bar{y} \quad \boxed{\text{Implication}}$$

$$\rightarrow f_{12} = \bar{x} \quad \boxed{\text{NOT}}$$



$$\rightarrow f_{13} = \bar{x} + y \quad \boxed{\text{Implication}}$$

### Logic Gate Symbols

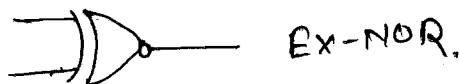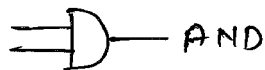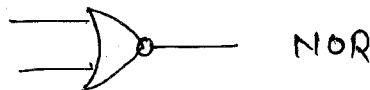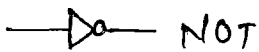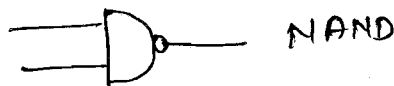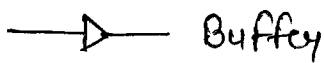

Basic logic gates - NOT, AND, OR

Universal logic gates - NAND, NOR

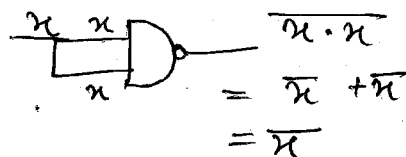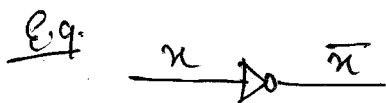



# # Trick / Short-cut.

	NAND	NOR
NOT	1	1
AND	2	3
OR	3	2
EX-OR	4	5
EX-NOR	5	4

## Duality

Step-1 Interchange the operator  $\rightarrow (\cdot, +)$


Step-2 Interchange the identity  $\rightarrow (0, 1)$

AND	OR
$x \cdot x = x$	$x + x = x$
$x \cdot 0 = 0$	$x + 0 = x$
$x \cdot 1 = x$	$x + \bar{x} = 1$
$x \cdot \bar{x} = 0$	$x + 1 = 1$

E.g. i)  $x \cdot 0 = 0$   
 $x + 1 = 1$



ii)  $F = A'B + C$   
 $F^D = ?$


$F^D = (A+B) \cdot C$

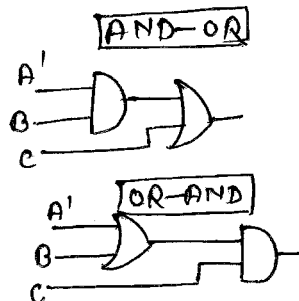
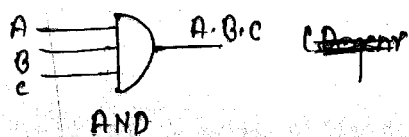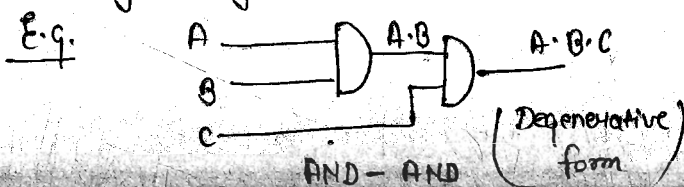
## Degenerative forms

When a two level logic gate system o/p is expressed with a single logic gate then the two level logic gate system is known as degenerated form for the single logic gate.



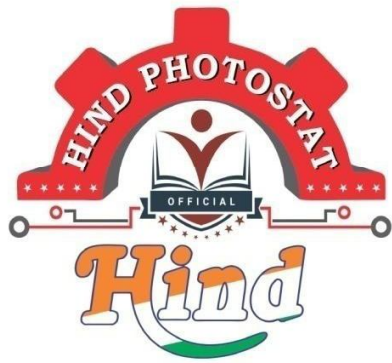

# HindPhotostat



## Hind Photostat & Book Store

Best Quality Classroom Topper Hand Written Notes to Crack GATE, IES, PSU's & Other Government Competitive/ Entrance Exams

### **MADE EASY** **ELECTRICAL ENGINEERING** Control System By.Haneef Sir

- Theory
- Explanation
- Derivation
- Example
- Shortcuts
- Previous Years Question With Solution

Visit us:-[www.hindphotostat.com](http://www.hindphotostat.com)

Courier Facility All Over India  
(DTDC & INDIA POST)  
Mob-9311989030



# HindPhotostat



**MADE EASY , IES MASTER , ACE ACADEMY , KREATRYX**

**ESE , GATE, PSU BEST QUALITY TOPPER HAND WRITTEN NOTES  
MINIMUM PRICE AVAILABLE @ OUR WEBSITE**

- |                                |                           |
|--------------------------------|---------------------------|
| 1. ELECTRONICS ENGINEERING     | 2. ELECTRICAL ENGINEERING |
| 3. MECHANICAL ENGINEERING      | 4. CIVIL ENGINEERING      |
| 5. INSTRUMENTATION ENGINEERING | 6. COMPUTER SCIENCE       |

**IES , GATE , PSU TEST SERIES AVAILABLE @ OUR WEBSITE**

❖ IES –PRELIMS & MAINS

❖ GATE

➤ **NOTE;- ALL ENGINEERING BRANCHS**

➤ **ALL PSUs PREVIOUS YEAR QUESTION PAPER @ OUR WEBSITE**

## **PUBLICATIONS BOOKS -**

**MADE EASY , IES MASTER , ACE ACADEMY , KREATRYX , GATE ACADEMY , ARIHANT , GK**

**RAKESH YADAV , KD CAMPUS , FOUNDATION , MC –GRAW HILL (TMH) , PEARSON...OTHERS**

**HEAVY DISCOUNTS BOOKS AVAILABLE @ OUR WEBSITE**

<b>F230, Lado Sarai New Delhi-110030 Phone: 9311 989 030</b>	<b>Shop No: 46 100 Futa M.G. Rd Near Made Easy Ghitorni, New Delhi-30 Phone:9711475393</b>	<b>F518 Near Kali Maa Mandir Lado Sarai New Delhi-110030 Phone: 9560 163 471</b>	<b>Shop No.7/8 Saidulajab Market Neb Sarai More, Saket, New Delhi-30</b>
--	--	--	--

**Website: [www.hindPhotostat.com](http://www.hindPhotostat.com)**

**Contact Us: 9311 989 030**


**Courier Facility All Over India**

**(DTDC & INDIA POST)**
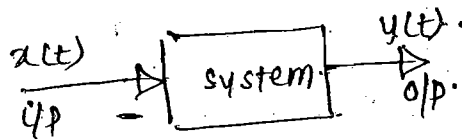
# Control System

(\*) System:- It is a means of <sup>change</sup> transforming a signal.

Signal is a fn of one or more independent variable.  
We are representing it with  $f(x)$ .



$$y(t) = T[x(t)]$$


$\mathcal{L}$  transformation.

(\*) Control System:- It is a system which produces desired o/p for a given i/p.


o/p of a system can be controlled by user in control system.

Control system is that means by which any quantity of interest is maintained or altered according to a desired manner.

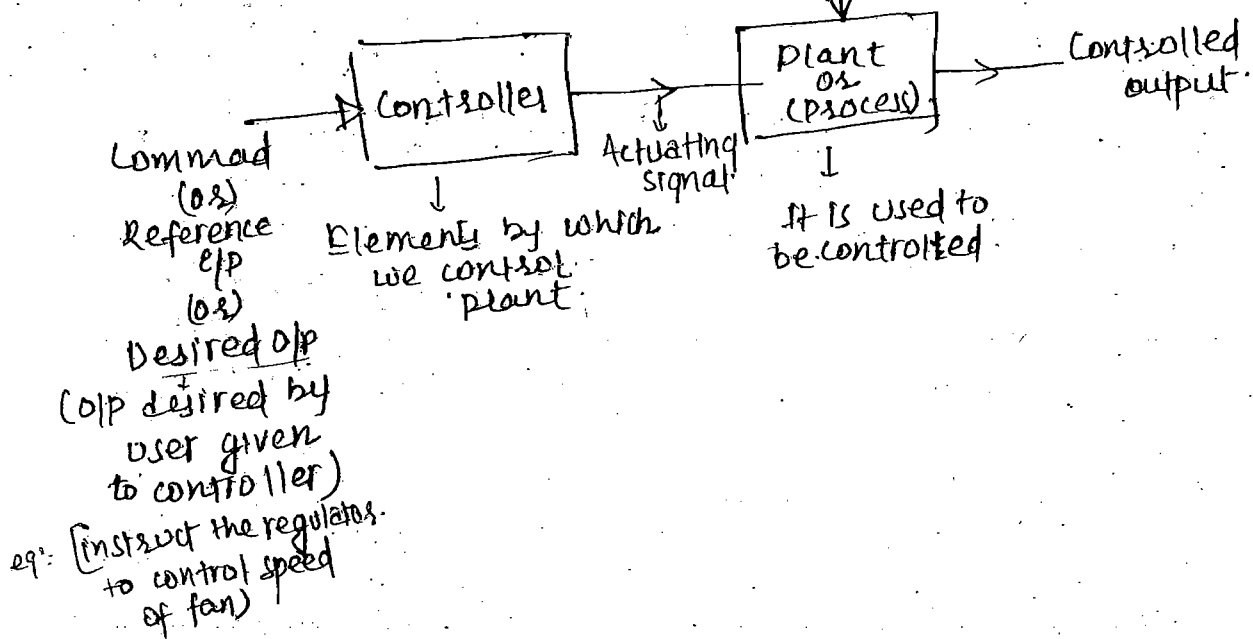We need atleast two elements to make a control system.



## ⊗ Practical control system:-

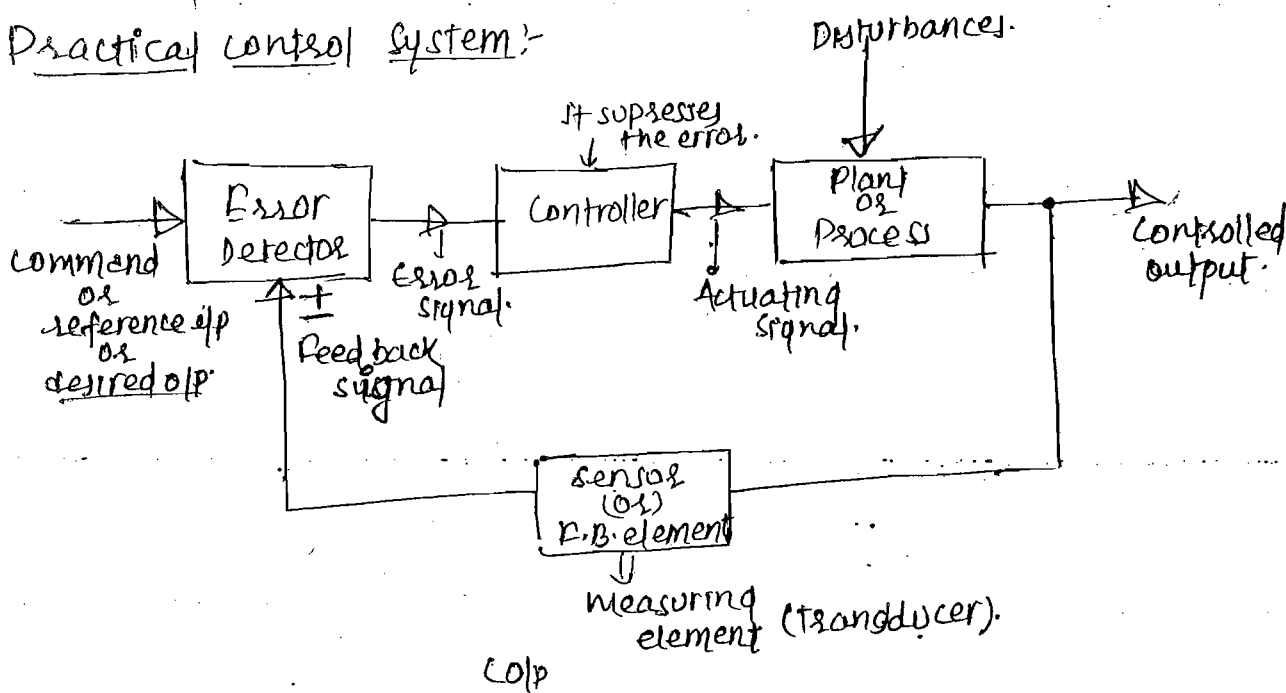

→ The objective of any control system is to ensure that the controlled o/p becomes same as the command or desired o/p. This state of system is known as steady state.

But if any disturbance occurs then the controlled o/p differs from set value. To restore the o/p to its original value, control system is modified as shown above.

→ Error detector with the help of sensor produces error signal which is the difference b/w desired o/p and actual o/p, which is suppressed by the controller. Hence the effect of disturbance is removed from control system. It is used to identify the disturbances offered by plant, not of its <sup>own</sup> disturbances.

→ A control system can reach to steady state with 100% o/p only at  $t \rightarrow \infty$ . because controlled system is designed s.t. disturbance effect associated with the plant is eliminated but disturbances associated with other parts may still be present.

$$10V = 10 \angle 0^\circ \rightarrow +ve \text{ feedback signal}$$

$$-10V = 10 \angle 180^\circ \rightarrow -ve \text{ feedback}$$

↓  
only phase shift


→ Feedback in control system is employed mainly to improve its accuracy but it also affects other characteristics of s/y. like gain, b/w, speed, stability, sensitivity, etc.

$\uparrow y = m \uparrow x \rightarrow +ve \text{ feedback.}$   
 [Effect] [Cause]

$\downarrow y = m \uparrow x \rightarrow -ve \text{ feedback.}$   
 [Effect] [Cause]

### Control System

NEBCS / OLCs

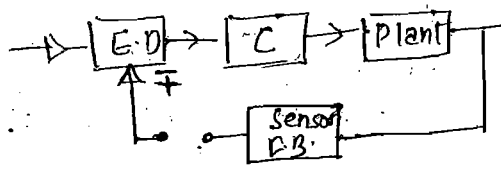

Sensors without sense.  
 eg: A blind man with eye but without vision.

- Washing machine
- The opp of the system is made independent of sensor or feedback.

FBcs / CLCS

Man-machine      Automatic

Signal will be circulated along a closed path.

- One which man & machine closes the loop together. → Machine alone forms the close loop.
- We need to make open loop system first then human involves and closes the loop.

(\*) Differences b/w the performance of an open loop C.S and a CL control system.

Open loop C.S.	Close-Loop C.S.
1. The behaviour of the open loop system doesn't change if its opp changes hence OLCs is not accurate.	1. The behaviour of CLCS does change if its opp changes hence CLCS is accurate.
2. In open-loop system sense is not present but usually sensor is present.	2. In close-loop system sense is always present either manually or automatically.
3. Time constant of OLCs is larger due to which transients takes large time to die out hence OLCs is slow.	3. Time constant of CLCS is smaller due to which transients die out rapidly hence CLCS is fast.

4. The effect of external disturbance and internal parameter variation is more in OLCs. i.e. OLCs is more sensitive.

5. OLCs is simple and economical.

6. Open loop-system is usually stable but can't be stabilized if become unstable.

4. The effect of external disturbance and internal parameter variation is less in close loop system i.e. CLCs is less sensitive.

5. CLCs is complex and expensive.

6. CLCs can become unstable but can be stabilized.

→ Only stable system can reach steady state.

Q. If a OLCs is stable, and if we apply -ve feedback to it, then what can be said about stability of system.

→ The stability of system can't be determined exactly it can increase or decrease.

Note: - No feedback guarantees stability whereas -ve feedback gives better stability as compared to +ve feedback.

2. In spite of having -ve F.B C.S. can still become unstable due to:

① High open loop gain.

② High type no.

③ High sensitivity.

④ High transportation delay (or) lag phase.

⊗ Differences b/w -ve and +ve feedback system:-

Performance criteria	-ve F.B system	+ve F.B system
1. Gain	↓	↑
2. B.W.	↑	↓
3. Time constant	↓	↑
4. Speed	↑	↓

5. Sensitivity	↓	↑	$AS \cdot Gain \times B \cdot W = K$ $V \times S = K_1$ $Speed \times Torque = K$ $\rightarrow E_p \times P \cdot D = K$
6. Stability	↑	↓	

→ C.S. was invented in year 1710 → to control speed of steam engine (Flyball)

Syllabus:-

Mathematical Analysis of C.S.:-

- Based on two standard Mathematical Models:-
  1. T.F. Model (Classical Method) → (LTI)
  2. state Model (Modern Method) → (Any system)

	To Domain	Freq. Domain
✓ Cont. Time	L.T	F.T.
Discrete Time	Z.T	DTFT.

(\*) Transfer Function [T.F] :-

→ T.F. is ratio of output and input variables such that initial condn. are zero. (Initially relaxed system)

Since, total response =  $\frac{ZSR}{s} + \frac{ZSR}{s}$

↓ (due to initial condn)

(s/p) → Dynamic (or) transient state

→ static (or) steady state

$$T.F. = \frac{L[O(s)]}{L[U(s)]} = \frac{L[SR]}{L[U(s)]} = \frac{L[RR]}{L[U(s)]} = \frac{L[PR]}{L[\frac{1}{2}U(s)]}$$


changed by changing the components of system.

$$= L[IR] = s_1 L[SR] = s_2 L[RR] = s_3 L[PR]$$

Note:- Transfer fn of a system is ~~const same~~ unique. But two systems can have same transfer fn. but for a single system there is only one T.F.

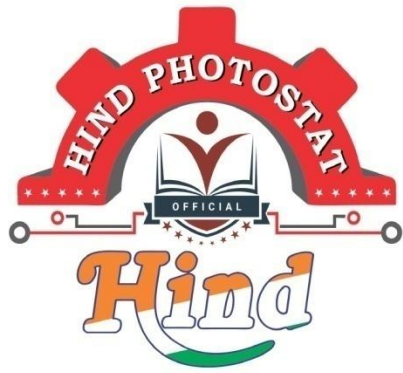2. T.F. always depends only on system components. It doesn't depend on input and output of system.





# HindPhotostat



## Hind Photostat & Book Store

**Best Quality Classroom Topper Hand Written Notes to Crack GATE, IES, PSU's & Other Government Competitive/ Entrance Exams**

**MADE EASY**  
**ELECTRICAL ENGINEERING**  
**Analog Electronics**  
**By.A.Rajkumar Sir**

- Theory
- Explanation
- Derivation
- Example
- Shortcuts
- Previous Years Question With Solution

**Visit us:-[www.hindphotostat.com](http://www.hindphotostat.com)**

**Courier Facility All Over India**  
**(DTDC & INDIA POST)**  
**Mob-9311989030**

## Subject : Analog Electronics

- COURSE DETAILS : ① Diodes - [P-n diodes, Zener diodes\*]  
② BJT [Testing\*, Biasing, Amplifiers\*]  
③ Op-Amp [Multistage basics, Differential Amplifier, Op-amp Applications\*]  
④ FET [JFET, MOSFET] [Testing, Biasing\*, Amplifiers]

## IMPORTANT TOPICS :

### DIODES

- ① DC Equivalent model of diode
- ② AC equivalent model of diode
- ③ Clippers, peak detectors, clamper, Voltage multiplier
- ④ Zener Regulators

### BJT



- \* ① Testing (Dual battery)
- ② Biasing (BJT, FET)
- \* ③ \* Current Mirror biasing techniques
- \* ④ BJT & MOSFET Amplifiers

### OP-AMP

- ① Amplifier designs
- ② Mathematical operations
- ③ Non-linear.

# # DIODES
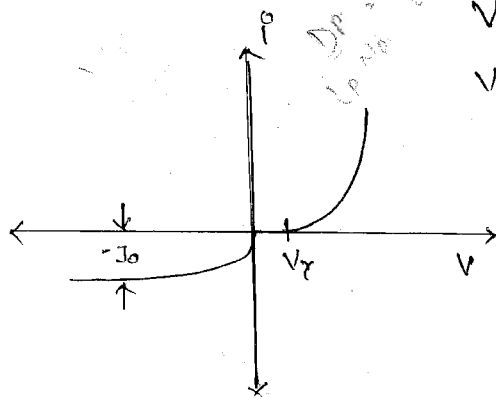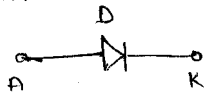
## 1) DIODE CURRENT EQUATION [V-I CHARACTERISTICS]



$V_\gamma$  - cut-in voltage

$$V_\gamma = V_T \ln \left[ \frac{N_A \cdot N_D}{n_i^2} \right]$$

$V_\gamma$  [Ge] = 0.1V to 0.3V

$V_\gamma$  [Si] = 0.5V to 0.7V

$I_0$  - Reverse saturated current (or) Leakage current (or) Minor current

$I_0 \propto \text{Area}$

$I_0 \propto \frac{1}{\text{Doping Concentration}}$

$I_0 \propto \text{Temperature}$

$$I_0 = Aq \left[ \frac{D_P}{L_P N_D} + \frac{D_N}{L_N N_A} \right] n_i^2$$

$I_0$  [Ge]  $\rightarrow \mu A$

$I_0$  [Si] =  $\eta A$

Si  $\rightarrow T_{\text{Limit}} [200^\circ C]$

Ge  $\rightarrow T_{\text{Limit}} [300^\circ C]$

$$\Rightarrow I_D = I_0 \left[ e^{V_D / \eta V_T} - 1 \right]$$

where



$I_D$  = Total current through a diode

$I_0$  = Leakage current

$V_D$  = Voltage drop across diode



$\rightarrow V_F < V_\gamma$  D OFF

$V_F \geq V_\gamma$  D ON

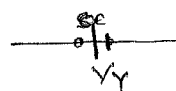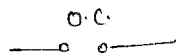

$V_D = V_F$  or  $V_R$


$V_D = V_\gamma$

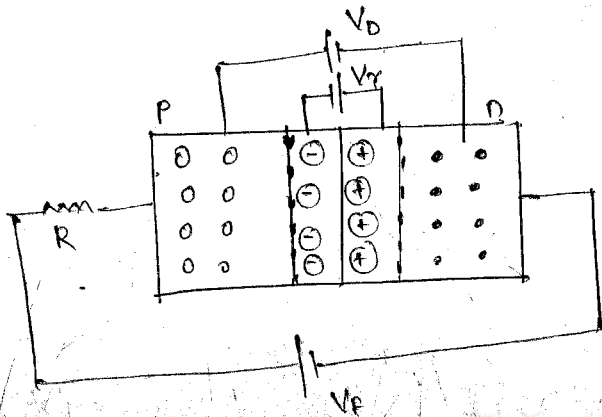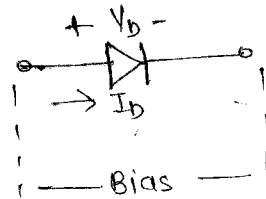

$\eta =$  Idealised factor


$$\eta = [1] \text{ Si}$$

for integrated diodes

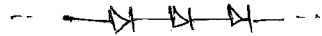

$$\eta = [2] \text{ Si}$$

for one diode

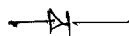

$\rightarrow V_T =$  Thermal voltage or volt eq. temperature

$$V_T = \frac{kT}{q} = \frac{T}{q/k}$$

$$\therefore V_T = \frac{T}{11,600} \text{ Volts}$$

FORWARD BIAS:  $V_D \geq V_Y$

$$I_D = I_0 [e^{V_D/V_T} - 1]$$

$$V_D = V_Y = 0.7V \text{ [Si]}$$

$$V_T = \frac{300K [27^\circ C]}{11,600}$$

$$V_T = 25 \text{ mV}$$

$$I_D = I_0 [e^{0.7/25 \times 10^{-3}} - 1]$$

$$I_D = I_0 [e^{28 \text{ mV}} - 1]$$

$$I_D = I_0 e^{V_D/V_T} \rightarrow \text{exponential } [I_D]$$

$$V_D = V_T \ln \left( \frac{I_D}{I_0} \right) \rightarrow \log [V_D]$$

REVERSE BIAS

$$I_D = I_0 [e^{V_D/V_T} - 1]$$

$$V_D = V_R = -1V$$

$$V_T = \frac{300K (27^\circ C)}{11,600} = 25 \text{ mV}$$

$$I_D = I_0 [e^{-1/25 \text{ mV}} - 1]$$

$$I_D = I_0 [e^{-40 \text{ mV}} - 1]$$

$$I_D = I_0 [e^{-\frac{1000 \text{ mV}}{25 \text{ mV}}} - 1]$$

$$I_D = -I_0$$

### # ANALYSIS

1)  $V_T$  is nearly constant for  $10^\circ C$  rise in temperature.

$$T_1 = 27^\circ C \quad V_{T1} = \frac{300K}{11,600} = 25 \text{ mV}$$

$$T_2 = 37^\circ C \quad V_{T2} = \frac{310K}{11,600} = 26 \text{ mV}$$

2)  $I_0$  increases by  $7\%/^\circ C$  rise in temperature

(OR)

$I_0$  doubles for every  $10^\circ C$  rise in temperature.

$$I_{02} = I_{01} 2^{\frac{(T_2 - T_1)}{10}}$$

$$T_1 = 27^\circ C \quad T_2 = 37^\circ C$$

$$I_{01} = 10 \text{ nA} \quad I_{02} = ?$$

$$I_{02} = I_{01} 2^{(T_2 - T_1)/10} \Rightarrow I_{02} = 20 \text{ nA}$$


3)  $V_D$  decreases by  $-2.5 \text{ mV}/^\circ C$  rise in temperature

$$\frac{\partial V_D}{\partial T} = -2.5 \text{ mV}/^\circ C$$

$$V_D = V_T \ln \left( \frac{I_D}{I_0} \right)$$

Battery

Temp

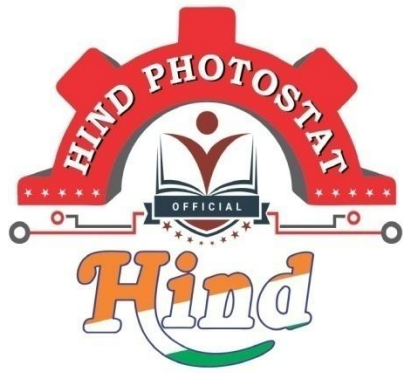

# HindPhotostat



## Hind Photostat & Book Store

**Best Quality Classroom Topper Hand Written Notes to Crack GATE, IES, PSU's & Other Government Competitive/ Entrance Exams**

**MADE EASY**  
**ELECTRICAL ENGINEERING**  
**Material Science**  
**By.V.kumar Sir**

- Theory
- Explanation
- Derivation
- Example
- Shortcuts
- Previous Years Question With Solution

**Visit us:-[www.hindphotostat.com](http://www.hindphotostat.com)**

**Courier Facility All Over India  
(DTDC & INDIA POST)  
Mob-9311989030**

## 2020 Technical Material science for ECE and EEE

- ② Conductor materials → 2 to 12
- ③ Crystallography → 13 to 46
- ④ properties of dielectric materials in static electric fields → 47 to 80
- ⑤ properties of dielectric materials in Alternating fields → 80 to 89
- ⑥ magnetic properties of materials → 89 to 108-2
- ⑦ Super conductors → 109 to 113
- ⑧ Hall effect → 114 to 118
- ⑨ Nano materials → 119 to 128-2
- ⑩ Extra notes of technical material science → 129 to 172

V. KUMAR  
SIR  
EX. IES  
MADE EASY  
Faculty

⇒ Technical material science work book key for EEE & ECE → 303-304


### Basics of material science.

- ① Basics → 173 to 184
  - ①① Chemical bonds → 185 to 192
  - ①② Composites → 193 to 198-2
  - ①③ polymers → 199 to 212-2
  - ①④ ceramics → 213 to 228
  - ①⑤ mechanical properties of materials → 229 to 242-2
  - ①⑥ Ferrous metals → 243 to 252
  - ①⑦ Non Ferrous metals → 253 to 258-2
  - ①⑧ phase diagrams → 259 to 296
- ⇒ Basics of material science work book key → 297 to 302


# 2. Conductor materials

Notes: Classification of materials based on energy gap  $[E_g]$ :

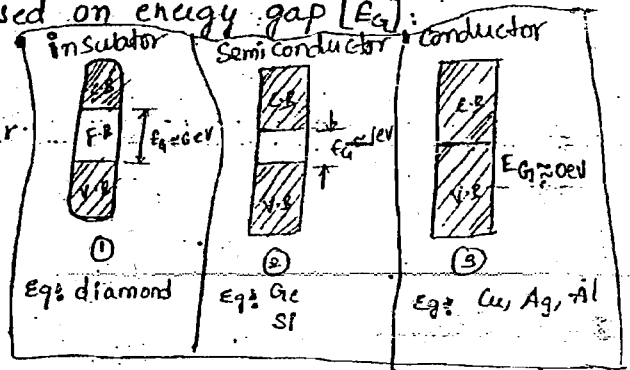- 1) Insulator
- 2) Semi-conductor
- 3) Conductor



## Ohm's Law Of Electricity :-

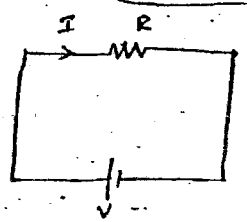

$V$  is the applied voltage  
 $I$  is the produced current  
 $R$  is the resistance of a resistor

$$R = \frac{l}{\sigma A} = \frac{\rho \cdot l}{A} \text{ (ohm) (}\Omega\text{)}$$

According to Ohm's law  $V \propto I$

$$V = \text{constant} \times I$$

$$V = RI \quad \text{--- (1)}$$

$$V = \frac{l}{\sigma A} I \Rightarrow \frac{I}{A} = \sigma \frac{V}{l} \Rightarrow \boxed{\vec{J} = \sigma \vec{E}} \quad \text{--- (2)}$$

$l$  = length of conductor  
 $A$  = Cross sectional area

Force on electron having 'm' mass and acceleration 'a' is

$$F = ma \quad \text{--- (3)}$$


Force on electron having 'q' charge due to applied electric field intensity 'E' is  $\vec{F} = q\vec{E} \rightarrow \ominus$

$\sigma \rightarrow$  electrical conductivity  $(\frac{1}{\Omega m})$

$$\sigma = \frac{l}{RA} \left( \frac{m}{\Omega m^2} = \frac{1}{\Omega m} \right)$$

$\rho \rightarrow$  electrical resistivity  $(\Omega m)$

$$\rho = \frac{1}{\sigma}$$

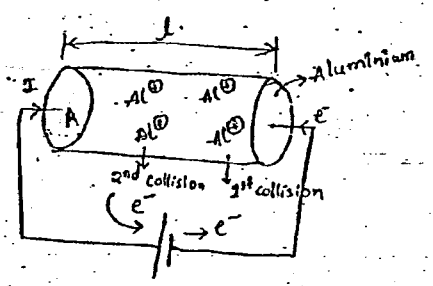

$$\textcircled{3} = \textcircled{4} \Rightarrow ma = qE \Rightarrow a = \frac{qE}{m} \quad \text{--- } \textcircled{5}$$

$$\text{Drift velocity } \vec{v}_d = a \tau_c \quad \text{--- } \textcircled{6}$$

$$\left(\frac{m}{\text{sec}}\right) \quad \left(\frac{m}{\text{s}^2}\right)(s)$$

Put  $\textcircled{5}$  in  $\textcircled{6}$

$$v_d = \frac{qE}{m} \tau_c$$

$$\vec{v}_d = \left(\frac{q\tau_c}{m}\right) \vec{E} \quad \text{--- } \textcircled{7}$$

$E =$  electric field intensity  $\left(\frac{V}{m}\right)$

$$\boxed{\vec{v}_d = \mu \vec{E}}$$

$$\mu = \text{mobility} = \frac{q\tau_c}{m} \left(\frac{m^2}{(\text{Volt})(\text{Sec})}\right)$$

$$\vec{J} = nq \vec{v}_d \quad \text{--- } \textcircled{8}$$

$$\left(\frac{A}{m^2}\right) \quad \left(\frac{1}{m^3}\right) (C) \quad \left(\frac{m}{\text{Sec}}\right)$$

Put  $\textcircled{7}$  in  $\textcircled{8}$

$$\vec{J} = nq\mu \vec{E} \quad \text{--- } \textcircled{9}$$

Compare  $\textcircled{2}$  and  $\textcircled{9}$

$$\sigma = nq\mu \quad \text{--- } \textcircled{10}$$

$$\sigma = nq \left(\frac{q\tau_c}{m}\right)$$

$$\boxed{\sigma = \frac{nq^2\tau_c}{m}}$$

$$n = \text{electron density} = \frac{\text{number of electrons}}{m^3} \left(\frac{1}{m^3}\right)$$

$q =$  charge of charge particle.

$m =$  mass of charge particle.

$\tau_c =$  collision time (second).

$\tau_c$  is the average time b/w two successive collisions.

NOTE:  $**$  In conductor (or) metals when temperature is increased metal ions vibrate and number of collisions increase and collision time decreases, so conductivity decreases and resistivity increases. Metals



have positive temperature coefficient of resistivity and resistance.

It is found that  $\gamma_c \propto \frac{1}{\sqrt{T}}$

$$\sigma \propto n \gamma_c$$

$$\sigma \propto \frac{n}{\sqrt{T}}$$

T = temperature

Factors affecting the resistivity:

\* ① temperature (T): In conductor the temperature is increased the  $\rho$  increases according to the following equation.

$$\rho_T = \rho_{RT} (1 + \alpha \Delta T) \quad \text{--- ① also } R_T = R_{RT} (1 + \alpha \Delta T)$$

$\rho_T$  = resistivity at operating temperature

$\rho_{RT}$  = Resistivity at room temperature ( $T_{RT}$ )

$$\Delta T = T - T_{RT}$$

$\Delta T$  = change of temperature

$\alpha$  = temperature coefficient of resistivity ( $\frac{1}{K}$  or  $\frac{1}{K}$ )

$\alpha$  is positive for metals


$R_T$   $\rightarrow$  Resistance at T temperature  
 $R_{RT}$   $\rightarrow$  Resistance at room temperature Reference temp.  
 $\Delta T = T - T_{RT}$  = change of temp  
 $\alpha$  = temperature coefficient of resistance

\* ② Alloying Effect: Adding impurity atoms to pure metals.

If percentage of alloy content is increased then irregular in atomic arrangement increases, so resistivity increases (independent of temperature). This is called as residual resistivity ( $\rho_{residual}$ )

Total resistivity is  $\rho_{alloy} = \rho_{thermal} + \rho_{residual}$  --- ②

Eqn ② is called as Matthiessen rule.

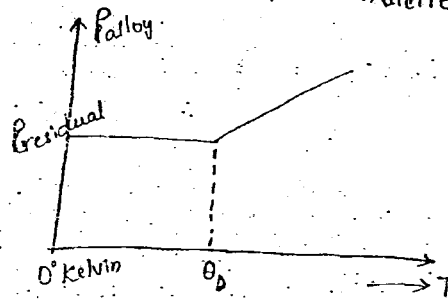

$\theta_D$  is called as Debye temperature. It is the temperature after which  $\rho$  increases linearly with temperature

### 3) Deformation:


Deformation  $\rightarrow$  change of shape (or) length (or) diameter (or) volume.

$\Rightarrow$  Deformation in conductors increases the irregularity of atomic arrangement. So  $\rho$  increases. This increase of  $\rho$  is called as  $\rho_{\text{deformation}}$  for alloy having deformation.

$$\text{Total resistivity } \rho_{\text{alloy}} = \rho_{\text{thermal}} + \underbrace{\rho_{\text{residual}} + \rho_{\text{deformation}}}_{\text{permanent i.e. independent of temperature}}$$

### Observation:

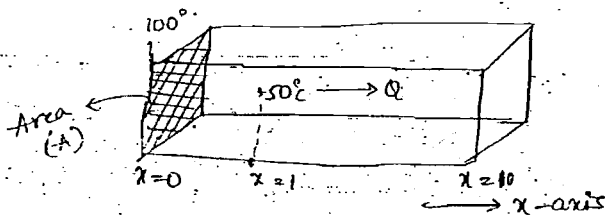1) In conductors (or) metals thermal energy is transferred due to random motion of free electrons as well as vibrations of metal ions. But most of the % of thermal energy is transferred due to free electrons. In conductors the thermal power crossing the area is given by



$$Q = -k \frac{dT}{dx} \left( \frac{\text{watt}}{\text{m}^2} \right) \quad \text{--- (1)}$$

$$\frac{dT}{dx} = \text{temperature gradient } \left( \frac{^{\circ}\text{Kelvin}}{\text{m}} \right)$$

where  $k$  is thermal conductivity  $\left( \frac{\text{Watt}}{^{\circ}\text{K} \cdot \text{m}} \right)$

for conductors  $k$  due to free e<sup>-</sup>s is given by

$$k = \frac{1}{3} \frac{n \pi^2 k^2 T \tau_c}{m} \quad \text{--- (2)}$$

$$\text{for conductors } \sigma = \frac{n q^2 \tau_c}{m} \quad \text{--- (3)}$$

$$\frac{(2)}{(3)} \quad \frac{k}{\sigma} = \frac{\frac{1}{3} n \pi^2 k^2 T \tau_c}{\frac{n q^2 \tau_c}{m}}$$

$$\frac{k}{\sigma T} = \frac{1}{3} \frac{\pi^2 k^2}{q^2}$$

after substituting values we get

$$\frac{k}{\sigma T} = 2.45 \times 10^{-8}$$

$$\frac{k}{\sigma T} = L \quad \text{--- (4)}$$


Mr. Kumar Sir  
Ex. IES  
Faculty  
made easy

$L = 2.45 \times 10^{-8} =$  Lorentz number.

Eq<sup>n</sup> (4) is called as weidemann Franz law of conductors, which says the ratio of thermal conductivity ( $k$ ) and electrical conduct ( $\sigma$ ) at any temperature ( $T$ ) is constant

\*\*  
Thermoelectric effects:

\* Seebeck effect:-

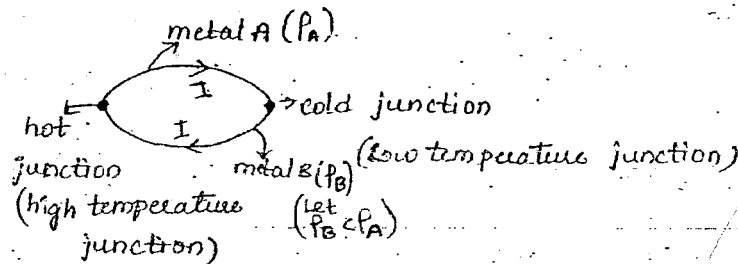

If two dissimilar metals (A, B) having different resistivities are joined. If one end is maintained at high temperature, other is maintained at low temperature then electromotive force (emf) is produced. This emf makes the current flow in the loop. This is called as seebeck effect.  $\Rightarrow$  Seebeck invented thermocouple

\* Peltier Effect:- (converse of seebeck effect)

If two dissimilar metals are joined, if current is flown in the loop then one junction goes to high temperature and other junction goes to low temperature. This is called peltier effect.

Peltier effect is used in refrigerator.

(7)

## Types of Conductors:

### \*\*1) Low resistivity conductors:

These are used in transmission and distribution of electrical current. Ex: Copper (Cu), Aluminium (Al).

### \*\*2) High resistivity conductors:

These are used in manufacturing resistors, electrical heating devices, thermocouples. These materials must withstand high temperature.

They are generally alloys of metals.

Ex: Constantan (60% Cu, 40% Ni)

Nichrome  $\left\{ \begin{array}{l} 75 \text{ to } 78\% \text{ Ni} \\ 20 \text{ to } 30\% \text{ Cr} \\ 1.5\% \text{ Mn} \\ \text{remaining is Fe} \end{array} \right.$

### \*\*3) Low melting point conductors:

Metals having low melting point are used in soldering joints.

Ex: tin, lead (Pb)

→ Soldering materials [Tin (Sn), Lead (Pb)] have low melting point and high electrical conductivity.

- \*Note:- Tin (Sn):
- (i) tin is a silvery white (or) shining white colour
  - (ii) conductivity of tin is less (or) poor compared to copper ( $\sigma_{Sn} = 0.917 \times 10^7 (\Omega\text{-m})^{-1}$  at  $20^\circ\text{C}$ )
  - (iii) tin can be drawn into wires because it is soft and malleable
  - (iv) tin is used in alloys with lead and copper
  - (v) tin is used for fuses and cable sheathing.
  - (vi) tin is corrosion resistant because of formation of oxide layer.

ESE

(Q) A resistor measures  $4\Omega$  at  $40^\circ\text{C}$  and  $6\Omega$  at  $80^\circ\text{C}$ . At  $0^\circ\text{C}$  the resistor will measure (A)  $1.5\Omega$  (B)  $2\Omega$  (C)  $3\Omega$  (D)  $4\Omega$

→  $R_T = R_0 (1 + \alpha \Delta T)$  where  $R_0$  is resistance at  $0^\circ\text{C}$  and  $\Delta T = T - 0$


at  $T = 40^\circ\text{C} \Rightarrow 4 = R_0 (1 + \alpha 40) \rightarrow \text{②}$

at  $T = 80^\circ\text{C} \Rightarrow 6 = R_0 (1 + \alpha 80) \rightarrow \text{③}$

$\text{②} \div \text{③} \Rightarrow \frac{4}{6} = \frac{1 + 40\alpha}{1 + 80\alpha} \Rightarrow \alpha = \frac{1}{40} \rightarrow \text{④}$

put ④ in ②  
 $4 = R_0 (1 + \frac{1}{40} 40) \Rightarrow R_0 = 2\Omega$

(B)

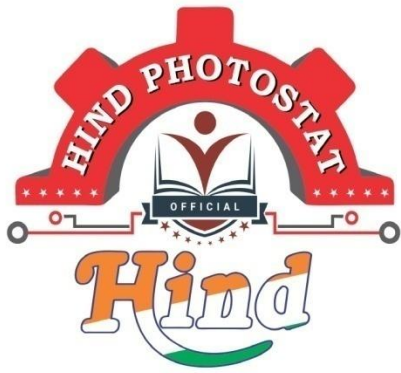

# HindPhotostat



## Hind Photostat & Book Store

**Best Quality Classroom Topper Hand Written Notes to Crack GATE, IES, PSU's & Other Government Competitive/ Entrance Exams**

**MADE EASY**  
**ELECTRICAL ENGINEERING**  
**Microprocessor**  
**By.Vijay Sir**

- Theory
- Explanation
- Derivation
- Example
- Shortcuts
- Previous Years Question With Solution


**Visit us:-[www.hindphotostat.com](http://www.hindphotostat.com)**

**Courier Facility All Over India**  
**(DTDC & INDIA POST)**  
**Mob-9311989030**

## 1947 - Transistor

- SSI → < 10 Transistor (small scale integration)
- MSI → 10 - 100 Transistor (medium scale — " — )
- LSI → 100 - 10K Transistor (large — " — )
- VLSI → > 10K Transistors (very large — " — ) (✓)
- ULSI → :
- SLSI → :

## Block diagram of a computer

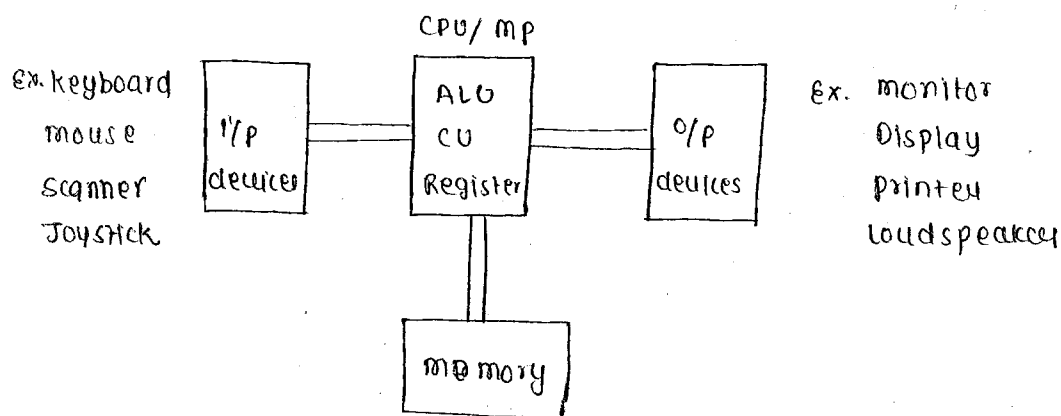

## Microprocessor

It is a semiconductor component designed by using VLSI technology and it contains ALU, CU and Registers of a CPU in a single package

NOTE - for a micro processor memory is connected externally, the registers inside the processor can not be considered as memory, as they are used to hold the data temporarily. Latest processor may have some memory inside to store frequently used data or instruction

Ex. Cache memory

Bit → Binary digit

→ 0/1

↓ Nibble → 4 Bits

↓ Byte → 8 Bits

word length → depends on type of  $\mu p$

## Word length

No. of Bits that can be processed by a processor parallelly at a time

Ex. 8 Bit  $\mu p \rightarrow$  8 bits (word length) / 1 Byte

16 Bit  $\mu p \rightarrow$  16 Bits / 2 Byte

32-bit  $\mu p \rightarrow$  4 Bytes

1971  $\rightarrow$  Intel 4004  $\rightarrow$  4 Bit  $\mu p$

1972  $\rightarrow$  Intel 8008  $\rightarrow$  8 Bit  $\mu p$

1974  $\rightarrow$  Intel 8080  $\rightarrow$  8 Bits  $\mu p$


1977/78  $\rightarrow$  Intel 8085  $\rightarrow$  8 Bit  $\mu p \rightarrow$  Gate +  $\mu ES$

1979  $\rightarrow$  Intel 8086  $\rightarrow$  16 Bit  $\mu p \rightarrow$   $\mu ES$


8088, 80186, 80286, 80386 [32 Bits]

PenHum ----- Dual core, ----- i3, i5, i7 (64 Bit)


## Dual core

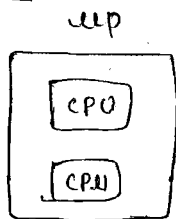

## quad core

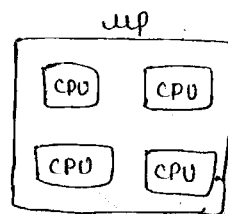



## micro controller

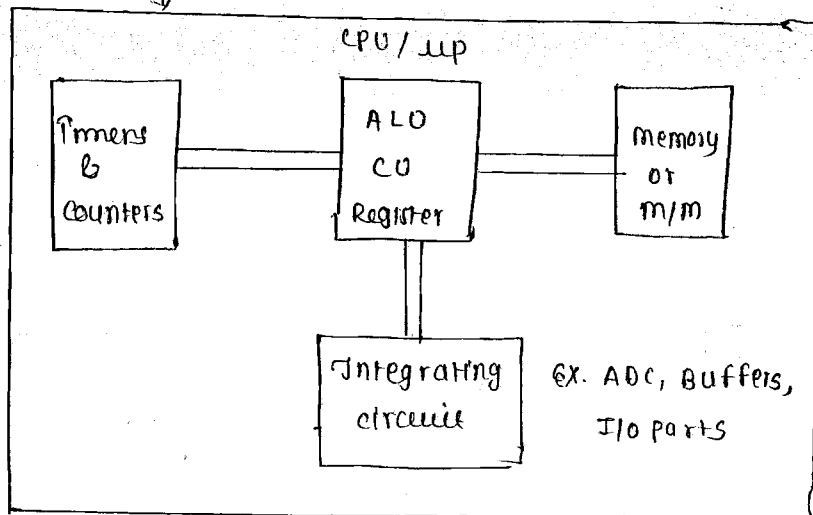


microprocessor ( $\mu$ P)	microcontroller ( $\mu$ C)
(1) It has ALU, CU, Register (2) No Internal memory (m/m) (3) No interfacing circuit's Timers/counters (4) used for general purpose application (5) Ex. Intel 8085, i7, - mc 6800, Z80 (Z80), AMD, Phillips, Toshiba, Qualcomm, national Semiconductors, Rockwell, fairchild	(1) It has ALU, CU, Registers (2) has Internal/on-board m/m (3) has interfacing circuit, Timers/counters (4) used for specific purpose of application (5) Ex. TMS 1000 (4Bit), Intel 8085 (8Bit) Intel 80196 (16 Bit), PIC $\rightarrow$ 8 Bit & 16 Bit AT89C51, Motorola, Phillips, Toshiba, Dallas semiconductors

Based on How programmes and data are stored in the memory there are two types of Architecture

- (1) Von-Neumann or Princeton architecture
- (2) Harvard Architecture

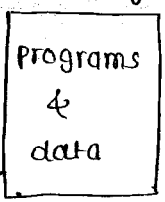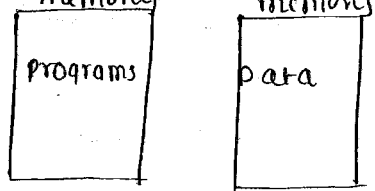Von-Neumann or Princeton Architecture	Harvard Architecture
same memory for programme & data <div style="text-align: center;">             memory   </div> ex. Intel 8085 Intel 8086	separate memory for programme & data <div style="display: flex; justify-content: space-around; align-items: center;"> <div style="text-align: center;">             (ROM) memory   </div> </div> ex. Intel 8051 (microcontroller)



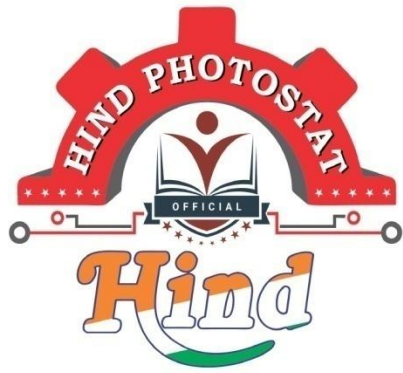

# HindPhotostat



## Hind Photostat & Book Store

**Best Quality Classroom Topper Hand Written Notes to Crack GATE, IES, PSU's & Other Government Competitive/ Entrance Exams**

**MADE EASY**  
**ELECTRICAL ENGINEERING**  
**Communication System**  
**By.Reddy Sir**

- Theory
- Explanation
- Derivation
- Example
- Shortcuts
- Previous Years Question With Solution

**Visit us:-[www.hindphotostat.com](http://www.hindphotostat.com)**


**Courier Facility All Over India**  
**(DTDC & INDIA POST)**  
**Mob-9311989030**


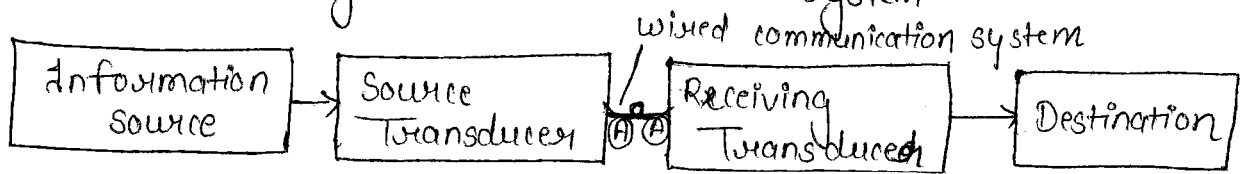
# Communication

"Communication is the process of transmitting information from one place to another."


Basic block diagram of communication system:



Voice Signal - 300 Hz - 3.5 kHz

Audio Signal - 20 Hz - 20 kHz

Video Signal - 0 - 4.5 MHz

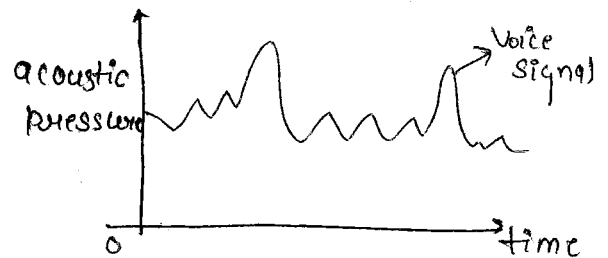

Source Transducer:

It converts physical signal into electrical equivalent.

eg - microphone

Wired communication system:

It is preferred only for short distance communication.


For long distance communication 'wireless transmission' is preferred in which signal propagates through 'free space'.

Receiving Transducer:

It converts electrical signal into physical equivalent.

e.g. - loudspeaker.

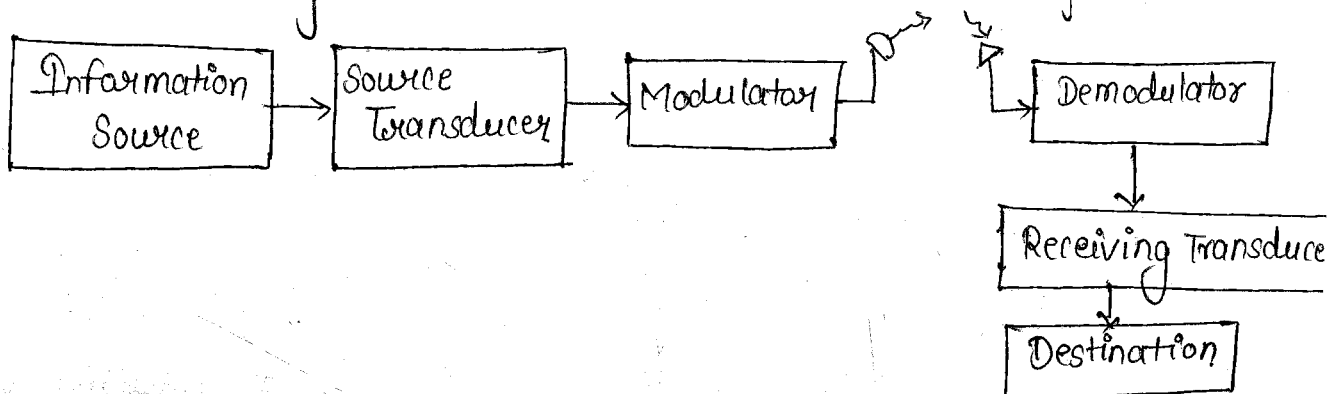Block Diagram of wireless communication system:



Generally without modulation long distance communication through free space is not possible.

### Need for modulation -

1) Reducing antenna height:



$$h_t = \frac{\lambda}{4}$$

$$\lambda = \frac{v}{f}$$

$$v = c$$

$$\lambda = \frac{c}{f}$$

$$h_t = \frac{c}{4f}$$

i)  $f = 15 \text{ kHz}$

$$h_t = \frac{3 \times 10^8}{4 \times 15 \times 10^3} = 5 \text{ km} \quad (\text{Practically not possible to construct antenna with this height})$$

ii)  $15 \text{ kHz} \rightarrow \text{Modulator} \rightarrow 1 \text{ MHz}$

$$h_t = \frac{3 \times 10^8}{4 \times 10^6} = 75 \text{ m.} \quad (\text{Possible})$$

- for faithful radiation of a signal antenna height should be atleast of ' $\frac{\lambda}{4}$ '.
- Transmitting antenna converts electrical signal into electro magnetic, resulting propagates with light velocity.

### NOTE -

Modulation is the process of increasing frequency of the signal to reduce antenna height requirements.

2) Multiplexing: It is the process of transmitting multiple number of signal through a single channel.


- Generally without modulation, multiplexing is not possible.

## Fourier Transform:

Fourier transform is basically used to find frequencies present in the given time domain signal.


$$x(t) \longrightarrow X(f)$$
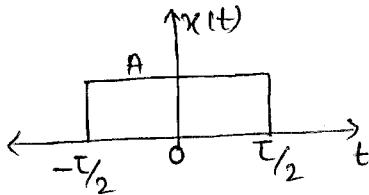
$$X(f) = \int_{-\infty}^{\infty} x(t) e^{-j2\pi ft} dt$$




$$X(f) = AT \operatorname{sinc}(fT)$$

E.g.

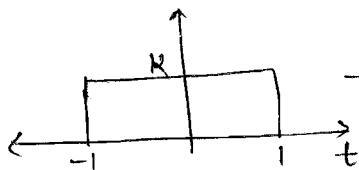
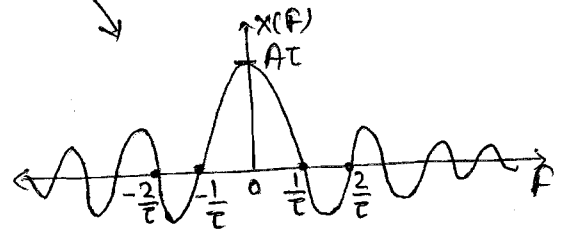
$$\longrightarrow 2K \operatorname{sinc}(2f)$$



Signal Bandwidth = Highest +ve freq. - Lowest +ve freq.

Channel bandwidth  $\geq$  signal bandwidth.


Channel standards -

Co-axial cable - 0 - 600 MHz


Parallel wire - 0 - 200 K

Fiber optic cable - GHz =  $10^9$  Hz = 1000 MHz

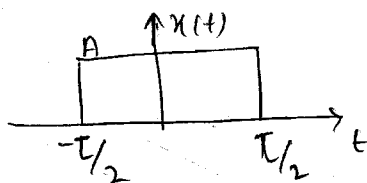- For proper transmission of above signal, channel bandwidth or infinite is required but bandwidth offered by practical channel will be finite only so that before transmission it should be bandlimited by using 'Bandlimiting Process'.



$$E = \int_{-\infty}^{\infty} x^2(t) dt = A^2 T = \int_{-\infty}^{\infty} |X(f)|^2 df$$

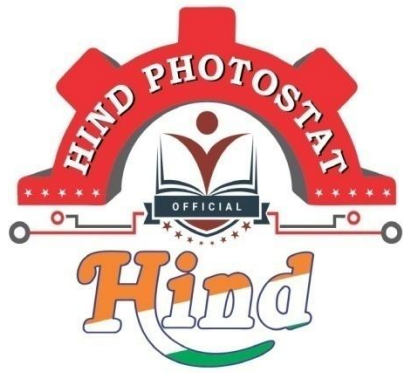

# HindPhotostat



## Hind Photostat & Book Store

**Best Quality Classroom Topper Hand Written Notes to Crack GATE, IES, PSU's & Other Government Competitive/ Entrance Exams**

**MADE EASY  
ELECTRICAL ENGINEERING  
Computer Fundamental  
By.Sagar Sir**

- Theory
- Explanation
- Derivation
- Example
- Shortcuts
- Previous Years Question With Solution


**Visit us:-[www.hindphotostat.com](http://www.hindphotostat.com)**

**Courier Facility All Over India  
(DTDC & INDIA POST)  
Mob-9311989030**

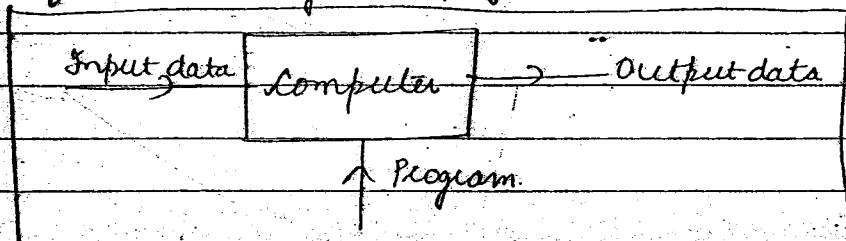
# Computer Fundamentals

Keywords :-

Computer → It is a computational machine used to process the data under the control of a program. ∴ computer system functionality is program execution.



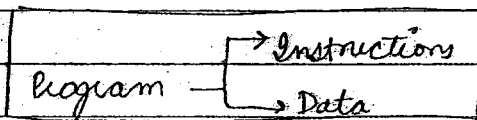Program :- Program is a sequence of instructions along with a data.




Instruction :- It is a binary code, which is designed inside the processor to perform some task.

Binary code - binds with - operation.

Ex:- CPU-X supports 8 different operations, then

$$\text{opcode} = \log_2 8 = 3 \text{ bit}$$

opcode operation

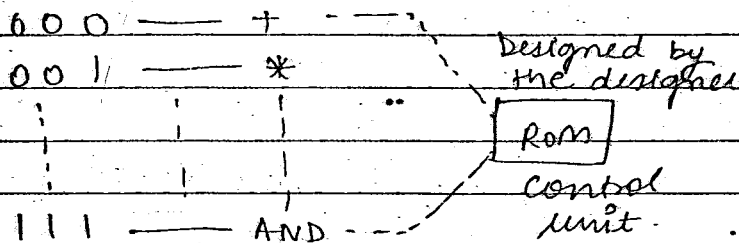

how we are writing the program - is stored in RAMs

Q 6 bit opcode  $\rightarrow$  No. of operations?

$$2^6 = (64)$$

Data  $\Rightarrow$  It is a binary code, which is associated with a value based on the data format.

Binary code - kind - value  
with

Ex.  $101 = 5$ ,  $-1$ ,  $-2$ ,  $-3$ , fraction.  
 $\begin{array}{r} 2 \ 1 \ 0 \\ 1 \ 0 \ 1 \end{array}$   $\uparrow$  sign magnitude format  
 $4 + 1 = 5$

$$\begin{array}{r} 101 \\ -1 \end{array}$$

$$\begin{array}{r} 101 \\ -2 \end{array} \rightarrow 1's \text{ complement format}$$

$$\begin{array}{r} 101 \\ -10 \\ -11 \end{array} = -3 \rightarrow 2's \text{ complement format}$$


fraction = floating point format.

- $\rightarrow$  Fixed point data
- $\rightarrow$  Floating point data

Topic 1: Data Representation



# Data formats

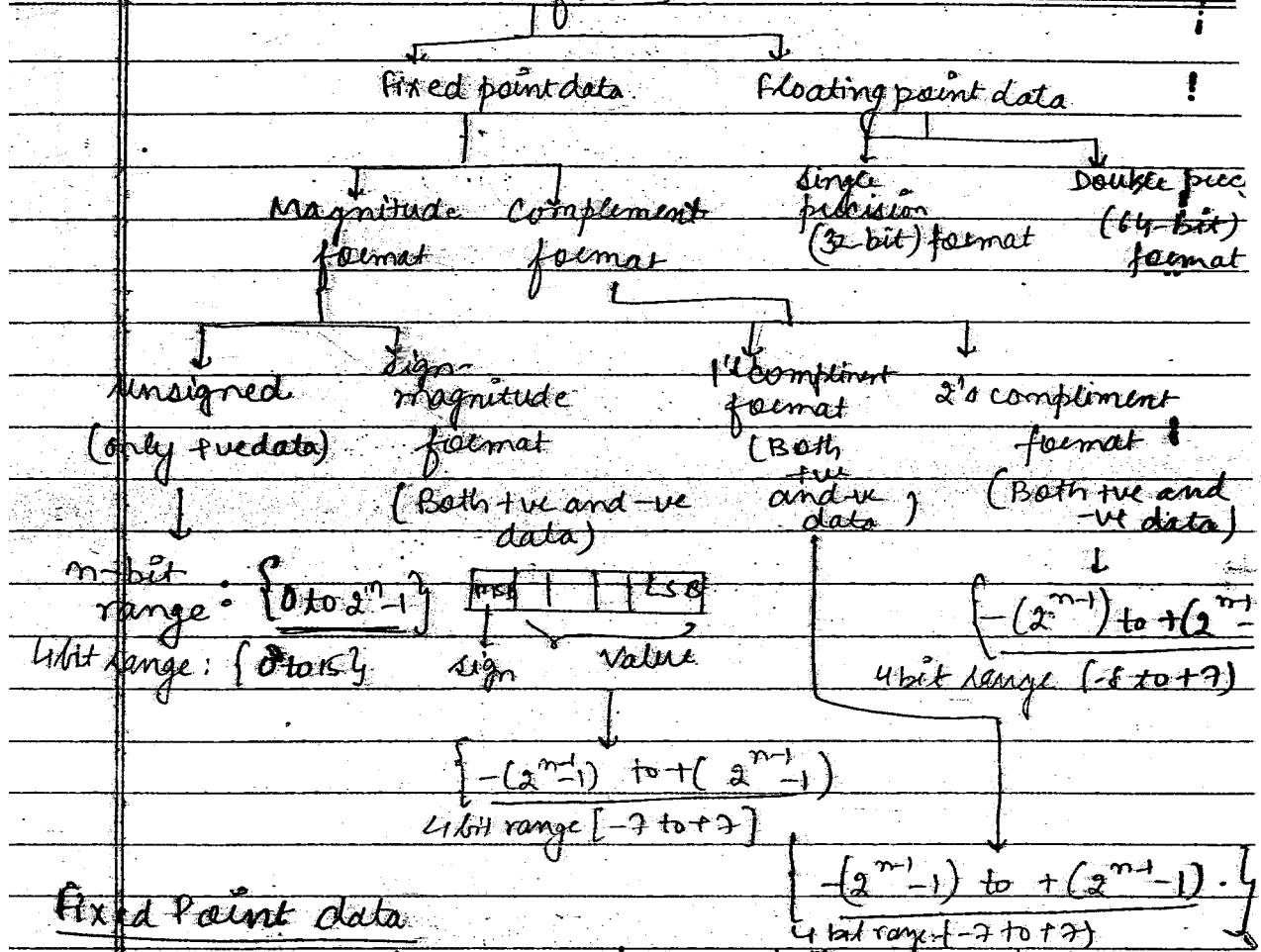

## Fixed Point data

4-bit binary	Unsigned data	Sign mag.	1's complement data	2's complement data
0000	0	+0	+0	+0
0001	1	+1	+1	+1
0010	2	+2	+2	+2
0011	3	+3	+3	+3
0100	4	+4	+4	+4
0101	5	+5	+5	+5
0110	6	+6	+6	+6
0111	7	+7	+7	+7
1000	8	-0	-7	-8
1001	9	-1	-6	-7
1010	10	-2	-5	-6
1011	11	-3	-4	-5
1100	12	-4	-3	-4

	Unsigned data	Sign mag	1's comp	2's complement
	1101	13	-5	-3
	1110	14	-6	-2
	1111	15	-7	-1
			Not in use	Not in use

→ In computers, binary data (base-2) - computers use decimal (base-10) - user data

→ eg. 8 bit single unit - fixed point data  
 " " in multiple units - floating point data

→ sign magnitude format: drawback of data redundancy (it was just the concept and rejected this format)

0000 → 0

1000 → -0

1111 → -7

→ In computer only 1's and 2's complement are there, not other complements

→ same problem of +0 and -0 in 1's complement format ∴ rejected

→ No data redundancy in 2's complement format ∴ it was implemented


some 1's complement - 1000 → -7      1001 → -6  
 111                                      110

2's complement

$\begin{array}{r} 1000 \rightarrow -8 \\ 0111 \\ \hline 1000 \end{array}$	$\begin{array}{r} 1001 \rightarrow -7 \\ 0110 \\ \hline 0111 \end{array}$
---	---

fixed point data   
 → unsigned data (unsigned format)   
 → signed data (2's complement format)

Unsigned data

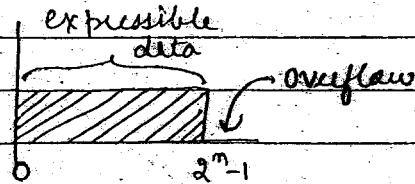

eg 4-bit range: {0 to 15}

15: 1111   
 (+) 15: 1111   
 --- 30 1110

overflow   
 5 bit data (0 to 31)

overflow: no's out of range of (0 to 15) all are overflow.


Test with 5 bit data: {0 to 31}

$n\text{-bit} + n\text{-bit} = (n+1)\text{ bit}$

- ↓
- 1 bit storage space
- ↓
- 1-flip flop
- ↓
- Flag
- ↓
- carry flag.

→ Multiplication

<p>Multiplicand</p> <p>1111</p>	<p>Multiplier</p> <p>111</p>	<p>ESB</p>
<p>-----</p>		
<p>2 1</p> <p>3 1 1 1</p> <p>3 1 1 1</p> <p>2 1 1 1</p> <p>1 1 1 1</p>	<p>} partial products.</p>	<p>↑ carry</p> <p>2 → 10</p> <p>4 → 100 car</p> <p>6 → 110 cy</p> <p>8 → 101</p> <p>cy</p>
<p>-----</p> <p>11100001</p> <p>-----</p>		
<p>} final product</p>		

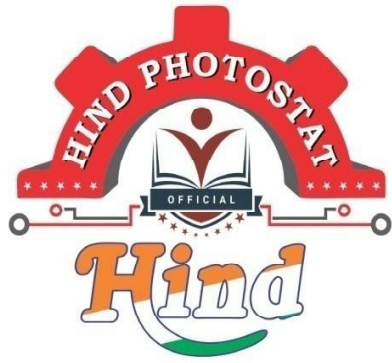

# HindPhotostat



## Hind Photostat & Book Store

Best Quality Classroom Topper Hand Written Notes to Crack GATE, IES, PSU's & Other Government Competitive/ Entrance Exams

### MADE EASY ELECTRICAL ENGINEERING Basic Electronics By.Rajender Sir

- Theory
- Explanation
- Derivation
- Example
- Shortcuts
- Previous Years Question With Solution

Visit us:-[www.hindphotostat.com](http://www.hindphotostat.com)

Courier Facility All Over India  
(DTDC & INDIA POST)  
Mob-9311989030



# HindPhotostat



**MADE EASY , IES MASTER , ACE ACADEMY , KREATRYX**

**ESE , GATE, PSU BEST QUALITY TOPPER HAND WRITTEN NOTES  
MINIMUM PRICE AVAILABLE @ OUR WEBSITE**

- |                                |                           |
|--------------------------------|---------------------------|
| 1. ELECTRONICS ENGINEERING     | 2. ELECTRICAL ENGINEERING |
| 3. MECHANICAL ENGINEERING      | 4. CIVIL ENGINEERING      |
| 5. INSTRUMENTATION ENGINEERING | 6. COMPUTER SCIENCE       |

**IES , GATE , PSU TEST SERIES AVAILABLE @ OUR WEBSITE**

❖ IES –PRELIMS & MAINS

❖ GATE

➤ **NOTE;- ALL ENGINEERING BRANCHS**

➤ **ALL PSUs PREVIOUS YEAR QUESTION PAPER @ OUR WEBSITE**

## **PUBLICATIONS BOOKS -**

**MADE EASY , IES MASTER , ACE ACADEMY , KREATRYX , GATE ACADEMY , ARIHANT , GK**

**RAKESH YADAV , KD CAMPUS , FOUNDATION , MC –GRAW HILL (TMH) , PEARSON...OTHERS**

**HEAVY DISCOUNTS BOOKS AVAILABLE @ OUR WEBSITE**

<b>F230, Lado Sarai New Delhi-110030 Phone: 9311 989 030</b>	<b>Shop No: 46 100 Futa M.G. Rd Near Made Easy Ghitorni, New Delhi-30 Phone:9711475393</b>	<b>F518 Near Kali Maa Mandir Lado Sarai New Delhi-110030 Phone: 9560 163 471</b>	<b>Shop No.7/8 Saidulajab Market Neb Sarai More, Saket, New Delhi-30</b>
--	--	--	--

**Website: [www.hindPhotostat.com](http://www.hindPhotostat.com)**

**Contact Us: 9311 989 030**

**Courier Facility All Over India**

**(DTDC & INDIA POST)**

## Books!..

1) Semiconductor Physics and Devices  
- DONALD NEAMEN.

2) GATE

↳ Basics } Solved Examples  
↳ Diode } of Donald Neamen.  
↳ \*\* FET }

## \* CLASSIFICATION OF TEMPERATURE (T):

\* Divided into three parts:

1) ABSOLUTE TEMPERATURE ( $0\text{K} = -273^\circ\text{C}$ )

2) ROOM TEMPERATURE ( $300\text{K} = 27^\circ\text{C}$ )

3) AMBIENT TEMPERATURE ( $T_A$ ) ( $290\text{K} = 17^\circ\text{C}$ )

old Notation  
\*  
 $^\circ\text{K} = \text{K}$   
New Notation

\* Absolute Temperature is Practically not possible. It is only the Reference Temperature, and never used in Reality.

\* Absolute Temperature is just a Reference temperature

\* At Room temperature, all properties of Semiconductor Devices are max<sup>m</sup> at Room temperature.

\* All Properties of Comm<sup>n</sup> systems are taken at the Ambient Temp. ie  $290\text{K}$  or  $17^\circ\text{C}$ .

\* \*\*  
 $\text{TEMPERATURE in KELVIN} = \text{TEMPERATURE in } ^\circ\text{C} + 273$

## \* THERMAL VOLTAGE ( $V_T$ ) :-

\* Also called as the "VOLT EQUIVALENT OF TEMPERATURE".

\* Most of S.C devices properties changes with temperature.

\* Mathomatically,

$$** V_T = \frac{\bar{K} T}{q} \text{ volts}$$

Where,  $T$  = Temperature in Kelvin  
 $q$  = Magnitude of charge ( $1.6 \times 10^{-19} \text{C}$ )  
 $\bar{K} = 1.381 \times 10^{-23} \text{ J/}^\circ\text{K}$

Also,

$$V_T = \frac{T}{11600} \text{ volts}$$

Hence,

i) At  $T = 0\text{K} \Rightarrow V_T = 0 \text{ volts}$

ii) At  $T = 300\text{K} \Rightarrow V_T = \frac{300}{11600}$

\*\*  
 $V_T = 0.02568 \text{ volts}$   
 $= 26 \text{ mV.}$

Note:

i) For a large variation in Temperature, the variation in the Thermal voltage is negligible.

\* BOLTZMANN CONSTANT:

$$\bar{K} = 1.381 \times 10^{-23} \text{ J/}^\circ\text{K}$$

$$K = 8.62 \times 10^{-5} \text{ eV/}^\circ\text{K}$$

Hence, \*\*  
 $\bar{K} = 1.6 \times 10^{-19} \text{ K}$

Hence,  $V_T = \frac{\bar{K}T}{q} = \frac{qKT}{q}$


\*\*  
 $V_T = KT = \frac{\bar{K}T}{q}$

↳ Numerically equal values.

\* ENERGY GAP ( $E_G$  or  $E_g$ ):

\* Gap between Valence Band and Conduction Band is called as Energy Gap.

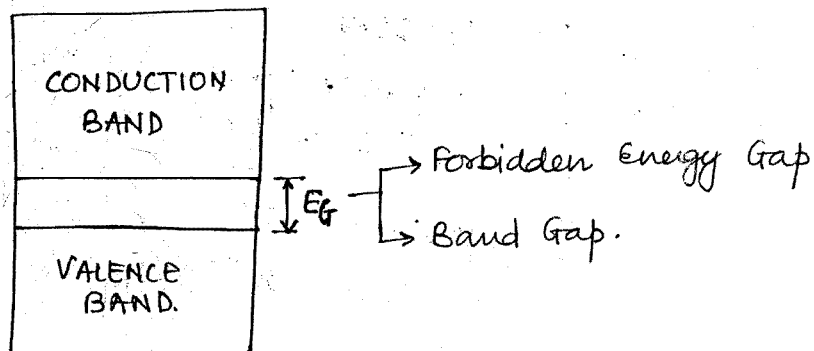\* Band diagram of Semiconductor (SC) is given as:



	$E_{G0}$	$E_{G300}$
Ge	0.782 eV	0.72 eV
Si	1.21 eV	1.1 eV

\*\* Energy Gap decreases with Temperature in a semiconductor.  
Mathematically,

$$E_G \propto \frac{1}{\text{Temp}}$$

\* To calculate  $E_G$  at different temp we can use:

$$E_G(T) = E_{G0} - \beta_0 T \text{ (eV)}$$

$\beta_0 =$  material constant (eV/°K)

\* For Germanium:


$$E_G(T) = 0.782 - 2.33 \times 10^{-4} T \text{ (eV)}$$

\* For Silicon:

$$E_G(T) = 1.21 - 3.6 \times 10^{-4} T \text{ (eV)}$$

\* For a semiconductor, Energy Gap is small

$$E_G \leq 1.5 \text{ eV}$$

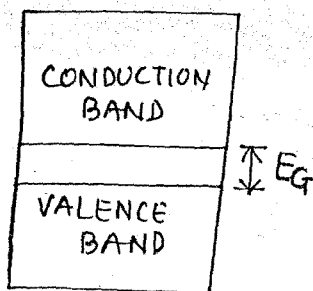

Note:

- 1) Semiconductors are BIPOLAR
- 2) Semiconductor can contribute DIFFUSION CURRENT.
- 3) Semiconductor has NTC of RESISTANCE


$$T \uparrow \quad R \downarrow$$



\*Note:

\* For Insulators, the Energy Gap is large

\*\*  $EG \gg 5eV$

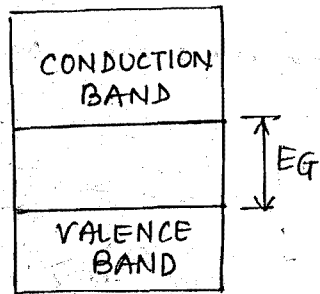

\* Insulators are Bad conductors of current, and their conductivity is negligible.

\* For Ideal Insulator, Conductivity is zero.


Note:

1) If Energy Gap is small, less amount of additional energy is required for the  $e^-$  to jump from "VALENCE BAND" to "CONDUCTION BAND"


\* For Metals (conductors):

$EG = 0eV$  ← Practically negligible value.

↳ (Non Zero Energy Gap)

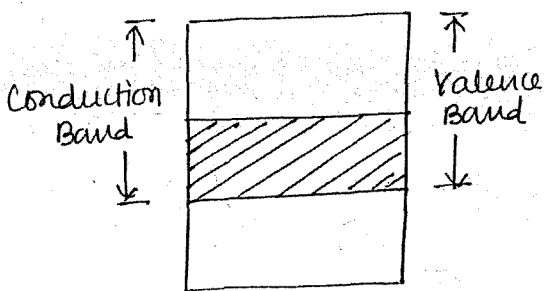

(at  $T = 300K$ )

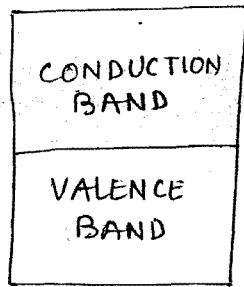

(at  $T = 0K$ )

\* For metals, the conductors ~~and~~ the Conduction Band and valence Band overlap each other and the overlapping increases with Temp.

\* Conductivity is very large in conductors

\* Only DRIFT CURRENT flows in conductor

\* Conductors are unipolar, current carried only by  $e^-$ .

\* PTC of Resistance: \*\*  $T \uparrow R \uparrow$  ← Exclusive Property of Metals.

Definition of Semiconductor:

\* Semiconductors are the elements whose conductivity lies in between in the conductivity of an insulators and the conductivity of a metal.

ELECTRON VOLT (eV):

\* Electron volt is a unit of ENERGY


\* Very small unit of Energy (almost fraction of unit of Energy i.e Joule).

\* Electron volt is the unit of ENERGY in Electronics

\* 1 eV is defined as the energy gained by the electron ( $e^-$ ) in moving through a potential difference of 1V.

Note:

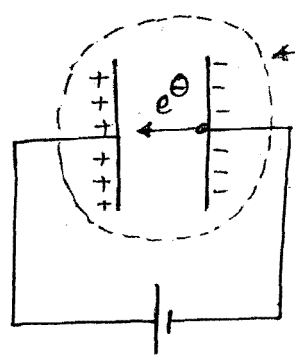\* Air is a perfect insulator, the Best insulator.



Vacuumised Glass Tube

Note:

\*  $e^-$  cannot move through air, hence air in the glass has been removed.

\*  $e^-$  can move through Vacuum  
 ↳ for eg → Vacuum Tubes

Mathematically,

$$1 eV = |q| \times \text{Potential difference}$$

$$= 1.6 \times 10^{-19} C \times 1V$$

$$= 1.6 \times 10^{-19} CV$$

Or  $1 eV = 1.6 \times 10^{-19} \text{ Joules}$   
 $= 1.6 \times 10^{-19} \text{ Coulomb-Volt}$

Note:

\* Electron volt is the Kinetic Energy Gained by the  $e^-$  or the Potential energy lost by the  $e^-$ .

Mathematically,

\*\* Kinetic Energy =  $\frac{1}{2} m v^2$   
 $m = \text{mass of } e^-$   
 $= 9.1 \times 10^{-31} \text{ Kg}$

\*\* Potential Energy =  $q \times V$   
 $V = \text{Potential difference}$

By definition:

KE gained = PE lost

$\frac{1}{2} m v^2 = q V$

\*\* Velocity of  $e^-$ ,  $v = \sqrt{\frac{2qV}{m}}$  m/s

\* ELECTRIC FIELD INTENSITY ( $\epsilon$  or  $E$ ) :-

- \* Also called Field Intensity
- \* Also called as Field Gradient
- \* Also called as Field.


\* Mathematically,

\*\*  $\epsilon_0 = -\frac{dV}{dx}$  Volt/metre

Also, \*\*

$|\epsilon_0| = \frac{\text{magnitude of voltage existing}}{\text{distance or space}}$

Note :-

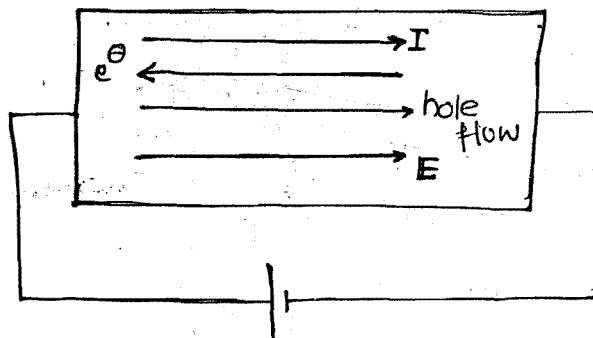



# HindPhotostat



## Hind Photostat & Book Store

**Best Quality Classroom Topper Hand Written Notes to Crack GATE, IES, PSU's & Other Government Competitive/ Entrance Exams**

### **MADE EASY**

**IES/GATE/PSU**

**REASONING**

**BY-DHEERAJ SIR**

- Theory
- Explanation
- Derivation
- Example
- Shortcuts
- Previous Years Question With Solution

**Visit us:-[www.hindphotostat.com](http://www.hindphotostat.com)**

**Courier Facility All Over India  
(DTDC & INDIA POST)  
Mob-9311989030**

\* NUMBER SYSTEM:

- V → Vinculum (BAR)
- B → Bracket. {}
- O → of.
- D → Division. (÷)
- M → Multiplication (x)
- A → Addition. (+)
- S → Subtraction (-)

Q1) Convert the following recurring terms into their corresponding P/Q forms?

a)  $27.\overline{17}$

↓  
Complete Bar

$27.171717\dots$

(Bar immediately after point).

b)  $27.2\overline{17}$

↓  
Partial Bar

$27.21717\dots$

c)  $0.00\overline{17}$

↓  
Partial Bar

$0.00171717\dots$

Soln. a)  $27.\overline{17}$

$$x = 27.171717\dots$$

$$100x = 2717.1717\dots$$

$$100x - x = 2717.1717\dots - 27.1717\dots$$

$$99x = 2690$$

$$x = \frac{2690}{99}$$

SHORTCUT

$$x = 27.\overline{17}$$

$$P/Q = \frac{2717 - 27}{99}$$

$$= \frac{2690}{99}$$

b)  $27.2\overline{17}$

$$x = 27.21717\dots$$

$$\frac{P}{Q} = \frac{27217 - 272}{990}$$

$$\frac{P}{Q} = \frac{26945}{990}$$

c)  $0.00\overline{17}$

$$\frac{P}{Q} = \frac{00017 - 000}{9900}$$

$$\frac{P}{Q} = \frac{17}{9900}$$

Q2)  $27 \cdot 27 \times 33 + 6$

Soln:  $\frac{(2727 - 27)}{443} \times 33 + 6$

$= \frac{2700 \times 33}{3} + 6$   
 $= 300 \cdot 906$

Q3) What is the unit's digit in the expansion of  $(766)^{136}$ .

Soln: a)  $(766)^{136}$  ← Based on cyclicity or power cycle →

- b)  $(277)^{134}$
- c)  $(454)^{41}$
- d)  $(888)^{103}$
- e)  $(1028)^{100}$
- f)  $(459)^{40}$

- $0^N = 0$
- $1^N = 1$
- $2^N =$
- $2^1 = 2$
- $2^2 = 4$
- $2^3 = 8$
- $2^4 = 16$
- $2^5 = 32$
- $2^6 = 64$
- $2^7 = 128$
- $2^8 = 256$
- $2^9 = 512$

→ cyclicity of  $2^N$  is 4 ie 2, 4, 8, 6

$3^N$  ← cyclicity is 4 ie (3, 9, 7, 1)

- $3^1 = 3$
- $3^2 = 9$
- $3^3 = 27$
- $3^4 = 81$
- $3^5 = 243$
- $3^6 = 729$
- $3^7$

$4^N$  ← cyclicity is (4, 6)

- $4^1 = 4$
- $4^2 = 16$
- $4^3 = 64$
- $4^4 = 256$
- $4^5 = 1024$

NUMBERS	FREQN OF NOS. as POWER CYCLE
0, 1, 5, 6	STAY AS IT IS
2, 3, 7, 8	4
4, 9	2

a)  $(766)^{136} \rightarrow$  unit digit = 6.

b)  $(277)^{134} \rightarrow 4$

c)  $(454)^{134} \rightarrow 2$

d)  $(222)^{103} \rightarrow 4$

a)  $(766)^{136} = 766 \times 766 \times 766 \times 766 \times \dots \times 766$  136 times.  
 $= \dots 6 \times \dots 6 \times \dots 6 \times \dots 6 \times \dots$   
 $= \dots 6$

$(\dots 0/1/5/6)^{\alpha \times \dots \times \alpha} = \dots 0/1/5/6$

b)  $(277)^{134} = 277 \times 277 \times 277 \times 277 \times \dots \times 277$  134 times.  
 $= \dots 7 \times \dots 7 \times \dots 7 \times \dots 7 \times \dots$  134 times.

$\dots \times \dots \times \dots \times \dots \times (277 \times 277)$

$\downarrow$   
 49  
 $\downarrow$   
 units digit is (9)

33 ← Complete sections.

$$\begin{array}{r} 4 \overline{)134} \\ \underline{12} \\ 14 \\ \underline{12} \\ 2 \end{array}$$

$\nearrow$

Short cut:

$(277)^{134} \rightarrow$  Power cycle = 4

$$\begin{array}{r} 4 \overline{)134} \\ \underline{12} \\ 14 \\ \underline{12} \\ 2 \end{array}$$

$\times 2$   
 $\times 7 = 49$

$\downarrow$   
 units place (units digit)

\*  $(454)^{41} \rightarrow$  Power cycle = 2

$$\begin{array}{r} 20 \\ 2 \overline{) 41} \\ \underline{40} \\ 1 \end{array}$$

$4^1 = 4$

\*  $(1028)^{100} \rightarrow$  Power cycle = 4

$$\begin{array}{r} 25 \\ 4 \overline{) 100} \\ \underline{100} \\ 000 \end{array} \leftarrow \text{Remainder}$$

$8^0 = 1$

\*  $(888)^{103} \rightarrow$  Power cycle = 4

$$\begin{array}{r} 25 \\ 4 \overline{) 103} \\ \underline{100} \\ 3 \end{array}$$

$8^3 = 512$

\*  $(459)^{40} \rightarrow$  Power cycle = 2

Remainder = 0

\* Special case of Remainder zero:

\* All complete sections.

\* NO incomplete section.

$(1028)^{100} \rightarrow$  P.C = 4

$$\begin{array}{r} 25 \\ 4 \overline{) 100} \\ \underline{100} \\ 0 \end{array}$$


$8^4 = 8^2 \times 8^2$   
 $= 64 \times 64$   
 $= \dots (6)$

\*  $(459)^{40} \rightarrow$  P.C = 2

$$\begin{array}{r} 20 \\ 2 \overline{) 40} \\ \underline{40} \\ 00 \end{array}$$

$9^2 = 9 \times 9 = 81$

\* Remainder 0 short cut:

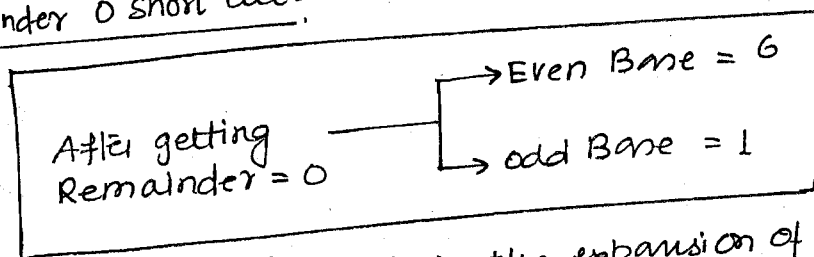

Q4) What is the unit's digit in the expansion of the following expression:

$(666)^{666} \times (877)^{134} + (959)^{20}$

$$\begin{array}{r} 33 \\ 4 \overline{) 134} \\ \underline{132} \\ 2 \end{array}$$

$7^2 = 49$


Soln:  $(\dots 6 \times \dots 9) + \dots + 1$   
 $= (\dots 4) + (\dots 1) = \dots 5$

$$\begin{array}{r} 5 \\ 9 \overline{) 20} \\ \underline{20} \\ 00 \end{array}$$

$(959) \rightarrow$  odd Base = 1



SUMMARY

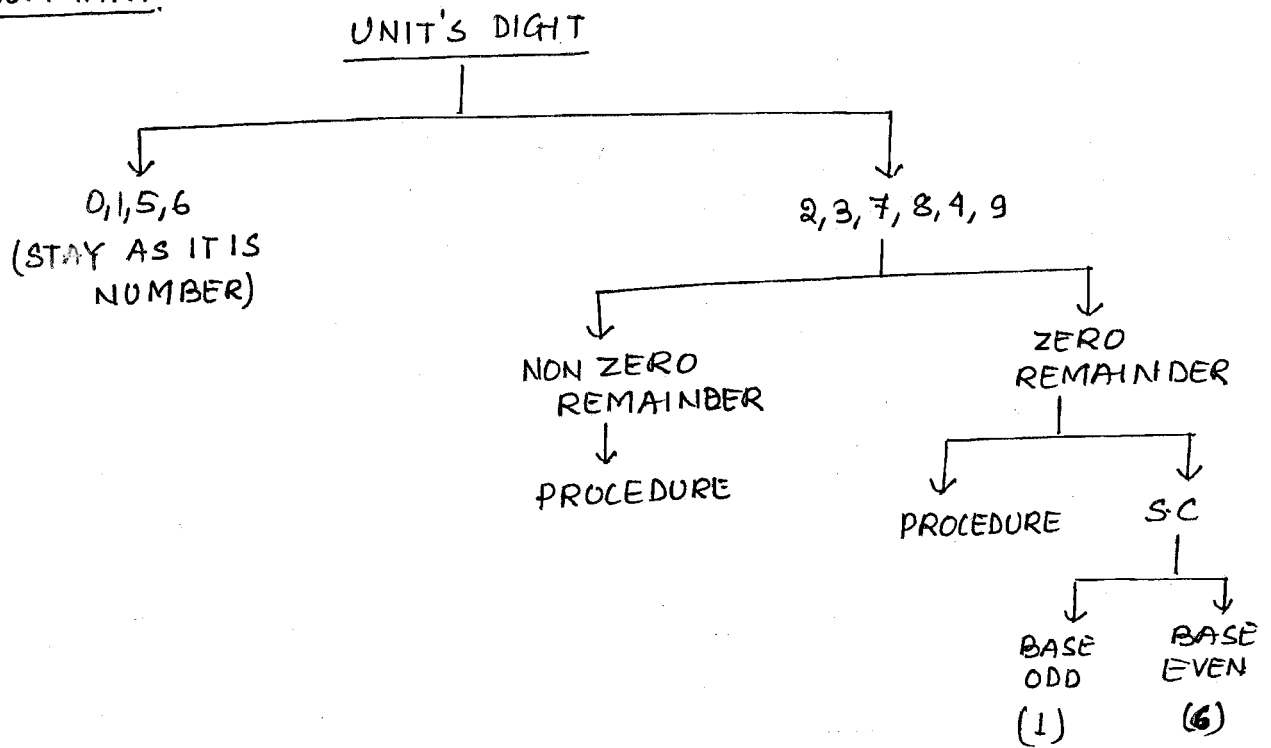

Q) How many zeroes are there at last in the expansion of

- a)  $25 \times 4 \times 8 \times 7 \times 10 \times 16 \times 100$   
 b)  $(25)^{125} \times 4^{40}$

Soln: a)  $25 \times 4 \times 8 \times 7 \times 10 \times 16 \times 100$   
 $100 \times 56 \times 16 \times 1000$   
 $= 56 \times 16 \times 100000$

b)  $(25)^{125} \times (4)^{40}$   
 $(5)^{250} \times 2^{80}$   
 80 ZERO ← LEAST POWER

$$5^2 \times 2^2 \times 2^3 \times 7 \times 5 \times 2 \times 2^4 \times 2^2 \times 5^2$$

$$= 2^{12} \times 5^5 = 2^7 \times 2^5 \times 5^5 \text{ least power}$$

$$= 2^7 \times 10^5$$

← = 5 ZEROS

Note:  $7^{125} \times 4^{50}$   
 $7^{125} \times 2^{100}$   
 NO ZEROS

ZERO'S AT LAST CONDITION :-

- i) Multiple of 10. → direct multiple ie 10, 100, 1000, ...
  - ii) Hidden multiple → (2, 5)
- \*The total no. of (2x5) combinations = no. of zeroes at last in the expansion

(total no. of (2x5) comb<sup>n</sup>) = (no. of zeroes at last in expansion)

Q6) How many zeros are there at last in the expansion of !.

- a) 6!
- b) 10!
- c) 100!
- d) 145!
- e) 1000!

Note !.

1! = 1; 2! = 2; 3! = 6; 4! = 24

5! = 120

↓ onwards only zeros will start coming not before that.

Soln a) 6! = 6 × 5 × 4 × 3 × 2 × 1  
 = 6 × 5<sup>1</sup> × 3 × 2<sup>3</sup>  
 = 1 ZERO

b) 10! = 10 × 9 × 8 × 7 × 6 × 5 × 4 × 3 × 2 × 1  
 = 2 × 5 × 9 × 2<sup>3</sup> × 7 × 3 × 2 × 5 × 2<sup>2</sup> × 3 × 2 × 1  
 = 2<sup>8</sup> × 5<sup>2</sup>  
 = 2 ZEROS

c) 100!  
 ↓  
 100 → 20 × 5  
 95 → 19 × 5  
 90 → 18 × 5  
 85 → 17 × 5  
 80 → 16 × 5  
 75 → 15 × 5 = 3 × 5 × 5  
 70 → 14 × 5

65 → 13 × 5	30 → 6 × 5
60 → 12 × 5	25 → 5 × 5
55 → 11 × 5	20 → 5 × 4
50 → 10 × 5 = 2 × 5 × 5	15 → 3 × 5
45 → 9 × 5	10 → 2 × 5
40 → 8 × 5	5 → 1 × 5
35 → 7 × 5	

Note ∴ for 100! zeros are by default. They will come by default and no. of zeros depends on no. of 5's present in it.

100! = 1 × 2 × 3 × 4 × 5 × 6 × 7 × 8 × 9 × 10 × 11 × 12 × 13 × 14 × 15 × 16 × 17 × 18 × 19 × 20 × ... × 100

$\frac{100}{5} = 20$  sections ← divide the complete 100! in 20 sections.

\* In these sections some special nos (which contain 2 5's will also be there). such as:

Already taken into account in dividing sections.


25 → 5 × 5 (NOT TAKEN INTO ACCOUNT IN 20 SECTIONS)

50 → 5 × 5 × 2

75 → 5 × 5 × 3

100 → 5 × 5 × 4

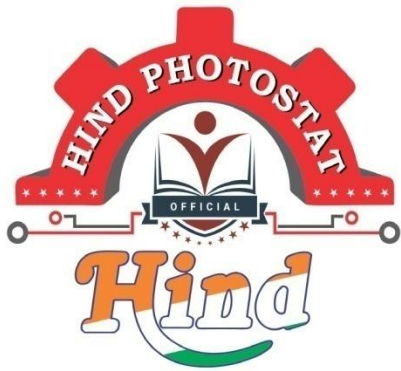→ NOW taking =  $\frac{100}{5} + \frac{100}{25} = 24$ .



# HindPhotostat



## Hind Photostat & Book Store

Best Quality Classroom Topper Hand Written Notes to Crack GATE, IES, PSU's & Other Government Competitive/ Entrance Exams

### MADE EASY IES/GATE/PSU MATHEMATICS BY-RAMU MALADI SIR

- Theory
- Explanation
- Derivation
- Example
- Shortcuts
- Previous Years Question With Solution

Visit us:-[www.hindphotostat.com](http://www.hindphotostat.com)


Courier Facility All Over India  
(DTDC & INDIA POST)  
Mob-9311989030

\* LINEAR ALGEBRA ∴

Analysis

$$\begin{aligned} x+2y &= 3 \\ 2x+3y &= 5 \end{aligned}$$

so,  $x=1, y=1$   
Intersecting line

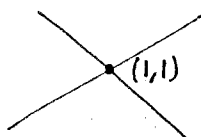

(x' and y')

\* Any 1st degree 2 dimensional equation in  $x+y$  represents a line in the  $xy$  PLANE. (LINEAR SYSTEM OF EQUATION IN 2 VARIABLES)

Note ∴

\* The study of LINEAR SYSTEM OF EQUATIONS is called LINEAR ALGEBRA.

$$\begin{aligned} x+2y &= 3 \\ 2x+3y &= 5 \end{aligned}$$

on solving the equation  
 $x=1; y=1$   
(UNIQUE SOLUTION)

$$\begin{aligned} x+2y &= 3 \\ 2x+4y &= 6 \end{aligned}$$

let  $y=k$   
 $x=3-2k$   
(INFINITE NO. OF SOLUTION)

$$\begin{aligned} x+2y &= 3 \\ x+2y &= 5 \end{aligned}$$

(NO SOLUTION)

\* To study about the linear system of equations, we require the concept "RANK OF MATRIX". Hence we study about MATRICES in the concept LINEAR ALGEBRA.

\* MATRIX ∴

\* Arrangement of elements or numbers in Rows and Columns such that each row will have same no. of element and each column will have same no. of element is called a MATRIX.

## \*Operation on Matrices:

- 1) Addition
- 2) Subtraction
- 3) Multiplication  $\{ A_{m \times l} \times B_{l \times n} = C_{m \times n} \}$
- 4) TRACE OF SQUARE MATRIX:

\*The sum of the PRINCIPAL DIAGONAL ELEMENTS OF A SQUARE MATRIX is called TRACE.

## 5) SYMMETRIC MATRIX:

When  $A^T = A$

$$\begin{bmatrix} 1 & 5 & -1 \\ 5 & 2 & 9 \\ -1 & 9 & 3 \end{bmatrix}$$

the matrix A is ~~is~~ Symmetric

## 6) SKEW SYMMETRIC MATRIX:

When  $A^T = -A$

$$\begin{bmatrix} 0 & 3 & -5 \\ -3 & 0 & 9 \\ 5 & -9 & 0 \end{bmatrix}$$

then Matrix A is SKEW SYMMETRIC.

COMPULSORY CONDITION  
(diagonal elements should be zero)

## \*DETERMINANT OF SQUARE MATRIX:

\*For a 1x1 MATRIX, the no. ~~itself~~ itself is the Determinant

\*For a 2x2 MATRIX of the form:

$$\begin{bmatrix} a & b \\ c & d \end{bmatrix}$$

the determinant is given by (ad-bc)

## \*MINOR OF AN ELEMENT:

let

$$\begin{bmatrix} a_{11} & a_{12} & a_{13} \\ a_{21} & a_{22} & a_{23} \\ a_{31} & a_{32} & a_{33} \end{bmatrix}$$

then Minor of  $a_{11} = \begin{vmatrix} a_{22} & a_{23} \\ a_{32} & a_{33} \end{vmatrix} = (a_{22}a_{33} - a_{32}a_{23})$

Minor of  $a_{21} = \begin{vmatrix} a_{12} & a_{13} \\ a_{32} & a_{33} \end{vmatrix} = (a_{12}a_{33} - a_{32}a_{13})$

\* COFACTOR of an element :-

\* Minor of  $a_{ij}$  is  $M_{ij}$ ; then cofactor of  $a_{ij}$  is

$$\text{Cofactor of } a_{ij} = (-1)^{i+j} \cdot M_{ij}$$

\* The Determinant of square matrix is defined as "The sum of product of elements of any row or any column with the corresponding cofactors"

\* Analysis :-

let  $A = \begin{bmatrix} 1 & 0 & 2 & 1 \\ 1 & 0 & 1 & -1 \\ 1 & 2 & 3 & 1 \\ 1 & 0 & 2 & 0 \end{bmatrix}$

\* we have to find the determinant of given  $4 \times 4$  matrix. For this choose any row or column having the max<sup>m</sup> no. of zeroes.

using 2<sup>nd</sup> column we get:

$$2(-1)^{3+2} \begin{vmatrix} 1 & 2 & 1 \\ 1 & 1 & -1 \\ 1 & 2 & 0 \end{vmatrix}$$

$$= -2 \{ 1(0+2) - 2(0+1) + 1(2-1) \}$$

$$= -2$$

using 4<sup>th</sup> column we get

$$1 \cdot (-1)^{4+1} \begin{vmatrix} 0 & 2 & 1 \\ 0 & 1 & -1 \\ 2 & 3 & 1 \end{vmatrix} + 2(-1)^{4+3} \begin{vmatrix} 1 & 0 & 1 \\ 1 & 0 & -1 \\ 1 & 2 & 1 \end{vmatrix}$$

$$= -1 \{ 2(2) + 1(-2) \} - 2 \{ 1(1+2) + 1(-2) \}$$

$$= -6 - 8 = -14$$

Note :-

\* A matrix is said to be NON SINGULAR when

$$\text{DET}(A) \neq 0$$

and is said to be SINGULAR when

$$\text{DET}(A) = 0$$

\*\*  $\text{Det}(A \cdot B) = (\text{Det } A)(\text{Det } B)$

\*\*  $\text{Det}(A+B)$  is not necessarily  $(\text{Det } A) + (\text{Det } B)$

\*\* If any two rows are same or constant multiples (columns) then Determinant of that Matrix is zero.

\*\* If ~~one~~ <sup>SUM</sup> of the elements in every row or every column is zero then the determinant of such matrix is zero.

for eg.

$$\begin{bmatrix} 1 & 2 & -3 \\ 0 & 2 & -2 \\ 1 & 1 & -2 \end{bmatrix} \left[ \begin{array}{l} \leftarrow \\ \leftarrow \\ \leftarrow \end{array} \right. \text{Sum of Rows zero.} \\ \text{(Sum of each row is zero).}$$

### \* ADJOINT OF SQUARE MATRIX :

\* It is the Transpose of Cofactor Matrix ie

$$\text{if } A = \begin{bmatrix} a_{11} & a_{12} & a_{13} \\ a_{21} & a_{22} & a_{23} \\ a_{31} & a_{32} & a_{33} \end{bmatrix}$$

then the cofactor of  $a_{ij} = A_{ij}$

$$\text{then } \text{Adj } A = \begin{bmatrix} A_{11} & A_{21} & A_{31} \\ A_{12} & A_{22} & A_{32} \\ A_{13} & A_{23} & A_{33} \end{bmatrix}$$

NOTE!:

\*\*  $A(\text{adj } A) = (\det A) I$   $I \rightarrow$  Identity matrix.

\*\*  $\det(\text{adj } A) = (\det A)^{n-1}$  ;  $n =$  order of matrix

\*\*  $\text{Adj}(\text{adj } A) = (\det A)^{n-2} A$

### \* INVERSE OF SQUARE MATRIX :

\* A matrix B is said to be inverse of a non singular matrix A if

\*\*  $AB = BA = I$

\* To find  $A^{-1}$  we have

\*\*  $A^{-1} = \frac{\text{Adj } A}{\det A}$

\* For Matrix A;

$$A = \begin{bmatrix} a & b \\ c & d \end{bmatrix}$$

\*\*  $A^{-1} = \frac{1}{ad-bc} \begin{bmatrix} d & -b \\ -c & a \end{bmatrix}$  ;  $ad-bc \neq 0$

$$\det(A^T) = \frac{1}{(\det A)}$$

### \*ELEMENTARY TRANSFORMATION ON A MATRIX\*:

\*There are only 3 elementary transformations; they are:

✓1) Interchanging of any two rows ( $R_1 \leftrightarrow R_2$ )

✓2) Multiplication of a row by a constant ( $R_2 \rightarrow 3R_2$ )

✓3) Addition of 1 row to the corresponding elements of some other row ( $R_2 \rightarrow R_2 + R_1$ ).

Note:.

\*  $R_2 \rightarrow R_2 + 3$  } Not elementary x'mation.  
 \*  $R_2 \rightarrow R_2 \times R_1$  }

### \*Inverse of Matrix (using elementary x'mation)

#### \*GAUSS JORDAN METHOD\*:

Q1) Find the Inverse of

$$A = \begin{bmatrix} 1 & 3 & 3 \\ 1 & 4 & 3 \\ 1 & 3 & 4 \end{bmatrix}$$

Use this element to make all the elements below/above this as zero.

Soln:

$$\left[ \begin{array}{ccc|ccc} 1 & 3 & 3 & 1 & 0 & 0 \\ 1 & 4 & 3 & 0 & 1 & 0 \\ 1 & 3 & 4 & 0 & 0 & 1 \end{array} \right]$$

$$(R_2 \rightarrow R_2 - R_1); (R_3 \rightarrow R_3 - R_1)$$

$$\left[ \begin{array}{ccc|ccc} 1 & 3 & 3 & 1 & 0 & 0 \\ 0 & 1 & 0 & -1 & 1 & 0 \\ 0 & 0 & 1 & -1 & 0 & 1 \end{array} \right]$$

$$(R_1 \rightarrow R_1 - 3R_2)$$

$$\left[ \begin{array}{ccc|ccc} 1 & 0 & 3 & 4 & -3 & 0 \\ 0 & 1 & 0 & -1 & 1 & 0 \\ 0 & 0 & 1 & -1 & 0 & 1 \end{array} \right]$$

$$R_1 \rightarrow R_1 - 3R_3$$

$$\left[ \begin{array}{ccc|ccc} 1 & 0 & 0 & 7 & -3 & -3 \\ 0 & 1 & 0 & -1 & 1 & 0 \\ 0 & 0 & 1 & -1 & 0 & 1 \end{array} \right]$$

Hence,

$$A^{-1} = \begin{bmatrix} 7 & -3 & -3 \\ -1 & 1 & 0 \\ -1 & 0 & 1 \end{bmatrix}$$



(Q2) Find the inverse of  $A = \begin{bmatrix} 1 & 0 & 0 & 3 \\ 0 & 1 & 0 & -2 \\ 0 & 0 & 1 & 0 \\ 0 & 0 & 0 & 1 \end{bmatrix}$

Soln: By Gauss Jordan method:

$$\left[ \begin{array}{cccc|cccc} 1 & 0 & 0 & 3 & 1 & 0 & 0 & 0 \\ 0 & 1 & 0 & -2 & 0 & 1 & 0 & 0 \\ 0 & 0 & 1 & 0 & 0 & 0 & 1 & 0 \\ 0 & 0 & 0 & 1 & 0 & 0 & 0 & 1 \end{array} \right]$$

$(R_1 \rightarrow R_1 - 3R_4); (R_2 \rightarrow R_2 + 2R_4)$

$$\left[ \begin{array}{cccc|cccc} 1 & 0 & 0 & 0 & 1 & 0 & 0 & -3 \\ 0 & 1 & 0 & 0 & 0 & 1 & 0 & 2 \\ 0 & 0 & 1 & 0 & 0 & 0 & 1 & 0 \\ 0 & 0 & 0 & 1 & 0 & 0 & 0 & 1 \end{array} \right]$$

So,  $A^{-1} = \begin{bmatrix} 1 & 0 & 0 & -3 \\ 0 & 1 & 0 & 2 \\ 0 & 0 & 1 & 0 \\ 0 & 0 & 0 & 1 \end{bmatrix}$

\*MINOR OF A MATRIX:

let

$$A = \begin{bmatrix} a_1 & b_1 & c_1 & d_1 & e_1 \\ a_2 & b_2 & c_2 & d_2 & e_2 \\ a_3 & b_3 & c_3 & d_3 & e_3 \\ a_4 & b_4 & c_4 & d_4 & e_4 \end{bmatrix} 4 \times 5$$

\* For finding the No. of minors of given order choose no. of rows or columns from given no. of Rows or Columns.

Note:

- $(4 \times 4)$   $\checkmark$  No. of minors of order 4 is 5. ( ${}^4C_4 \times {}^5C_4 = 5$ )
- $(3 \times 3)$   $\checkmark$  No. of minors of order 3 is  ${}^4C_3 \times {}^5C_3 = 4 \times 10 = 40$  (choose any 3 rows or columns)
- $(2 \times 2)$   $\checkmark$  No. of minors of order 2 is  ${}^4C_2 \times {}^5C_2 = 6 \times 10 = 60$  (choose any 2 rows or columns).
- $(1 \times 1)$   $\checkmark$  No. of minors of order 1 is  $4 \times 5 = 20$ .

\* In general, for matrix  $A_{m \times n}$ :

i) ~~The~~ The no. of minors of order 'r' that can be generated is  $({}^m C_r \times {}^n C_r)$ .

ii) The order of greatest minor that can be obtained for this matrix is  $\min(m, n)$ .  $\begin{cases} A_{5 \times 2} \Rightarrow A_{2 \times 2} \rightarrow \text{greatest minor of } NO(A_{3 \times 3}). \\ A_{3 \times 7} \Rightarrow A_{3 \times 3} \rightarrow \text{greatest minor of } NO(A_{4 \times 4}). \end{cases}$

## RANK OF A MATRIX :

\*Exists for both square as well as Rectangular matrix.

\*A no. "r" is said to be the "RANK OF A MATRIX A" if :

- i) there exist a minor of order "r" of A which is not zero.
- ii) all minors of order more than "r" of A must be zero.

for eg.:

\*All red dotted minors A = have det = 0.

\*Green dotted minor don't then have det = 0.

$$A = \begin{bmatrix} 1 & 2 & 3 \\ 2 & 4 & 6 \\ 3 & 6 & 10 \end{bmatrix}$$

$$\det A = 0$$

and  $\det \begin{bmatrix} 4 & 6 \\ 6 & 10 \end{bmatrix} \neq 0 \Rightarrow 40 - 36 = 4$

\*Note: For given 3x3 matrix, the Minor of 3rd order is the given matrix itself. Also the det. of given minor is zero Hence, also no. other minor of order 4x4 is available Hence the matrix A cannot have P(A)=3. We need to search for 2x2 minor and check for availability of such minor whose det ≠ 0.

Hence, there exist a minor of order 2x2 whose det is not zero. Hence

$$\text{Rank} = 2$$

$$P(A) = 2$$

← Rank of Matrix can also be defined as the order of Largest non zero minor of the matrix (Here 2x2 minor).

Note:

\*To find the Rank of the matrix we can use ELEMENTARY OPERATIONS.

\*By converting, the given matrix into its "ECHELON FORM"; the no. of NON ZERO ROWS in the "ECHELON FORM IN THE MATRIX" represents the rank of the matrix.

Note: Calculation of Rank through Minor calculation is very time taking. Hence we use Rank calculation through "ECHELON FORM".

\*ECHELON FORM:

\*By applying elementary transformations we can convert a given matrix into a form in which :

i) All zero rows must be present below non zero rows.

ii) In the non zero rows; the no. of zeroes before the 1st non zero no. to the next row must increase.

\*Such a form is called "ECHELON FORM OF GIVEN MATRIX".

Q3) Find the Rank of :

$$A = \begin{bmatrix} -2 & -1 & -3 & -1 \\ 1 & 2 & 3 & -1 \\ 1 & 0 & 1 & 1 \\ 0 & 1 & 1 & -1 \end{bmatrix}$$

\*Note: Going through MINOR Calculations to obtain RANK OF MATRIX is time taking. Hence ECHELON FORM FORMATION is used to calculate the Rank of A MATRIX

$$P(A) = \text{RANK OF MATRIX A}$$

$$A = \begin{bmatrix} -2 & -1 & 3 & -1 \\ 1 & 2 & 3 & -1 \\ 1 & 0 & 1 & 1 \\ 0 & 1 & 1 & -1 \end{bmatrix}$$

$$R_2 \rightarrow 2R_2 + R_1$$

$$R_3 \rightarrow 2R_3 + R_1$$

\* NO Zeros before (-)

\* 1 Zero before 3.

Hence no. of zero increased from going from 1st row to 2nd row.

$$\begin{bmatrix} -2 & -1 & -3 & -1 \\ 0 & 3 & 3 & -3 \\ 0 & -1 & -1 & 1 \\ 0 & 1 & 1 & -1 \end{bmatrix}$$

\* 1 Zero before (-)

hence no increase in no. of zero from 2nd to 3rd row.

Hence not in ECHELON FORM.

$$R_3 \rightarrow 3R_3 + R_2$$

$$R_4 \rightarrow 3R_4 - R_2$$

$$\begin{bmatrix} -2 & -1 & -3 & -1 \\ 0 & 3 & 3 & -3 \\ 0 & 0 & 0 & 0 \\ 0 & 0 & 0 & 0 \end{bmatrix}$$

All zero Row present below Non zero Row.

$$\boxed{\rho(A) = 2}$$

Note: (Assumption) ↓

$$\begin{bmatrix} -2 & -1 & -3 & -1 \\ 0 & 3 & 3 & -3 \\ 0 & 0 & 0 & 5 \\ 0 & 0 & 0 & 0 \end{bmatrix}$$

matrix in Echelon form only.

$$\boxed{\rho(A) = 3}$$

Q4) Find the Rank of

$$A = \begin{bmatrix} 2 & 3 & 4 & 5 & 6 \\ 3 & 4 & 5 & 6 & 7 \\ 4 & 5 & 6 & 7 & 8 \\ 5 & 6 & 7 & 8 & 9 \end{bmatrix}$$

Soln:

$$A = \begin{bmatrix} 2 & 3 & 4 & 5 & 6 \\ 3 & 4 & 5 & 6 & 7 \\ 4 & 5 & 6 & 7 & 8 \\ 5 & 6 & 7 & 8 & 9 \end{bmatrix}$$

$$R_2 \rightarrow 2R_2 - 3R_1$$

$$R_3 \rightarrow R_3 - 2R_1$$

$$R_4 \rightarrow 2R_4 - 5R_1$$


$$A = \begin{bmatrix} 2 & 3 & 4 & 5 & 6 \\ 0 & -1 & -2 & -3 & -4 \\ 0 & -1 & -2 & -3 & -4 \\ 0 & -3 & -6 & -9 & -12 \end{bmatrix}$$

$$R_3 \rightarrow R_3 - R_2$$

$$R_4 \rightarrow R_4 - 3R_2$$

$$A = \begin{bmatrix} 2 & 3 & 4 & 5 & 6 \\ 0 & -1 & -2 & -3 & -4 \\ 0 & 0 & 0 & 0 & 0 \\ 0 & 0 & 0 & 0 & 0 \end{bmatrix}$$

$$\boxed{\rho(A) = 2}$$

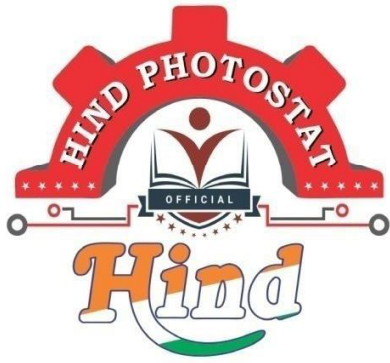

# HindPhotostat



## Hind Photostat & Book Store

Best Quality Classroom Topper Hand Written Notes to Crack GATE, IES, PSU's & Other Government Competitive/ Entrance Exams

### MADE EASY GATE/PSU GENERAL ENGLISH BY-SAPANA MAIM

- Theory
- Explanation
- Derivation
- Example
- Shortcuts
- Previous Years Question With Solution

Visit us:-[www.hindphotostat.com](http://www.hindphotostat.com)

Courier Facility All Over India  
(DTDC & INDIA POST)  
Mob-9311989030



# HindPhotostat



**MADE EASY , IES MASTER , ACE ACADEMY , KREATRYX**

**ESE , GATE, PSU BEST QUALITY TOPPER HAND WRITTEN NOTES  
MINIMUM PRICE AVAILABLE @ OUR WEBSITE**

- |                                |                           |
|--------------------------------|---------------------------|
| 1. ELECTRONICS ENGINEERING     | 2. ELECTRICAL ENGINEERING |
| 3. MECHANICAL ENGINEERING      | 4. CIVIL ENGINEERING      |
| 5. INSTRUMENTATION ENGINEERING | 6. COMPUTER SCIENCE       |

**IES , GATE , PSU TEST SERIES AVAILABLE @ OUR WEBSITE**

- ❖ IES –PRELIMS & MAINS
- ❖ GATE

➤ **NOTE;- ALL ENGINEERING BRANCHS**

➤ **ALL PSUs PREVIOUS YEAR QUESTION PAPER @ OUR WEBSITE**

## **PUBLICATIONS BOOKS -**

**MADE EASY , IES MASTER , ACE ACADEMY , KREATRYX , GATE ACADEMY , ARIHANT , GK**

**RAKESH YADAV , KD CAMPUS , FOUNDATION , MC –GRAW HILL (TMH) , PEARSON...OTHERS**

**HEAVY DISCOUNTS BOOKS AVAILABLE @ OUR WEBSITE**

<b>F230, Lado Sarai New Delhi-110030 Phone: 9311 989 030</b>	<b>Shop No: 46 100 Futa M.G. Rd Near Made Easy Ghitorni, New Delhi-30 Phone:9711475393</b>	<b>F518 Near Kali Maa Mandir Lado Sarai New Delhi-110030 Phone: 9560 163 471</b>	<b>Shop No.7/8 Saidulajab Market Neb Sarai More, Saket, New Delhi-30</b>
--	--	--	--

**Website: [www.hindPhotostat.com](http://www.hindPhotostat.com)**

**Contact Us: 9311 989 030**

**Courier Facility All Over India**

**(DTDC & INDIA POST)**

# ENGLISH

Sapna

gate

Critical Reasoning  
Inferential Reasoning  
Logical deduction


Ludhani.Sapna@gmail.com  
9911629948

Parajumbles

Reading Comprehension


gate

Vocabulary

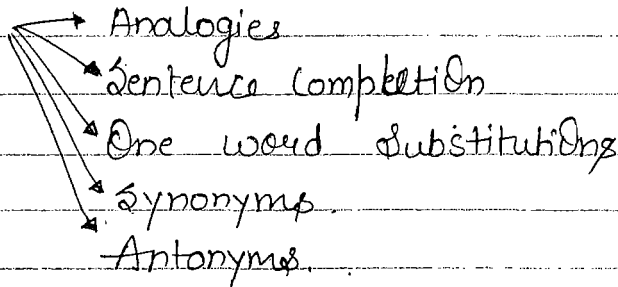

gate

Grammar

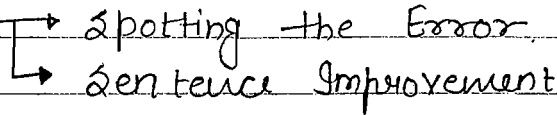

## Analogy { Relationship }

### Gladiator

Q. Gladiator : Arena  
(warrior) (Platform)

a) Dance : Stage

b) Commuter : train

c) Teacher : Classroom

d) ✓ Lawyer : Courtroom

a) performer

b) fighter

c) opponent

d) End result  $\begin{cases} \text{win} \\ \text{lose} \end{cases}$   
(Traveler - Commutator)

Q. Frequency [ Antonym ? ]

a) Periodicity

✓ b) Rarity

c) Gradualness

d) persistence (continuity) Perseverance

↳ continuous determination

Q. Children : Pediatrician  
(child specialist)

a) Adult : Orthopaedist (Bone specialist)

✓ b) females : Gynaecologist (female specialist)

c) Kidney : Nephrologist (deal with kidney & urine)

d) Skin : Dermatologist (deal with skin)

Q. Nocturnal : Bat  
(active at night)

✓ a) Amphibian : frog  $\rightarrow$  Stay land & water

b) Sly : cat  $\rightarrow$  cunning (deceitful)

c) Carnivorous : cow  $\rightarrow$  eating flesh

d) Aquatic : liz.  $\rightarrow$  Lizard.

(live in water).

5. Xenophobia : foreigners.  
Fear of foreigners & strangers

least  
(~~most~~ similar)

a) Bibliophobia : Books

b) Anglophobia : English

c) Hemophobia : Blood

vd) Claustrophobia : Height (fear of height is Acrophobia)  
(fear of confined or closed spaces)  
or Constricted place.

Phobia

↓  
fear

Mania

↓  
obsession,  
(craze)

Vibrant (full of happiness, energy)

~~Charming~~  
~~depressed~~

Clumsy

- ↓
- dirty, unpleasant
  - unskilled

Synonyms

Antonyms

◦ Lively

◦ Vivacious

◦ Vigorous

◦ Enthusiastic

◦ Energetic

◦ Passionate

◦ Zealous

◦ Zestful

◦ Exuberant

◦ Active

◦ Lazy

◦ Lethargic

◦ Sluggish

↳ Slow & Inactive

◦ Dormant

◦ Indolent

◦ Dizzy

◦ Drowsy

↳ Sleepy

◦ Lackadaisical

Fatigue

↳ tiredness