

HindPhotostat



Hind Photostat & Book Store


Best Quality Classroom Topper Hand Written Notes to Crack GATE, IES, PSU's & Other Government Competitive/ Entrance Exams

MADE EASY ELECTRICAL ENGINEERING Analog Electronics By.A.Rajkumar Sir

- Theory
- Explanation
- Derivation
- Example
- Shortcuts
- Previous Years Question With Solution

Visit us:-www.hindphotostat.com

 Courier Facility All Over India
(DTDC & INDIA POST)
Mob-9311989030



HindPhotostat



EASY, ,ACE, KREATRYX

ESE, GATE, BEST Y KW, / EE
D/E/D DW @

1. KE E /E /
2. E /E /
- D, E /E /
4. / E /E /
- /E DE /KE E /E /
6. KD /

,GATE, TEST @

❖ -W / & D /

❖ GATE

➤ E - ALL E /E / E

➤ ALL sW / YEAR Y /KEW @

W / /K K -

EASY, ,ACE, KREATRYX, GATE /, ,GK

, YADAV, KD D, &K E /KE, -GRAW, D, W KE...K s

/ K @

<p>F230, Lado Sarai New Delhi-110030 Phone: 9311 989 030</p>	<p>Shop No: 46 100 Futa M.G. Rd Near Made Easy Ghitorni, New Delhi-30 Phone:9711475393</p>	<p>F518 Near Kali Maa Mandir Lado Sarai New Delhi-110030 Phone: 9560 163 471</p>	<p>Shop No.7/8 Saidulajab Market Neb Sarai More, Saket, New Delhi-30</p>
--	--	--	--

Website: www.hindPhotostat.com

Contact Us: 9311 989 030


Courier Facility All Over India

(DTDC & INDIA POST)

-: Analog Electronics :-

-: Chapter-1 Diode models :-

Ideal model :-

 

Indication:

A → Anode (+)

K → Cathode (-)

J → Junction

Arrow → unidirectional device

↓
[impedance are different]

conditions for ideal model of diode :-

$V_A - V_K > 0$ then $D = ON$ $\xrightarrow{S.C.}$ $V_D = 0, I_D > 0$

$V_A - V_K < 0$ then $D = OFF$ $\xrightarrow{O.C.}$ $V_D = V_B, I_D = 0$

$V_A - V_K = 0$ then D just ON $\xrightarrow{S.C.}$ $V_D = 0, I_D = 0$

$V_B =$ Battery voltage

Testing method to check diode status :-

a. Short circuit Test (SC Test) [Failure when KVL violates in the ckt]

b. open circuit Test (OC Test) [Failure when KCL violates in the ckt]

Procedure to check diode status using SC Test :-

Rule 1:- Assume all the diodes to be S.C.


Rule 2:- Indicate the current direction of each diode from A to K.

Rule 3:- check & calculate I_D of each diode by using KVL or KCL


Status: $I_D > 0$; $D = ON$

$I_D < 0$; $D = OFF$

 Example 1: Check the status of diode D in the given ckt



Solution:-

 


$$I_D = \frac{10 - (-10)}{1k}$$


$$= 20\text{mA} > 0$$

↳ D ON

 Example 2: Check the status of D_1 & D_2 in the given ckt



Solution:-

 

$$I_{D1} = \frac{10 - (0)}{10k} = 1\text{mA} > 0$$

↳ D_1 ON

$$I_x = \frac{0 - (-10)}{5k} = 2\text{mA}$$

KCL @ node 'a'


$$I_{D1} + I_{D2} = I_x$$

$$I_{D2} = 2\text{mA} - 1\text{mA}$$





$$I_{D2} = 1\text{mA} > 0$$

↳ D_2 ON

 Q.N:- what are the states of the three ideal diodes of the circuit



Solution:-

    


$$I_x = \frac{10-0}{1} = 10A \quad I_{D2} = \frac{0-5}{1} = -5A < 0 \rightarrow D_2 \text{ is OFF}$$

KCL at node a $I_x = I_{D1} + I_{D2}$

$$I_{D1} = 10 - (-5)$$

$$I_{D1} = 15A > 0 \rightarrow D_1 \text{ is ON}$$

Conclusion:-

 

$$V_A = 5V, V_B = 3V, V_C = 1V$$

Failure of KVL in the short circuit test.
It violates KVL

$$V_{out} = 5V$$

Procedure to check diode status using open circuit test :-



Rule 1: Assume all the diodes to be OFF

Rule 2: Indicate V_A & V_K of each diodes

Rule 3: Calculate $V_A - V_K$ difference of each diodes

Status: $V_A - V_K > 0 \quad D = ON$

$V_A - V_K < 0 \quad D = OFF$

  


$$V_{A1} - V_{K1} = 5 - 0 = 5 > 0$$

$$V_{A2} - V_{K2} = 1 - 0 = 1 > 0$$

Two diodes ON simultaneously
Then recheck condition

 Select D_1 ON first because it is more FB




$$V_{A2} - V_{K2} = 1 - 5 = -4 < 0$$

$\rightarrow D_2$ become OFF

Highest voltage will be ON first.

V-I characteristic of ideal diode :-

 

Indication: R_f = forward diode resistance

R_r = Reverse diode resistance

In forward bias : slope = $\frac{1}{R_f} = \infty \Rightarrow R_f = 0$ ideal diode

In reverse bias : slope = $\frac{1}{R_r} = 0 \Rightarrow R_r = \infty$ ideal diode

CVD model :-

CVD means constant voltage drop model

Practical diode will have cut in voltage V_γ .


V_γ (si) \rightarrow 0.5V to 0.7V

$V_D = V_\gamma$ then $V_D = V_{D,ON}$


condition for CVD model :- $V_A - V_K > V_{D,ON}$ then D ON

$V_A - V_K < V_{D,ON}$ then D = OFF


$V_A - V_K = V_{D,ON}$ then D just ON.

 

 EX 1 :- Check the status of diode and calculate V_o and I using Ideal & CVD model.



Solution :- Ideal condition :- [sc Test]

 


$$I = \frac{10 - 0}{1K}$$

$$= 10mA > 0 \text{ then } D \text{ ON}$$

$$V = 0, I = 10mA$$


CVD condition :- [sc Test]

 


$$I = \frac{10 - 0.7}{1K} = 9.3mA > 0 \text{ then } D \text{ ON}$$

$$V_o = 0.7V \text{olt}, I = 9.3mA$$

 Q.N:14 The voltage at V_1 & V_2 of the arrangement shown in figure will be respectively $V_1 = 0.6$ volt



Solution:-

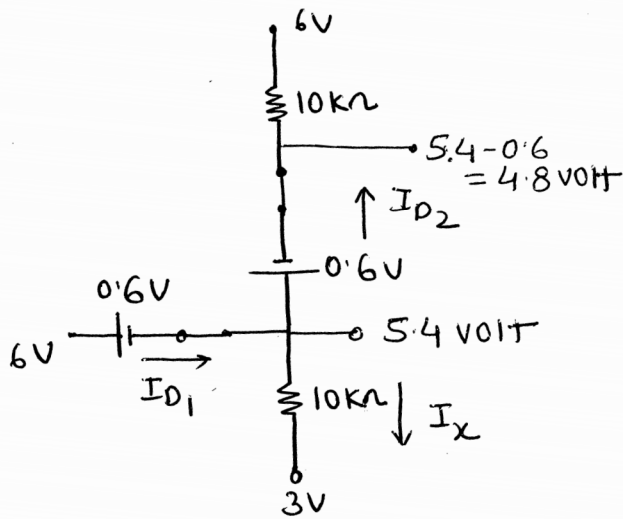

$$I_X = \frac{5.4 - 3}{10K} = 0.24 \text{ mA}$$


$$I_{D_2} = \frac{4.8 - 6}{10K} = -0.12 \text{ mA} < 0$$

↳ D_2 is in OFF condition


KCL @ 5.4V

$$I_{D_1} = I_{D_2} + I_X = -0.12 + 0.24 = 0.12 \text{ mA} > 0$$

↳ D_1 is in ON condition

 

V-I characteristic of CVD model :-

 

In forward bias slope = $\frac{1}{R_f} = \infty$ $R_f = 0$

In reverse bias slope = $\frac{1}{R_{re}} = 0$ $R_{re} = \infty$

PWL model :-


PWL means piece wise linear model

In PWL model : V_{D0} , R_f will be given.

V_{D0} : cut in voltage (V_{D0N})

R_f : forward resistance of diode

V-I characteristic of PWL model :-

 


In forward bias slope = $\frac{1}{R_f} = \frac{I_D - 0}{V_D - V_{D0}}$

$$R_f = \frac{V_D - V_{D0}}{I_D}$$

conditions in PWL model :-

$V_A - V_K > V_{D0}$ D = ON

 

$V_A - V_K < V_{D0}$ D = OFF

