


Diode Circuit - Part I

- ④ Clamped
- ⑤ Small signal model of diode.
- Robert L. Boylestad } Notes + R.K. Kanodia
- Millman Halikias }
- Sedra Smith }


Diode with respect to DC source.

- ② Clipped Circuit
- ③ DC Power supply design → Rectifier + filter + Voltage Regulator

Diode:



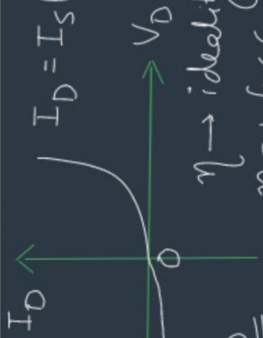$I_D = I_S (e^{\frac{V_D}{\eta V_T}} - 1)$




$\eta \rightarrow$ ideality factor
 $\eta = 1$ for Ge
 $\eta = 2$ for Si } Generally


$V_T \rightarrow$ Thermal voltage
 $V_T = T / 11,600$ T → Kelvin
 $I_S \rightarrow$ Reverse saturation current.

Diode Model:

① ideal diode:




Diode application → As a switch




$V_D < 0 : I_D = 0$
 $V_D > 0 : I_D \neq 0$

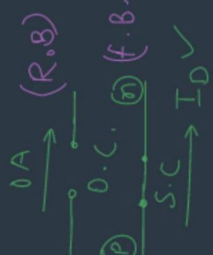$\text{slope} = \infty = \frac{\Delta I_D}{\Delta V_D}$
 $R_f = 0 \Omega$




②

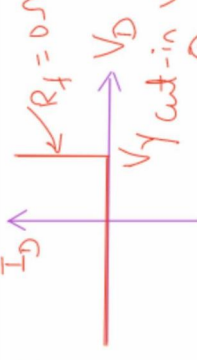


$R_f = 0 \Omega$
 $V_D < V_f : I_D = 0$
 $V_D > V_f : I_D \neq 0$


V_f cut-in voltage



③

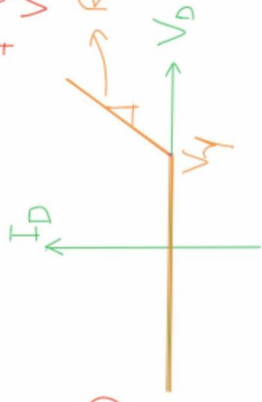

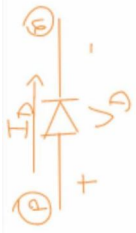
$R_p = \frac{1}{\text{slope}} = \frac{1}{(\Delta I_D / \Delta V_D)}$




$$V_D < V_Y : I_D = 0 \quad \text{①} \quad \text{O.C.} \quad \text{②} \quad \text{(off)}$$

$$V_D > V_Y : I_D \neq 0 \quad \text{③} \quad \text{0A} \quad \text{④} \quad \text{(ON)}$$

procedure: (general)

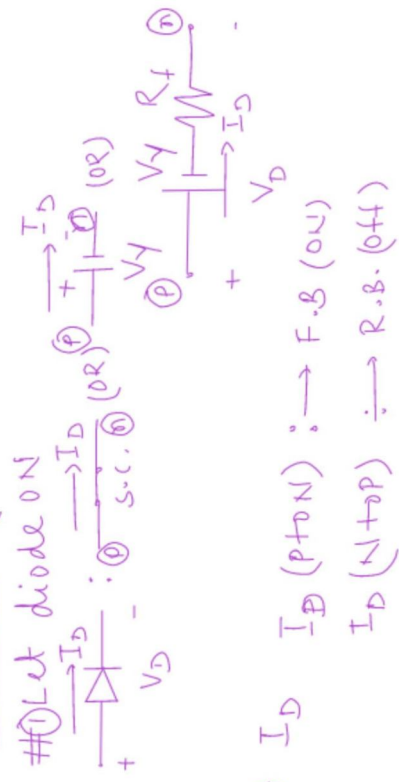

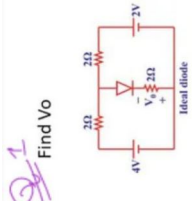② find I_D I_D (P to N) \rightarrow F.B. (ON)
 I_D (N to P) \rightarrow R.B. (OFF)




(OR) 2nd way:


① Let diode off

$$\frac{+}{-} \frac{I_D}{V_D} = \frac{\text{①} + V_D - \text{②}}{\text{O.C.}} \rightarrow 0A$$

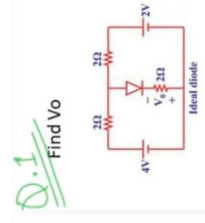② If $V_D > 0$ (OR) $V_D > V_Y$ (OR) $V_D > V_Y$
 : Diode ON ✓
 if $V_D < 0$ (OR) $V_D < V_Y$ (OR) $V_D < V_Y$
 : Diode off



\rightarrow Let diode is (off):

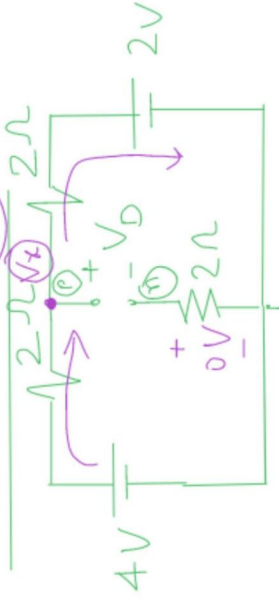


$$\frac{4 - V_x}{2} = 0 + \frac{V_x - 2}{2} \Rightarrow 6 = 2V_x$$

$$\boxed{V_x = 3V} = V_D$$

$V_D > 0$: (Diode ON)

owl Assumption is wrong.

Diode ON!

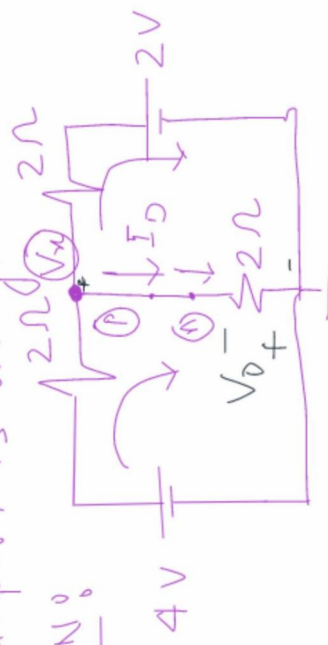

$$4 - V_x = \frac{V_x - 0}{2} + \frac{V_x - 2}{2} \Rightarrow 3V_x = 6$$

$$\boxed{V_x = 2V}$$

$$I_D = \frac{V_x - 0}{2} = 1A \text{ (0.10A)}$$

Really diode is ON.

$$V_0 = -V_x = -2V \text{ Ans.}$$


Question

Rahul Gupta
sir, V₀ and threshold voltage same hai kya?


yes

Q.2

D1, D2: Ideal. Find V₀

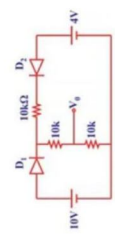

Let D1 ON, D2 OFF :-

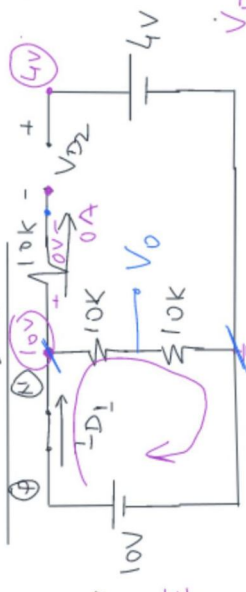

$$V_{D2} = 4 - 10$$

$$V_{D2} = -6V$$

$$D2 \rightarrow \text{OFF}$$


$$I_{D1} = \frac{10}{2 \times 10k} = 0.5 \text{ mA} > 0 \text{ : } (D1 \text{ ON})$$

owl Assumption is correct.


$$V_0 = \frac{10 \times 10}{10 + 10} = 5V \text{ Ans.}$$

$$(0.5 \text{ mA}) \quad V_0 \approx I_{D1} \times 10k = 5V$$

Q.3

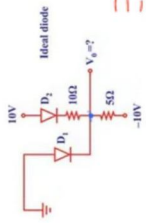

Let D_1 ON, D_2 ON :

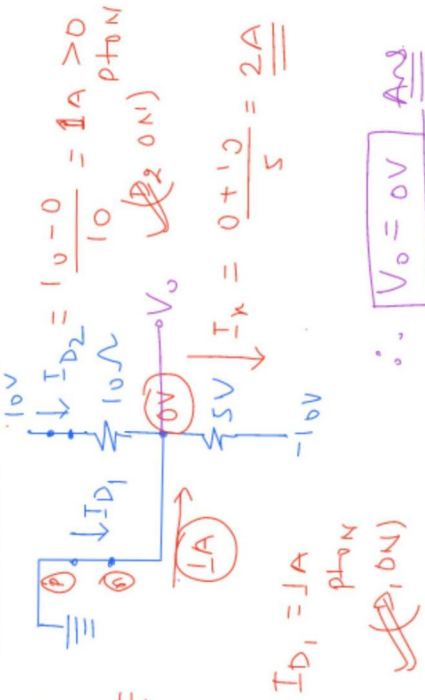


$$I_{D2} = \frac{10 - 0}{100} = 1A > 0$$

$$I_{D1} = \frac{0 - (-10)}{50} = 2A$$


$$I_{D1} = 1A$$

$$V_0 = 0V$$

Q.5V

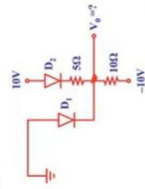

Let D_1 OFF & D_2 ON \Rightarrow

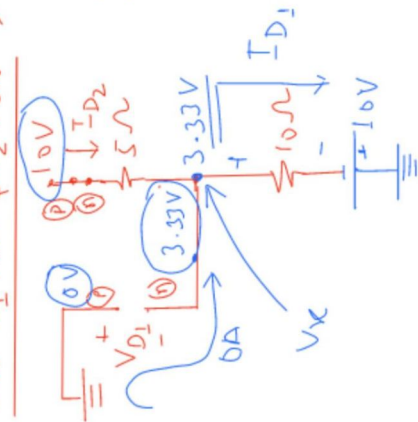


$$I_{D2} = \frac{10 + 10}{50 + 100} = \frac{20}{150} = \frac{4}{3}A > 0$$

$$V_x = -10 + 10(I_{D1}) = -10 + 10 \times \frac{4}{3} = -\frac{30 + 40}{3} = -\frac{70}{3} = -23.33V$$

Q.4 $I_{D1}, I_{D2} = ?$ Let D_1 OFF, D_2 ON

Diode ideal.

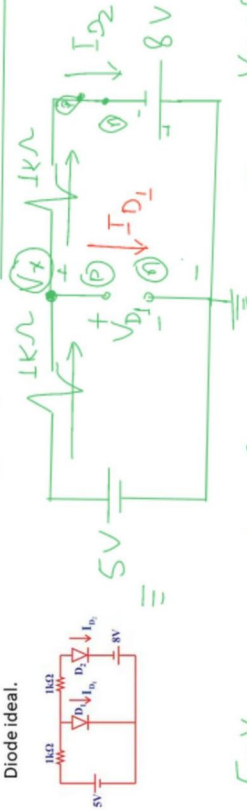

$$\frac{5 - V_x}{1k} = 0 + \frac{V_x + 8}{1k}$$

$$2V_x = -3$$

$$V_x = -1.5V = V_{D1} < 0$$

($D_1 \rightarrow$ OFF)

$$I_{D2} = \frac{V_x + 8}{1k} = \frac{-1.5 + 8}{1k} = \frac{6.5}{1k}$$

$$I_{D2} = 6.5mA > 0$$



$$V_{D1} = 0 - 3.33 = -3.33V < 0$$

$$V_0 = 3.33V_{out}$$

Next class : 9 PM

Diode Circuit - Part II

Q.6

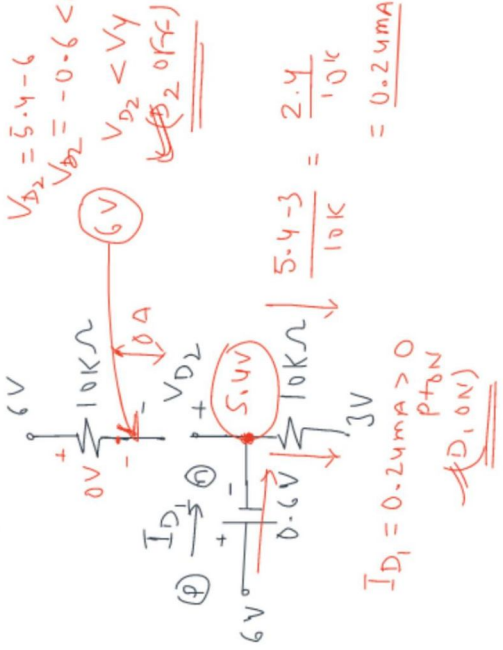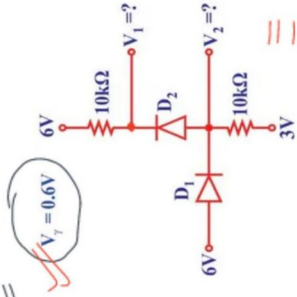


$$V_1 = 6V$$

$$V_2 = 5.4V$$

$$I_{D1} = 0.24\text{mA} > 0$$

$D_{1, ON}$

(OR)

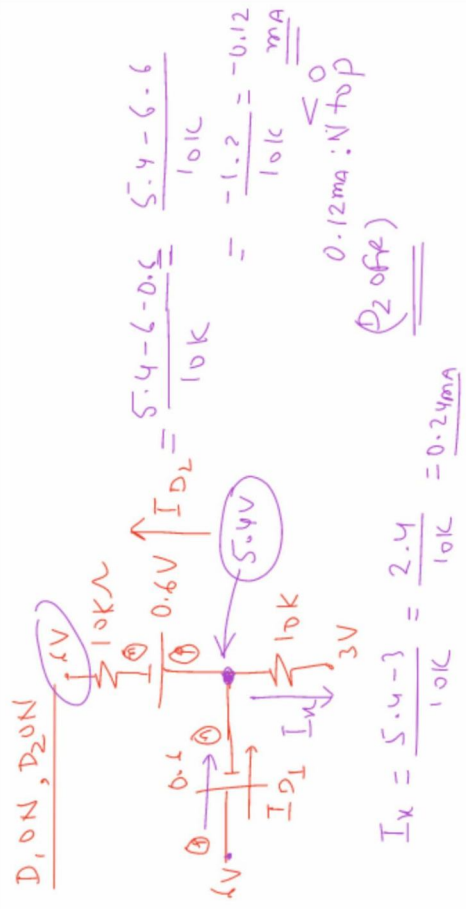


$$I_x = \frac{5.4-3}{10k} = 0.24\text{mA}$$

$$I_{D1} = I_x + I_{D2} \Rightarrow I_{D1} = 0.24 + (-0.12\text{mA}) = 0.12\text{mA} > 0$$

$D_{1, ON}$

our Assumption is wrong.
 $\rightarrow D_{1, ON}, D_{2, OFF} \rightarrow$ check & find Ans.
 $\rightarrow x \rightarrow y \rightarrow x$

Q.7

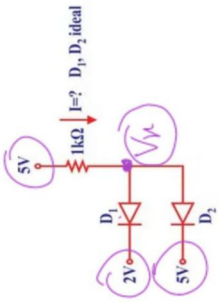


Possibility:


- ① D_{1ON}, D_{2ON} : X not possible
Violation of KVL
 - ② D_{1OFF}, D_{2OFF} : $V_x = 5V$
X not possible
 - ③ D_{1OFF}, D_{2ON} : (not possible)
if $(D_{2ON}) \rightarrow V_x = 5V \rightarrow$ it makes (D_{1ON})
- D_{1ON}, D_{2OFF} : $V_x = 2V \rightarrow D_{2OFF}$
 $I = 5 - 2 / 1k = 3mA$

$V_x \neq \min(2, 5, 5)$

Q.8

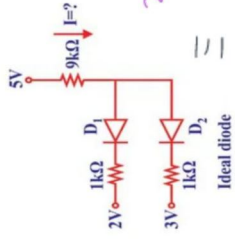

Let D_{1ON}, D_{2OFF} :

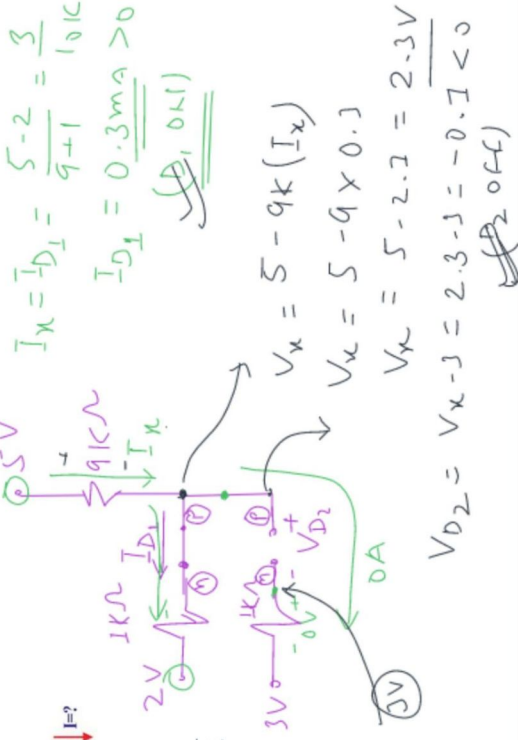

$$I_x = I_{D1} = \frac{5-2}{9+1} = \frac{3}{10k}$$


$$I_{D1} = 0.3mA > 0$$

$$V_x = 5 - 9k(I_x)$$


$$V_x = 5 - 9 \times 0.3 = 2.3V$$

$$V_{D2} = V_x - 3 = 2.3 - 3 = -0.7 < 0$$

Q.9

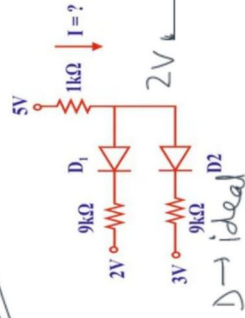

Let D_{1ON}, D_{2OFF} :

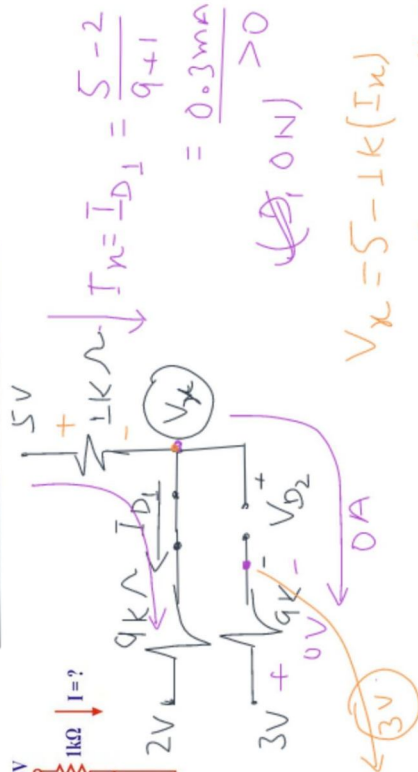


$$I_x = I_{D1} = \frac{5-2}{9+1} = \frac{3}{10k} > 0$$

$$V_x = 5 - 1k(I_x)$$

$$= 5 - 0.3 = 4.7V$$

$$V_{D2} = V_x - 3V = 4.7 - 3 = 1.7V > 0$$

$V_{D2} = 1.7V > 0$ (D_{2ON})

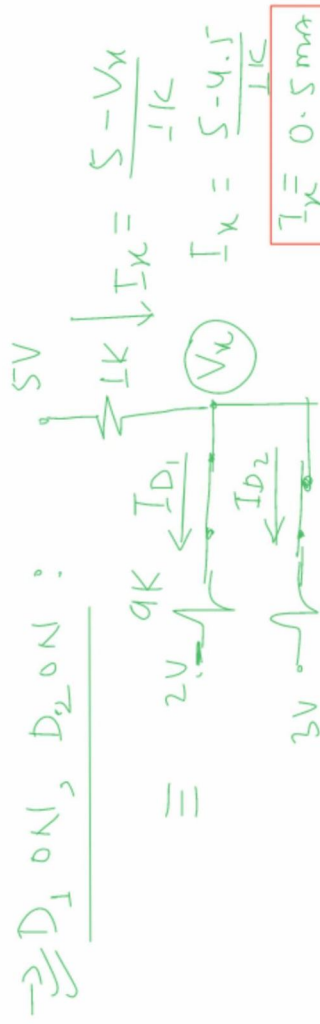

$$I_x = \frac{5 - V_x}{1k}$$

$$I_x = \frac{5 - 4.7}{1k} = 0.3mA$$

$$V_x = 4.5V$$