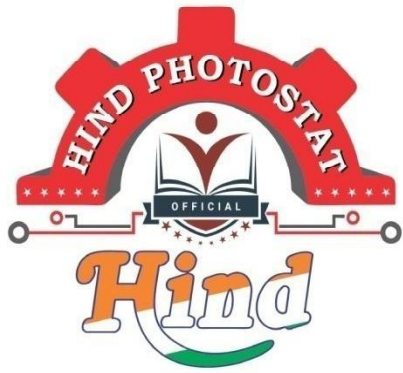




HindPhotostat



Hind Photostat & Book Store

Best Quality Classroom Topper Hand Written Notes to Crack GATE, IES, PSU's & Other Government Competitive/ Entrance Exams

MADE EASY ELECTRONICS ENGINEERING Analog Electronics By-Ifteqar Ahamad Sir

- Theory
- Explanation
- Derivation
- Example
- Shortcuts
- Previous Years Question With Solution

Visit us:-www.hindphotostat.com

**Courier Facility All Over India
(DTDC & INDIA POST)
Mob-9311989030**



HindPhotostat



ALL NOTES BOOKS AVAILABLE ALL STUDY MATERIAL AVAILABLE COURIERS SERVICE
AVAILABLE

MADE EASY, IES MASTER, ACE ACADEMY, KREATRYX

**ESE, GATE, PSU BEST QUALITY TOPPER HAND WRITTEN
NOTES MINIMUM PRICE AVAILABLE @ OUR WEBSITE**

- | | |
|--------------------------------|---------------------------|
| 1. ELECTRONICS ENGINEERING | 2. ELECTRICAL ENGINEERING |
| 3. MECHANICAL ENGINEERING | 4. CIVIL ENGINEERING |
| 5. INSTRUMENTATION ENGINEERING | 6. COMPUTER SCIENCE |

IES, GATE, PSU TEST SERIES AVAILABLE @ OUR WEBSITE

❖ IES –PRELIMS & MAINS

❖ GATE

➤ **NOTE;- ALL ENGINEERING BRANCHS**

➤ **ALL PSUs PREVIOUS YEAR QUESTION PAPER @ OUR WEBSITE**

PUBLICATIONS BOOKS -

MADE EASY, IES MASTER, ACE ACADEMY, KREATRYX, GATE ACADEMY, ARIHANT, GK

RAKESH YADAV, KD CAMPUS, FOUNDATION, MC –GRAW HILL (TMH), PEARSON...OTHERS

HEAVY DISCOUNTS BOOKS AVAILABLE @ OUR WEBSITE

HIND PHOTOSTAT AND BOOK CENTER F230, Lado Sarai New Delhi-110030 Phone: 9311 989 030	Shop No: 46 100 Futa M.G. Rd Near Made Easy Ghitorni, New Delhi-30 Phone:	F518 Near Kali Maa Mandir Lado Sarai New Delhi-110030 Phone:	Shop No.7/8 Saidulajab Market Neb Sarai More, Saket, New Delhi-30
--	---	--	---

9560 163 471

Website: www.hindPhotostat.com

Contact Us: 9311 989 030

24/06/25

(1) BJT Circuits $\left\{ \begin{array}{l} \text{Biasing} \\ \text{Amplifier} \end{array} \right\} 2-3 \text{ Que.}$

v.v. (2) MOSFET Circuits $\left\{ \begin{array}{l} \text{Biasing} \\ \text{Amplifier} \end{array} \right\} 3-4 \text{ Marks}$

Gate - 12 Marks

(3) Opamp } 3-4 Marks

(4) Diode Circuits } 3 Marks

(5) other topic

i) Multistage Amplifier

ii) Feedback "

iii) Differential "

iv) oscillator

1-2 Marks

Extra topic for ESE

(i) JFET Biasing & Amplifier

(ii) Power amplifier

(iii) Tuned amplifiers

only basics

iv) Timer IC (IC 555)

Analog sig

Prelims ESE : 12 to 15 Question.

Mains : 100 Marks.


Books:-

(i) Microelectronic Circuits
— Sedra & Smith

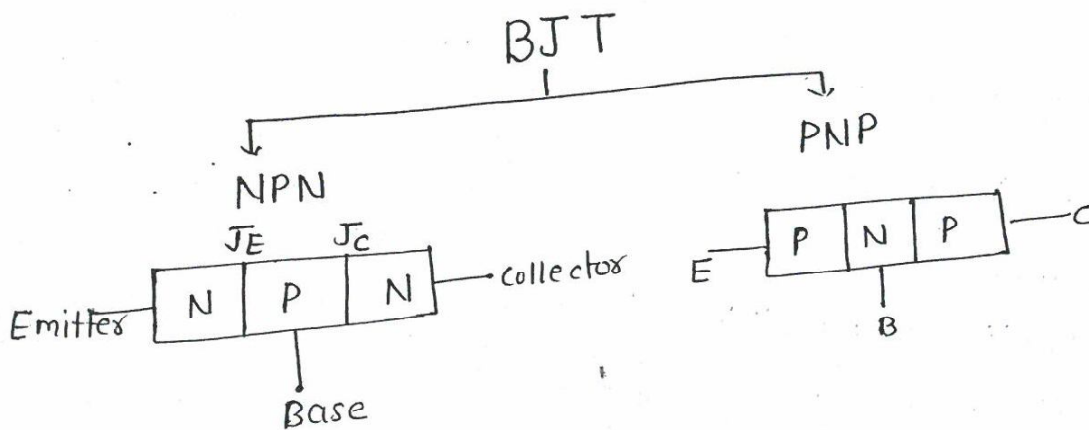(ii) Electronic Circuit
— Neamen

Bipolar Junction Transistor (BJT) - Chapter-3

BJT → Bipolar (current flow due to majority & minority charge)
 MOSFET → unipolar (current flow only due to majority charge)





J_E : Emitter - base junction
 J_C : Collector - base junction.

Mode of operation	J_E	J_C	Application
<1> Cut-off	RB	RB	off switch (very high resistance)
<2> Saturation	FB	FB	ON switch (very low resistance)
<3> Active Mode/ Forward active mode.	FB	RB	Amplifier (Excellent Transistor Action)
<4> Reverse Active/ Inverse Active.	RB	FB	BJT is not used in reverse active mode because BJT behave as attenuator (Gain < 1)

→ BJT is used digitalized (used in switch).

$$\text{Gain} = \frac{O/P}{i/P}$$

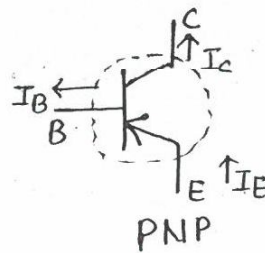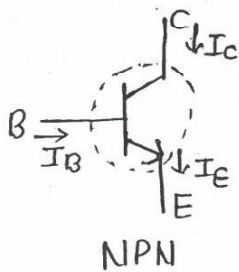I/P Transistor TTL → Reverse active mode.



KCL: $I_E = I_B + I_C$ ** $\rightarrow$ for both NPN & PNP.

$\rightarrow$ If BJT is in active region then

(i) $I_C = \alpha I_E + I_{CO}$ * $\cong \alpha I_E$

(ii) $I_C = \beta I_B + (1 + \beta) I_{CO}$ * $\cong \beta I_B$

I_{CO} : Reverse saturation current of collector junction (J_C)

α : Common base current gain

$\alpha = \beta^* \gamma$

Ideal BJT ($\alpha = 1$)

practical BJT ($\alpha < 1$)

β : Common emitter current gain

$\beta = \frac{\alpha}{1 - \alpha}$ **

$\alpha = \frac{\beta}{1 + \beta}$ **

	α	β
Ideal BJT	1	∞
practical BJT	$\cong 1$	large value.

$\rightarrow N_E \gg N_B \Rightarrow \gamma \cong 1$

$\rightarrow W_B \ll \text{Diffusion Length} \Rightarrow \beta^* \cong 1$

$\left. \begin{array}{l} \alpha \cong 1 \\ \beta: \text{large value.} \end{array} \right\}$

$\rightarrow \beta$ is a measure of amplification property of BJT.

Large $\beta \Rightarrow$ Better amplification.

Note:-

$$I_E = I_{ES} (e^{V_{BE}/V_T} - 1) \text{ for NPN}$$

$$I_E = I_{ES} (e^{V_{EB}/V_T} - 1) \text{ for PNP}$$

I_{ES} : Reverse saturation current of J_E

$$I_{ES} \cong A q n_i^2 \times \frac{D_B}{W_B} \times \frac{1}{N_B}$$

A = Area of emitter junction (J_E)

→ Current in a BJT is proportional to the area of emitter junction.

D_B = Diffusion Const. of minority carrier in base region.

W_B = Base width.



N_B = Base doping.

V_{BE} or V_{EB} : Voltage across emitter junction (J_E)


V_T : Thermal voltage $\left[V_T = \frac{T}{11600} \right]$

At $T = 300 \text{ K}$,
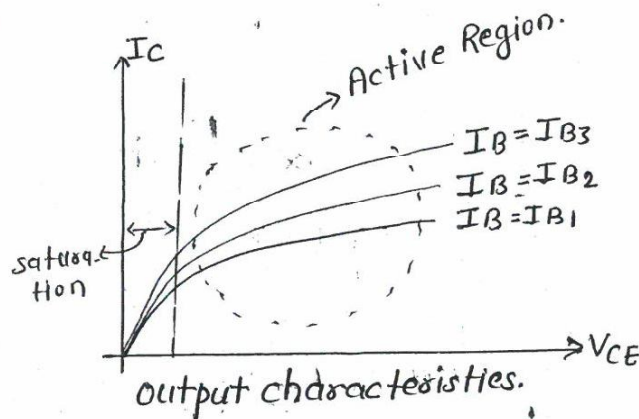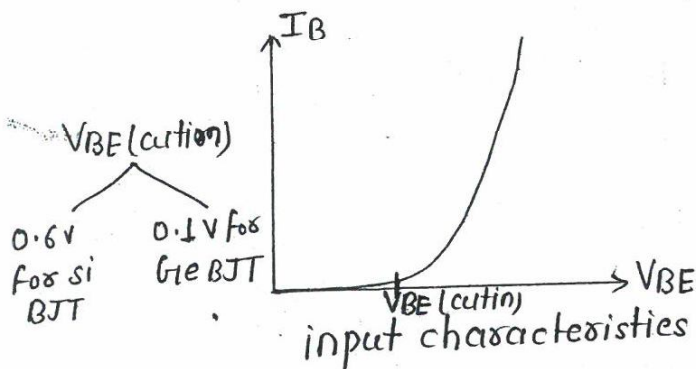
$$V_T = 25.8 \text{ mV} \cong 26 \text{ mV}$$



→ BJT behaves as a circuit:-

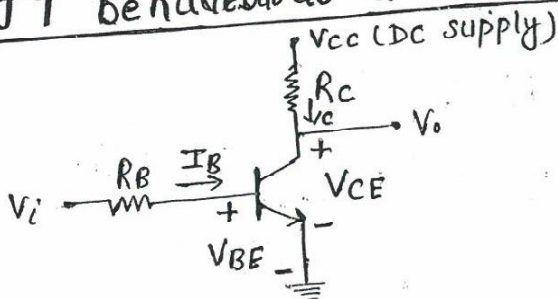

V_i : Input voltage.

Assume that V_i is varied.

V_{AB}
↓ ↓
+ -

Case (i): If $V_i < V_{BE}$ (cut in)

→ BJT remains OFF.

$$I_B = 0, I_C = 0$$

$$\Rightarrow V_{CE} = V_{CC} - I_C R_C$$

$$V_{CE} = V_{CC}$$

Case (ii): If $V_i > V_{BE}$ (cut in)

→ BJT starts conduction (allow for current is flow)

i.e. I_B & I_C will flow.

$$I_B = \frac{V_i - V_{BE}}{R_B}$$

$$I_C \cong \beta I_B$$

↓
Active region.


$$V_{CE} = V_{CC} - I_C R_C$$

If $V_i \uparrow \Rightarrow I_B \uparrow \Rightarrow I_C \uparrow \Rightarrow$ voltage drop $\uparrow = V_{CE} \downarrow$
($I_C \times R_C$)

→ In a BJT circuit I_C and V_{CE} has opposite variation i.e. if I_C increases then V_{CE} decreases and vice-versa.

[In practical BJT
 V_{CE} decreases upto
a minm value V_{CEsat} $\left\{ \begin{array}{l} 0.2V \text{ for Si} \\ 0.1V \text{ for Ge} \end{array} \right.$ **]

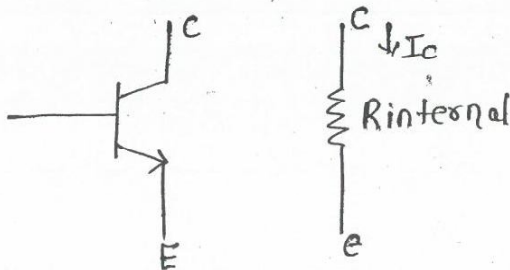→ V_{CEsat} the minimum possible voltage drop between collector & emitter this voltage drops due to internal resistance of BJT.



→ For ideal BJT V_{CE} can decrease upto zero (0) i.e. $V_{CEsat} = 0$
 → If V_{CE} will become V_{CEsat} then collector current (I_C) also const. then I_C can't increase further w/p voltage. Then BJT is said to be in saturation.

****** If BJT is in saturation then

(i) $V_{CE} = V_{CEsat}$ *

(ii) I_C remains constant at I_{Csat} .

$$I_{Csat} = \frac{V_{CC} - V_{CEsat}}{R_C} \rightarrow \text{Saturated } I_C \text{ (or) Maximum } I_C$$

(iii) I_B keeps increasing with V_i and hence $I_C = \beta I_B$ becomes invalid.

(iv) $\beta I_B > I_C$ (or) $I_C < \beta I_B$ **

(or) $I_B > \frac{I_{Csat}}{\beta}$

(v) I_E also increases with V_i becomes $I_E = I_B + I_C$

(vi) Forced β :—
 → It is the ratio of I_{Csat} and I_B when BJT is in saturation.

$$\beta_{forced} = \frac{I_{Csat}}{I_B} \rightarrow \text{It is } \beta \text{ when BJT is in a saturation.}$$

→ If $V_i \uparrow \Rightarrow I_B \uparrow \Rightarrow \beta_{forced} \downarrow$

$$\beta_{forced} < \beta_{Active}$$

(vii) Overdrive (or) Degree of saturation:—

→ It is the ratio of actual β and forced β .

$$\text{Overdrive} = \frac{\beta}{\beta_{forced}}$$


→ Overdrive is a measure of saturation level.

**

Overdrive = 1 $\Rightarrow$ onset of saturation.

overdrive > 1 $\Rightarrow$ weak saturation. [eg:- 1.5, 2, 2.1 etc]


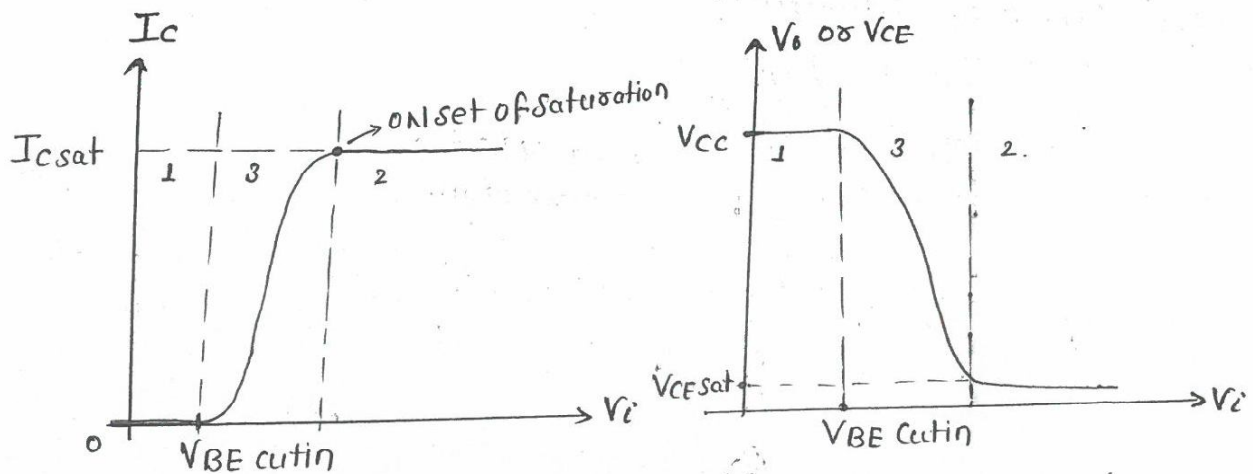
overdrive >> 1 $\Rightarrow$ strong saturation [Ex:- overdrive = 10, 11, 12 etc]



Region-(i) cutoff region [$I_c = 0$, $V_{CE} = V_{CC}$] $\rightarrow$ open ckt (or) OFF switch

Region-(ii) Saturation region [I_c remains const. w.r.t V_i]

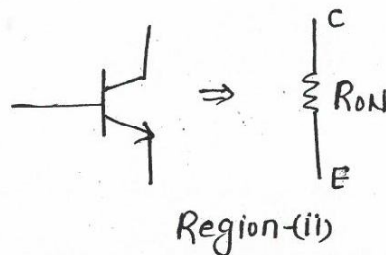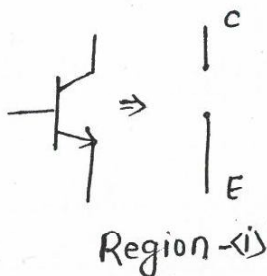$I_c = I_{c \text{ sat}}$
 $V_{CE} = V_{CE \text{ sat}}$ } ON switch



R_{ON} : ON resistance of BJT

**

$$R_{ON} = \frac{V_{CE \text{ sat}}}{I_{c \text{ sat}}}$$

R_{ON} : A few Ω

→ A practical BJT can't act as fully ON switch due to internal resistance.

→ For ideal BJT, $R_{ON} = 0$

Region-(iii) Active region [I_c and V_{CE} vary with V_i]

** A BJT is said to be active if ' I_c ' varies according to input Voltage (V_i)

→ When BJT is used as small signal amplifier. BJT is operated in active region. so that small variation in V_i can cause proportional change ' I_c '

→ The relation $I_c \cong \beta I_B$ is valid for active region upto onset of saturation.

→ At onset of saturation,

$$I_{csat} = \beta I_B$$

$$I_B = \frac{I_{csat}}{\beta} \rightarrow I_B \text{ at onset of saturation.}^{**}$$

$$I_{Bmin} = \frac{I_{csat}}{\beta} \rightarrow \text{It is min base current required to operate BJT in saturation.}^{**}$$

$$\begin{aligned} I_B \geq I_{Bmin} &\Rightarrow \text{BJT is in saturation.} \\ I_B < I_{Bmin} &\Rightarrow \text{BJT is in active region.} \end{aligned}^{**}$$

Procedure to find operating region of BJT:-

Method-I

① Assume BJT in saturation.

$$V_{CE} = V_{CE sat} < \begin{cases} 0.2V & \text{for si BJT} \\ 0.1V & \text{for Ge BJT} \end{cases}$$

V_{BE} = use given value.

② Calculate I_B and I_c independently.

③ Calculate I_{Bmin}

$$I_{Bmin} = \frac{I_{csat}}{\beta}^{**}$$

④ Compare I_B and I_{Bmin}

$I_B \geq I_{Bmin} \Rightarrow$ BJT is in saturation.

$I_B < I_{Bmin} \Rightarrow$ BJT is in Active region.