

Analog Electronics

Syllabus Overview :-

(1) Diode Family

1.1 Clipper circuit

1.2 Clamper circuit

1.3 C/S of Diode

*** 1.4 Zener diode regulator

1.5 Rectifier and Filter.

(2) Transistor Family

2.1 Biasing

2.2 Region.

2.3 Current mirror circuit.

(3) op-Amp & its Application.

(4) BJT & MOSFET Amplifier

(5) Feed Back Amplifier & Oscillator

Marks In Gate.

EC/IN

EE

10-12 Marks

6-8 Marks

EE (Basic Discussion)

EC/IN (Details Discussion)

ANALOG ELECTRONICS BY UMESH DHANDE SIR








Chapter - 1

Diode Family

Chapter - 1


Clipper Circuit

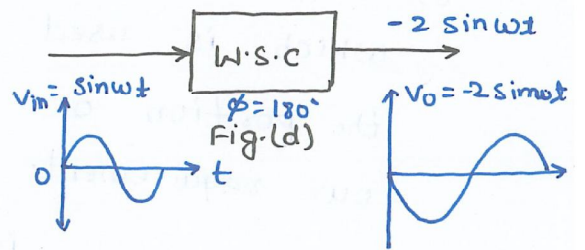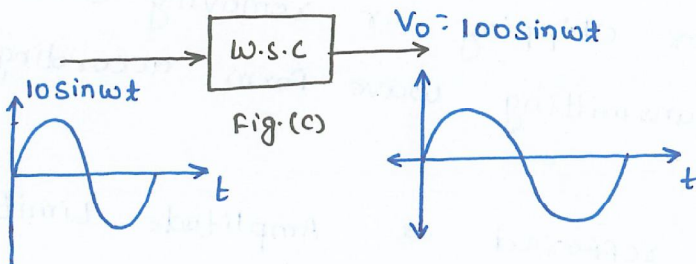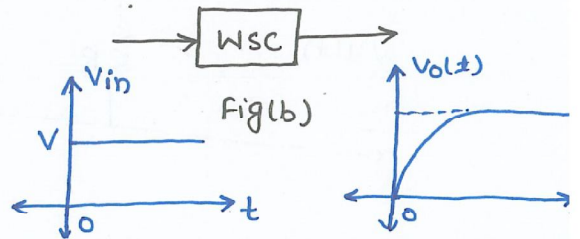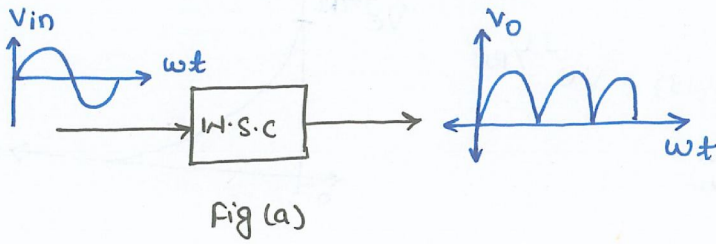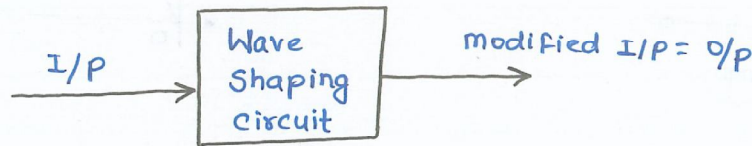

Wave Shaping circuit


Linear W.S.C

Eg:- R, L, C, RC LPF, RC HPF




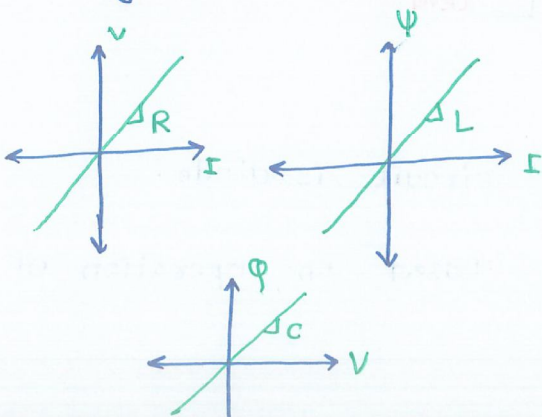


Non Linear W.S.C


Eg:- Diode, Transistor

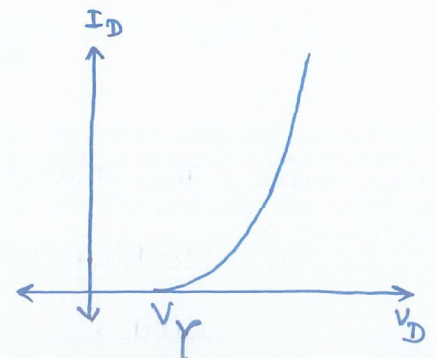


Example of Linear W.S.C

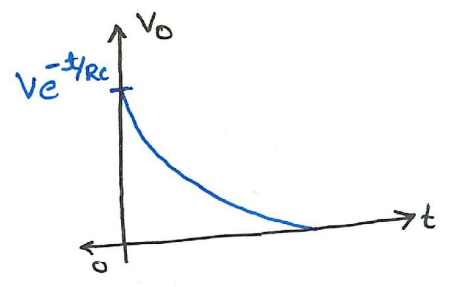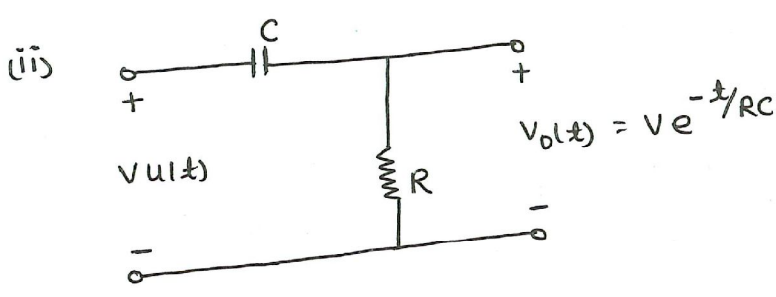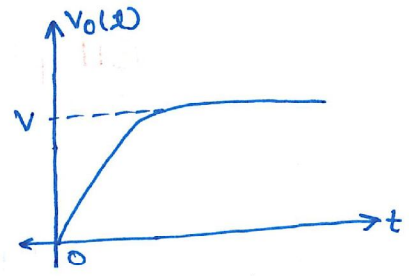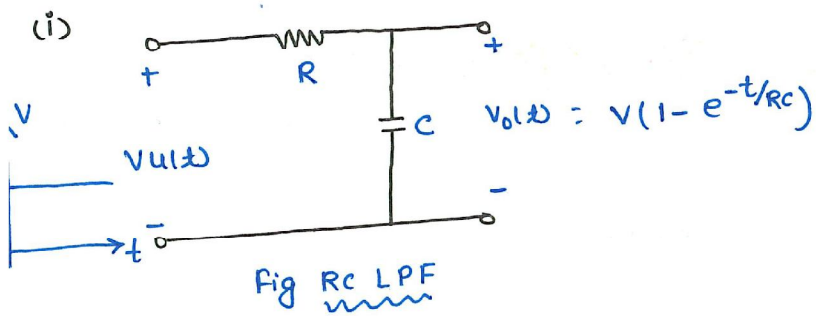

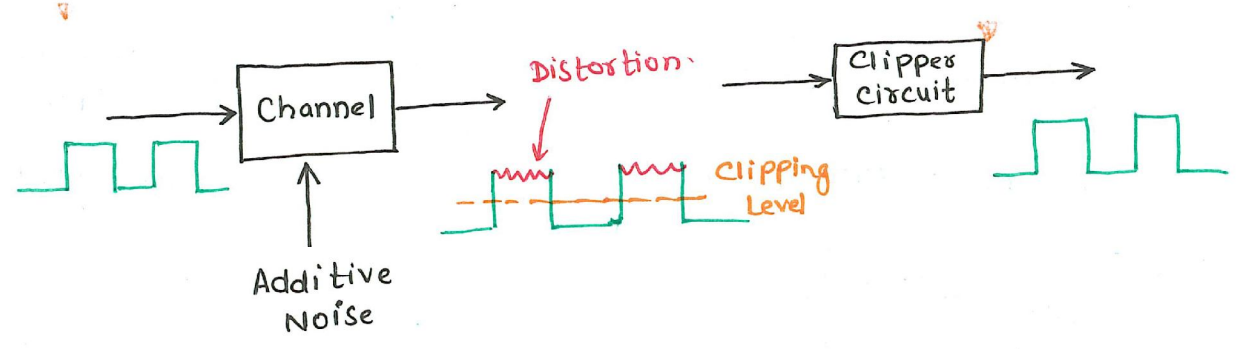- (i) clipper circuit is non linear wave shaping ext. which is used for clipping or removing some of the portion of transmitting wave form according to our requirement.
- (ii) clipper ext. is referred as Amplitude Limiter or selector circuit.
- (iii) clipper circuit can be used for eliminating the effect of noise in digital communication.



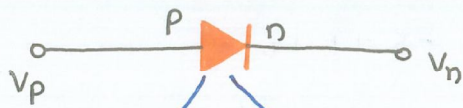- (iv) The main element in clipper circuit is diode.
- (v) Working of clipper circuit is based on operation of diode.



$V_p > V_n$ $V_n > V_p$

Forward Biased

Reverse Biased

Ideal diode

Practical diode


Ideal

Practical

Forward Biased

Ideal diode

ON/s.c/FB

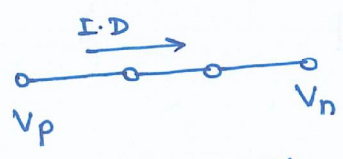

$V_D = 0 \text{ volt}$

$I_D > 0 \text{ Amp.}$


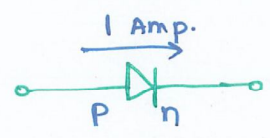


Fig. FB/ON


Practical diode.

$V_f = 0.6 \text{ volt (Assume)}$

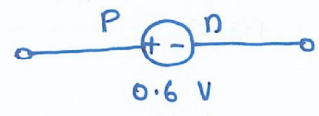

$I_D \text{ From P to n.}$

$I_D > 0 \text{ Amp.}$

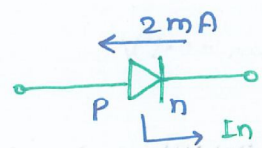

In diode current flow in only P to n.



Fig. Not possible.

Possibility



D = OFF

$I_D = 0 \text{ Amp.}$


Limiting resistor.

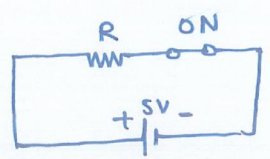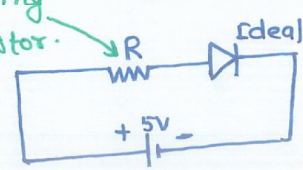

→

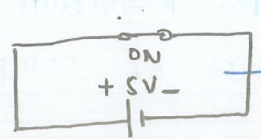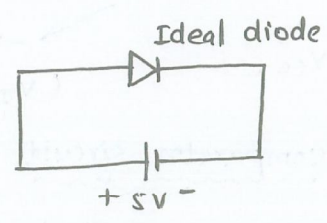

→ KVL violated.

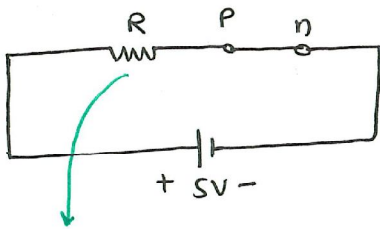

$$-5 + R I_D = 0$$

$$I_D = 5/R$$

(i) $R = 1 \Omega$

$$I_D = 5 A$$

(ii) $R = 1 K \Omega$

$$I_D = 5 mA$$

(iii) $R = 1 M \Omega$

$$I_D = 5 \mu A$$

- In this case, the value of Resistor can't change behavior of Diode.

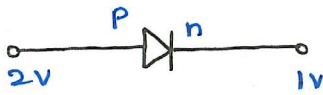


Fig (a)

→ Forward Biased [2V]

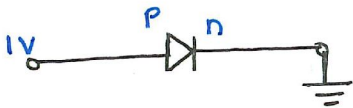


Fig (b)

→ Forward Biased [1V]



Fig (c)

→ Forward Biased [2V & -3V]

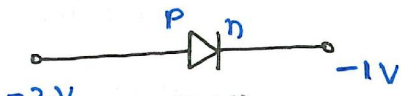


Fig (d)

(higher Neg. Potential)

Lower Neg. potential

→ If Both value are Negative then higher Negative potential decide the Diode operation.

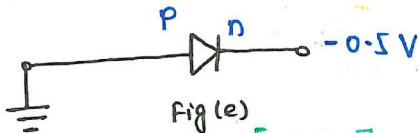


Fig (e)

FB [-0.5V]


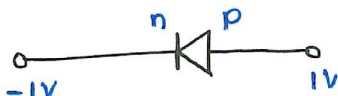


Fig (b)

F-B [Both -1V & 1V]

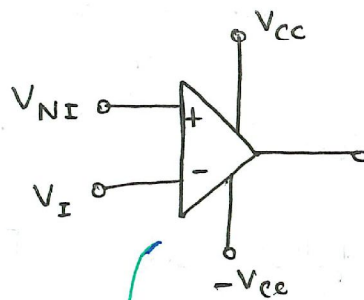

$$V_{NI} > V_I$$

$$V_O \rightarrow +V_{Cc}$$

$$V_O \rightarrow -V_{Cc}$$

$$(V_I > V_{NI})$$

Fig Comparator circuit

In Comparator magnitude decide the behavior of comparator.

Basic Clipper circuit

Series Clipper circuit





Shunt Clipper circuit

Positive S.C.C.

Negative S.C.C.

Positive Shunt clipper


Negative Shunt clipper

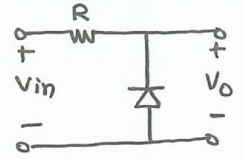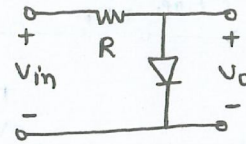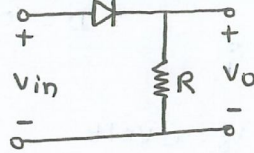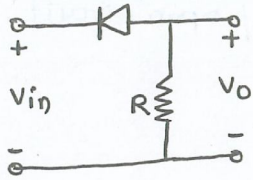


- (i) In series clipper ckt. diode is connected in series with input.
- (ii) In shunt clipper ckt. diode is connected in shunt with output.
- (iii) In positive clipper ckt. we remove maximum ^{positive} portion of transmitted waveform.
- (iv) In negative clipper ckt we remove maximum negative portion of transmitted waveform.

Key point :- IF there is NO information about Diode then we will consider Ideal diode.


(1) Positive series Clipper circuit :-

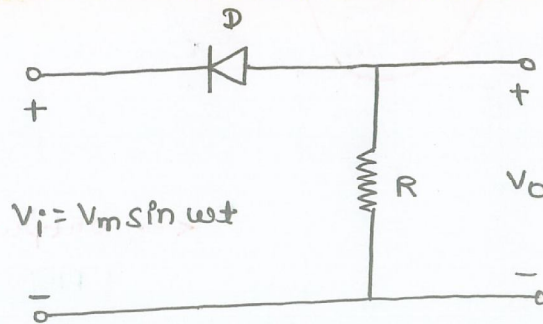

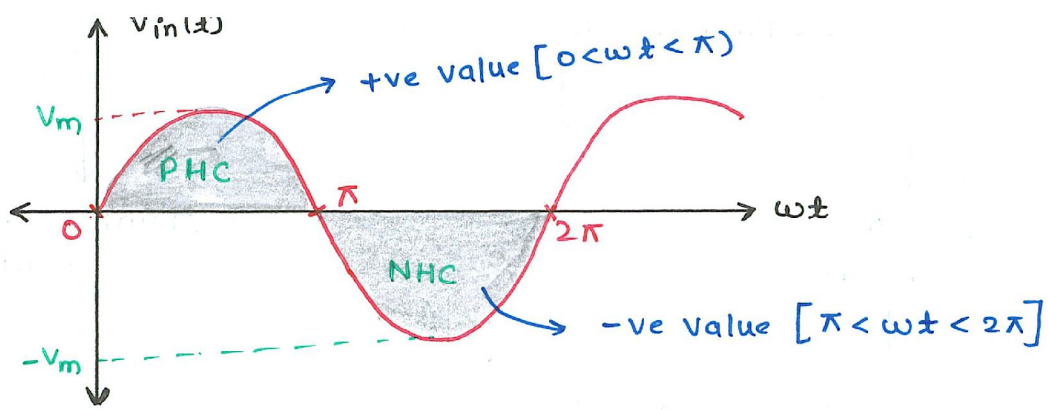

Case - 1

During PHC [$0 < \omega t < \pi$]



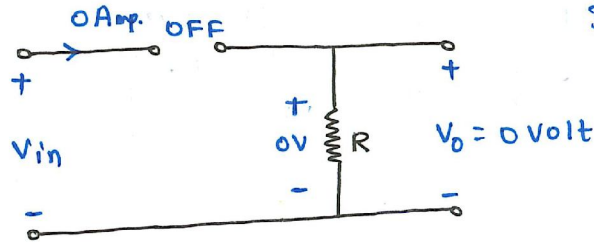


$D = \text{OFF} / \text{RB} / \text{open circuit}$

Case - 2

During NHC [$\pi < \omega t < 2\pi$]

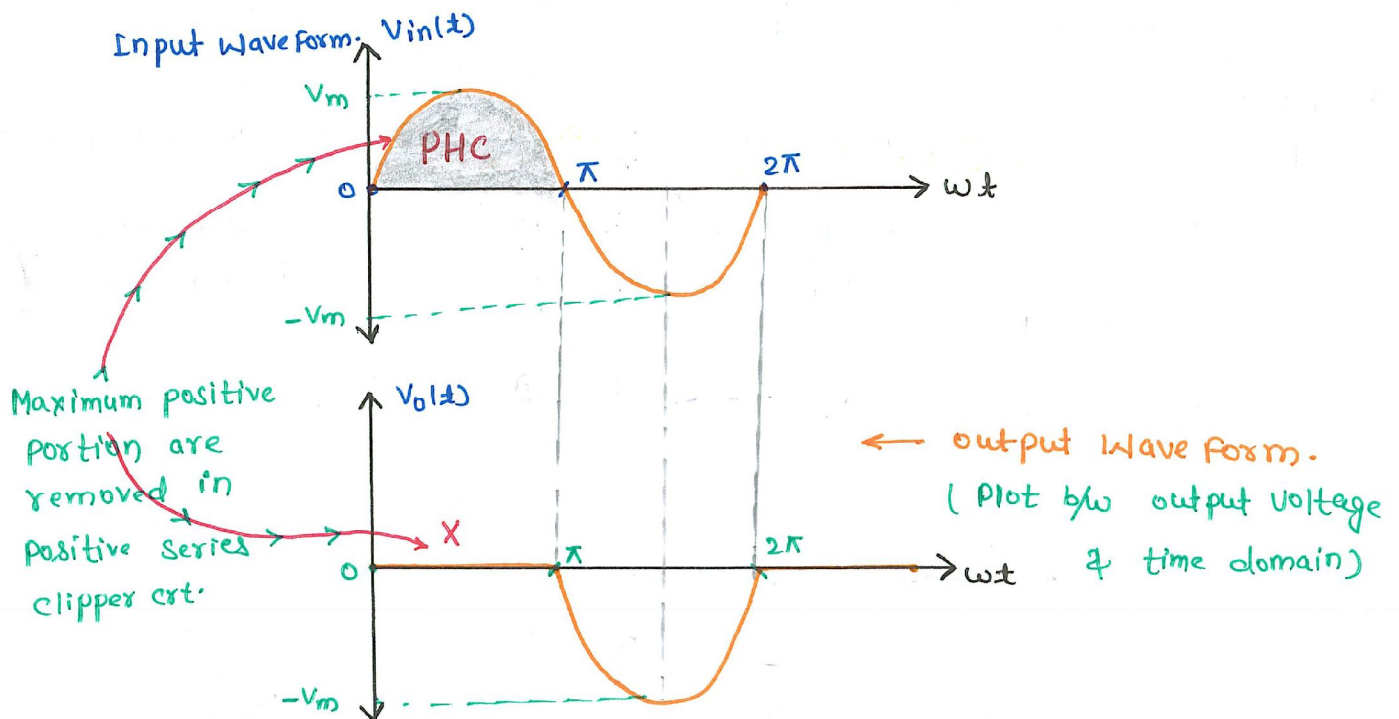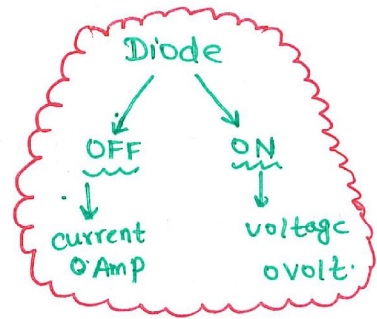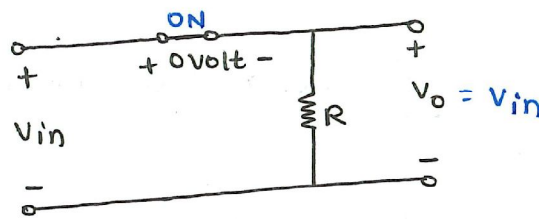$D = \text{ON} / \text{FB} / \text{short circuit}$



Transfer Characteristics

- output voltage vs Input voltage is referred as Transfer characteristics.


IF O/p Follow I/p then graph always in 1st & 3rd quadrant.

NHC


$V_o = V_i$

$y = mx$

Slope = +1

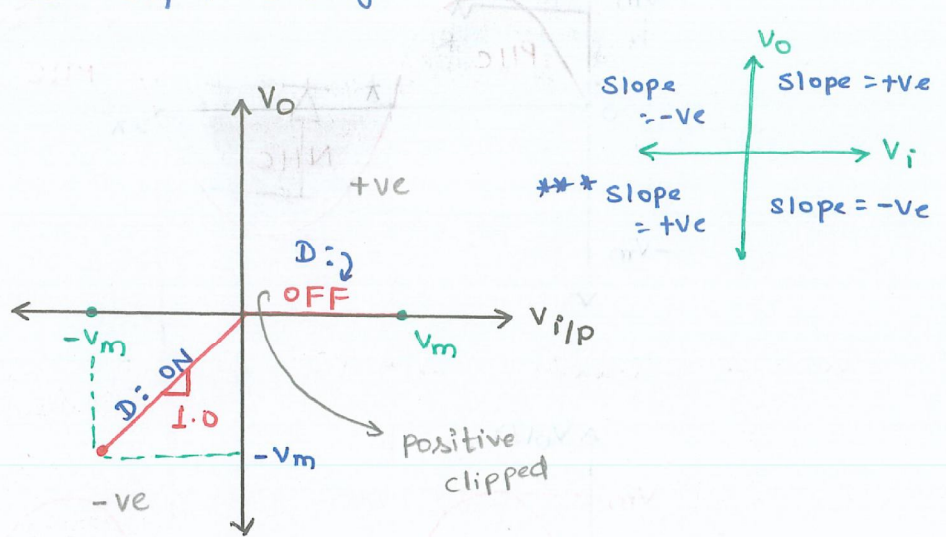


(2) Negative Series clipper circuit

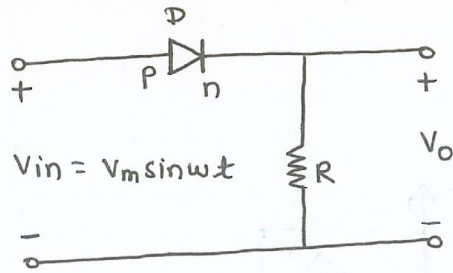

Case - 1

During PHC $[0 < \omega t < \pi]$


D = FB/ON/short circuit

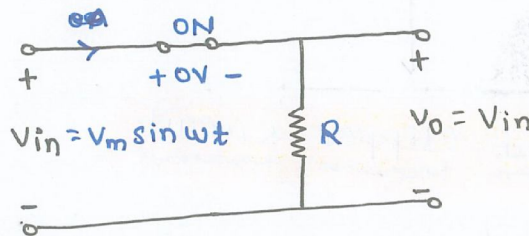


Case - 2


During NHC $[\pi < \omega t < 2\pi]$

D = RB/OFF/open circuit.

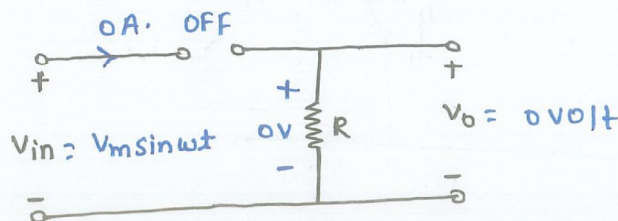

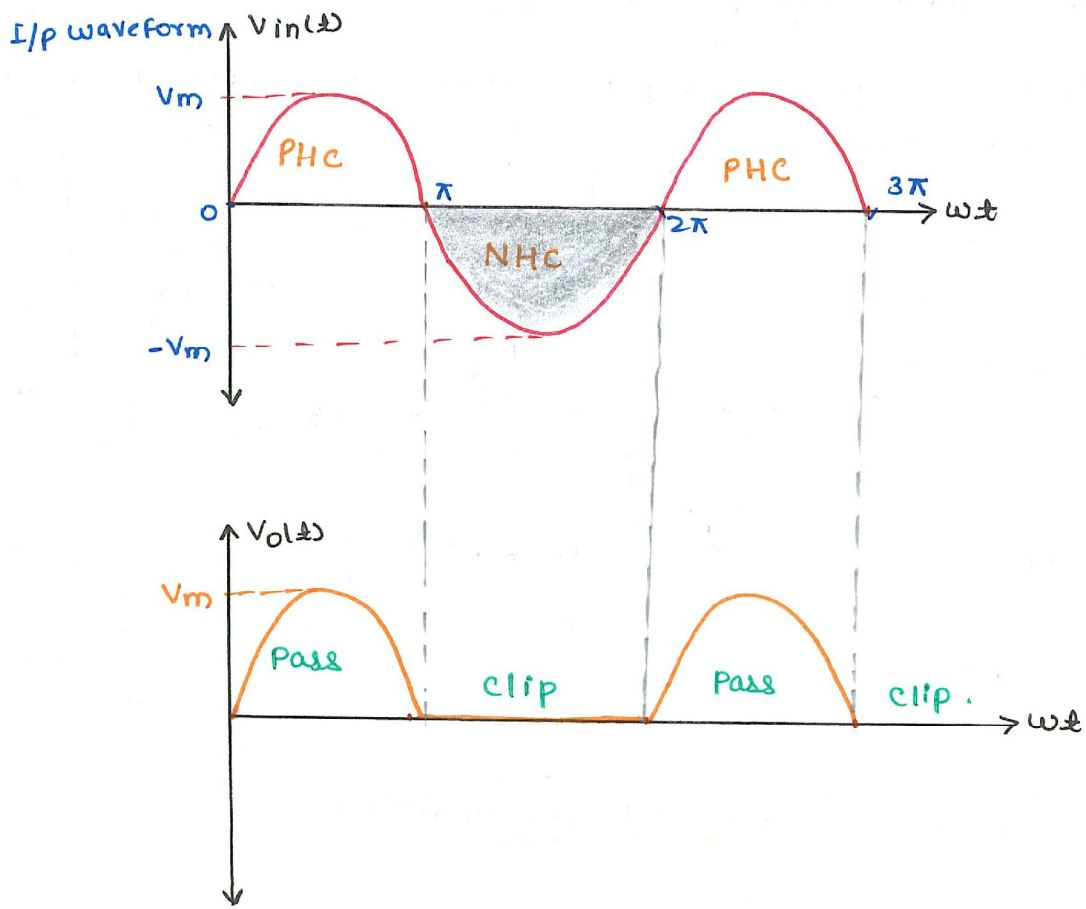

Transfer Characteristics :-

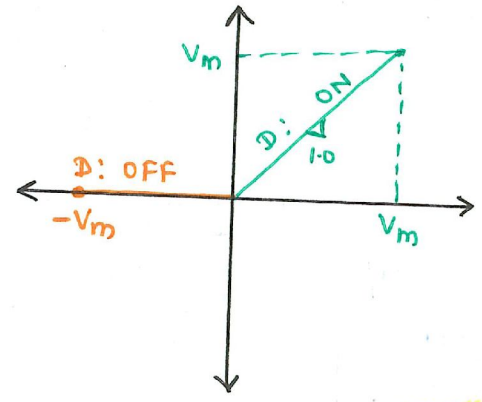

(3) Positive shunt clipper circuit

