

HindPhotostat



Hind Photostat & Book Store

Best Quality Classroom Topper Hand Written Notes to Crack GATE, IES, PSU's & Other Government Competitive/ Entrance Exams

MADE EASY ELECTRICAL ENGINEERING Digital Electronics By.Ramesh Sir

- Theory
- Explanation
- Derivation
- Example
- Shortcuts
- Previous Years Question With Solution

Visit us:-www.hindphotostat.com

Courier Facility All Over India
(DTDC & INDIA POST)
Mob-9311989030



HindPhotostat



MADE EASY , IES MASTER , ACE ACADEMY , KREATRYX

**ESE , GATE, PSU BEST QUALITY TOPPER HAND WRITTEN NOTES
MINIMUM PRICE AVAILABLE @ OUR WEBSITE**

- | | |
|--------------------------------|---------------------------|
| 1. ELECTRONICS ENGINEERING | 2. ELECTRICAL ENGINEERING |
| 3. MECHANICAL ENGINEERING | 4. CIVIL ENGINEERING |
| 5. INSTRUMENTATION ENGINEERING | 6. COMPUTER SCIENCE |

IES , GATE , PSU TEST SERIES AVAILABLE @ OUR WEBSITE

- ❖ IES –PRELIMS & MAINS
- ❖ GATE

➤ **NOTE;- ALL ENGINEERING BRANCHS**

➤ **ALL PSUs PREVIOUS YEAR QUESTION PAPER @ OUR WEBSITE**

PUBLICATIONS BOOKS -

MADE EASY , IES MASTER , ACE ACADEMY , KREATRYX , GATE ACADEMY, ARIHANT , GK

**RAKESH YADAV, KD CAMPUS , FOUNDATION , MC –GRAW HILL
(TMH) , PEARSON...OTHERS**

HEAVY DISCOUNTS BOOKS AVAILABLE @ OUR WEBSITE

HIND PHOTOSTAT AND BOOK CENTER F230, Lado Sarai New Delhi-110030 Phone: 9311 989 030	Shop No: 46 100 Futa M.G. Rd Near Made Easy Ghitorni, New Delhi-30 Phone:	F518 Near Kali Maa Mandir Lado Sarai New Delhi-110030 Phone:	Shop No.7/8 Saidulajab Market Neb Sarai More, Saket, New Delhi-30
---	--	---	--

9560 163 471

Website: www.hindPhotostat.com

Contact Us: 9311 989 030

Courier Facility All Over India

DIGITAL ELECTRONICS

①

Electronics: The study of motion of electron inside a semiconductor is known as electronics.

- * semiconductors having controlled conductivity.
- * for n -variables we get 2^n combination 2^{2^n} possible functions.

Boolean logic ideas:

These are classified into three parts -

1. Produce in the constant (0, 1)
 - ↓ null operation
 - ↘ identity operation
2. Unary operation (Buffer, not)
 - ↓ transfer
 - ↓ Complementary operation.
3. Binary operations (AND, OR, NAND, NOR, Ex-OR, Ex-Nor, Inhibition, Implication)

Truth Tables

x	y	f_0	f_1	f_2	f_3	f_4	f_5	f_6	f_7	f_8	f_9	f_{10}	f_{11}	f_{12}	f_{13}	f_{14}	f_{15}
0	0	0	0	0	0	0	0	0	0	1	1	1	1	1	1	1	1
0	1	0	0	0	0	1	1	1	1	0	0	0	0	1	1	1	1
1	0	0	0	1	1	0	0	1	1	0	0	1	1	0	0	1	1
1	1	0	1	0	1	0	1	0	1	0	1	0	1	0	1	0	1

$f_0 = 0$ Null

$f_1 = x \cdot y$ AND
 $x \cap y$

$f_2 = x \cdot \bar{y}$ Inhibition
(x but not y)

$f_3 = x$ transfer Buffer.

$f_4 = \bar{x} \cdot y$ Inhibition

(y but not x)


1

$f_5 = y$ Buffer (transfer)

$f_6 = x \oplus y$ EX-OR
 $= \bar{x}y + x\bar{y}$

NOTE:

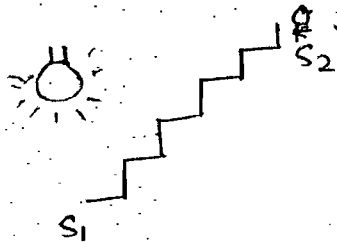For stair case, & escalator EX-OR logic is used.



S_2	S_1	$S_2 \oplus S_1$ bulb
0	0	0
0	1	1
1	0	1
1	1	0

$f_7 = x + y$ OR $x \cup y$

$f_8 = \overline{x+y}$ NOR $x \downarrow y$

$f_9 = x \oplus y$ EX-NOR $\overline{\bar{x}y + x\bar{y}}$

NOTE: Ex-nor is also known as co-incidence logic, equivalence logic gate.

$f_{10} = \bar{y}$ NOT complimentary

$f_{11} = x + \bar{y}$ Implication

$f_{12} = \bar{x}$ NOT complimentary

$f_{13} = \bar{x} + y$ Implication

$f_{14} = \overline{x \cdot y}$ NAND
 $x \uparrow y$

$f_{15} = 1$ Identity

Basic logic gates: NOT, AND, OR.

Combinational logic gate:

NAND } universal logic gate
NOR }

EX-OR } Arithmetic logic gate
EX-NOR }

Symbols for logic gate:

