



HindPhotostat



Hind Photostat & Book Store

Best Quality Classroom Topper Hand Written Notes to Crack GATE, IES, PSU's & Other Government Competitive/ Entrance Exams

MADE EASY
ELECTRICAL ENGINEERING
Network Theory
BY-Kiran Sir

- Theory
- Explanation
- Derivation
- Example
- Shortcuts
- Previous Years Question With Solution

Visit us:-www.hindphotostat.com

Courier Facility All Over India
(DTDC & INDIA POST)
Mob-9311989030

bit.ly/33IEMRD

Sadik book

9440819611



bit.ly/3ufwiH

⇒ Home work

bit.ly/WBNT2025

⇒ work back
8a

Network

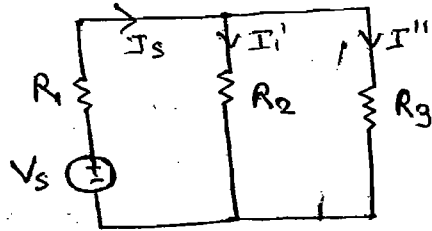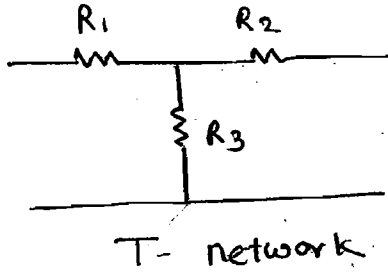

Network -

Network is a combination of elements, it may or may not consist of closed path & it may or may not consist of atleast one independent source

e.g. wireless-communication system (Internet)

Circuit Circuit is a combination of element it should consist of closed path

& it should consist of atleast one independent source.

e.g. Electrical transmission line

$$Q = \int_{-\infty}^t I dt$$


$$Q = \int_{-\infty}^0 I dt + \int_0^t I dt$$

$$Q = Q_0 + \int_0^t I dt$$


↓
Initial charge

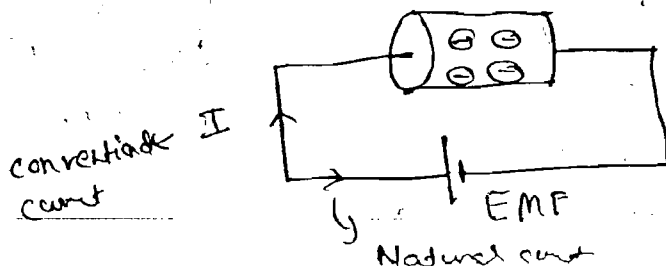(-1.602×10^{-19} coulomb)

$$I = \frac{dQ}{dt} \text{ (coulomb/sec or Amp)}$$



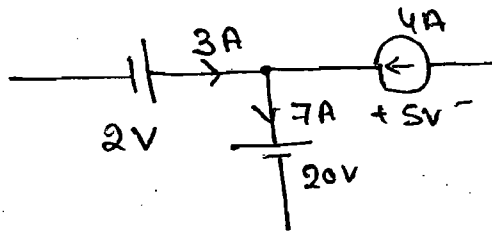8) find total Power absorbing of the figure shown :-



$$P_{20} = 20 \times 7 = 140 \text{ W (absorb)}$$

$$P_{2V} = 2 \times 3 = 6 \text{ W (Deliver)}$$

$$P_{4A} = 5 \times 4 = 20 \text{ W (Deliver)}$$


Total absorbing Power

$$P_T = 140 - 20 - 6 = 114 \text{ W (Total Absorbing Power)}$$

$$W = \int_0^t P dt \text{ watt-sec or Joule}$$

$$W = \text{Power} \times \text{Time}$$

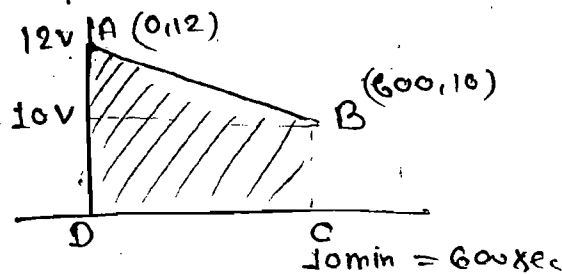9) A fully charged mobile phone is good for 10 min talk time. During talk time battery delivers a const. current of 2 Amp find Energy of the battery during talk time.



Method-1

$\Rightarrow V \cdot T$

$$\text{Area ABCD} = \frac{1}{2} \times (12 + 10) \times 600 = 6600 \text{ J}$$

$$W = P \times t = VI \times t$$

$$W = 6600 \times 2 = 13200 \text{ J} = 13.2 \text{ kJ}$$

method-2

$$y - y_1 = m(x - x_1)$$

$$V - 12 = \left(\frac{10 - 12}{600 - 0} \right) \times (t - 0)$$

$$V = \frac{-t}{300} + 12$$

$$w = \int_0^{600} P \cdot dt = \int_0^{600} v i dt = \int_0^{600} \left(\frac{-t}{300} + 12 \right) 2 dt$$

$$= 18.2 \text{ kJ}$$


Q) find the current by using following figure -

method-1

$$\Rightarrow i = \frac{dq}{dt}$$

$$I = \frac{30 - 40}{200 - 0} = \frac{-10}{200}$$

$$I = -\frac{1}{20} \text{ A}$$

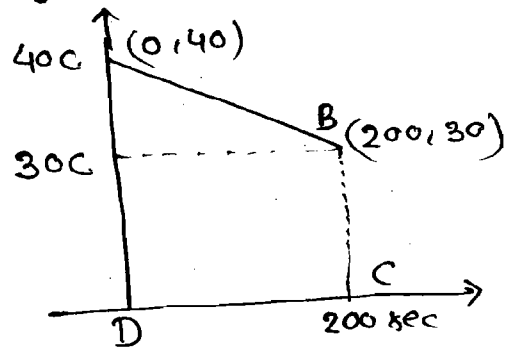

method-2


$$y - y_1 = m(x - x_1)$$

$$Q - 40 = \frac{30 - 40}{200 - 0} (t - 0)$$

$$Q = \frac{-t}{20} + 40$$

$$I = \frac{dq}{dt} = -\frac{1}{20} \text{ A}$$

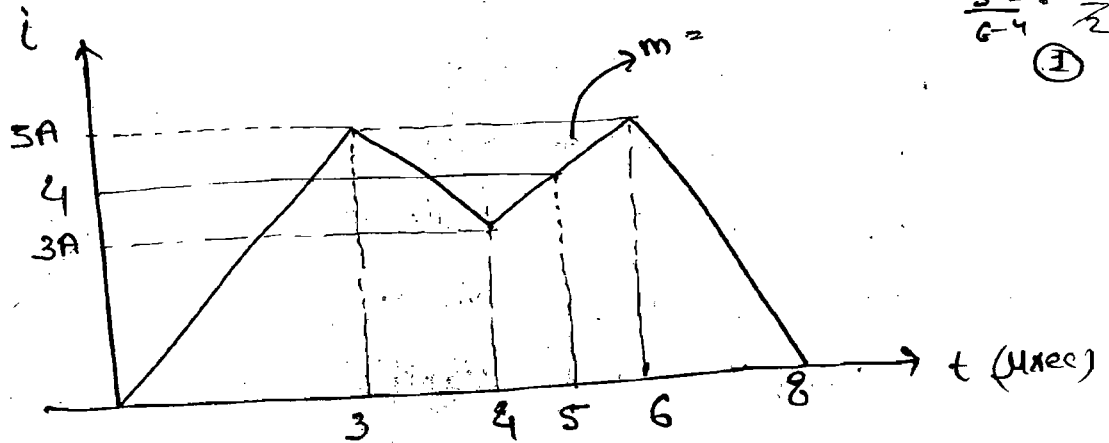8) Find charge acquired by capacitor in 5 μsec



$$\frac{5-3}{6-4} = \frac{2}{2}$$

(1)

$$i = \frac{dq}{dt}$$

$$\int dq = \int i dt \Rightarrow \text{Area under the curve of } i \text{ vs } t \text{ character}$$

$$Q = \int_0^5 i dt \Rightarrow \int_0^3 i dt + \int_3^4 i dt + \int_4^5 i dt$$


$$\Rightarrow \frac{1}{2} \times 3 \times 5 + \frac{1}{2} (5+3) \times 1 + \frac{1}{2} [3+4] \times 1$$

$$\Rightarrow \frac{15}{2} + \frac{8}{2} + \frac{7}{2} \Rightarrow \text{Coulomb}$$

$$\Rightarrow 7.5 + 4 + 3.5 = 15 \mu\text{C}$$

Classification of elements :-

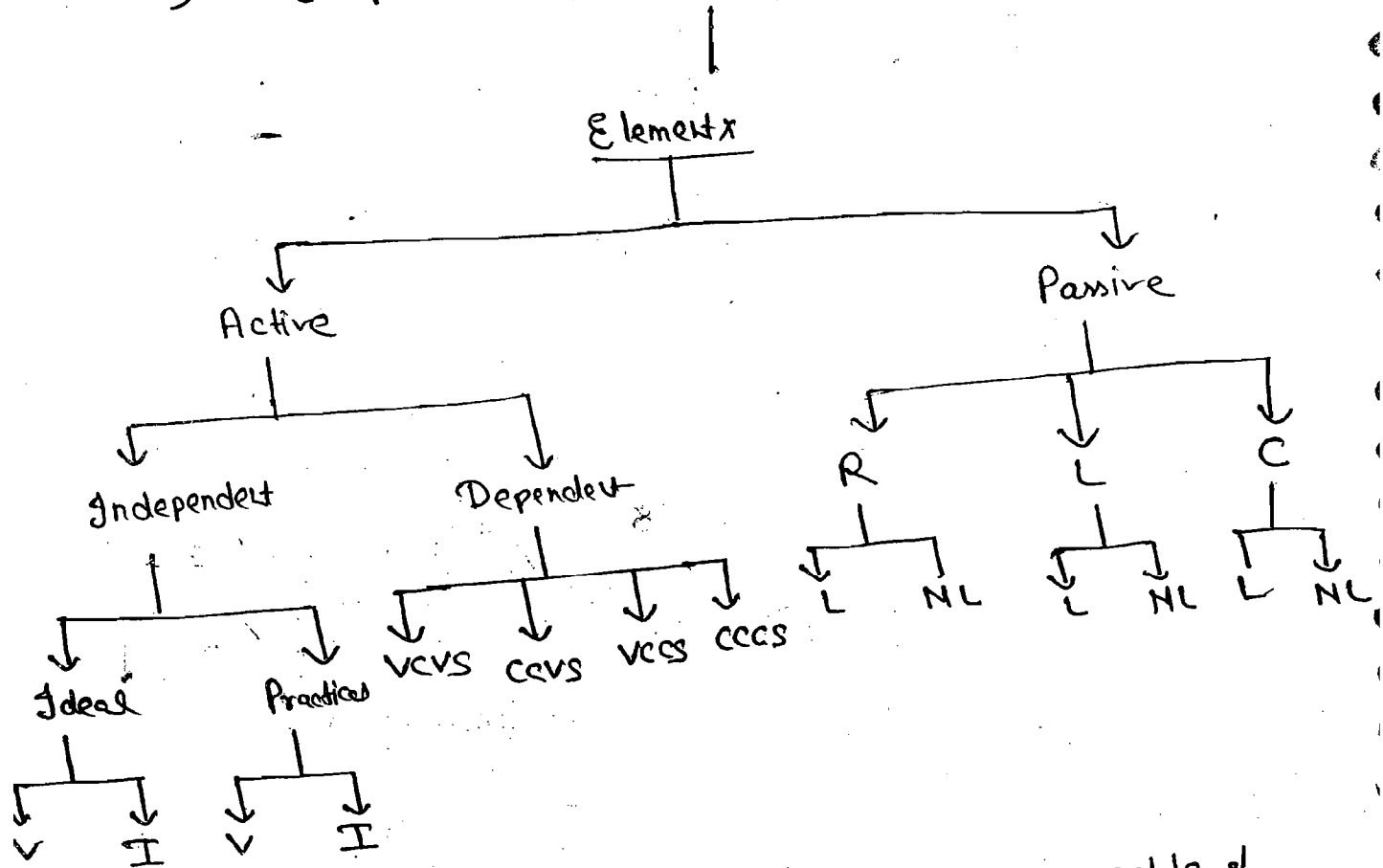
- 1) Active and Passive
- 2) Linear + Non-Linear
- 3) Unidirectional + Bidirectional
- 4) Time variant + time invariant
- 5) Lumped and Distributed.



Active elements :- When the element is capable of delivering energy independently for long time (Approx ∞ time) @

OR
When the element is having property of internal amplification then it is known as Active element

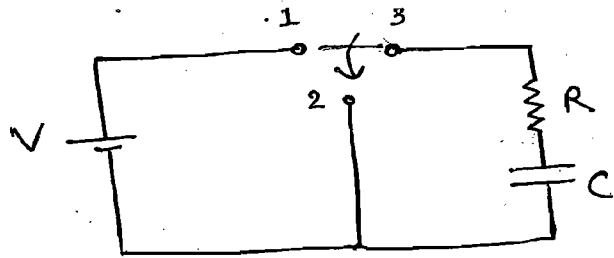e.g. Voltage source, current source (transistor + op-amp)
Independent source (dependent source)



$t > 0$ $C \Rightarrow$ Discharging

Note \rightarrow




During discharging capacitor can deliver the energy independently for short time & capacitor is not having internal amplification property.

Passive elements! - When the element is not capable of delivering energy independently then it is known as passive element




- e.g.
- 1) Resistor
 - 2) Bulb
 - 3) Transformer $[V_1 I_1 = V_2 I_2]$
 \hookrightarrow Inductor

Voltage -

Ideal :-

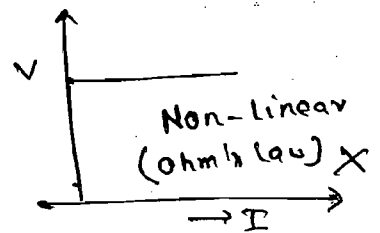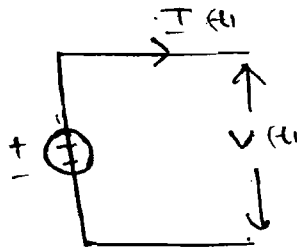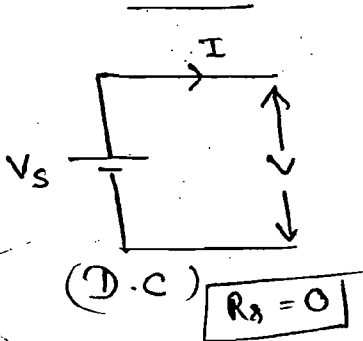

Practical :-

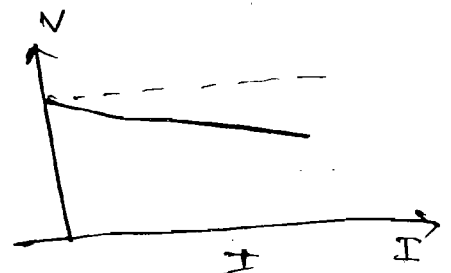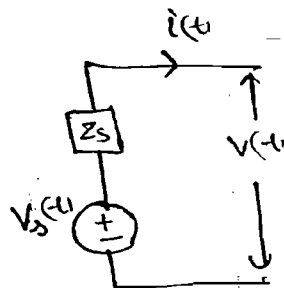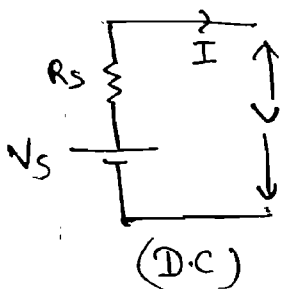

$$V_s = V - IR_s$$

$$V = V_s - IR_s$$

- 1) Ideal Voltage source delivers energy at specified voltage which is independent on current delivered by the source.
- 2) Internal resistance of ideal voltage source is equal zero
- 3) Practical Voltage source delivers energy at specified voltage (V) which depends on current delivered by the source
 e.g. 1) Battery
 2) Generator.
- 4) Independent Voltage source does not obey the Ohm's law
 $\therefore V-I$ characteristic is non-linear.

