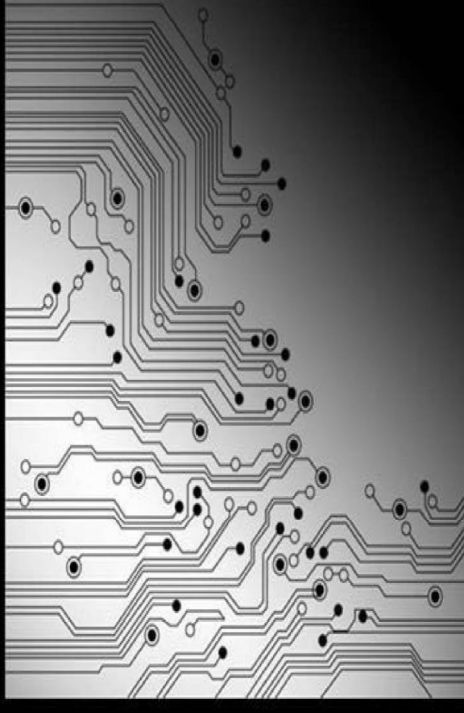


Diode circuits

- ① Diode with respect D.C.
- ② clipper circuits
- ③ clamper circuits
- ④ D.C. power supply $\rightarrow$ (Rectifiers + Filter + Zener regulators)
- ⑤ Small signal model of the diode.



Diode Circuits PART-1



Diode with D.C. Source

$\eta \rightarrow$ ideality factor

$\eta = 1 \rightarrow \text{Ge}$

$\eta = 2 \rightarrow \text{Si}$

V_T : Thermal voltage


$$V_T = \frac{T}{11,600} \rightarrow (\text{kelvin})$$

Application: Diode act as a switch





$$I_D = I_S (e^{V_D / \eta V_T} - 1)$$

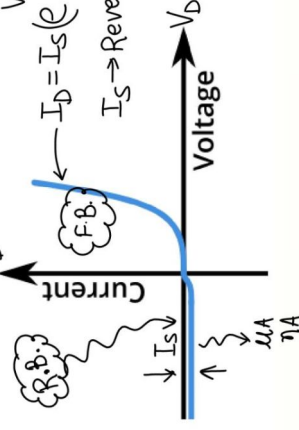$I_S \rightarrow$ Reverse Saturation current [μA (or) nA]




(1) Ideal Diode Model

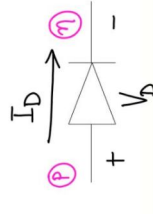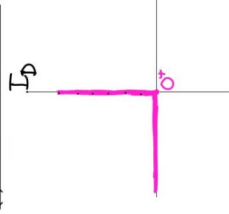

Diode Models

- If $V_D < 0 \Rightarrow I_D = 0 \Rightarrow$ open circuit
- If $V_D > 0 \Rightarrow I_D \neq 0 \Rightarrow$ short circuit

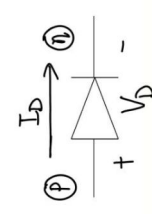
- If $V_D < V_Y : I_D = 0 \Rightarrow$ open circuit
- If $V_D > V_Y : I_D \neq 0$



Note: Si diode $V_Y \approx 0.7$ volt
Ge diode $V_Y \approx 0.3$ volt



Question 1

Find V_0 in the given circuit

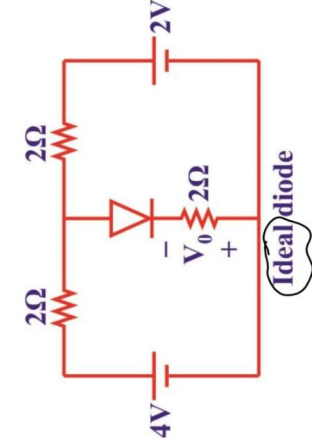

Procedure:
 (1) Let Diode is off
 $V_D = ?$
 If $V_D < 0$ (or) $V_D < V_Y \Rightarrow$ Yes diode is really off.
 If $V_D > 0$ (or) $V_D > V_Y \Rightarrow$ Diode is ON

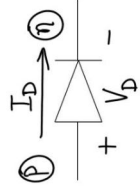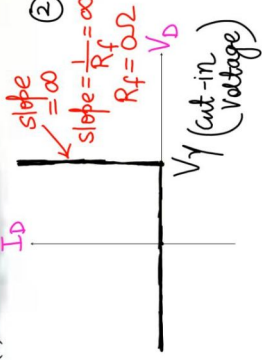- If $V_D < V_Y : I_D = 0 \Rightarrow$ open circuit
- If $V_D > V_Y : I_D \neq 0 \Rightarrow$ short circuit






If $I_D > 0$ (ON) $\Rightarrow$ Diode is really ON
 If $I_D < 0$ (OFF) $\Rightarrow$ Diode is OFF

Question.1

Find V_0 in the given circuit

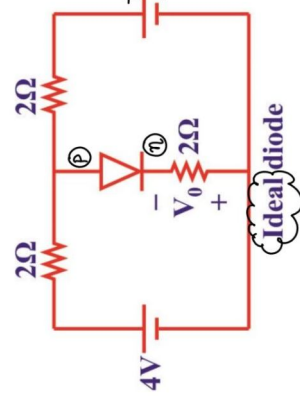

Solⁿ Let diode is ON

$$I = \frac{V_L - 0}{2} = 1A$$


(P to N)
 (Diode is really ON)

$$4 - V_L + \frac{2 - V_L}{2} = \frac{V_L - 0}{2}$$

$$6 - 2V_L = V_L$$

$$3V_L = 6$$

$$V_L = 2V$$

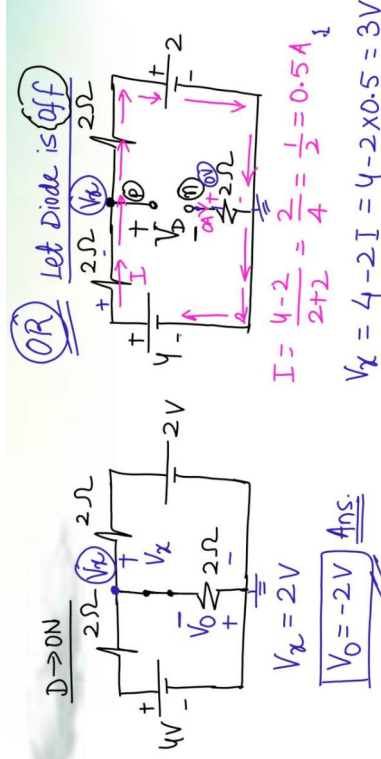

Let Diode is OFF

$$V_D = V_L = 3V$$

$$V_D > 0 \Rightarrow \text{Diode is ON}$$


$$I = \frac{4 - 2}{2 + 2} = \frac{2}{4} = 0.5A$$

$$V_L = 4 - 2I = 4 - 2 \times 0.5 = 3V$$


Diode is ON, our Assumption is wrong.

Question.2

Find V_0 , Assume Diodes are Ideal

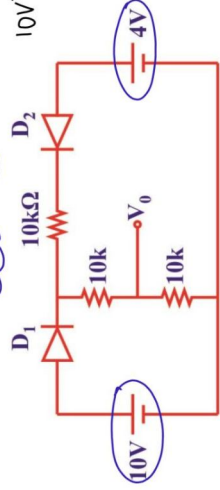

Let D_1 ON & D_2 off

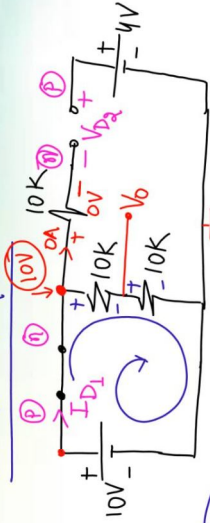

$$10 - 10I_{D1} - 10I_{D2} = 0$$


$$I_{D1} = \frac{10}{20} = \frac{1}{2} \text{ mA} = 0.5 \text{ mA (p to n)}$$

$(D_1 \rightarrow \text{ON})$

$$V_{D2} = 4 - 10 = -6 \text{ V}$$

$(D_2 \rightarrow \text{off})$


Our Assumption is correct.

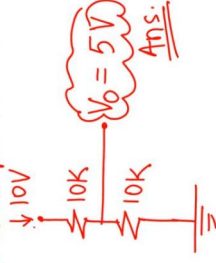

8 AM

Question.3

Let D_1 ON, D_2 ON

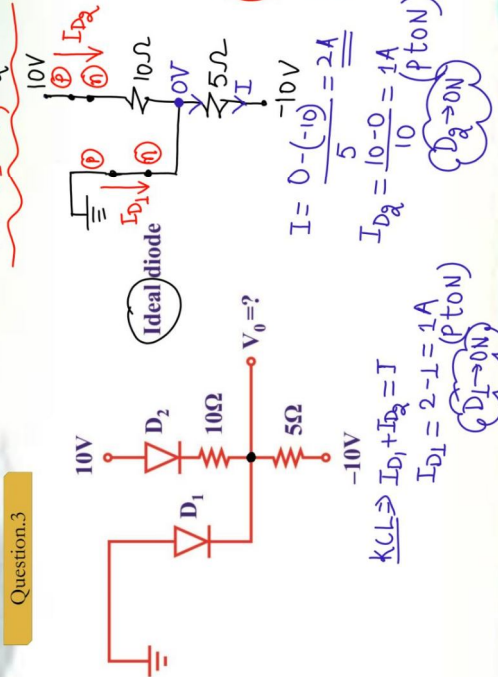

$$KCL \Rightarrow I_{D1} + I_{D2} = I$$


$$I_{D1} = 2 - 1 = 1 \text{ A (p to n)}$$

$(D_1 \rightarrow \text{ON})$

$$I = \frac{0 - (-10)}{5} = 2 \text{ A}$$

$$I_{D2} = \frac{10 - 0}{10} = 1 \text{ A (p to n)}$$


$(D_2 \rightarrow \text{ON})$

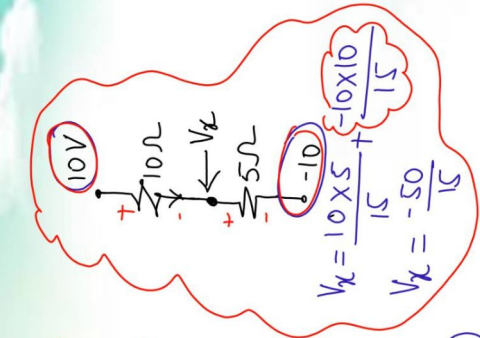

Our Assumption is correct.

$V_0 = 0 \text{ V}$ Ans.

OR Let D_1 off, D_2 off

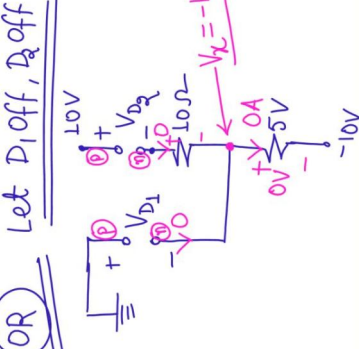


$$V_{D1} = 0 - (-10) = 10 \text{ V}$$

$(D_1 \text{ ON})$

$$V_{D2} = 10 - (-10) = 20 \text{ V}$$


$(D_2 \text{ ON})$

$D_1 \text{ ON \& } D_2 \text{ ON}$

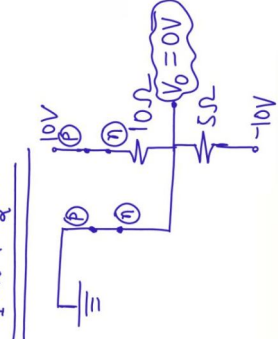


Question 4

Assume Diodes are Ideal

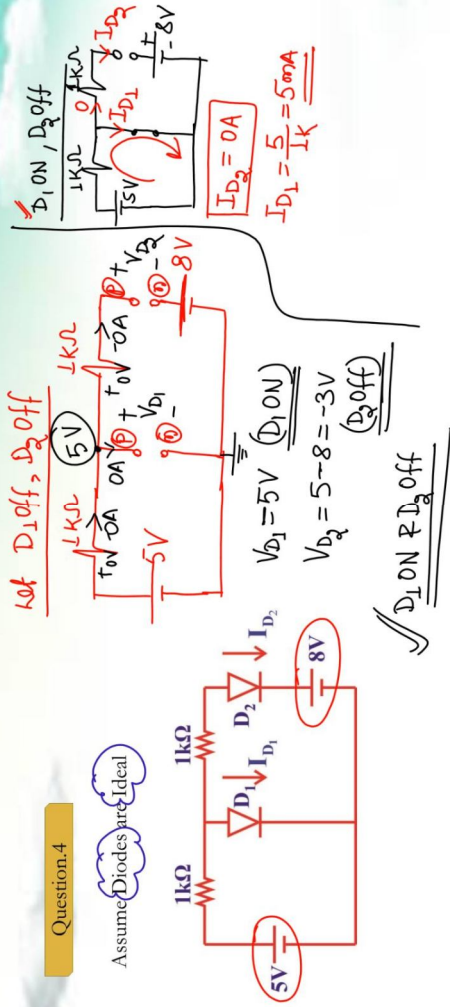

Question 5

$D \rightarrow$ ideal

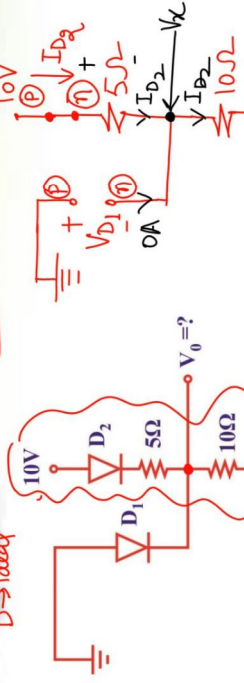

$$I_{D2} = \frac{10 - (-10)}{10 + 5} = \frac{20}{15} = \frac{4}{3} A \quad (D_2 \text{ ON})$$

$$V_{D1} = 10 - 5 I_{D2}$$


$$= 10 - 5 \times \frac{4}{3} = 10 - \frac{20}{3} = \frac{10}{3} = 3.33V$$

Our Assumption is correct

$V_{D1} = 3.33V$

OR

Let D_1 OFF, D_2 ON

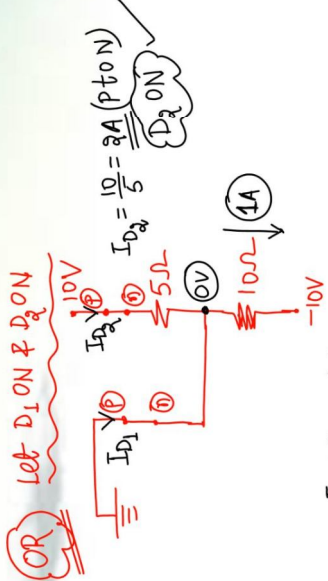

$$I_{D1} + I_{D2} = 1A$$

$$I_{D1} = 1A - 2A = -1A$$


$$I_{D1} = -1A \quad (D_1 \text{ OFF})$$

$\Rightarrow +1A$ (Not top) D_1 OFF


Diode Circuits PART-2

Lecture-2

Question 6

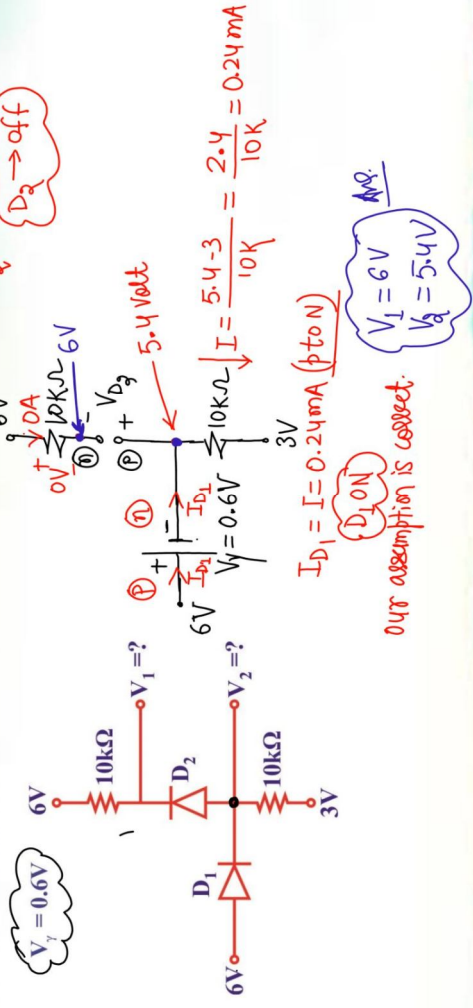


Question.7

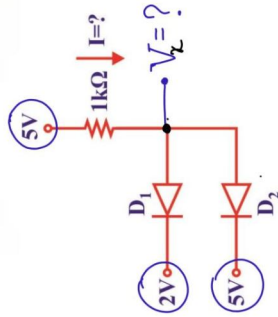


Possibilities

- x ① $D_1 \text{ ON}, D_2 \text{ ON} \Rightarrow$ Not possible
 $\Rightarrow$ Violation of KVL
- x ② $D_1 \text{ OFF}, D_2 \text{ OFF} \Rightarrow$ Not possible
 $\Rightarrow V_x = 5V \Rightarrow D_1 \text{ ON}$ for
- x ③ $D_1 \text{ OFF}, D_2 \text{ ON}$
If $D_2 \text{ ON} \Rightarrow D_1 \text{ ON}$ for
 $D_1 \text{ ON}, D_2 \text{ OFF}$ for

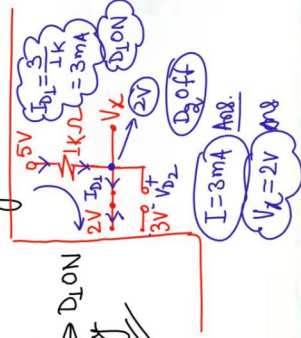

Question.8

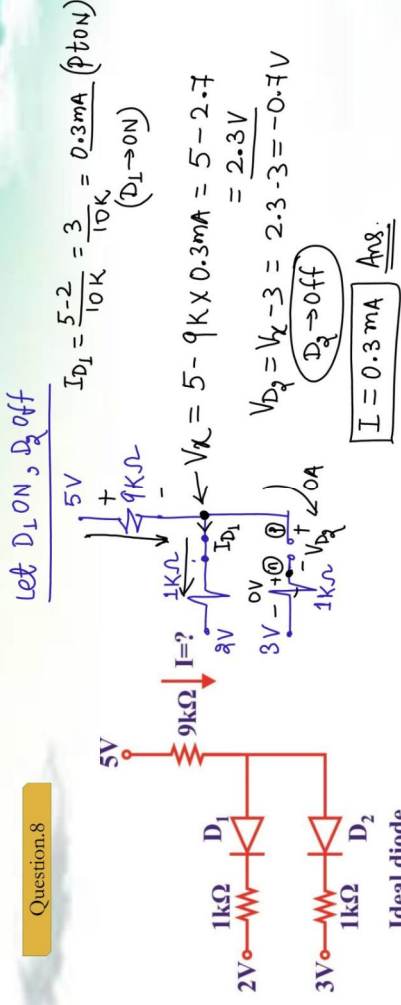

Let $D_1 \text{ ON}, D_2 \text{ off}$

$$I_{D1} = \frac{5-2}{10K} = \frac{3}{10K} = 0.3 \text{ mA} \quad (D_1 \rightarrow \text{ON})$$


$$V_x = 5 - 9K \times 0.3 \text{ mA} = 5 - 2.7 = 2.3 \text{ V}$$

$$V_{D2} = V_x - 3 = 2.3 - 3 = -0.7 \text{ V}$$

$D_2 \rightarrow \text{off}$

$I = 0.3 \text{ mA}$ Ans.

Question.9

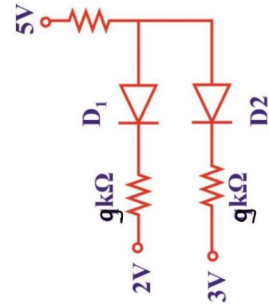


Let $D_1 \text{ ON}, D_2 \text{ off}$

$$I_{D1} = \frac{5-2}{10K} = 0.3 \text{ mA} \quad (D_1 \text{ ON})$$

$$V_x = 5 - 1K \times 0.3 \text{ mA} = 4.7 \text{ V}$$

$$V_{D2} = V_x - 3 = 4.7 - 3 = 1.7 \text{ V}$$

$D_2 \text{ ON}$

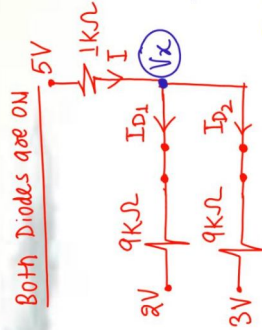

Both Diodes are ON

$$\frac{5-V_x}{1K} = \frac{V_x-2}{9K} + \frac{V_x-3}{9K}$$

$$9(5-V_x) = 2V_x-5 + V_x-3$$


$$45-9V_x = 3V_x-8$$

$$50 = 12V_x$$

$$V_x = \frac{50}{12} \text{ Volt}$$

$$I = \frac{5-V_x}{1K} = 5 - \frac{50}{12} \text{ mA}$$

Question.10

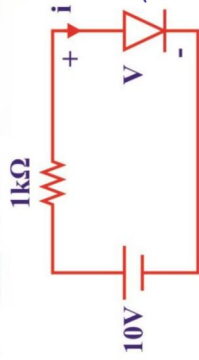

$i = \frac{V - 0.7}{500}$ Amp ✓ ; when $V \geq 0.7V$

= 0 ; when $V < 0.7V$


Find i in the circuit

$V_f = 0.7V$
 $D \rightarrow ON$
 $i = \frac{V - 0.7}{500}$ Amp
 $V_f = 0.7V$
 $R_f = 500\Omega$

$i = \frac{10 - 0.7}{1500\Omega} = 9.3 \text{ Amp} //$


$i = \frac{V - V_f}{R_f}$
 $i = \frac{V - 0.7}{500}$

Question.11

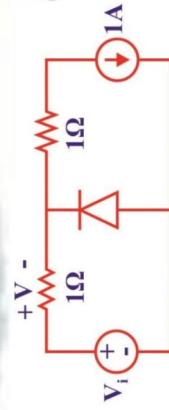

In the circuit shown, the diode is ideal. The Voltage V is given by

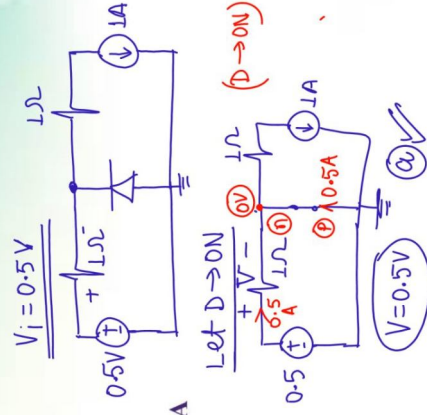- (a) Min ($V_i, 1$) (b) Max ($V_i, 1$)
 (c) Min ($-V_i, 1$) (d) Max ($-V_i, -1$)




$V_i = 1V$ } check


Student's Assignment-1

Question.1

The diode in the circuit given below has $V_{on}=0.7V$, but is ideal otherwise. The current (in mA) in the $4k\Omega$ resistor is _____.

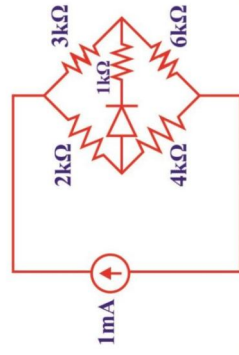

Question.2

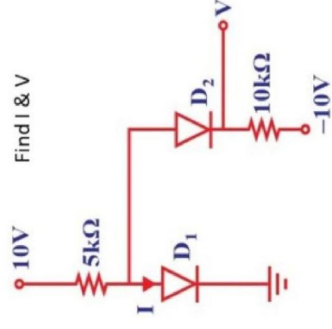


Question.3

In the following figure. Find out the voltage V_0 .


Given cut-in voltage for Si = 0.7V

Cut-in voltage for Ge = 0.3V

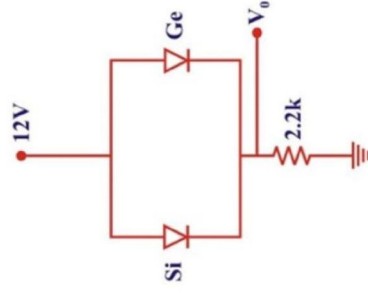

Question.4


Find the value of I_0 and V_0 .

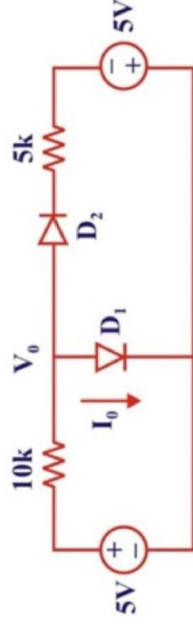

Assume diode to be ideal.

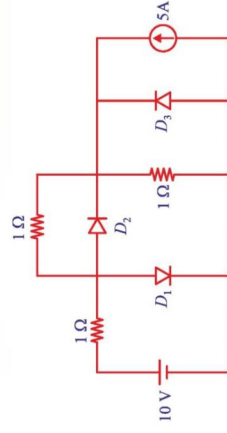Question.5


What are the states of the three ideal diodes of the circuit shown in figure?



- (a) D_1 ON, D_2 OFF, D_3 OFF
- (b) D_1 OFF, D_2 ON, D_3 OFF
- (c) D_1 ON, D_2 OFF, D_3 ON
- (d) D_1 OFF, D_2 ON, D_3 ON

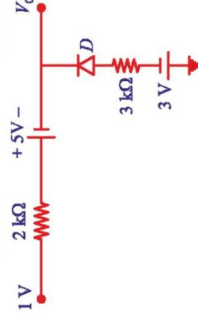Question.6

What is the output voltage V_0 for the circuit shown below assuming an ideal diode?



- (a) $-\frac{18}{5}V$
- (b) $\frac{18}{5}V$
- (c) $-\frac{13}{5}V$
- (d) $\frac{13}{5}V$