

Network Theory

Syllabus :-

(1) Basic concept of Network.

Part 1
↓
(2) Two port Network

(3) Network Theorems

(4) Transient Analysis

Part 2
↓
(5) Sinusoidal Steady State Analysis (SSSA)

(6) Phasor Diagram.

(7) Locus diagram

A.C. Analysis
Part 3
↓
(8) Resonance

(9) Complex power.

(10) Graph Theory (Not in Gate)

(11) Network Synthesis (ESE)

(12) Filter Analysis [simple]

[Faint, illegible text covering the majority of the page, possibly bleed-through from the reverse side.]



→ Network & circuit

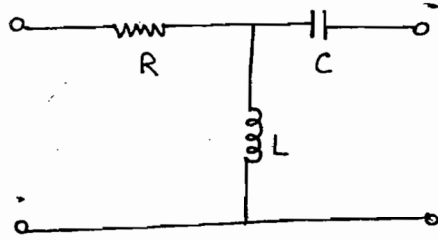


Fig. I N/w. Circuit X
NO

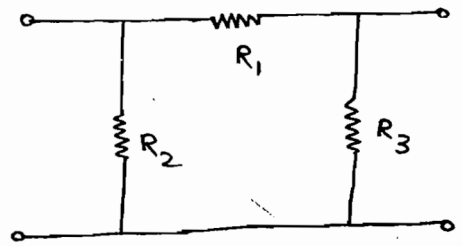


Fig II N/w
Circuit X NO.

- IF any source connected in Network is called circuit.

$$\text{Network} + \text{Source} = \text{circuit}$$

- All circuit is network but all network is not circuit.

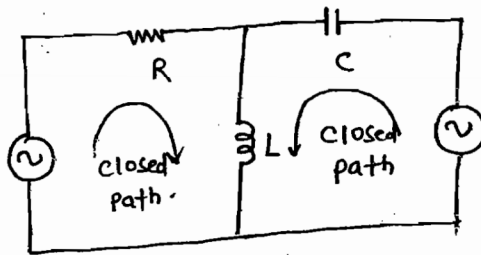


Fig. circuit & network.

circuit :-


- An electric circuit is a closed energized network.

$$\text{circuit} = \text{Network} + \text{Source} + \text{Atleast one closed path.}$$


Types of network element :-

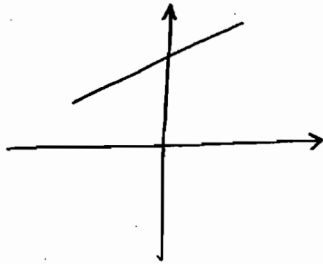(1) Linear and Non Linear Element :-


- characteristics of Linear element always passes through the origin in the form of straight line.



Non Linear

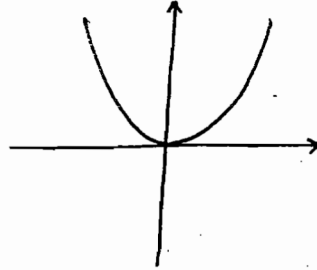

Non-Linear

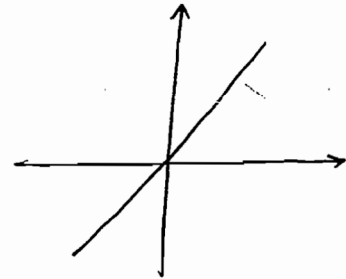


Linear

e.g. of Linear element :-


- Network elements (R, L, C)

e.g. of Non Linear element :-

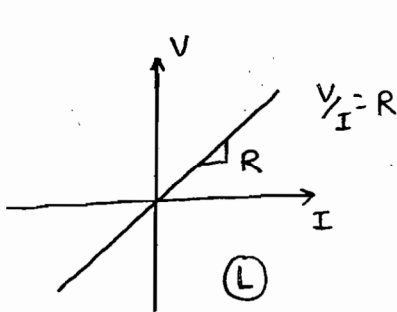
- Device Element (Diode, BJT, JFET, MOSFET)




Fig(a) V I plane

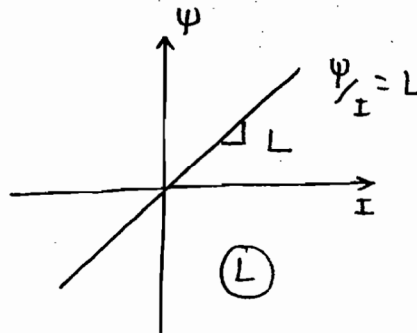


(b) Psi I Plane

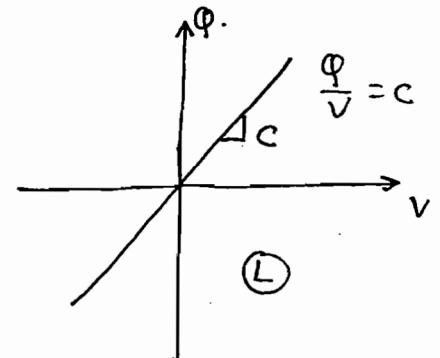


(c) qv plane.

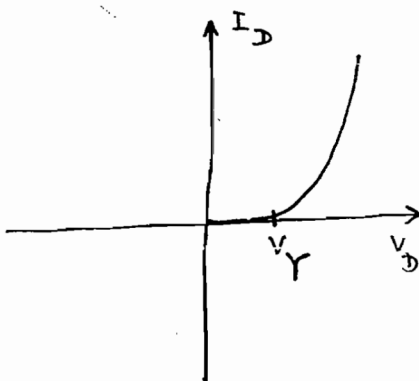

(a) forward Bias c/s of diode

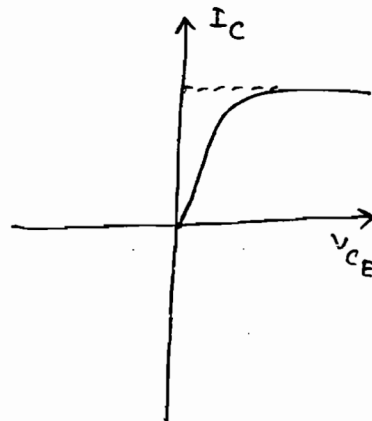

(b) o/p c/s of BJT





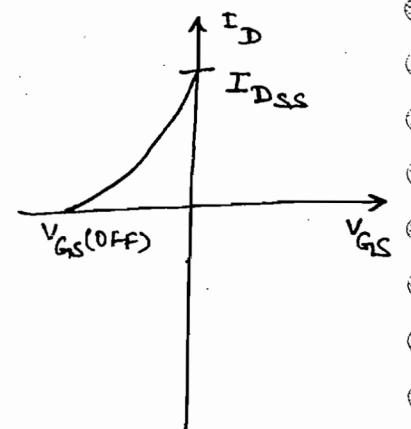


(c) X^{fer} c/s of JFET

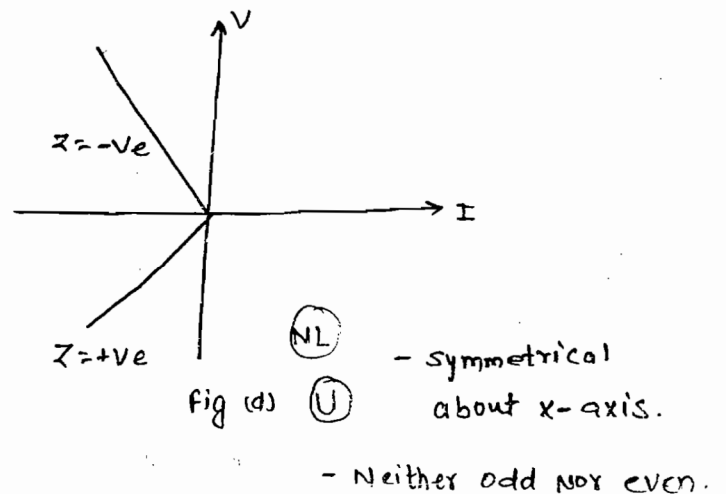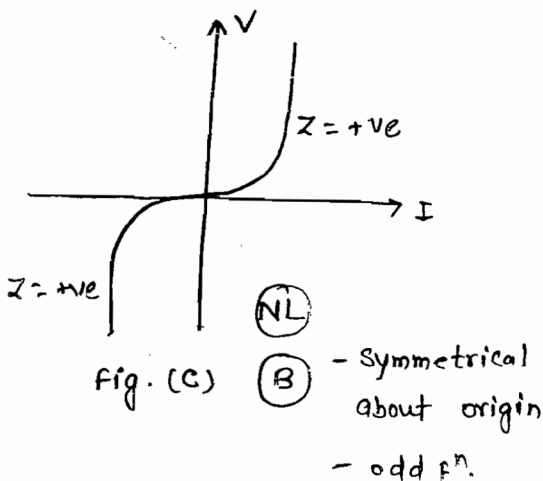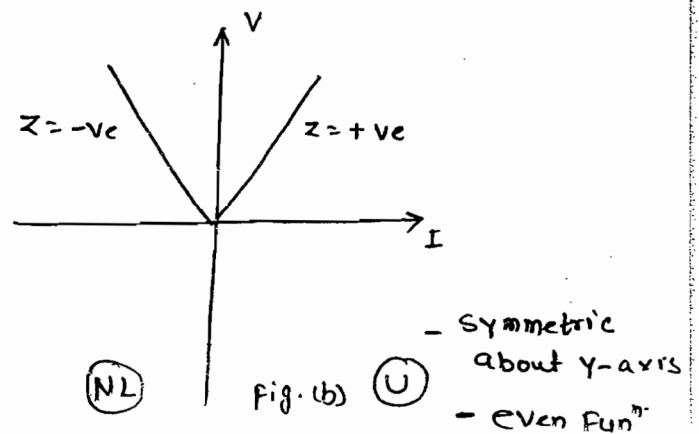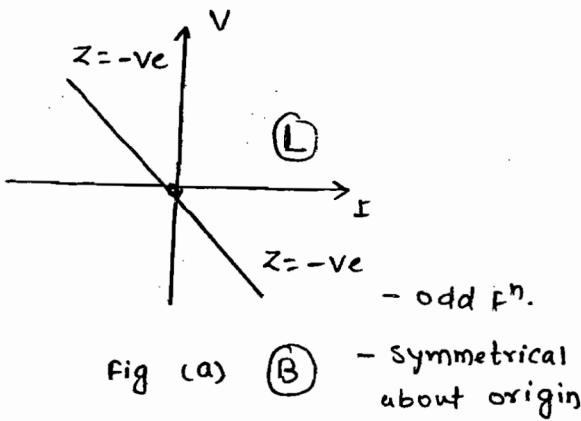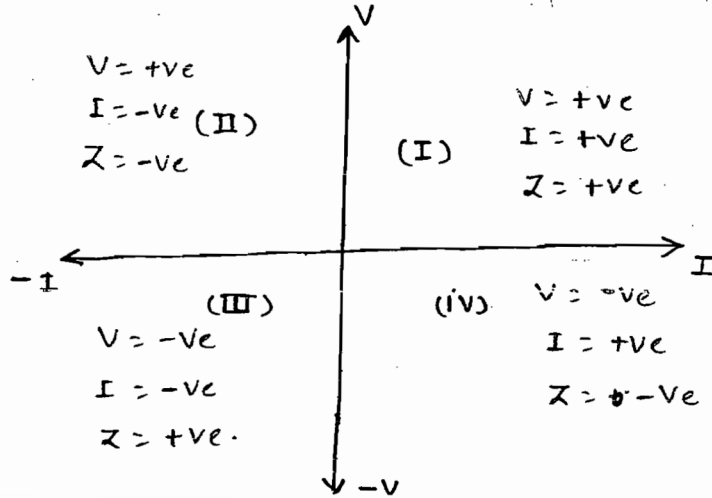(2) Bilateral and unilateral Element

- In case of V-I Plane Characteristics of bilateral element offer Same Impedance through out the Characteristics.
- In case of V-I Plane characteristics of unilateral element offer different Impedance in different region.

*** In case Generalized Plane or any Plane Charac. of bilateral element, is always symmetrical about origin.



<u>N/A element</u>	<u>B/U</u>
R	B
L	B
C	B




<u>Device element</u>	<u>B/U</u>
Diode	U
BJT	U
MOSFET	U

**




- In case of Bilateral element current will flow in both direction.

** - In case of Unilateral element current will flow in only one direction.

- Bilateral element :-

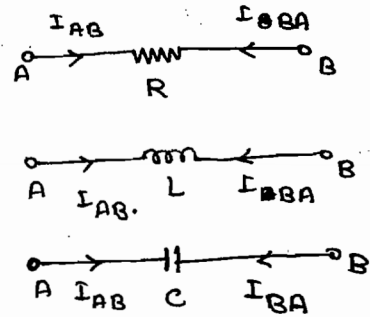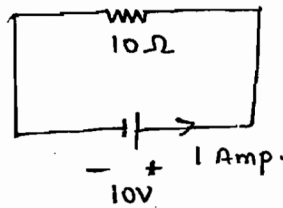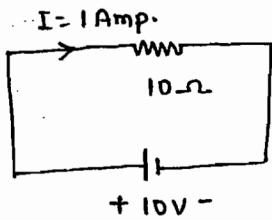

- Unilateral element :-

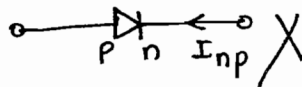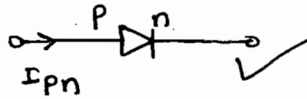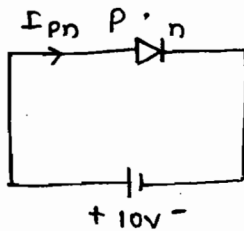

- All Linear element are Bilateral element but reverse is not True.






(3) Passive and Active Elements :-

(i) In case of V-I Plane characteristics of Passive Element always offer positive Impedance. whereas Active Element always offer Negative Impedance.

(ii) Passive Element always absorbs the energy whereas Active Element delivered energy.

(iii) Active Element Control the flow of Energy. whereas Passive Element dissipates or stored the energy.

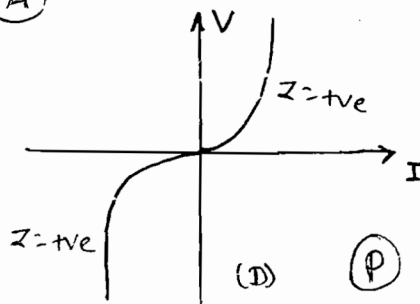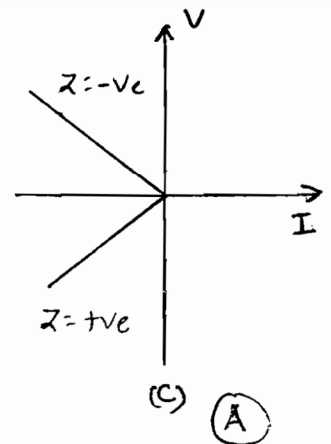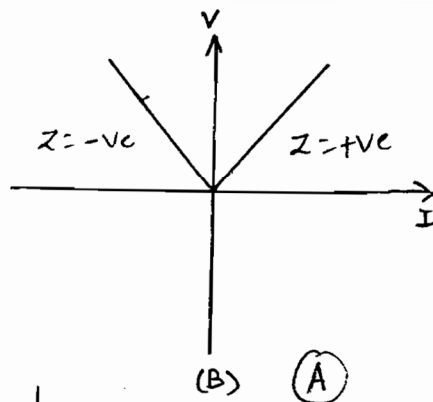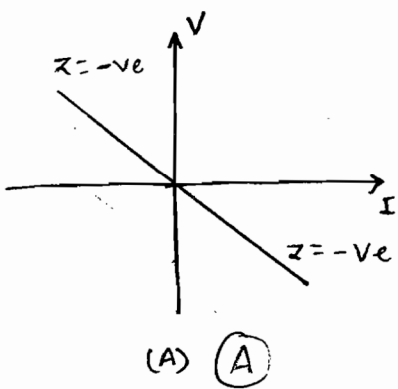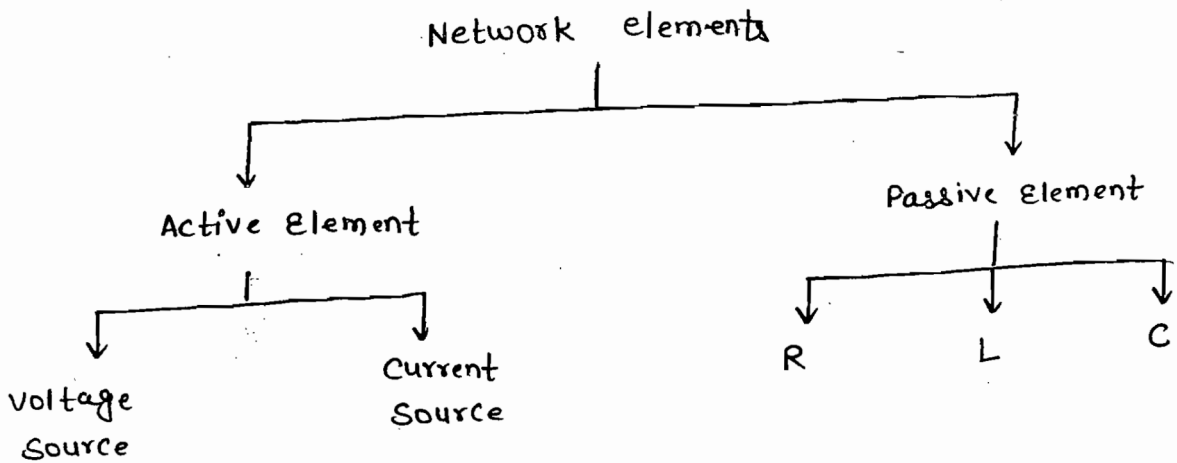(iv) IF element have capability of delevex the energy then it is referred as Active Element.



N/w Element

Passive

Active

R

$$R \geq 0$$

$$R < 0$$

L

$$L \geq 0$$

$$-L < 0$$


C

$$C \geq 0$$

$$C < 0$$

**

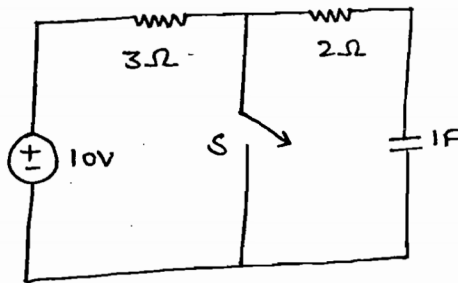- Globally Inductor (L) and capacitor (C) are Passive Element but in case of transient during discharging Inductor and capacitor behaves as Active element.



Condition, At $t > 0$, switch 's' is closed.

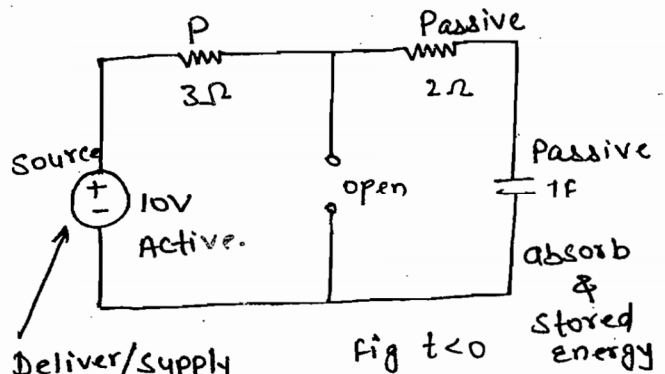


Fig $t < 0$
- source RC N/w
- charging N/w

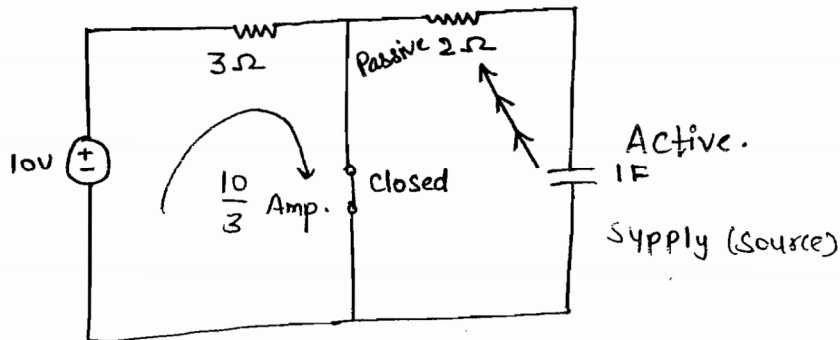


Fig. Source free RC N/w
or
Discharging N/w.

e.g. of Active Element :-

- Voltage Source
- Current source
- Generator
- op- Amp.
- Biased Transistor.

- किसी terminal की Impedance Negative हो सकता है।

$Z = V/I$ Should be Negative also possible.

- The value is Not Negative of R, L, and C element.

(4) Time Invariant and Time variant Element.

- Characteristics of TV element varies with time.

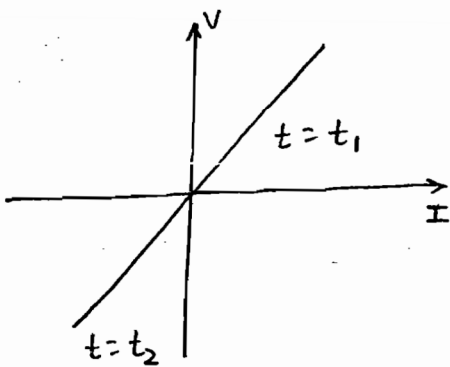


Fig. TIV


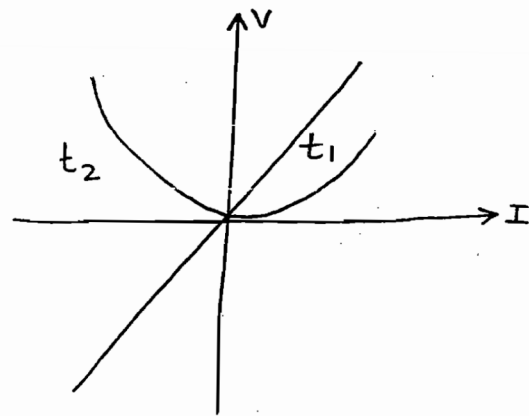


Fig TV


e.g. :-

$$R = R_0(1 - t/T)$$

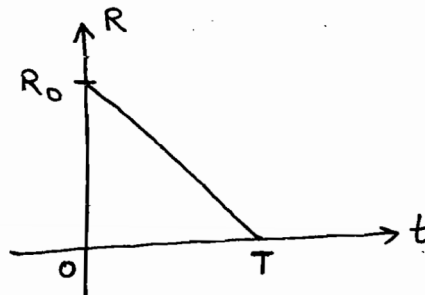

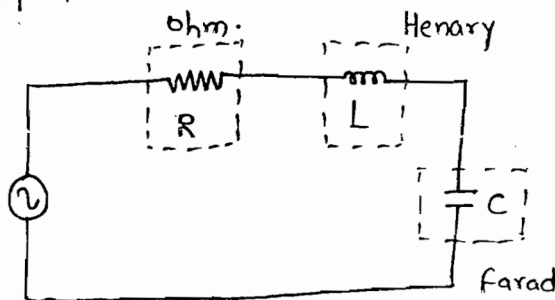
(5) Lumped and Distributed Element.

- Physically Separated Elements in the network is called as Lumped element.



- This N/W are physically Separated.

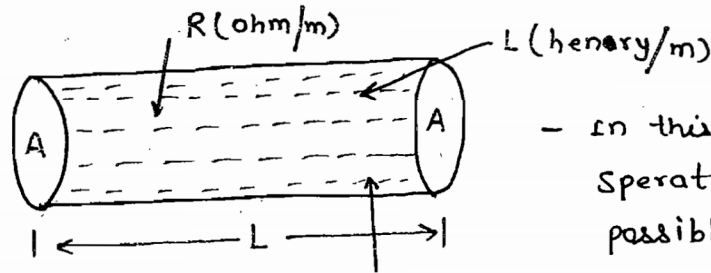- If element distributed along the line or length then it is referred as distributed element.



- in this fig. physically operation is not possible.

Fig. Transmission Line. C [Farad/m]


- ** - Concept of circuit theory is based on Lumped Element
- ** - Concept of field theory is based on distributed element (used in power system)

Conclusion :-

properties of N/w Element (R, L, C) :-

- Linear
- Bilateral
- Passive
- Time Invariant
- Lumped Element

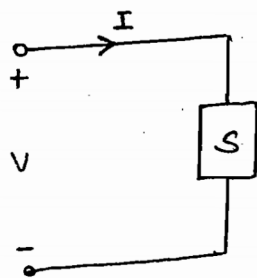Q. 1 Consider the N/w shown in below fig.



The relationship b/w V and I across element S is given by following fig. Identify the behavior of S .

