

HindPhotostat



Hind Photostat & Book Store

Best Quality Classroom Topper Hand Written Notes to Crack GATE, IES, PSU's & Other Government Competitive/ Entrance Exams

MADE EASY

**ELECTRICAL ENGINEERING
NETWORK THEORY
BY-Y.NARESH SIR**

- Theory
- Explanation
- Derivation
- Example
- Shortcuts
- Previous Years Question With Solution

Visit us:-www.hindphotostat.com

Courier Facility All Over India
(DTDC & INDIA POST)
Mob-9311989030



HindPhotostat



EASY, ,ACE, KREATRYX

ESE, GATE, BEST Y KW, / EE
D/E/D DW @

1. KE E /E /
2. E /E /
- D, E /E /
4. / E /E /
- /E DE /KE E /E /
6. KD /

,GATE, TEST @

❖ -W / & D /

❖ GATE

➤ E - ALL E /E / E

➤ ALL sW / YEAR Y /KEW @

W / /K K -

EASY, ,ACE, KREATRYX, GATE /, ,GK

, YADAV, KD D, &K E /KE, -GRAW, D, W KE...K s

/ K @

<p>F230, Lado Sarai New Delhi-110030 Phone: 9311 989 030</p>	<p>Shop No: 46 100 Futa M.G. Rd Near Made Easy Ghitorni, New Delhi-30 Phone:9711475393</p>	<p>F518 Near Kali Maa Mandir Lado Sarai New Delhi-110030 Phone: 9560 163 471</p>	<p>Shop No.7/8 Saidulajab Market Neb Sarai More, Saket, New Delhi-30</p>
--	--	--	--

Website: www.hindPhotostat.com

Contact Us: 9311 989 030

Courier Facility All Over India

(DTDC & INDIA POST)




Topic :-

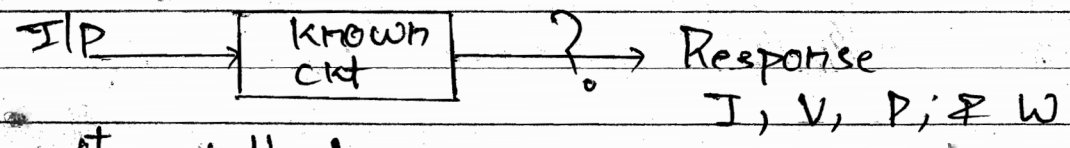- 1.) Basics
- 2.) Steady state analysis
- 3.) Theorems
- 4.) Transients And steady state Analysis
- 5.) Two - Port n/w
- 6.) Magnetic coupled ckt
- 7.) Graph theory
- 8.) Passive filters.

Network Synthesis :- It's consists of finding new ckt which provides a desirable response to a given I/p excitation.

Network Analysis :- It involves the calⁿ of the response of a known ckt to a given I/p.



Circuit variables :-

1) Current - The net out flow of e⁻ / charges across any cross section of a conductor is known as CURRENT.

$$i(t) = \frac{dq}{dt} \quad (\text{or}) \quad I = \frac{Q}{t} \quad \frac{C}{s} \quad (\text{or}) \quad \text{Ampere}$$

Instantaneous (or) dynamic
Steady state



$$i(t) = \frac{dq}{dt}$$

$$I = \frac{Q}{t}$$

$$\frac{dq}{dt} = i(t)$$

$$Q = I \cdot t \text{ coulombs}$$

$$q = \int_{-\infty}^t i(t) dt$$

$$q = \int_{-\infty}^0 i(t) dt + \int_0^t i(t) dt$$


$$q = q(0) + \int_0^t i(t) dt$$

Initial charge

current is varying w.r.t time.

Ques | The current through the capacitor. Determine the charge acquired by the capacitor up to 5 μ s.

Ans |

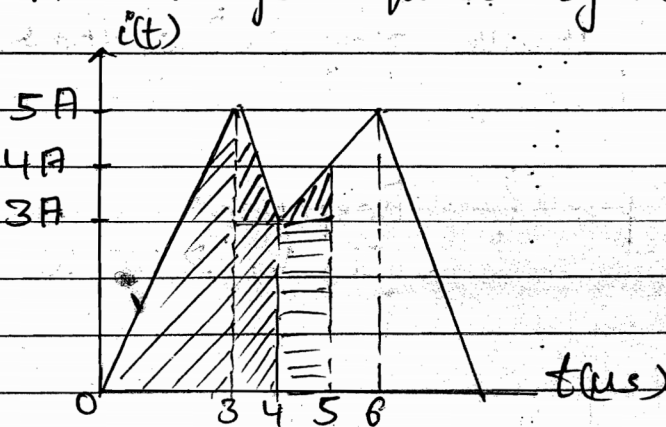

$$q = q(0) + \int_0^5 i(t) dt$$

$$q = \int_0^3 i(t) dt + \int_3^4 i(t) dt + \int_4^5 i(t) dt$$

$$= \frac{1}{2} \times 3 \times 5 + \frac{1}{2} \times 1 \times 2 + 1 \times 3 + \frac{1}{2} \times 1 \times 1 + 1 \times 3$$

$$= 7.5 + 1 + 3 + 0.5 + 3$$

$$q = 15 \mu C$$



2.) V/tg / Electro motive force / Potential :

The work done to move a unit +ve charge from infinity to some reference pt is known as Electro motive force (or) V/tg (or) potential.

$$V = \frac{dw}{dq} \quad (\text{or}) \quad V = \frac{w}{Q} \quad \text{energy per unit charge } J/C \quad (\text{or})$$

$E \rightarrow$ Electric field intensity

$$\boxed{\vec{E} = -\nabla V \quad (\text{or}) \quad E = \frac{V}{r}}$$

\Rightarrow Electric field is negative potential gradient.

3.) Power $\frac{J}{s}$ The rate of change of Energy.


$$P = \frac{dw}{dt} \quad (\text{or}) \quad P = \frac{w}{t} \quad \frac{J}{s} \quad (\text{or}) \quad \text{watts}$$

$$P = \frac{dw}{dq} \cdot \frac{dq}{dt} \quad \boxed{P = V \cdot I}$$


$$\boxed{P = V \cdot i}$$

Power

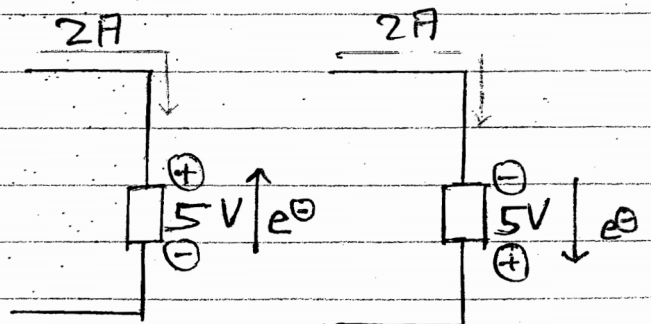- generated (or) delivered
- absorbed (or) consumed



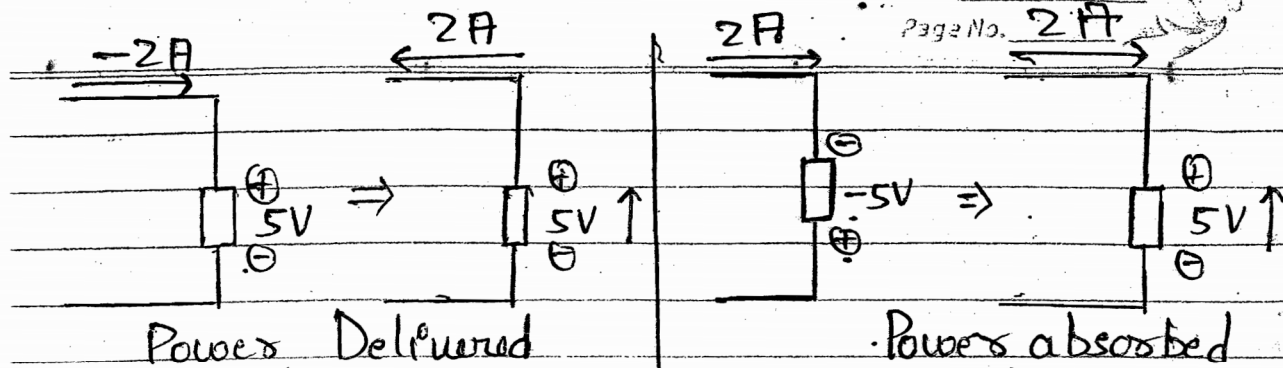\Rightarrow Power absorbed \Rightarrow Power delivered



Power delivered = - Power absorbed.

4.) Energy :- Capacity to do the work.

$$P = \frac{dw}{dt}$$

(or)

$$P = \frac{w}{t}$$

$$\frac{dw}{dt} = P$$

$$w = P \cdot t$$

$$w = \int v \cdot i \cdot dt \text{ Joules}$$


$$w = V \cdot I \cdot t \text{ Joules}$$

constant

varying w.r.t time

Ques] A fully charged mobile phone with a 12V battery is good for 10 min talk time. Assume that during the talk time, the battery delivers a constant current of 2A & it vltg drops linearly from 12V to 10V. How much energy does the battery deliver during this talk time?

Ans

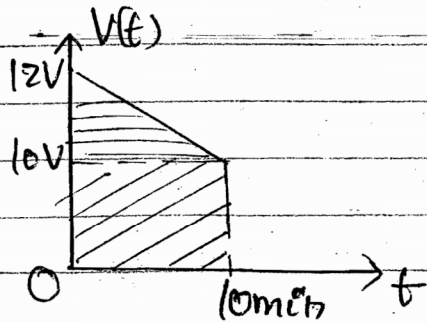

$$w = \int v i dt$$

$$w = (10 \times 2 \times 10) + \frac{1}{2} \times 10 \times 2 \times 2$$


$$\int v dt = 6600 \text{ V-s}$$

$$w = i \int v dt = 2 \times 6600 = 13.2 \text{ kJ}$$

Circuit Elements :

Date _____

Page No. _____

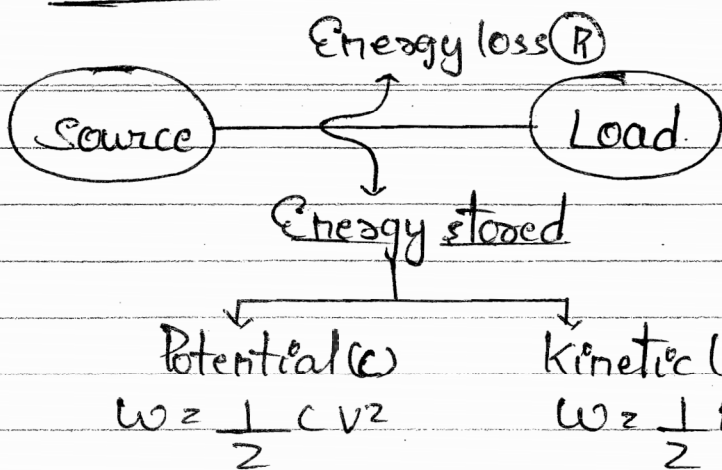

1.) Resistance : $V = IR$
 $I = \frac{V}{R}$

$V \propto I$

$J = \sigma E$

$\frac{I}{a} = \rho \cdot \frac{V}{l}$

J → current density (A/m²)

$I = \rho \frac{V a}{l}$

E → Electric field (E)

$J \propto E$ (Temp. constant)

$I = \frac{V}{R}$

$\vec{J} = \sigma \cdot \vec{E}$ ('σ' is prop. constant)

Ohm's law : At constⁿ tempⁿ the current density (J) ∝ Electric field intensity (E) is known as Pt form of Ohm's law.
 (or)

At constⁿ tempⁿ the current through a con^r to the potential diffⁿ b/w two ends

$R = \frac{V}{I}$ Volt / Amp (or) Ohm (Ω)

Observation : Resistance doesn't depend on current.

If resistance is independent of V/I it is said to be linear.

It is as sent then


Resistance depend upon

- 1) Type of material
- 2) Length
- 3) cross-sectional Area
- 4) Temperature

$$R \propto \frac{l}{a}$$

$$R = \rho \cdot \frac{l}{a}$$

$$\rho = \frac{Ra}{l}$$

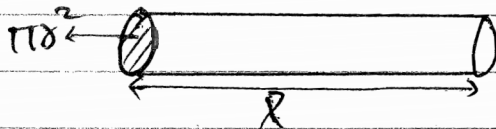

$$\text{Area} = 2\pi r l$$

$$C. \text{ Area} = \pi r^2 = \frac{\pi \cdot d^2}{4}$$

ρ : Specific Resistance
(or)

Resistivity

Units — Ohm-m

	R	T	
Conductors	↑	↑	→ +ve Temp. coefficient
Semi & Insulators	↓	↑	→ -ve Temp. coefficient

α : Temp coefficient
unit : $\frac{1}{^\circ\text{C}}$

$$R_t = R_0 [1 + \alpha(t_1 - t_0)]$$

$$\rho_t = \rho_0 [1 + \alpha(\rho_1 - \rho_0)]$$

Good conductors, an ↑ in tempⁿ will result in ↑ in the resistⁿ level. Consequently, they have a +ve tempⁿ coefficient.

Conductors & insulators, an ↑ in tempⁿ will result in ↓ in the resistⁿ level. Consequently, they have a -ve tempⁿ coefficient.




Ques | Condⁿ length l , Uniform C.S.A a & its R
 If length of the condⁿ is uniformly stretched to $2l$ then the new value of resistance?

solⁿ | $R = \frac{\rho l}{a}$, $R_2 = \frac{\rho_2 l_2}{a_2}$

$$R_2 = \frac{\rho \cdot (2l)}{a/2}$$

$$\boxed{R_2 = 4R}$$

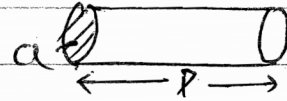

$$\text{Volume 1} = \text{Volume 2}$$

$$a \cdot l = a_2 \cdot l_2$$

$$a \cdot l = a_2 \cdot \frac{l}{2}$$

$$\boxed{a_2 = \frac{a}{2}}$$

Observation :

Res^{ce} depends upon type of material & dimensions but resistivity only depends upon type of material.

Power absorbed by Resistance :

$$P = V \cdot I$$

$$P = IR \cdot I$$

$$\boxed{P = I^2 R} \text{ watts}$$

Current through resistance

$$P = V \cdot I$$

$$P = \frac{V \cdot V}{R} = \frac{V^2}{R}$$

$$\boxed{P = \frac{V^2}{R}}$$

Voltage across Resistance

Energy absorbed by the Resistance :

$$W = P \cdot t$$

$$W = \frac{V^2}{R} \cdot t$$


$$W = I^2 R t$$

$$\underline{H = I^2 R t \text{ Joules}}$$


$$W = \int \frac{V^2}{R} dt$$

(or)


$$W = \int i^2 R dt \text{ Joules}$$

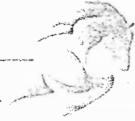

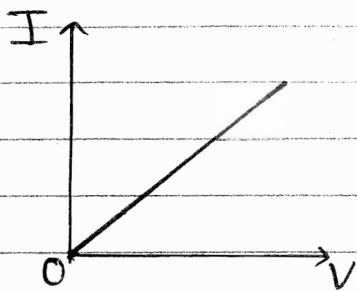Applications of Heaters, Iron box, starters, filters, potentiometers



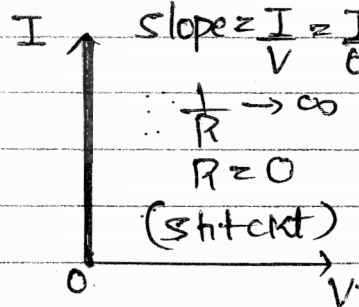
slope = $\frac{I}{V} = \frac{1}{R}$
(Linear)



slope = $\frac{I}{V} = \frac{I}{0} = \infty$
 $\therefore \frac{1}{R} \rightarrow \infty$
 $R = 0$
(short ckt)

$V = 0$
$I = I$
$R = 0$

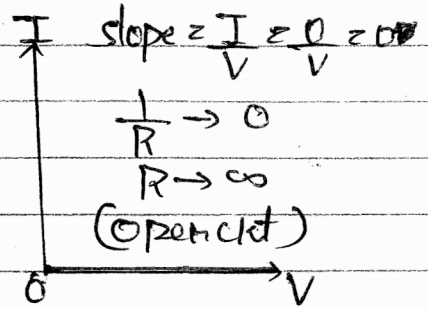→ Non-linear
Ohm's law is not applicable.
→ use KCL



slope = $\frac{I}{V} = \frac{0}{V} = 0$
 $\frac{1}{R} \rightarrow 0$
 $R \rightarrow \infty$
(open ckt)

→ Non-linear
→ Ohm's law not applicable.
→ use KVL
→ open ckt


Limitations of Ohm's Law : Ohm's law is only applicable to linear elements & that to temp is constant.

Ex : Ohm's law is not applicable to

- Semiconductors
- gaseous
- electrolytes
- Iron box.

Conductance (G) : Reciprocal of resistance is known as conductance (G)
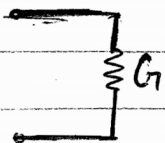
$$G = \frac{1}{R} = \frac{I}{V} \text{ A/V (or) MHO (or) Siemens (S)}$$



→ Reciprocal of Resistivity is known as conductivity (σ)

$$\sigma = \frac{1}{\rho} = \frac{1}{\Omega \cdot m} \text{ Siemens/m}$$