



VISIT US @ www.hindphotostate.com

MADE EASY , IES MASTER , ACE ACADEMY , KREATRYX

ESE , GATE, PSU BEST QUALITY TOPPER HAND WRITTEN NOTES

MINIMUM PRICE AVAILABLE @ OUR WEBSITE

- | | |
|--------------------------------|---------------------------|
| 1. ELECTRONICS ENGINEERING | 2. ELECTRICAL ENGINEERING |
| 3. MECHANICAL ENGINEERING | 4. CIVIL ENGINEERING |
| 5. INSTRUMENTATION ENGINEERING | 6. COMPUTER SCIENCE |

IES , GATE , PSU TEST SERIES AVAILABLE @ OUR WEBSITE

❖ IES –PRELIMS & MAINS

❖ GATE

➤ **NOTE;- ALL ENGINEERING BRANCHS**

➤ **ALL PSUs PREVIOUS YEAR QUESTION PAPER @ OUR WEBSITE**

PUBLICATIONS BOOKS -

MADE EASY , IES MASTER , ACE ACADEMY , KREATRYX , GATE ACADEMY , ARIHANT , GK

RAKESH YADAV , KD CAMPUS , FOUNDATION , MC –GRAW HILL (TMH) , PEARSON...OTHERS

HEAVY DISCOUNTS BOOKS AVAILABLE @ OUR WEBSITE

F230, Lado Sarai New Delhi-110030 Phone: 9311 989 030	Shop No: 46 100 Futa M.G. Rd Near Made Easy Ghitorni, New Delhi- 30 Phone: 8595 382 884	F518 Near Kali Maa Mandir Lado Sarai New Delhi-110030 Phone: 9560 163 471	Shop No.7/8 Saidulajab Market Neb Sarai More, Saket, New Delhi-30 Phone: 9654 353 111
---	--	---	---

Website: www.hindPhotostate.com

Contact Us: 9311 989 030

Courier Facility All Over India

(DTDC & INDIA POST)

Power System -


Power systems ?

1. Power system Generation
2. Transmission and distribution
 - ↳ Tx-line constants
 - ↳ Tx-line performance.
 - Wave nature
 - surges.
 - voltage sential
 - V_G cable.
 - insulators.
 - corona
 - Distribution Sy
 - HVDC
3. Fault Analysis → Geometrical component
 - sequence n/w
 - symmetrical fault
 - unsymmetrical fault
 - 7 bus based fault
4. P.S. stability → steady state stability
Transient stability
5. Protection →
6. load flow
7. economic dispatch (IES)

Weightage → (8-10) marks.

Books : JB Gupta
Cl. Wadhwa.


Introduction to Power system :-

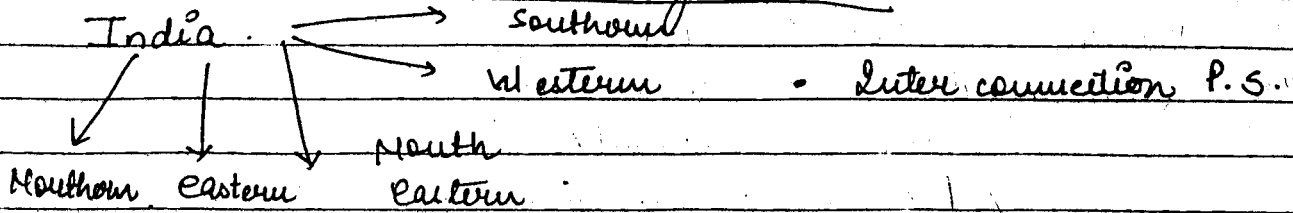

* India has 5 regional grids which are inter connected with each other in order to supply power from energy surplus areas to energy deficit areas.

* In inter connected P.S there is more efficient utilization of energy but at the same time there is a risk of fault propagation from one part of P.S to the other.

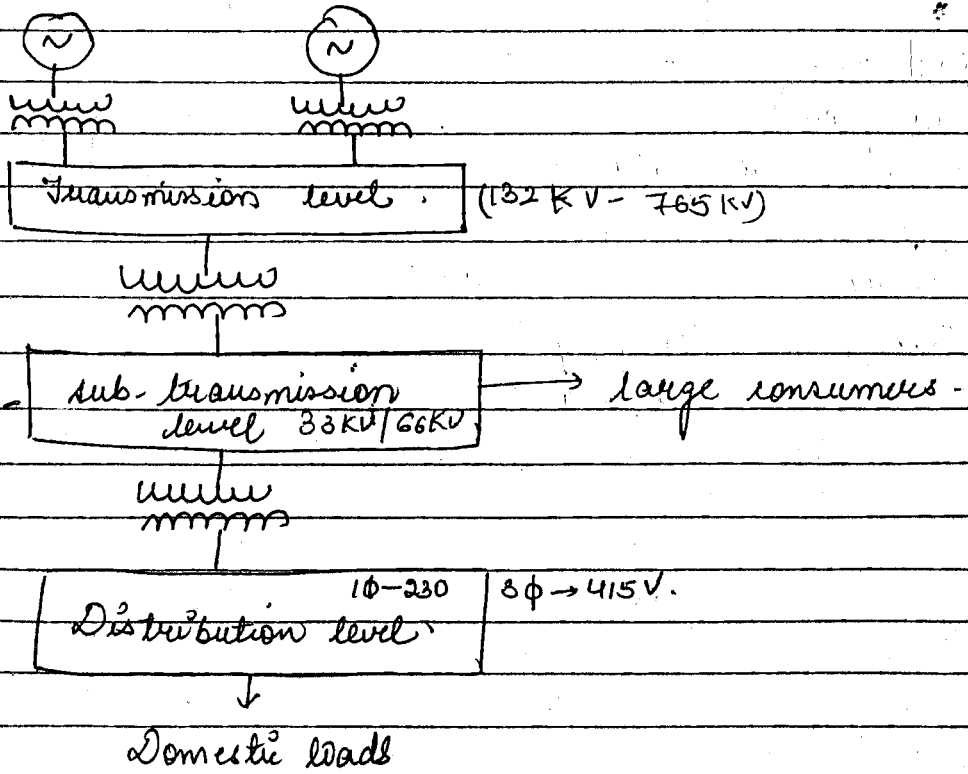* So, we realize the concept of smart grid in which load scheduling is automatic but there must be effective protection by developing communication b/w the substation.




Objectives of power system?

- ⇒ cost of per unit energy should be minimized. (per kWh).
 - ↳ economic generation
 - ↳ economic load dispatch \therefore (load sharing)
 - ↳ power generation method.
- ⇒ effective protection against fault.
 - ↳ fault analysis
 - ↳ switch gear and protection.
- ⇒ rated v/g and frequency must be supplied to consumer.
 - ↳ automatic v/g control.
 - ↳ load freq. control. \rightarrow speed governor.
- ⇒ power system must be stable.
 - ↳ power s/m stability
- ⇒ reliable power supply to consumer.
 - ↳ Transmission and distribution


Per unit System?

single line diagram?

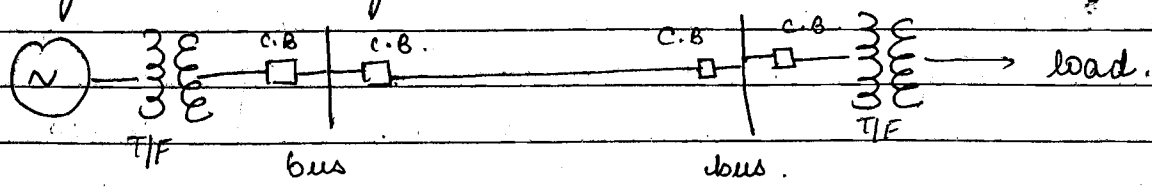


actual skt?

1. Generator.


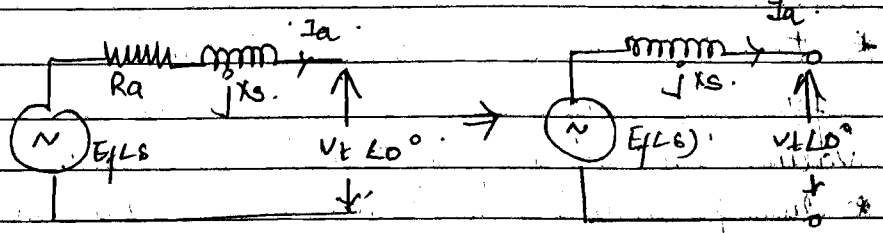


2. Transformer.

primary \Rightarrow

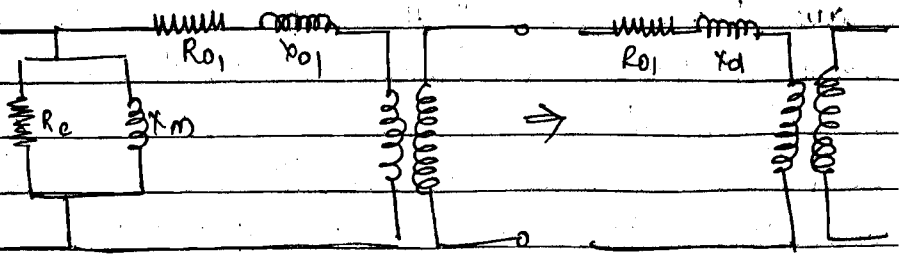


\Rightarrow shunt branch ignored.

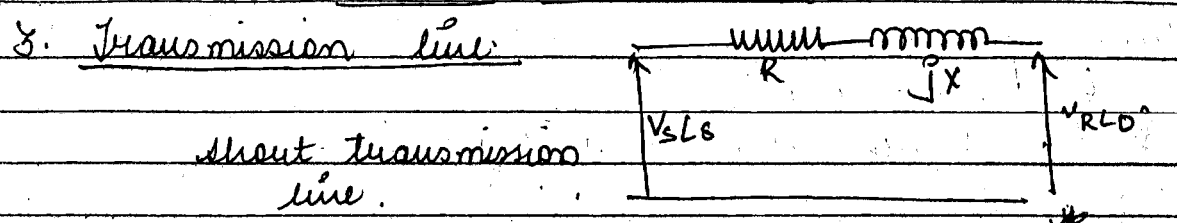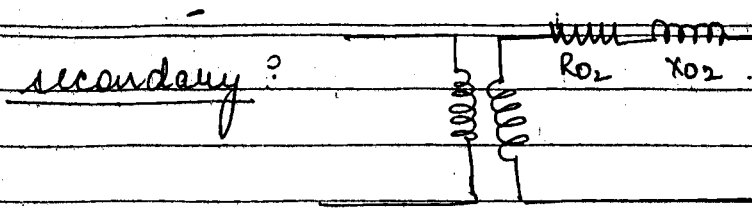

* the loads are generally modelled as constant power load where the real and reactive power of the load is specified.


Overall circuit

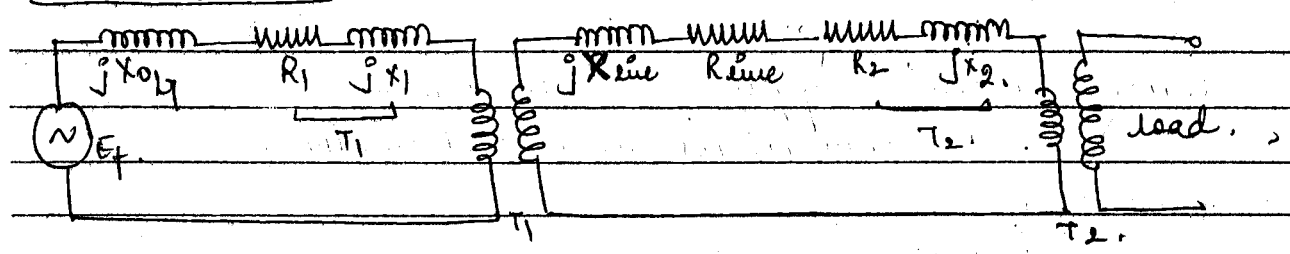

The eq circuit of P.S. is complicated due to multiple component being present but single line diagram is a specified representation which is easily readable.

* to analyze the given circuit, we need 3 KVL eq for 3 loops and hence analysis in absolute values is complicated.

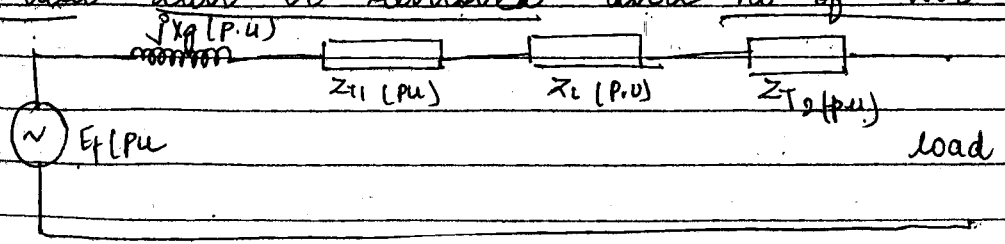
* In pu unit system, the pu values of all quantities are same on both sides of T once so the turns ratio can be removed and no of KVL eq reduces.



To convert a P.S in pu per unit? -

we must use a universal base so that results are consistent with the actual values.

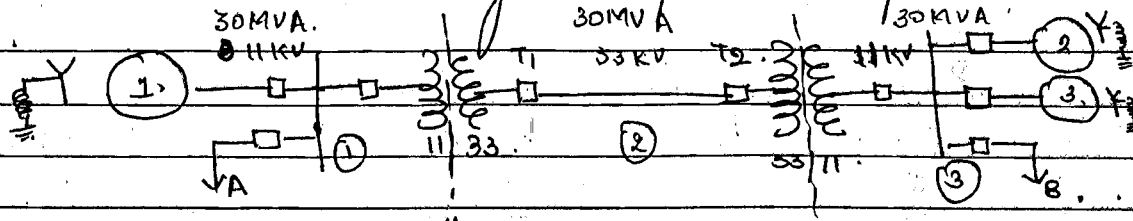Q Draw the reactance diagram for the p.s shown in fig.



$$G_1 :- 30 \text{ MVA}, 11 \text{ kV}, X'' = 1.6 \Omega$$

$$G_2 :- 15 \text{ MVA}, 6.6 \text{ kV}, X'' = 1.2 \Omega$$

$$G_3 :- 25 \text{ MVA}, 6.6 \text{ kV}, X'' = 0.56 \Omega$$

$$T_1 \& T_2 :- 15 \text{ MVA}, 33/11 \text{ kV}, X = 15.2 \Omega / \phi \text{ on 11 kV side.}$$

$$\text{Trans. line} \rightarrow 20.5 \Omega / \phi$$

P Base = 30 MVA. [power base will be same]

* While choosing the base, kVA base remain same for the entire p.s. but we only choose V/g base for 1 section and then scaled it on the basis of turns ratio or transformation ratio of X-men.

$$X_1 \text{ pu} :- \frac{1.6}{(11^2/30)} = 0.396$$


$$X_{T1} (\text{pu}) = \frac{15.2}{(33^2/30)} = 0.4187$$

$$X_{T \text{ line}} = \frac{20.5}{33^2/30} = 0.5647$$


$$X_{T2} (\text{pu}) = \frac{15.2}{33^2/30} = 0.418$$

$$X_2 = \frac{1.2}{(11^2/30)} = 0.297$$

$$X_3 = \frac{0.56}{11^2/30} = 0.138$$

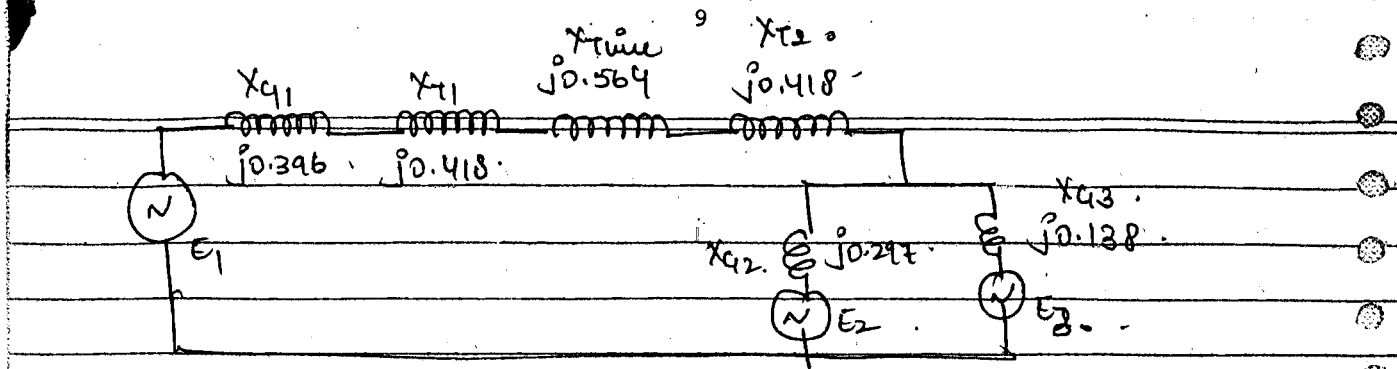

2. Draw the impedance diagram

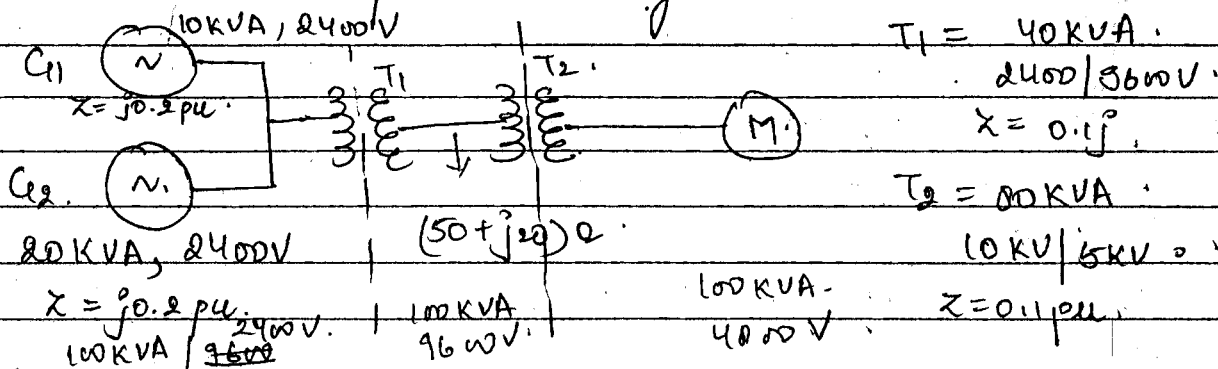

Choose base for generator 1 as
2400V / 100 KVA.

M = 25 KVA, 4KV
X = j0.3 pu.

Common Base = 100 KVA, 2400V.

$$X_{G1} = j0.2 \times \left(\frac{100}{10}\right) \times \frac{2400}{2400} = j0.2$$


$$X_{G2} = j0.2 \times \left(\frac{100}{20}\right) \times 7 = j1$$

$$X_{T1} = j0.1 \times \left(\frac{100}{40}\right) = 0.25 j$$

$$Z_L = \frac{50 + j20}{\frac{5600^2}{100 \times 10^3}} \Rightarrow 0.054 + j0.217$$

$$X_{T2} = j0.1 \times \left(\frac{100}{80}\right) \times \left(\frac{5000}{4000}\right)^2 = j0.135$$
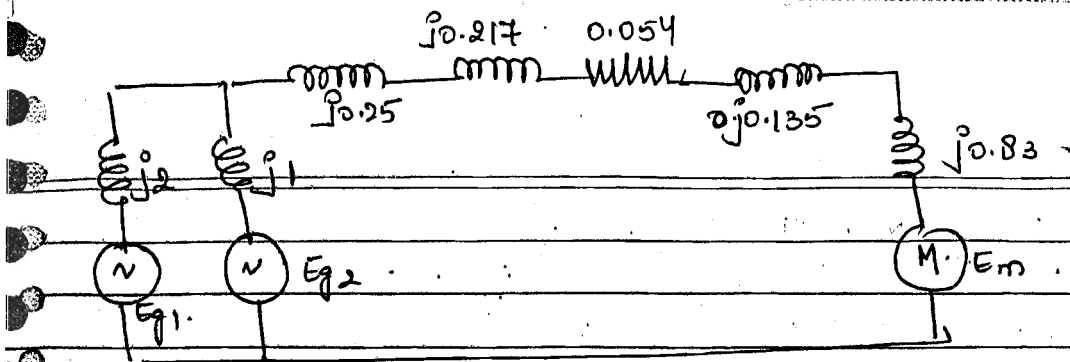
$$X_M = 0.3 j \times \left(\frac{100}{25}\right) \times \left(\frac{4000}{4000}\right)^2 = 0.833 j$$



A 3 bus system is given as shown in fig

- G_1 : 50 MVA, 13.8 KV, $X'' = 0.15$ pu
- G_2 : 40 MVA, 13.2 KV, $X'' = 0.2$ pu
- G_3 : 30 MVA, 11 KV, $X'' = 0.25$ pu
- T-1: 45 MVA, 11 KV Δ / 110 KV Y , $X = 0.1$ pu


T-2 = 25 MVA, 12.5 KV Δ / 115 KV Y , $X = 0.15$ pu

T-3 = 40 MVA, 12.5 KV Δ / 115 KV Y , $X = 0.1$ pu

line X : are shown in fig

Choose base values at 50 MVA, and 13.8 KV on

G_1 side.

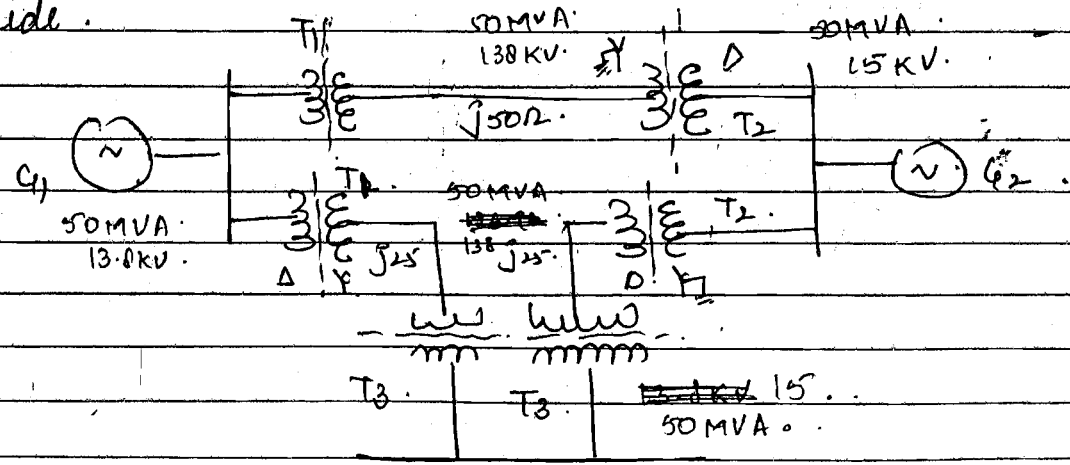

$$G_1 = 0.15 \times \left(\frac{50}{50}\right) \times \left(\frac{13.8}{13.8}\right)^2 = 0.15 \text{ pu}$$

$$G_2 = 0.2 \times \left(\frac{50}{40}\right) \times \left(\frac{13.2}{15}\right)^2 = 0.1936 \text{ pu}$$

$$G_3 = 0.25 \times \left(\frac{50}{30}\right) \times \left(\frac{11}{15}\right)^2 = 0.224 \text{ pu}$$


$$T_1 = 0.1 \times \left(\frac{50}{45}\right) \times \left(\frac{11}{13.8}\right)^2 = 0.0705$$

$$T_2 = 0.15 \times \left(\frac{50}{25}\right) \times \left(\frac{12.5}{15}\right)^2 = 0.208$$

$$X_{T3} = 0.1 \times \left(\frac{50}{40}\right) \times \left(\frac{12.5}{15}\right)^2 = \cancel{0.006} \cdot 0.0006$$

$$T_4 = 50 / (138^2 / 50) = 0.131$$

$$T_{L2} = T_{L3} = 0.065$$

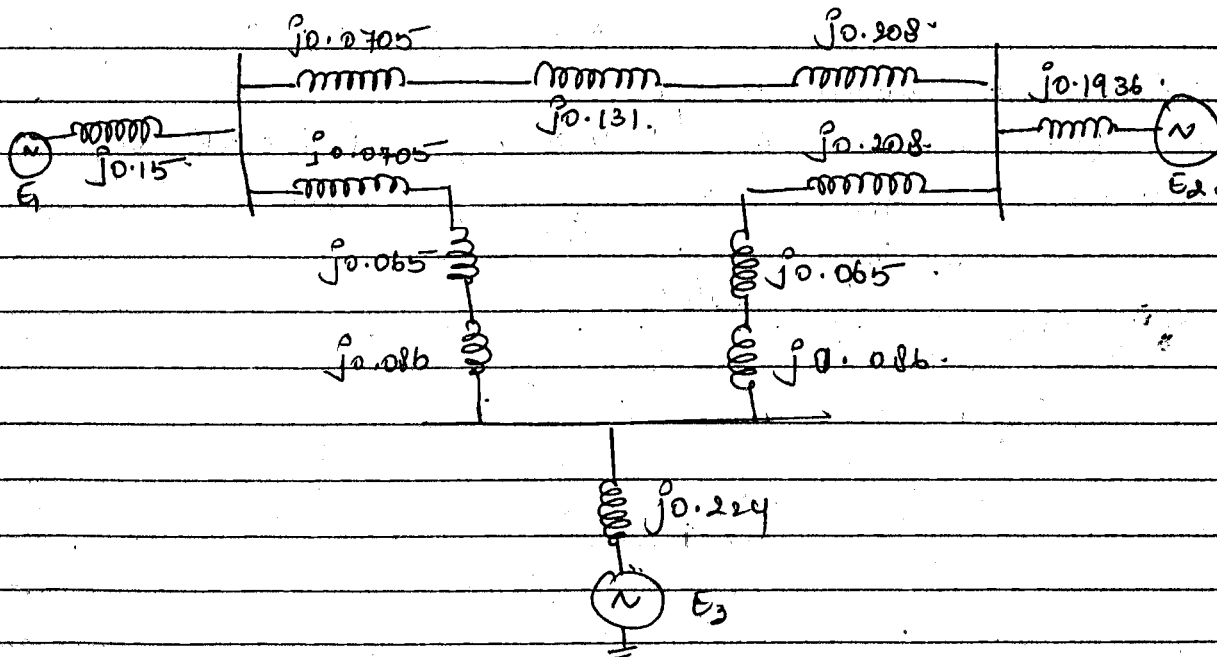

Q A 220 MVA, 66 kV, 3 ϕ generator has $X' = 30\%$, the G is connected to 3 Motors through a π -mission line and transformers as shown in fig, the motors have rated inputs of 60 MVA, 40 MVA, 100 MVA with 40% sub-transient reactance, the ratings of π -mission are shown in fig. draw the reactance diagram assuming π -mission line reactance = (100 Ω)