
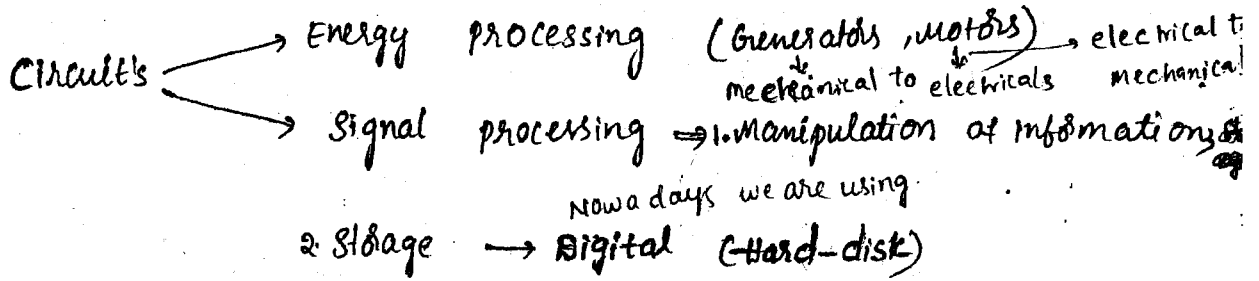


ANALOG CIRCUITS → Gain by a factor.


9:00 AM to 6 PM

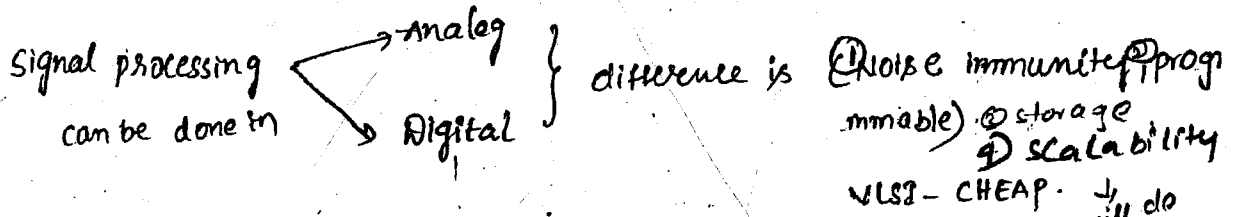

(manipulation, communication)



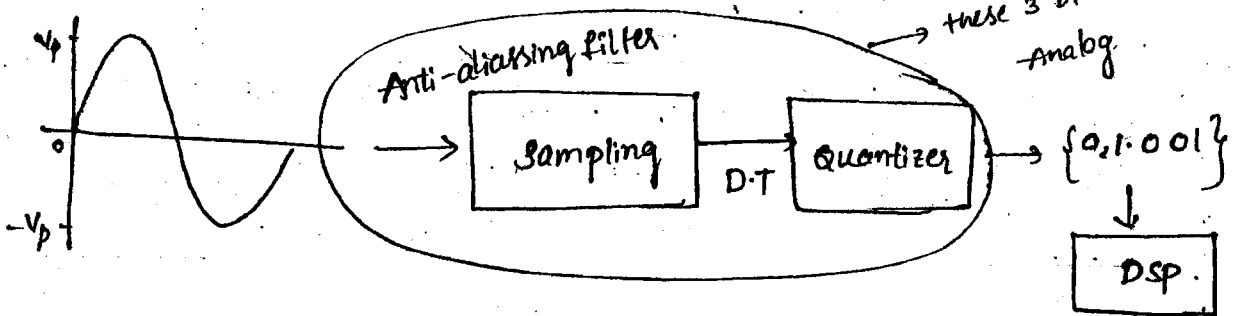All naturally occurring signals are Analog.



Real signal → Time limited → Infinite Band limited

Digital Circuits:- Logic gate is the building block's

Analog Circuits:- op-amp is the building block.


Designing using op-amp both are different

1. op-amp as a building block (Ideal op-amp)



2. Inside op-amp (100-50 Transistors (Tx))

Diode → BJT → Amplifiers using Tx

Real ← we will set inside op-amp

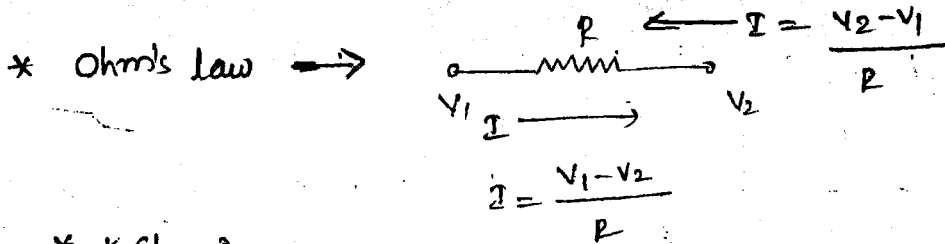

* KCL \rightarrow

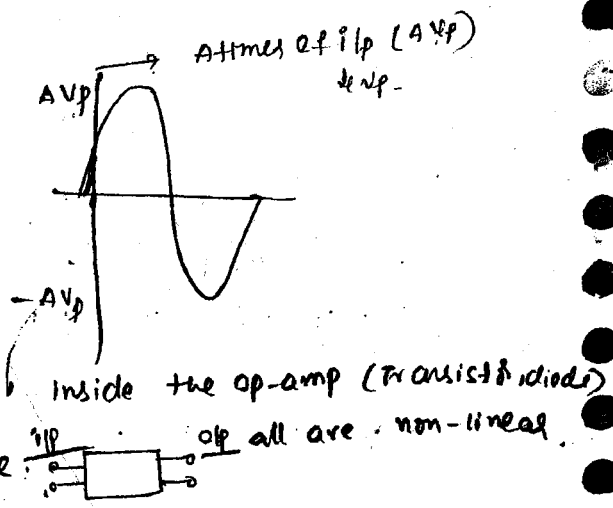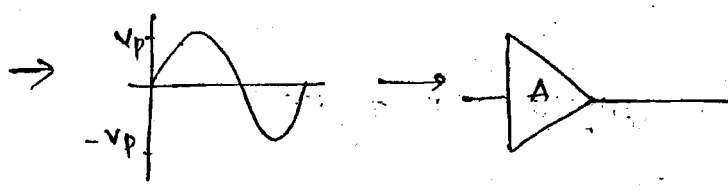


Voltage Amplifier:-

$V_o = AV_i \rightarrow$ linear

\rightarrow Opamp is a two terminal device

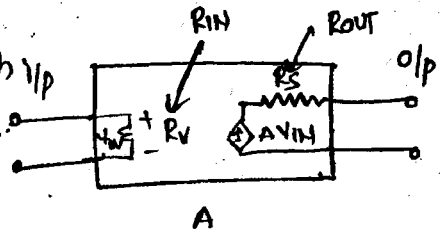\Rightarrow Voltmeter
 shunt resistance $\rightarrow \infty$
 series resistance $\rightarrow 0$



Voltage Amplifier ($i/p \rightarrow V$, $o/p \rightarrow V$)

$V_o = AV_{in}$
 \uparrow
 High

V_{in} - voltage measured by voltmeter at the i/p.
 R_v - resistance measured by the voltmeter.

\rightarrow The i/p port of the v-amplifier is measuring the applied i/p voltage \Rightarrow i/p port of the v-amplifier is like a voltmeter.

Here i/p voltage controlling the o/p voltage.

\rightarrow The o/p port is the like a VCVS.
 at i/p side we have only \rightarrow 1 resist $\rightarrow R_{in} = R_v$ (large) because it is in || (i.e. ideal voltmeter has ∞ resist) \rightarrow c.s.d.
 \rightarrow here also only one resist $\rightarrow R_{out} = R_s$ (small) because it is series with voltage. (i.e. I_{in} vs I_{out} vs resistance value $\rightarrow \infty$)


Current Amplifier:-

every ammeter having resistance.

\rightarrow The i/p to the current amplifier is (i/p) \rightarrow current
 o/p \rightarrow current

\Rightarrow ammeter
 shunt resist = less
 series resist = high $\rightarrow \infty$

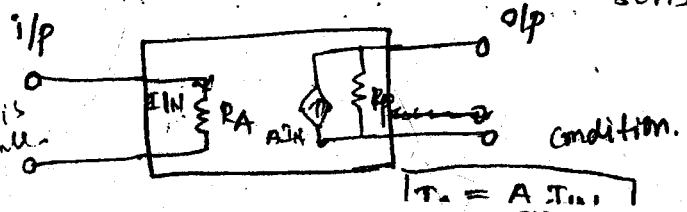Here i/p current controlling the o/p current
 \rightarrow ideal ammeter module zero resist




condition.

Here o/p current depends on the i/p current

$$R_{IN} = R_A \text{ (small)}$$

$$R_{OUT} = R_P \text{ (large)}$$

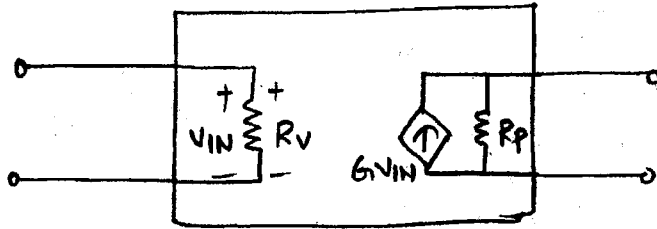3. Transconductance amplifier; - (VCCS) → here o/p is current so it is current source.




$$I_O = G V_{IN}$$

$$R_{IN} = R_V \text{ (large)}$$

$$R_{OUT} = R_P \text{ (large)}$$

i/p	o/p
→ V	V
→ I	I
→ V	I ✓
→ I	V

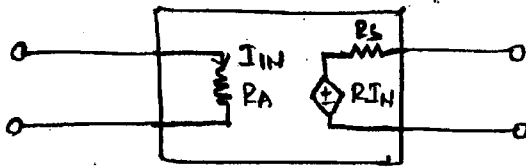4. Trans resistance amplifier; - (CCVS) → here o/p is voltage so it is voltage source



$$V_O = R_{IN} I_{IN}$$

$$R_{IN} = R_A \text{ (small)}$$


$$R_{OUT} = R_S \text{ (small)}$$

BROWSERS CAFE

Broadband Internet

Shop No. 45, Sarva Lakshmi Complex,
TINPOUNDRY HYDRABAD ✓
Ph: 4740992 Cell: 9949 9949

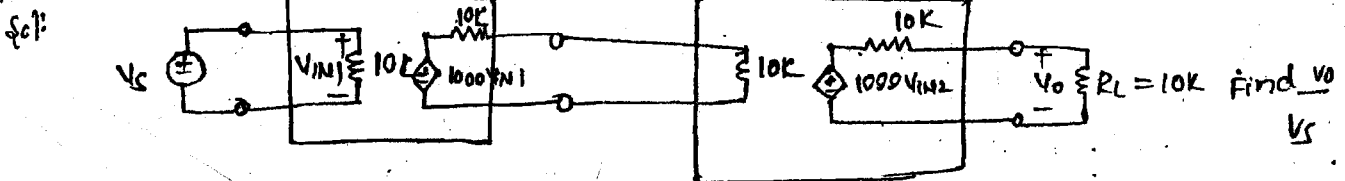* 2 Identical voltage amplifiers each with gain = 1000, $R_{IN} = 10K$, $R_{OUT} = 10K$ are connected in cascade. Find the overall voltage gain if $R_L = 10K$.





$$V_{IN1} = V_s$$


$$V_{IN2} = \frac{1000 V_{IN1}}{2} = 500 V_s$$

$$V_O = 1000 V_{IN2} = 500 \times 500 V_s$$

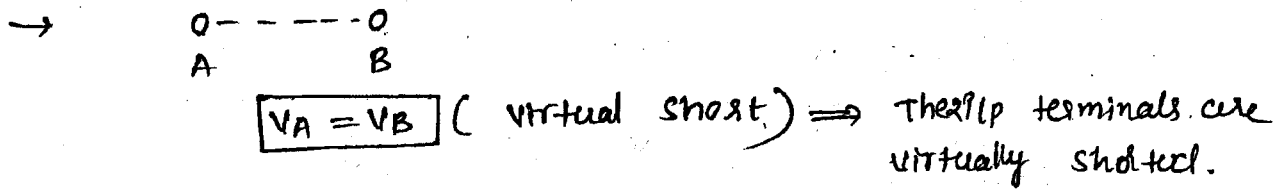
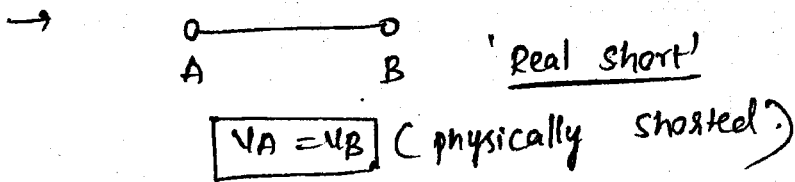
$$\frac{V_O}{V_s} = 500 \times 500 = 250K$$



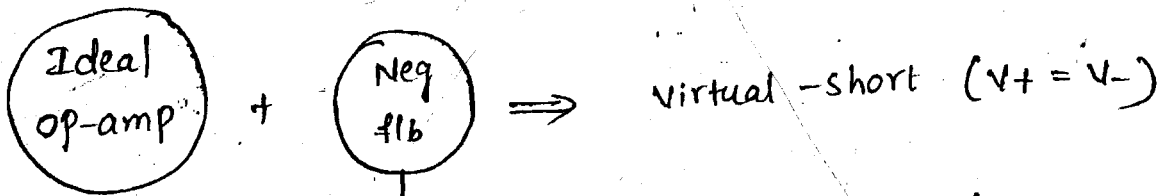⇒ op connected to $-$ input terminal ⇒ op-amp is in negative fb.



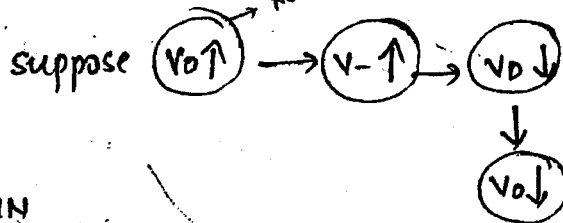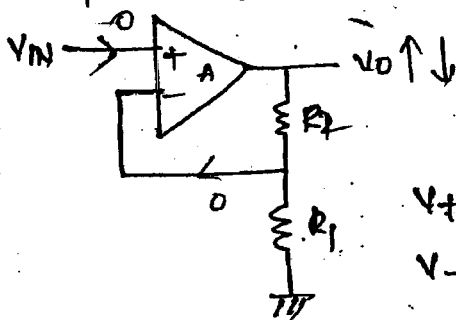*** op (V_o) is connected to $-$ ve terminal.
 & $-$ ve feedback op-amp stability: $+ve$ fb - op (V_o) is connected to $+ve$ terminal.
 No Res for unknown reason.



$$V_+ = V_{IN}$$


$$V_- = \frac{V_o \cdot R_1}{R_1 + R_2}$$

$$V_D = A V_D \downarrow$$

$$V_D = V_+ - V_- \uparrow$$

In neg fb ⇒ $V_o \rightarrow$ finite
 ⊕
 stable.

& $+ve$ feedback op-amp stability:-

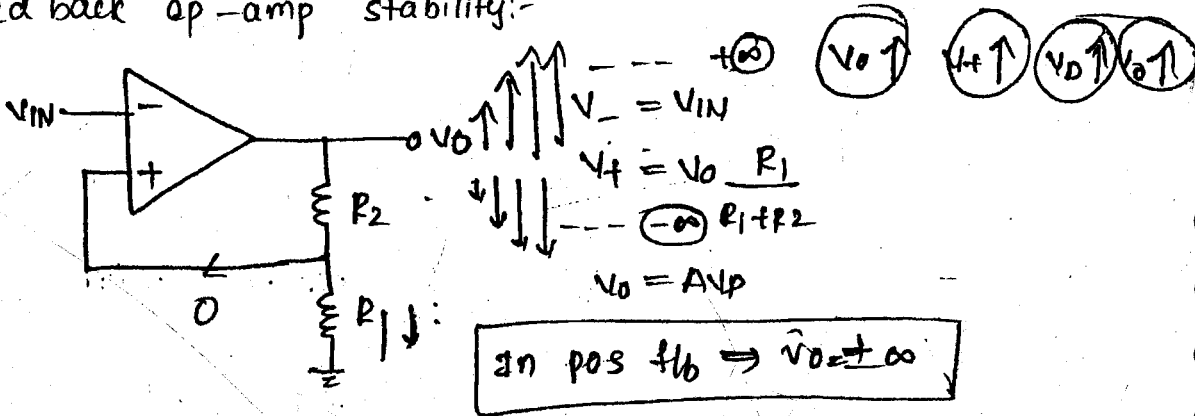

(checking virtual-short condition) for Ideal op-amp in neg f/b:-

$V_o \rightarrow F$ $F = \text{finite}$
 $A \rightarrow I$ $I = \text{infinite}$

$V_D = \frac{V_o}{A} = \frac{F}{I} = 0$

we know that

$V_D = V_+ - V_-$

$V_+ - V_- = 0$

$V_+ = V_-$ ← virtual short

$V_o = A V_D$

$\lim_{x \rightarrow 0} \sin x \cdot \frac{1}{x} \rightarrow 0 \cdot \infty = 1$
↓ ↓
small large

For Ideal op-amp in +ve f/b:-


$V_o \rightarrow I$
 $A \rightarrow I$

$V_+ \neq V_-$

$V_D = \frac{V_o}{A} = \frac{I}{I} \neq 0$

Non-Inverting amplifier:-

→

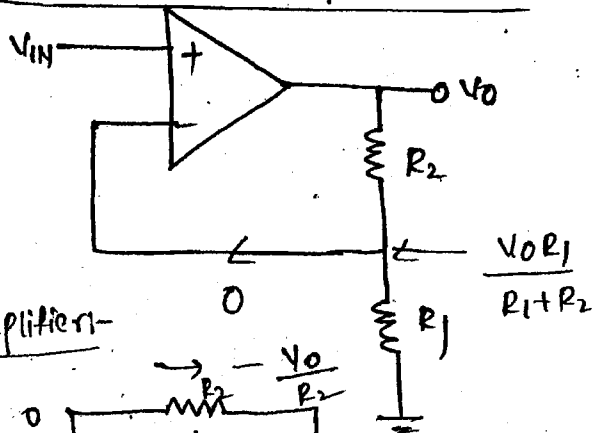


$V_+ = V_-$
 $V_{IN} = \frac{V_o R_1}{R_1 + R_2}$

$\frac{V_o}{V_{IN}} = 1 + \frac{R_1}{R_2}$

$V_o = (+ve \text{ number}) V_{IN}$
 Non-inverting op-amp
 V_o & V_{IN} have the same sign
 (same phase)

Inverting amplifier:-

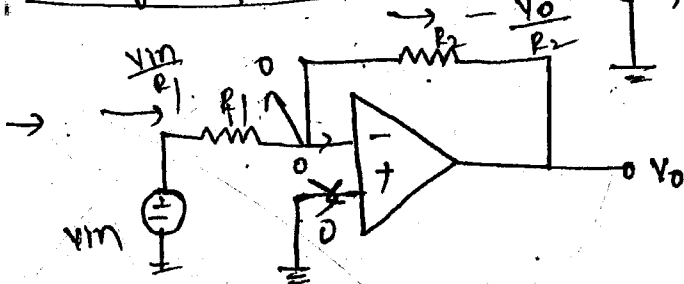

$\frac{V_{IN}}{R_1} = -\frac{V_o}{R_2}$

$\frac{V_o}{V_{IN}} = -\frac{R_2}{R_1}$
 $V_o = \left(-\frac{R_2}{R_1}\right) V_{IN}$
ve
iso
 V_o & V_{IN} are 180° out