

HindPhotostat



Hind Photostat & Book Store

Best Quality Classroom Topper Hand Written Notes to Crack GATE, IES, PSU's & Other Government Competitive/ Entrance Exams

MADE EASY ELECTRONICS ENGINEERING Digital Electronics By- M.V.R.Shastri Sir

- Theory
- Explanation
- Derivation
- Example
- Shortcuts
- Previous Years Question With Solution


Visit us:-www.hindphotostat.com

**Courier Facility All Over India
(DTDC & INDIA POST)
Mob-9311989030**


BOOLEAN ALGEBRA

Logic gates

AND gate:-

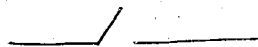


Switch

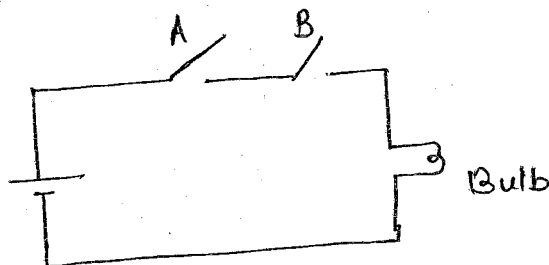

Bulb glows when both switches are ON.

Truth table:-

A	B	
0	0	0
0	1	0
1	0	0
1	1	1

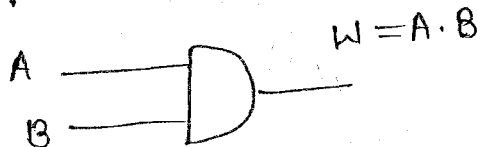

Hence from ckt it is clear that when switches are connected in series then results/as AND gate

AND gate also called as series switch.

Set theory **

$$X = \{2, 3, 5\}$$



$$Y = \{3, 6, 7\}$$

$$(X \cap Y) = \{3\}$$

Intersection

In set theory AND gate is called as intersection

OR gates-


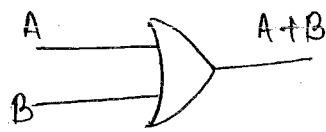
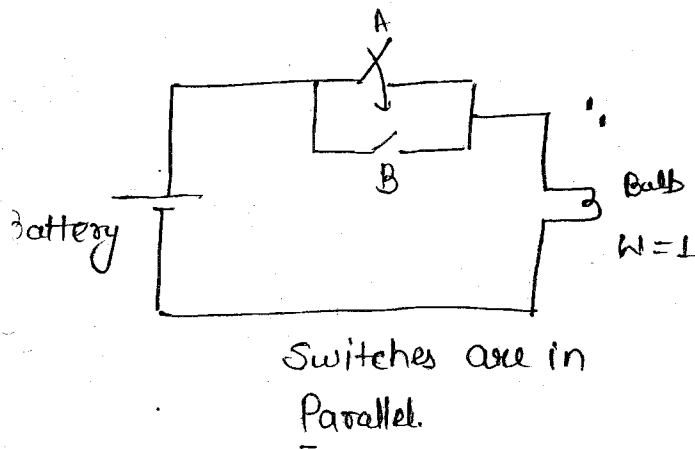


Truth table


A	B	W
0	0	0
0	1	1
1	0	1
1	1	1

* In set theory OR gate is represented as union.

NOT gates-

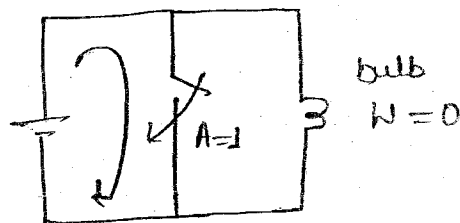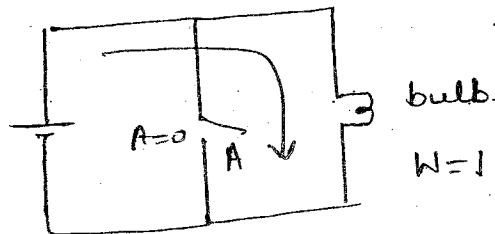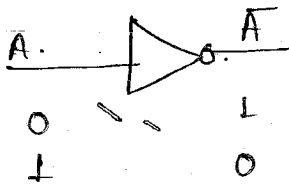

Current follows low resistance path

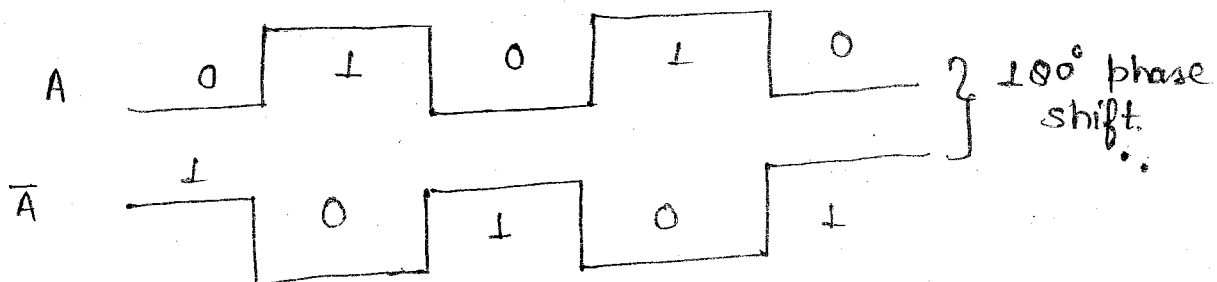

AND, OR, NOT gates are called basic gates

Precedence of operators

$$() > \text{NOT} > \text{AND} > \text{OR}$$

For example -

$$y = 2 * x + 3$$


(i) $2(x+3)$

(ii) $y = (2 * x) + 3$ (✓)

To get $y = 2 * x + 3$ first multiplication has to be done & followed by addition
hence option (ii) is correct.

So Multiplication has higher precedence.

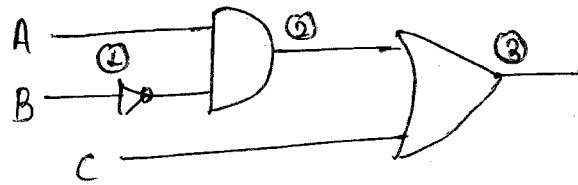Eg. To realize $f = A \cdot \bar{B} + C$.



Precedence order is NOT, AND, OR.

OR gate properties


- ① $A + 0 = A$
- ② $A + 1 = 1$
- ③ $A + A = A$
- ④ $A + \bar{A} = 1$


AND gate properties

- ① $A \cdot 0 = 0$
- ② $A \cdot 1 = A$
- ③ $A \cdot A = A$
- ④ $A \cdot \bar{A} = 0$

Proof of OR gate property ②

$$A + 1 = 1$$

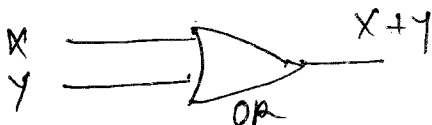

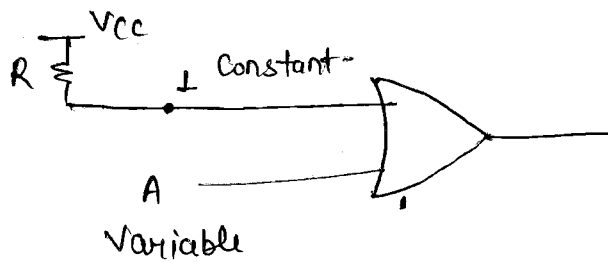

when $A = 0$. $O/P = 1 + 0 = 1$

when $A = 1$ $O/P = 1 + 1 = 1$.

Hence. for any value of A

$$\boxed{Y = A + 1 = 1} \quad \text{Proved.}$$

Distributive Property:-

(i) $A \cdot (B + C) = A \cdot B + A \cdot C$.

(ii) $(A + B) \cdot (A + C) = A + BC$

$$\text{L.H.S} = (A + B) \cdot (A + C)$$

$$= A \cdot A + A \cdot C + B \cdot A + B \cdot C$$

$$= A + AC + AB + BC$$

$$= A(1 + C + B) + BC \quad \rightarrow \text{using OR gate Id property } A + 1 = A.$$

$$= A + BC = \text{R.H.S} \quad \text{Proved.}$$

Q Prove

$$X + \bar{X}Y = X + Y.$$

$$\text{L.H.S} = X + \bar{X}Y = (X + \bar{X}) \cdot (X + Y)$$

$$= \cancel{X(Y + \bar{Y})} + \bar{X}Y = \cancel{X + X\bar{Y}} = 1 \cdot (X + Y)$$

$$= \cancel{XY + X\bar{Y}} + \bar{X}Y$$

$$= X + Y.$$

Proved

Question-

$$\bar{X} + XY = ?$$

$$\bar{X} + XY = \bar{X} + Y$$

(Take first element in second term's complement).

Question.- $DB + \bar{B}CD$

$$D(B + \bar{B}C)$$

$$D(\bar{B} + C)$$



De Morgan's Law:-

$$\overline{A+B} = \bar{A} \cdot \bar{B}$$



$$\overline{A \cdot B} = \bar{A} + \bar{B}$$

NAND gate:-

NAND gate means NOT of AND gate.

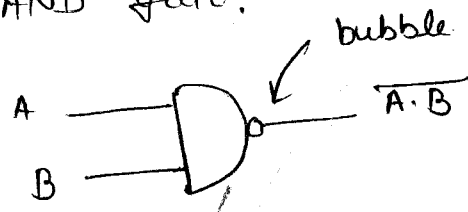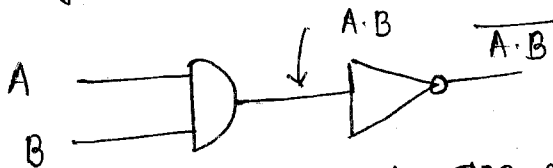

NAND gate in terms of OR gate

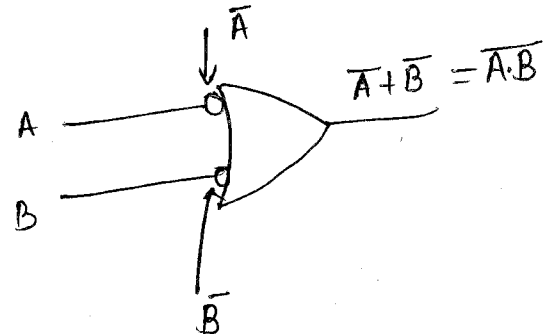
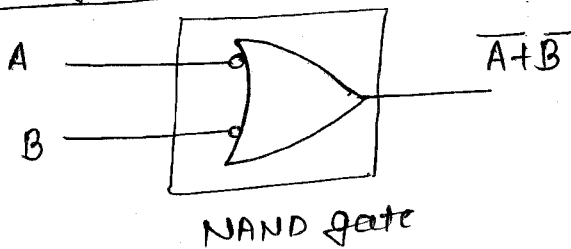


Truth table


A	B	$A \cdot B$	$\overline{A \cdot B}$
0	0	0	1
0	1	0	1
1	0	0	1
1	1	1	0

NOR gate

NOT of OR gate.

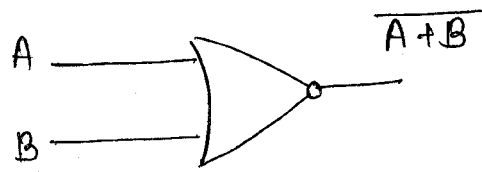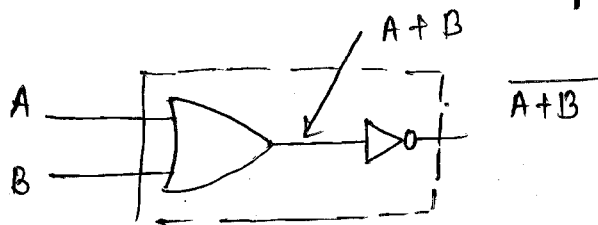

NOR gate in terms of AND gate:-

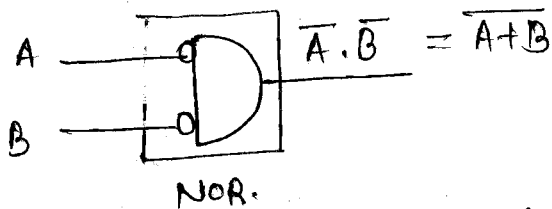

AB	A+B	$\overline{A+B}$
00	0	1
01	1	0
10	1	0
11	1	0

* NAND gate & NOR gate are called Universal gates.

UNIVERSAL GATE'S

* Universal means functionally complete.

Any boolean logic can be realized using universal gates.

Ex- 4P can be constructed using only NAND gates.



IES-4 Marks Prove NAND is universal.

TEST:- Realize basic gates {AND, OR, NOT}



NOT gate





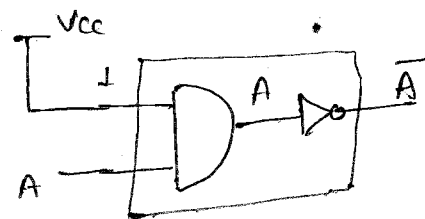
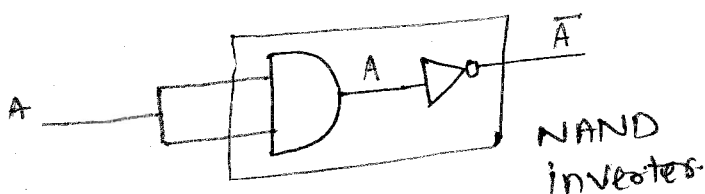
$$\therefore A \cdot A = A$$
$$A \cdot 1 = A$$



AND gate from NAND gate

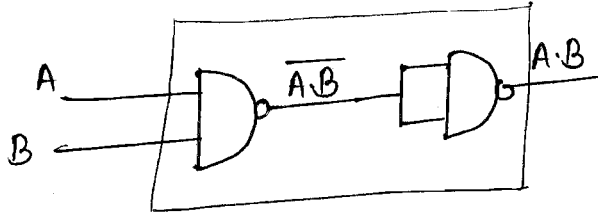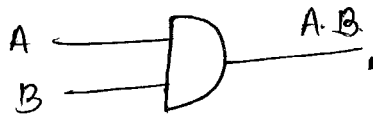

OR gate from NAND gate:-

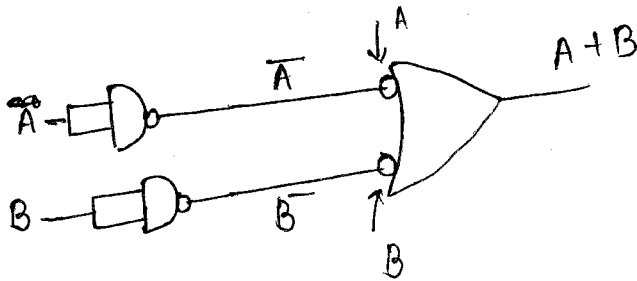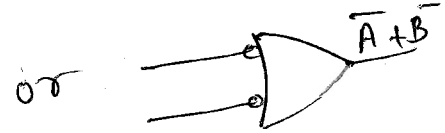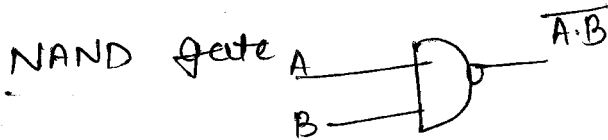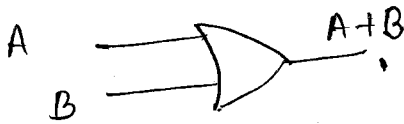

Proove NOR gate as universal gate?

Test - (OR, AND, NOT gate from NOR gate)


Property

$$A+0 = A$$





$$A+A = A$$

① NOT gate from NOR gate

NOT gate


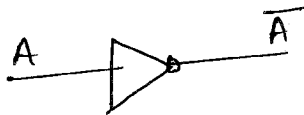


NOR gate

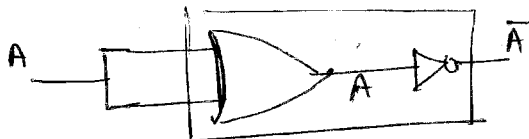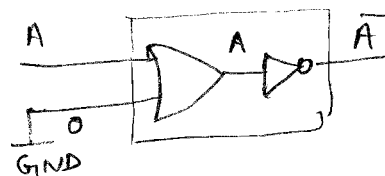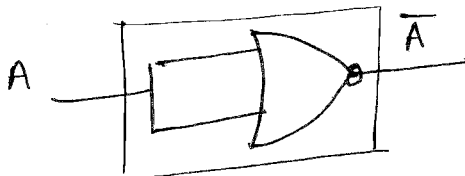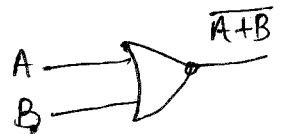

AND gate from NOR gate!:-



NOR gate

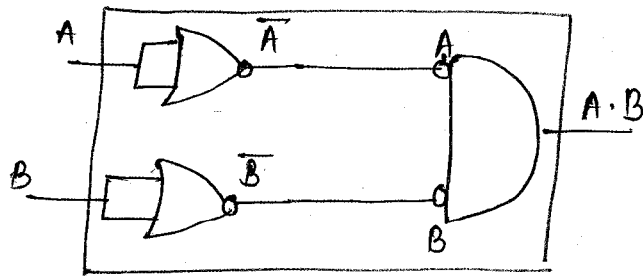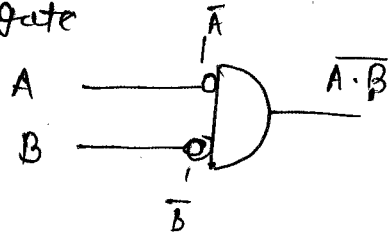

AND gate

OR gate from NOR gate:-

OR gate

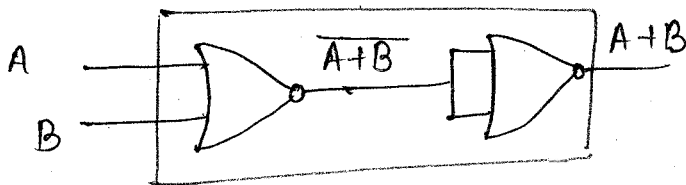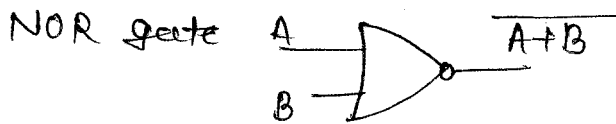

OR gate

Question- Gate EC- 2015 2Marks / IAS

Proove $\overline{A+B}$ is universal assume V_{cc} and ground are available.

