

HindPhotostat



Hind Photostat & Book Store

Best Quality Classroom Topper Hand Written Notes to Crack GATE, IES, PSU's & Other Government Competitive/ Entrance Exams

MADE EASY ELECTRICAL ENGINEERING Power System-2 By.Bhoopender Sir

- Theory
- Explanation
- Derivation
- Example
- Shortcuts
- Previous Years Question With Solution

Visit us:-www.hindphotostat.com

Courier Facility All Over India
(DTDC & INDIA POST)
Mob-9311989030



HindPhotostat



MADE EASY , IES MASTER , ACE ACADEMY , KREATRYX

**ESE , GATE, PSU BEST QUALITY TOPPER HAND WRITTEN NOTES
MINIMUM PRICE AVAILABLE @ OUR WEBSITE**

- | | |
|--------------------------------|---------------------------|
| 1. ELECTRONICS ENGINEERING | 2. ELECTRICAL ENGINEERING |
| 3. MECHANICAL ENGINEERING | 4. CIVIL ENGINEERING |
| 5. INSTRUMENTATION ENGINEERING | 6. COMPUTER SCIENCE |

IES , GATE , PSU TEST SERIES AVAILABLE @ OUR WEBSITE

❖ IES –PRELIMS & MAINS

❖ GATE

➤ **NOTE;- ALL ENGINEERING BRANCHS**

➤ **ALL PSUs PREVIOUS YEAR QUESTION PAPER @ OUR WEBSITE**

PUBLICATIONS BOOKS -

**MADE EASY , IES MASTER , ACE ACADEMY , KREATRYX , GATE ACADEMY , ARIHANT , GK
RAKESH YADAV , KD CAMPUS , FOUNDATION , MC –GRAW HILL (TMH) , PEARSON...OTHERS**

HEAVY DISCOUNTS BOOKS AVAILABLE @ OUR WEBSITE

F230, Lado Sarai New Delhi-110030 Phone: 9311 989 030	Shop No: 46 100 Futa M.G. Rd Near Made Easy Ghitorni, New Delhi-30 Phone:9711475393	F518 Near Kali Maa Mandir Lado Sarai New Delhi-110030 Phone: 9560 163 471	Shop No.7/8 Saidulajab Market Neb Sarai More, Saket, New Delhi-30
--	--	--	--

Website: www.hindPhotostat.com


Contact Us: 9311 989 030

Courier Facility All Over India

(DTDC & INDIA POST)

Power Analysis of AC circuit :-

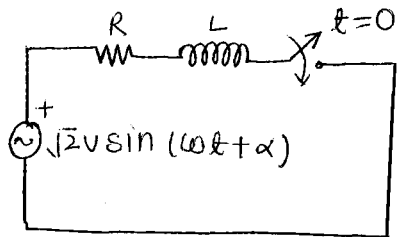(i) A circuit which is in steady state corresponding to a given sinusoidal excitation is called an AC circuit.



Not an AC circuit

because it is in transient state


∴ $i(t) = i_{SS} + i_{TR}$

i_{SS} = steady state response depends upon the source

i_{TR} = Transient response depends upon the circuit itself

$i(t) = \sqrt{2} I \sin(\omega t + \beta) + A e^{-t/\tau}$

∴ **Responses are non-sinusoidal**

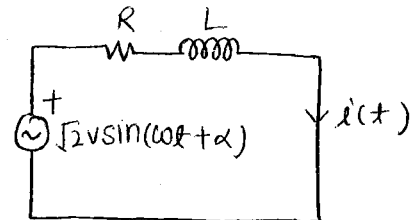

An AC circuit


$i(t) = \sqrt{2} I \sin(\omega t + \beta)$

Responses are sinusoidal and having same freq.


(ii) All the **responses** of an **An ac circuit** are **sinusoidal** with frequency **equal to** the **source frequency**.

(iii) The **magnitude (RMS value)** and **phase of a response** in an AC circuit is computed **using phasor technique**.

Ex:-

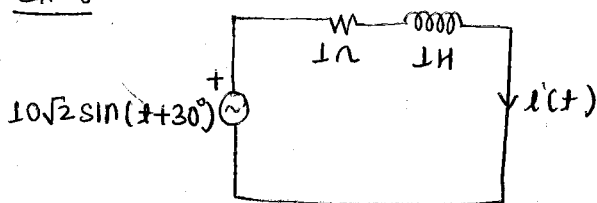

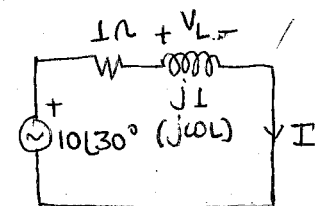Phasor domain eq^t ckt
ref. waveform = sin t



Reference waveform is selected such that frequency of ref. waveform should be equal to the frequency of source.

In phasor diagram equivalent ckt we have to take rms value.

$V_m = 10\sqrt{2} \Rightarrow V_{RMS} = 10$

	Time domain	Phase domain	Frequency domain
Inductance	Henry (H)	jX or $j\omega L$	sL
Capacitance	Farad (F)	$1/(j\omega C)$	$1/sC$
Resistance	R	R	R

$$I(t) = \frac{10 \angle 30^\circ}{1 + j1} = \frac{10}{\sqrt{2}} \angle -15^\circ = 10 \sin(t - 15^\circ)$$


\downarrow
RMS value
 \downarrow
Maximum value

By applying voltage division rule

$$V_L = 10 \angle 30^\circ \left(\frac{j1}{1 + j1} \right) = \frac{10}{\sqrt{2}} \angle 75^\circ = 10 \sin(t + 75^\circ)$$

Now power analysis of an AC circuit

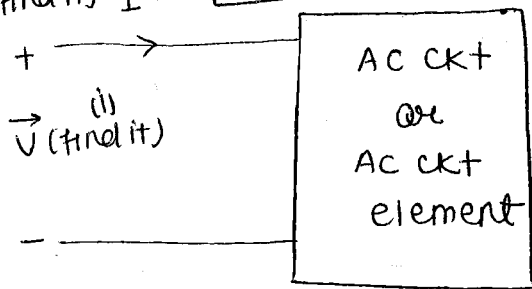(iii) (find it) $\vec{I} \rightarrow$ absorbed



complex power absorbed by AC CKT or element

$$S = \vec{V} \vec{I}^* \quad \text{(iii)} \\ = P + jQ$$

(iv) then;

P = Active power / useful power / Avg. power / power absorbed by AC CKT or AC CKT element (watt)

Q = Reactive power / lagging VAR absorbed by the AC CKT element or AC CKT. (VAR)


By default Active power

$P > 0 \rightarrow$ CKT absorbed active power

$P < 0 \rightarrow$ CKT delivers active power

$Q > 0 \rightarrow$ CKT. absorbed Reactive power / lagging VAR
or
CKT delivers leading VAR

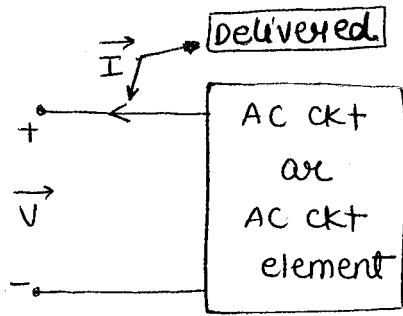$Q < 0 \rightarrow$ ckt delivers Reactive power / lagging VAr
 or
 ckt absorbs leading VAr.



complex power delivered by AC ckt or AC ckt element

$$S = VI^* = P + jQ$$

$P =$ Active power / useful power / Average Power / Power delivered by AC ckt or AC ckt element


$Q =$ Reactive power / lagging VAr delivered by the AC ckt element or AC ckt.

$P > 0 =$ ckt delivers active power
 $P < 0 =$ ckt absorbs active power

$Q > 0 =$ ckt. delivers Reactive power / lagging VAr
 or
 ckt absorbs leading VAr

$Q < 0 =$ ckt. absorbs Reactive power / lagging VAr
 or
 ckt delivers leading VAr

EX-0

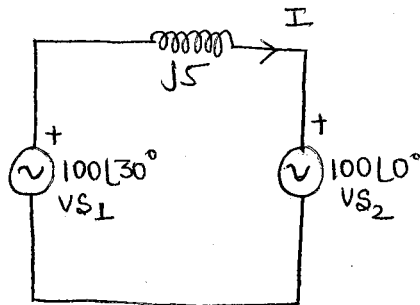

$$I = \frac{100 \angle 30^\circ - 100 \angle 0^\circ}{j5}$$

$$= 10.35 \angle 15^\circ$$

complex power absorbs by VS-2


$$S = (100 \angle 0^\circ) (10.35 \angle 15^\circ)^* = 1000 - j268$$

VS_2 : absorbs 1000W and delivers 268 VAr

complex power delivered by VS-1

$$S = 100 \angle 30^\circ (10.35 \angle 15^\circ)^* = 1000 + j268$$

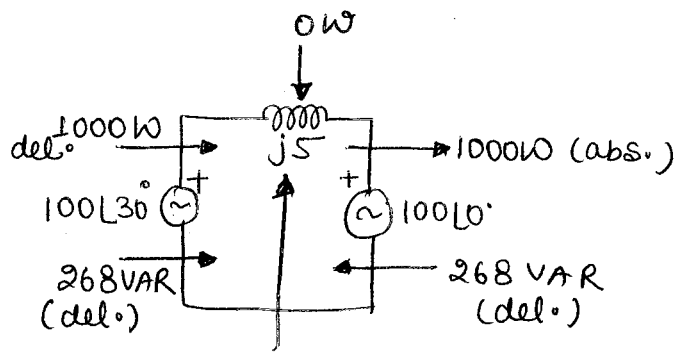VS_1 : delivered 1000W and delivers 268 VAr






$$536 \text{ VAR (abs.)}$$

$$= 268 \text{ VAR} + 268 \text{ VAR} \ \& \ \text{[Active power} = 0 \text{ (always)]}$$


NOTE:- In power system active power always flows from leading voltage source towards the lagging voltage source where as reactive power generally flow from voltage of high magnitude towards voltage of low magnitude.

EX:-

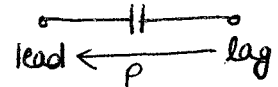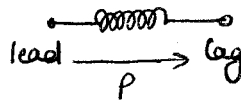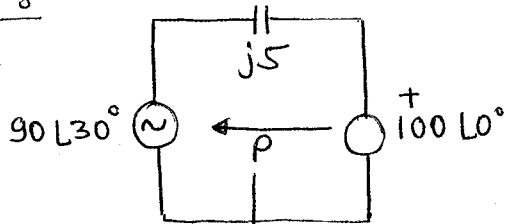

But in power system in series capacitor is not present i.e; not power system ckt.

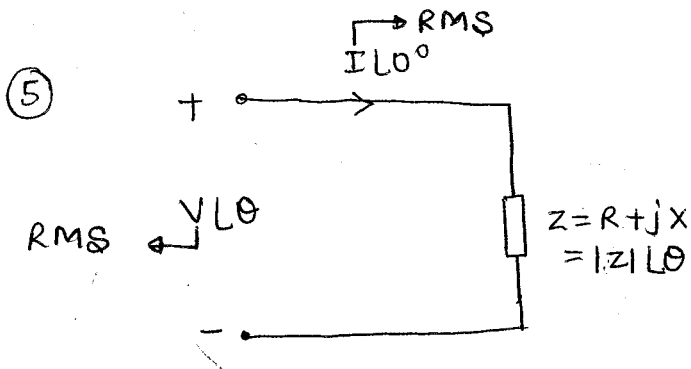i.e; flowing from lagging to leading voltage source because it is not power system ckt. b^o the series branch of power system is always inductive in nature.




$x = +ve \rightarrow$ inductance
 $x = -ve \rightarrow$ capacitance

$$Y = \frac{1}{Z} = G + jB$$

$B = -ve \rightarrow$ inductance
 $B = +ve \rightarrow$ capacitance

$$|Z| = \sqrt{R^2 + X^2}$$

$$\theta = \tan^{-1} \frac{X}{R}$$

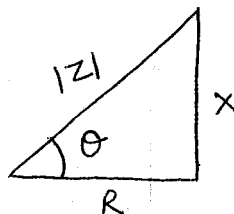

$$\cos \theta = \frac{R}{|Z|}$$

$$\sin \theta = \frac{X}{|Z|}$$

$$\vec{V} = \vec{I} \vec{Z}$$

$$= I L0^\circ Z L\theta$$



$$= I Z L\theta = V L\theta$$

So, complex power absorbed by $z = R + jX$

$$S = P + jQ = (V L \theta) (I L \theta)^* = VI \cos \theta + jVI \sin \theta$$

$$P = VI \cos \theta = VI \frac{R}{|Z|} = \boxed{I^2 R} \quad \text{RMS value}$$

$$Q = VI \sin \theta = VI \frac{X}{|Z|} = \boxed{I^2 X} \quad \text{RMS value}$$

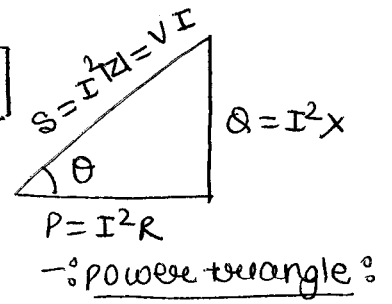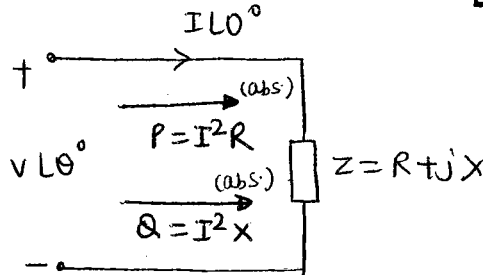





$$p.f. = \cos \theta = \frac{P}{S}$$

$R \geq 0 \rightarrow P \geq 0$ so, $z = R + jX$ can't deliver active power.

$X > 0$ (inductive) $\rightarrow Q > 0$ i.e; inductive Impedance absorbs Reactive power / lagging VAR
 (or) inductive Impedance delivers leading VAR


$X = 0$ (Resistive) $\rightarrow Q = 0$

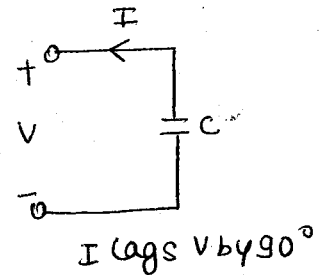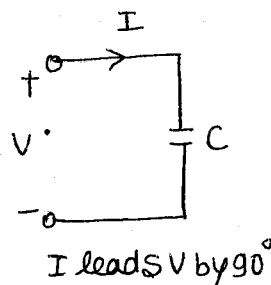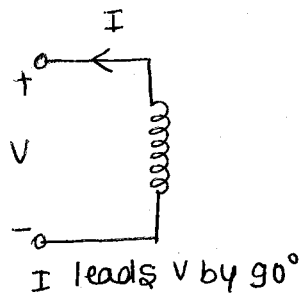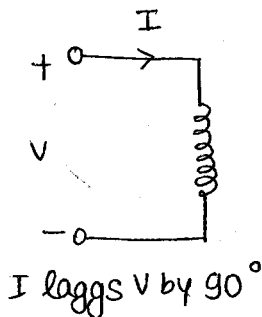$X < 0$ (capacitive) $\rightarrow Q < 0$ i.e; capacitive impedance delivers Reactive power / lagging VAR
 (or) capacitive Impedance absorbs leading VAR



(By default we take absorb current always)



EX-0:

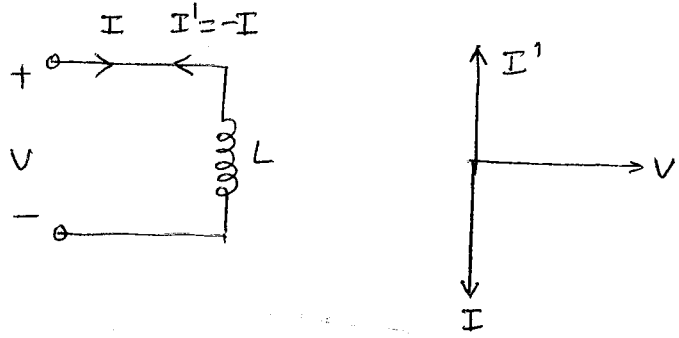

For I (अन्दर जाने वाली) current is lagging then it always absorbs lagging VAR.

For I' which is leads by V then it always delivers leading VAR.

NOTE-0:

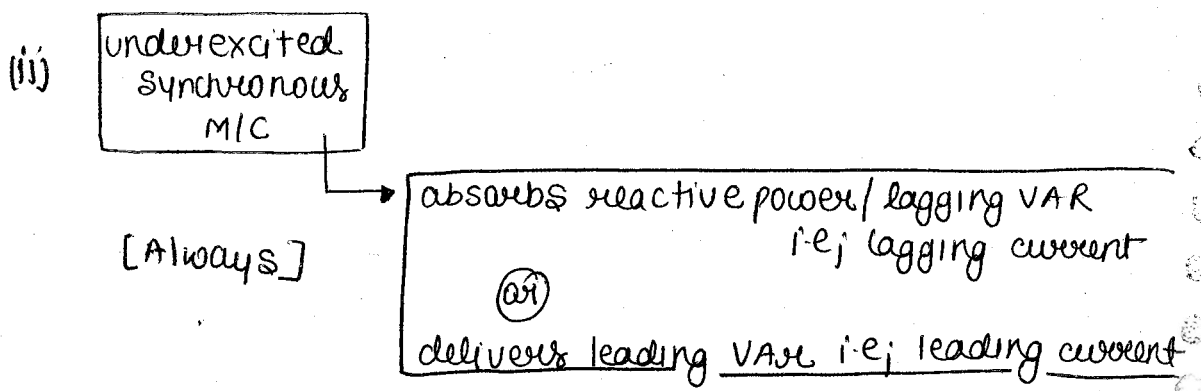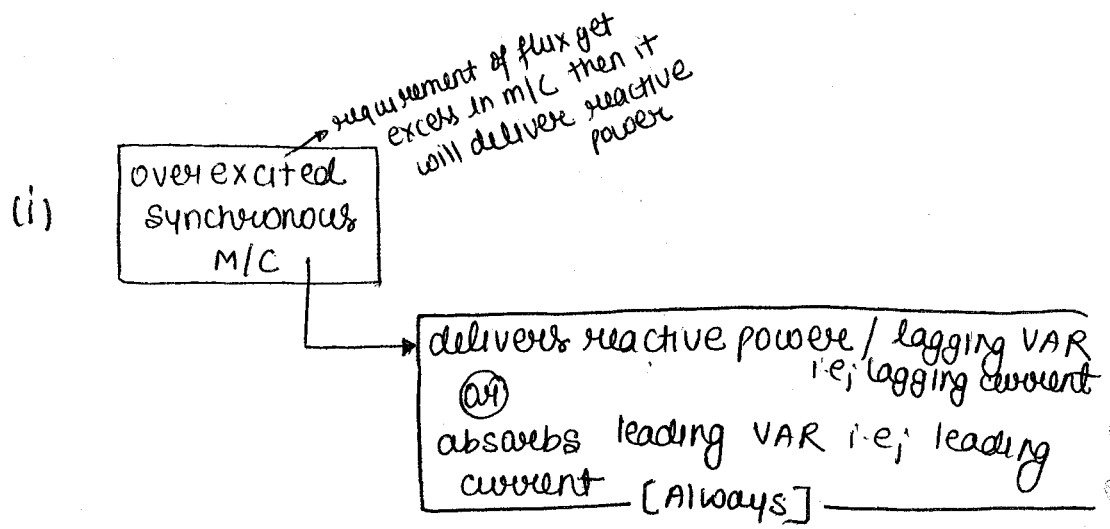

Now; Motor \rightarrow absorb the current & current may be leading or lagging in nature

Generator \rightarrow delivers the current & current may be leading or lagging in nature


Overexcited syn. motor \rightarrow motor absorbs the current i.e; absorbs leading VAR

we can say that $Pf \equiv$ leading

Over excited sync. generator \rightarrow Generator delivers i.e; delivered lagging VARS i.e lagging current

we can say that $P.F \equiv$ lagging


#

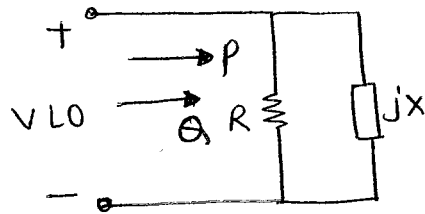

$$P = \frac{V^2}{R} \rightarrow \text{RMS value}$$

$$Q = \frac{V^2}{X} \rightarrow \text{RMS value}$$

Ex:-

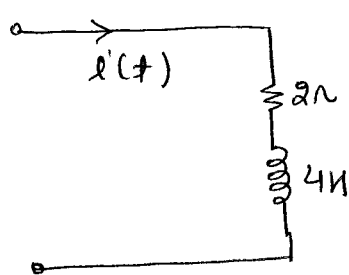

$$i(t) = 10 \sin(\omega t + 30^\circ)$$

$P = ? \quad Q = ?$

$$P = I^2 R = \left(\frac{10}{\sqrt{2}}\right)^2 \times 2 = 100 \text{ W}$$

$$[X = \omega L]$$

$$\omega = 2, L = 4$$

$$Q = I^2 X = \left(\frac{10}{\sqrt{2}}\right)^2 \times (2 \times 4) = 400 \text{ VAR}$$

$I = \text{RMS value}$

Balance 3- ϕ system / concept of phase sequence :-

A polyphase system is said to be balance if

- (i) The magnitude of corresponding quantity are equal in each phase.
- (ii) The phase difference b/w the corresponding quantities is given by


$\theta = \frac{360^\circ}{n} ; n \neq 2$
$\theta = 90^\circ ; n = 2$

Q.N:- The current in 2-phases of a two phase system is given below

$$i_a = \sqrt{2} I \cos(\omega t - \phi_1) \quad i_b = \sqrt{2} I \sin(\omega t - \phi_2)$$

Find the relationship b/w ϕ_1 and ϕ_2 so that the two phase system is balance system.

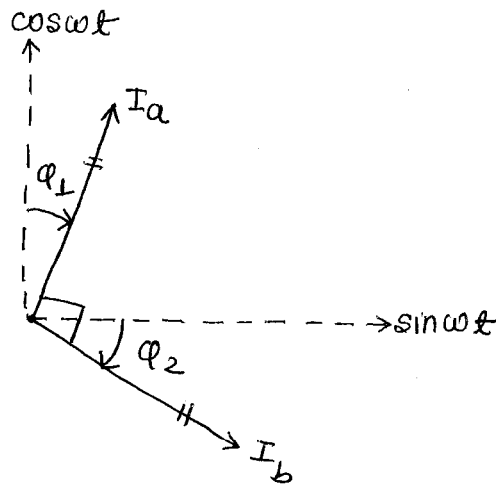Solution :- magnitude same i.e; rms value = I & $\theta = 90^\circ$ between I_a & I_b




To maintain the angle b/w I_a & $I_b = 90^\circ$ Then $\phi_1 = \phi_2$

lead	→ +ve	→ Anticlockwise
lag	→ -ve	→ clockwise


3φ Balance System :-

consider an (ideal) balance 3φ voltage source —

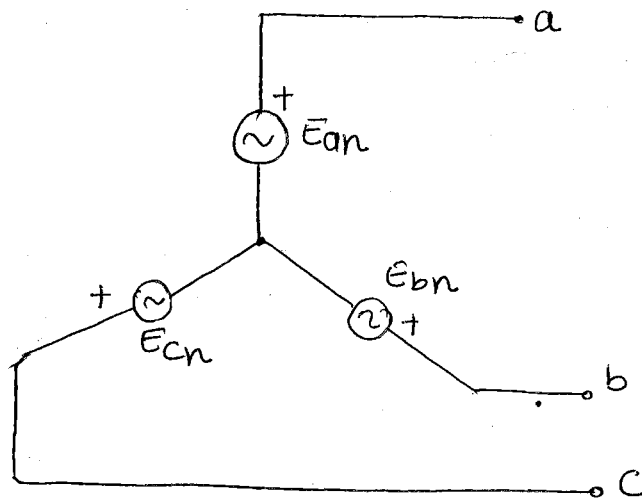
By default we have to take star connection



for balance system :-

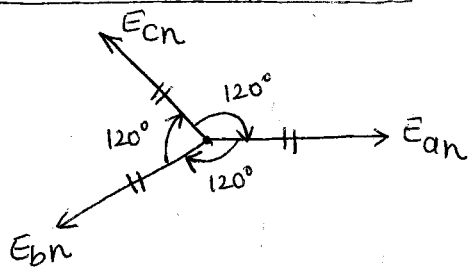

Phase sequence :- abc

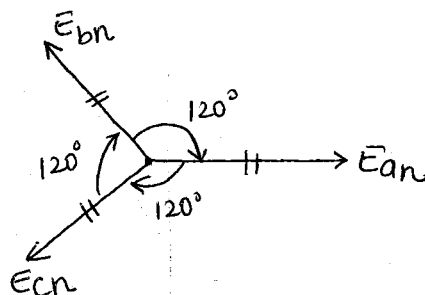

Phase sequence :- acb